


Question #1 (10 points)

You will design a high-pass 2nd order Butterworth filter using resistors, capacitors and/or inductors, with a cut-off frequency of $\omega_0 = 10^8$ rad/sec.

- Sketch the circuit, and write an expression for its transfer function.
- Determine the values of each resistor, capacitor, and/or inductor.
- Sketch a Bode plot of this transfer function. Use the straight-line approximation.

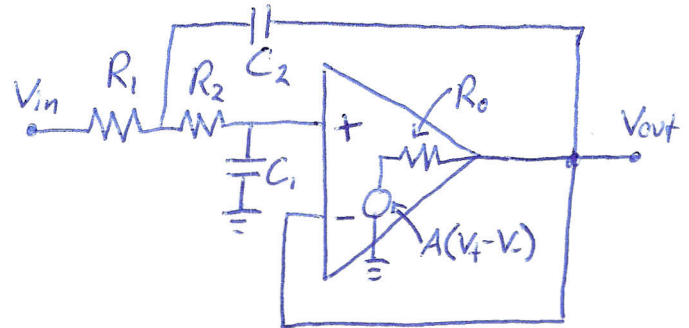Question #2 (15 points)

You will design a low-pass filter using the Sallen-Key circuit topology shown to the right, with a frequency of $\omega_0 = 10^5$ rad/sec and $\zeta = 1$. The filter must also have a minimum transmission of -60 dB in the high-frequency limit. Assume that $R_0 = 100\Omega$. For simplicity, also assume $R_1 = R_2 \gg R_0$. The transfer function for this circuit with an ideal op-amp is given for reference.



- Derive an approximate expression for the transfer function of this circuit in the high-frequency limit for the op-amp model shown. Assume that $A \rightarrow 0$ in the high-frequency limit.
- Find the minimum value of the resistors that allow this circuit to meet the high-frequency specification.
- Using the resistor values that you found in part b, find the values of both capacitors to meet the remaining specifications. For this calculation, you may assume an ideal op-amp.


For ideal op-amp:

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + sC_1(R_1 + R_2) + s^2R_1R_2C_1C_2}$$

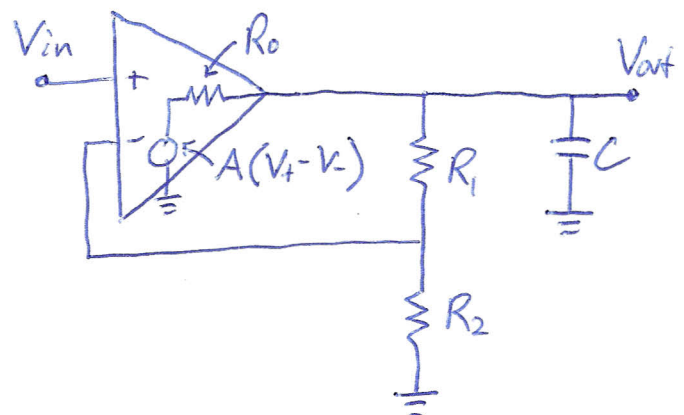Question #3 (15 points)

For the voltage follower circuit shown to the right, assume the op-amp gain is $A(s) = G/s$.


- Show that this circuit has a 2nd order transfer function by assuming that minimal current flows through the feedback resistors.
- Assuming $G = 10^7/\text{sec}$, $R_0 = 100\Omega$, $R_1 = 90\text{k}\Omega$, and $R_2 = 10\text{k}\Omega$, and $C = 250$ nF, determine whether you would expect the circuit to produce overshoot and ringing with a square wave input.
- If overshoot or ringing were observed in the output, what could be done to reduce this effect? Draw a modified circuit schematic.



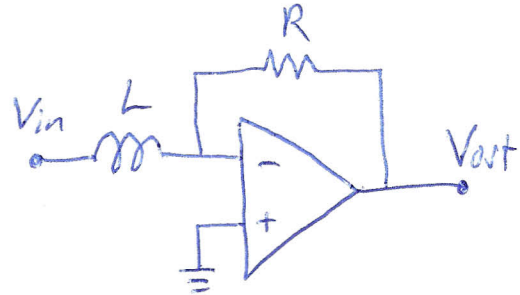Question #4 (15 points)

For the circuit shown to the right,


- Determine the transfer function, assuming an ideal op-amp model.
- What function does this circuit perform? Write a time-domain expression $V_{out}(t)$ as a function of $V_{in}(t)$.
- For a 50 kHz square wave input with 1 V magnitude, find the output waveform, including its magnitude. Assume that $R=100\Omega$ and $L=100\mu H$



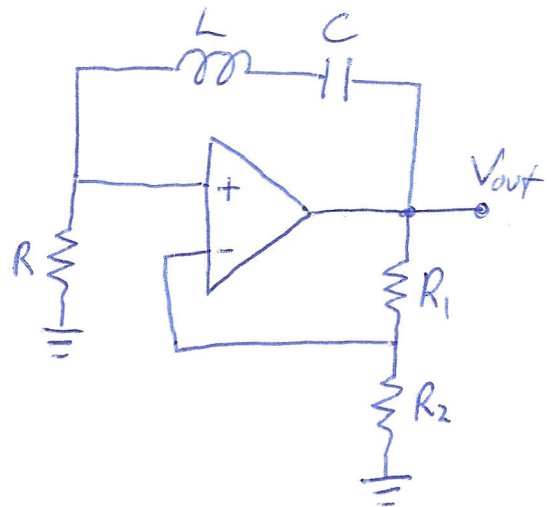Question #5 (15 points)

For the circuit shown to the right, $R_1=10k\Omega$, $R_2=10k\Omega$, and you may assume that minimal current flows through them. You may also assume that the op-amp, R_1 , and R_2 can be reduced to a simple amplifier.

- Sketch a Nyquist plot of the loop gain for this circuit assuming an ideal op-amp model.
- The op-amp uses supply voltages of ± 15 V, and it is turned on at $t=0$. Sketch what you would expect the output to look like as the circuit starts up.
- Is this a useful local oscillator for radio circuits? Why or why not?



Question #6 (15 points)

You will design an active band-reject filter. You do not need to include the coefficients of each s term, just the general form and circuit topology.

- Draw a signal flow graph for a 2nd order band-reject filter.
- Verify that your graph produces a band-reject response using Mason's gain formula.
- Implement the 2nd order band-reject filter with integrators, using the fewest op-amps possible.

Question 7 (15 points)

An oscillator consists of 3 inverters, which can be modeled as shown below.

- Write an expression for the loop gain of the circuit.
- Draw a Nyquist plot of the loop gain for this circuit
- Determine the condition for the minimum gain A_i required for the circuit to oscillate.

