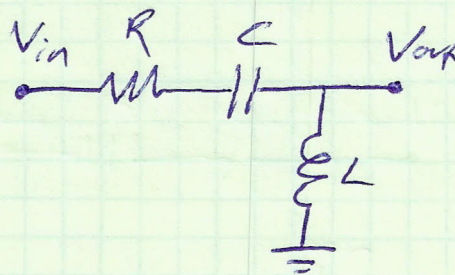


Question #1

a) High-pass filter:



$$\frac{V_{out}}{V_{in}} = \frac{sL}{sL + R + \frac{1}{sC}}$$

$$\frac{V_{out}}{V_{in}} = \frac{s^2 LC}{1 + sCR + s^2 LC}$$


$$b) \omega_0 = \frac{1}{\sqrt{LC}} = 10^8 \rightarrow LC = 10^{-16}$$

$$\zeta = \frac{1}{\sqrt{2}} \text{ for Butterworth } \frac{2\zeta s}{\omega_0} = sCR \rightarrow \zeta = \frac{1}{2} CR \cdot \frac{1}{\sqrt{LC}} = \frac{R}{2} \sqrt{\frac{C}{L}}$$

choose $L = 10^{-7} = 100 \text{ nH}$, and $C = 10^{-9} = 1 \text{ nF}$ to set ω_0


$$R = \frac{2}{\sqrt{2}} \sqrt{\frac{10^{-7}}{10^{-9}}} = 14 \Omega$$

(other values are possible too)

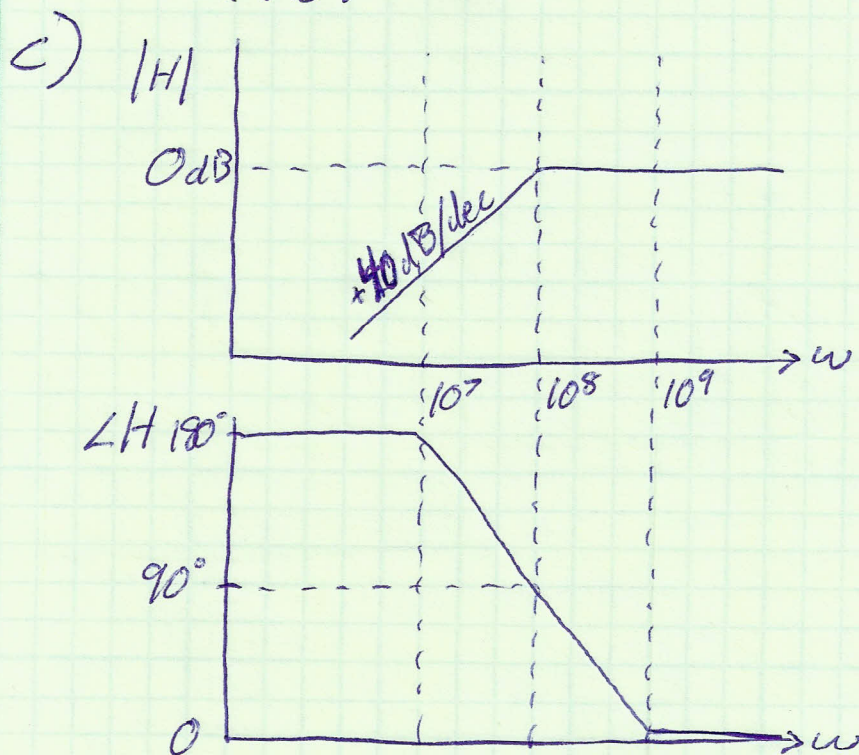

Question #2

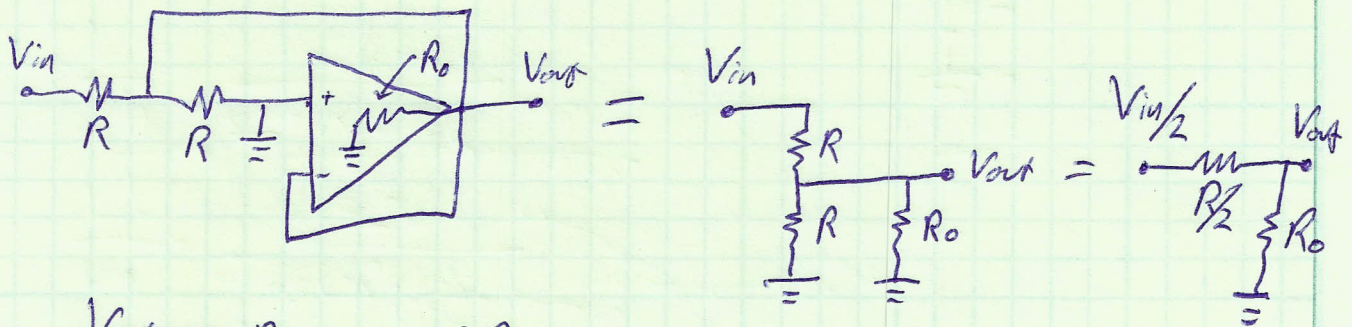a) High-frequency limit: as $\omega \rightarrow \infty$, $A \rightarrow 0$, caps $\rightarrow$ shorts



$$\frac{V_{out}}{V_{in/2}} = \frac{R_0}{R_0 + R/2} \approx \frac{2R_0}{R}$$

$$\frac{V_{out}}{V_{in}} \approx \frac{R_0}{R}$$

b) $\left| \frac{V_{out}}{V_{in}} \right|^2 = -60 \text{ dB} = 10^{-6}$

$$\frac{R_0^2}{R^2} = 10^{-6} \rightarrow R = 10^3 R_0, R_0 = 100 \Omega$$

$$R_{min} = 100 \text{ k}\Omega$$

c) $5C_1(R_1 + R_2) = \frac{2\pi s}{\omega_0}$

$$2 \times 10^5 C_1 = \frac{2}{10^5} \rightarrow C_1 = 10^{-10} = 100 \text{ pF}$$

$$\frac{1}{\sqrt{10^5 \times 10^5 \times 10^{-10} \times C_2}} = 10^5 \rightarrow C_2 = 10^{-10} = 100 \text{ pF}$$

Question #3

a) Transfer function:

$$B = \frac{R_2}{R_1 + R_2}, \quad A(V_{in} - BV_{out}) \cdot \frac{1/sC}{R_o + 1/sC} = V_{out}$$

$$\frac{G}{s} V_{in} - \frac{BG}{s} V_{out} = (1 + sR_oC) V_{out}$$

$$\frac{G}{s} V_{in} = (1 + sR_oC + \frac{BG}{s}) V_{out}$$

$$\frac{V_{out}}{V_{in}} = \frac{G/s}{1 + sR_oC + BG/s} = \frac{1}{B} \cdot \frac{1}{1 + \frac{s}{GB} + \frac{s^2 R_oC}{GB}}$$

b) no ringing if $\zeta \approx 1$ or greater


$$\frac{2\zeta\omega_0}{\omega_0} = \frac{s}{GB}, \quad \omega_0 = \sqrt{\frac{GB}{R_oC}}$$

$$\zeta = \frac{1}{2GB} \cdot \sqrt{\frac{GB}{R_oC}} = \frac{1}{\sqrt{4GBR_oC}}$$

$$\zeta = \frac{1}{\sqrt{4 \cdot 10^7 \cdot 0.1 \cdot 100 \cdot 2.5 \times 10^{-7}}} = \frac{1}{\sqrt{100}} = \frac{1}{10} < 1$$

There will be overshoot and ringing

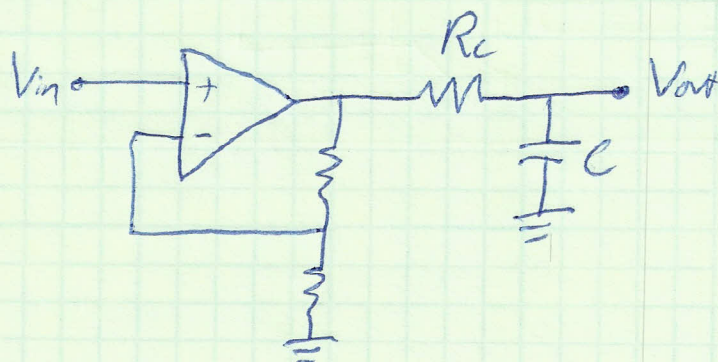c) This can be reduced with a compensation resistor:



Question #4

a) Transfer function:

$$\frac{V_- - V_{in}}{sL} + \frac{V_- - V_{out}}{R} = 0, \quad V_- = 0$$

$$\frac{V_{out}}{V_{in}} = \frac{-R}{sL}$$


b) This circuit is an integrator

$$V_{out}(t) = \frac{-R}{L} \int_{-\infty}^t V_{in}(\tau) d\tau$$

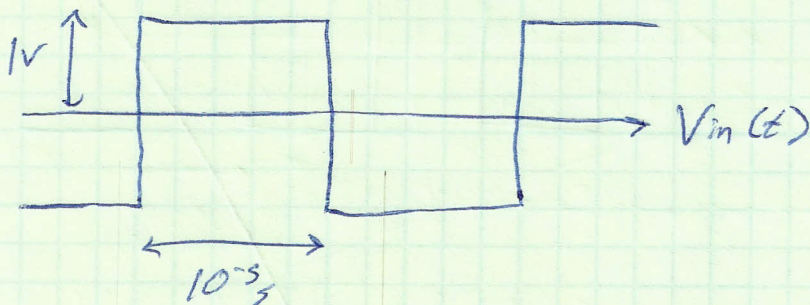
c) 50 kHz square wave with 1V magnitude

$$\text{period} = \frac{1}{5 \times 10^4} = 2 \times 10^{-5} \text{ s}$$

Output of integrator will be a triangle wave



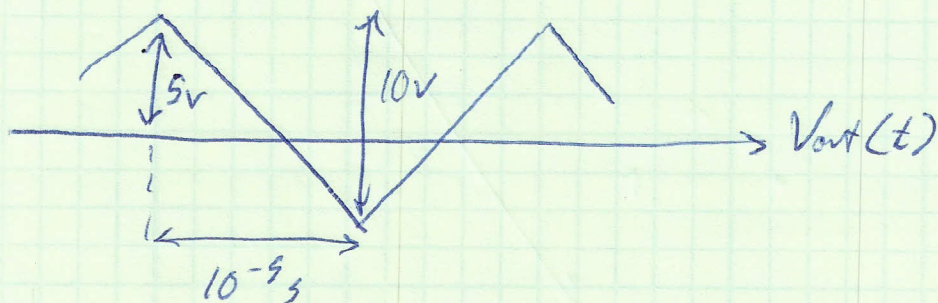
$$\text{change in voltage each half cycle} = \frac{-100}{100 \times 10^{-6}} \times 1 \times 10^{-5} = 10 \text{ V}$$



Output is 50 kHz triangle wave with 5V magnitude

Question #5

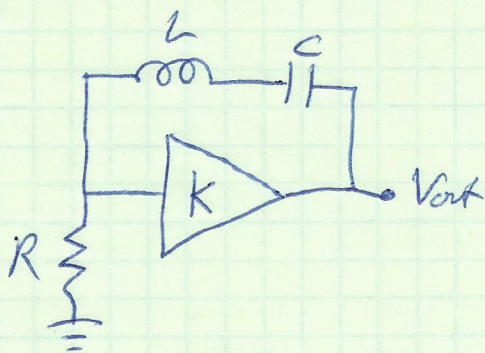- a) Op-amp behaves as amplifier with gain of $K = \frac{R_1 + R_2}{R_2} = 2$




Loop gain AB : $A = K$

$$B = \frac{-R}{R + sL + \frac{1}{sC}} = \frac{-sRC}{1 + sRC + s^2LC}$$

at $\omega = \frac{1}{\sqrt{LC}}$, $AB = \frac{-KsRC}{1 + sRC + s^2LC} = -K = -2$

Nyquist plot:

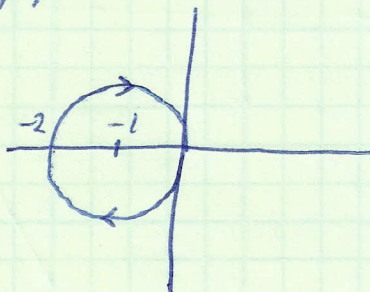

- b) Turn on $\pm 15V$ supply at $t=0$




- c) This is not a useful local oscillator for radio circuits because clipping will generate unwanted harmonics

Question #6

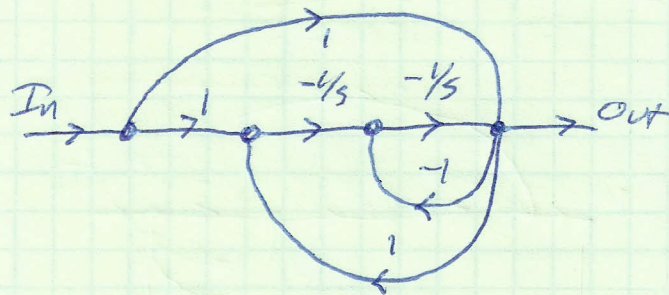a) Signal flow graph:

band reject = 1 - band pass

$$1 - \frac{s}{1+s+s^2} = \frac{1+s^2}{1+s+s^2}$$




b) Mason's gain formula:

$$\Delta = 1 + 1/s + 1/s^2$$

forward paths: 1 and $1/s^2$

$$H = \frac{1 + 1/s^2}{1 + 1/s + 1/s^2} = \frac{1+s^2}{1+s+s^2} \rightarrow \text{band reject filter}$$

c) circuit implementation:

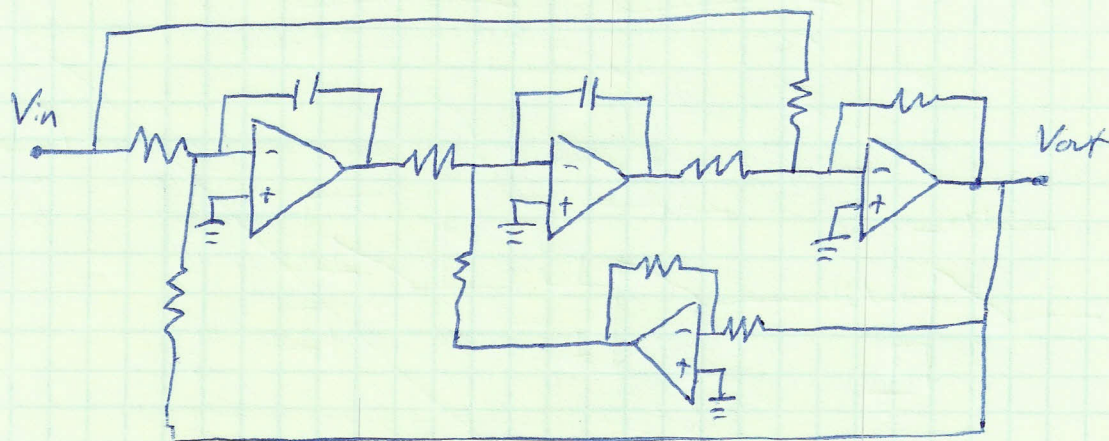


Question #7

a) loop gain:

each stage is $\frac{-A_i}{1+s\tau}$ $\tau = RC$ loop gain is $AB \rightarrow$

$$AB = (-1) \cdot \left(\frac{-A_i}{1+s\tau} \right)^3$$

$$AB = \frac{A_i^3}{(1+s\tau)^3} = \frac{A_i^3}{1 + 3s\tau + 3s^2\tau^2 + s^3\tau^3}$$

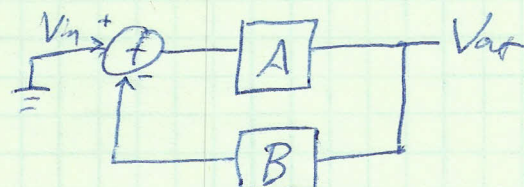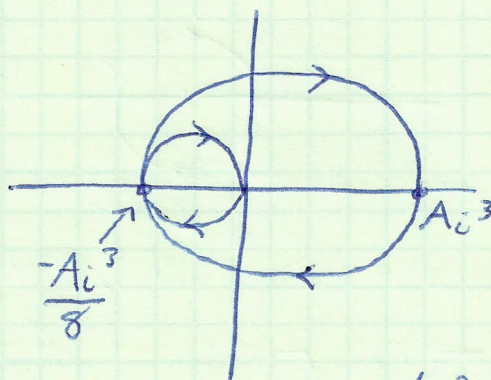

 $\tau = -1$ cancel negative signs

b) Nyquist plot:

Imaginary part = 0 $\rightarrow 3s\tau + s^3\tau^3 = 0$

$$\omega^2\tau^2 = 3 \rightarrow \omega = \frac{\sqrt{3}}{\tau}$$

$$AB = \frac{A_i^3}{1 + 3\left(\frac{\sqrt{3}}{\tau}\right)^2\tau^2} = \frac{-A_i^3}{8}$$

c) Circuit will oscillate if $\left| \frac{-A_i^3}{8} \right| > 1$ or $A_i > 2$