ECE100 Midterm Exam #1 Fall 2011

Don't forget:

- For all numerical answers, be sure to include units
- For plots, use a straight-line approximation. Label all relevant values for frequency, magnitude, phase, slope, intercept, etc.

Question #1

For the circuit shown at the right:

- a) Write the transfer function as a ratio of polynomials in s
- b) For L=100nH and C=1nF, what is ω_0 ?
- c) What value of R would make this a second order Butterworth filter?
- d) Sketch a Bode plot of this transfer function for the component values given above.

Question #2

You have an op-amp, a box of 100pF capacitors, and a variety of resistors having any value you need. The Sallen-Key filter topology has the transfer function:

 $\frac{V_{out}}{V_{in}} = \frac{Z_3 Z_4}{Z_1 Z_2 + Z_3 (Z_1 + Z_2) + Z_3 Z_4}$

a) Using only the components above, draw a Sallen-Key circuit that has a high-pass filter response

Vin

- b) Write the transfer function as a ratio of polynomials in s
- c) Using only 100pF capacitors, what resistor values will give $\omega_0=10^5$ and $\zeta=0.5$?

Question #3

For the voltage follower circuit, assuming the op-amp gain is A(s)=G/s

- a) Derive the output impedance Z_{out} for $R_d = \infty$, and $R_1 \& R_2 >> R_o$
- b) Find the effective capacitance or inductance seen at the output for $R_o=50\Omega$, G=10⁶ rad/s, R₁=10k\Omega, R₂=90k\Omega

Question #4

For the circuit shown at right, the op-amp is characterized by

 $A(s) = \frac{A_0}{1+s \tau_A}$ where $\tau_A=1$, and $A_0=10^6$. R=100k Ω and C=100pF.

- a) Write an expression for the loop gain (AB)
- b) Sketch a Bode plot of the loop gain.
- c) Estimate the phase margin for this circuit.
- d) Is it stable? Why or why not?



