

Question 1

$$a) \frac{V_{out}}{V_{in}} = \frac{1/SC}{1/SC + sL + R} = \frac{1}{1 + sCR + s^2LC}$$

$$b) \frac{1}{1 + sCR + s^2LC} = \frac{1}{1 + \frac{2\zeta s}{\omega_0} + \frac{s^2}{\omega_0^2}}$$



$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-7} \cdot 10^{-9}}} = \underline{10^8 \text{ rad/sec}}$$

$$c) \text{ Butterworth: } \zeta = \frac{1}{\sqrt{2}}$$


$$\frac{2\zeta s}{\omega_0} = sCR \quad \zeta = \frac{\frac{1}{2}CR}{\frac{1}{\sqrt{LC}}} = \frac{R}{2} \sqrt{\frac{C}{L}} \quad R = 2\zeta \sqrt{\frac{L}{C}}$$

$$R = 2 \cdot \frac{1}{\sqrt{2}} \cdot \sqrt{\frac{10^{-7}}{10^{-9}}} = \sqrt{2} \times 10 = \underline{14 \Omega}$$

d) $|H|$

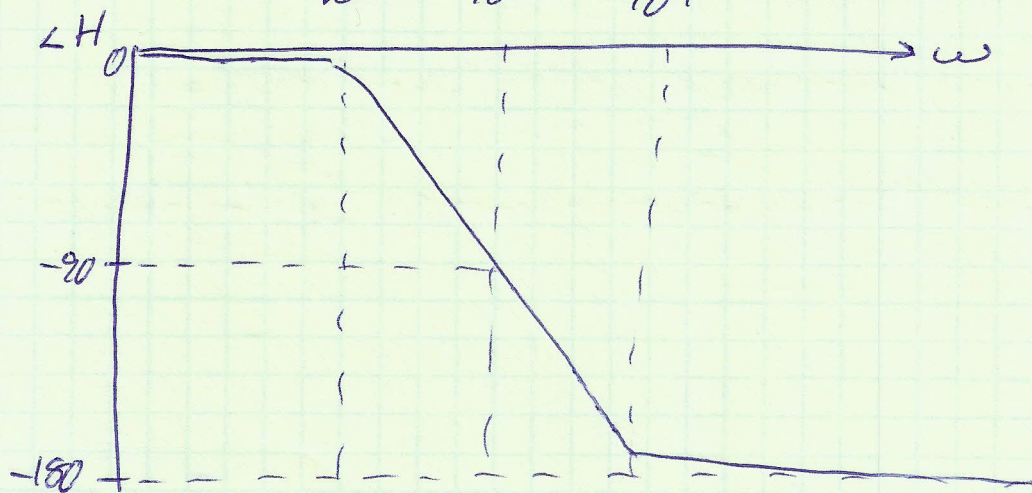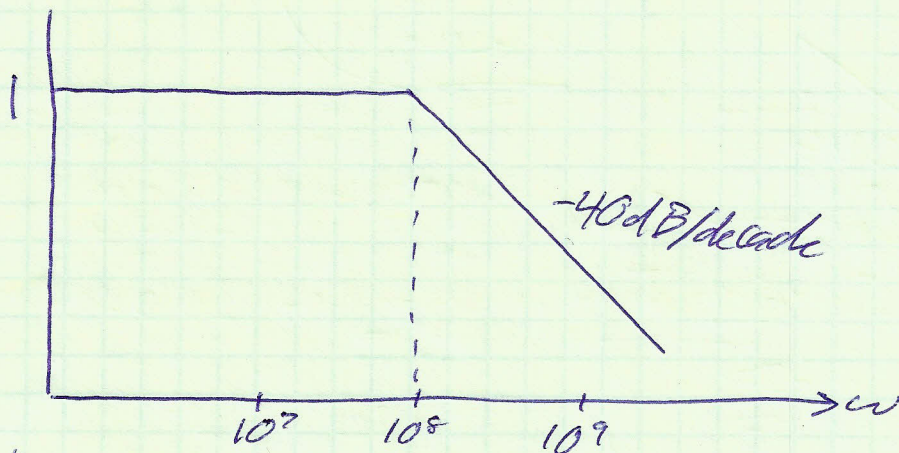

Question 2

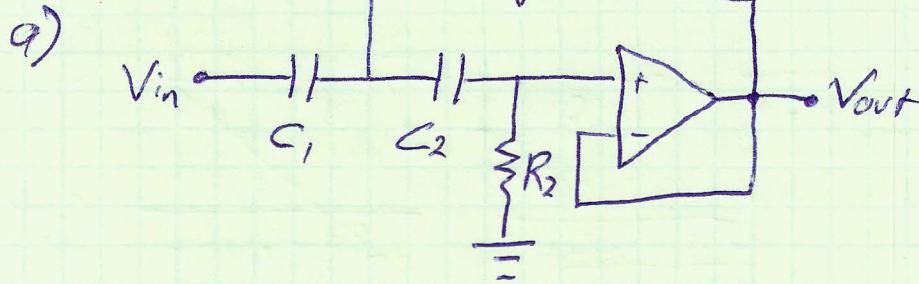

b)

$$\frac{V_{out}}{V_{in}} = \frac{R_1 R_2}{\frac{1}{s^2 C_1 C_2} + R_1 \left(\frac{1}{s C_1} + \frac{1}{s C_2} \right) + R_1 R_2}$$

$$= \frac{s^2 C_1 C_2 R_1 R_2}{1 + s R_1 (C_1 + C_2) + s^2 C_1 C_2 R_1 R_2}$$

c)

$$C_1 = C_2 = C = 100 \text{ pF}$$

$$s R_1 2C = \frac{2\zeta s}{\omega_0} \quad \omega_0 = \frac{1}{C \sqrt{R_1 R_2}}$$

$$\zeta = R_1 C \omega_0 = \sqrt{\frac{R_1}{R_2}}$$

define $R_1 = R_x$ and $R_2 = R/x$

$$\omega_0 = \frac{1}{CR} \quad \zeta = x = 0.5$$

$$R = \frac{1}{C \omega_0} = \frac{1}{10^{-10} \cdot 10^5} = 100 \text{ k}\Omega$$

$$\underline{R_1 = 50 \text{ k}\Omega} \quad \text{and} \quad \underline{R_2 = 200 \text{ k}\Omega}$$

Question 3

$$a) \quad V_{out} = A(V_{in} - BV_{out}) \quad B = \frac{R_1}{R_1 + R_2}$$
$$V_{out}(1 + AB) = AV_{in}$$

$$\text{open circuit: } V_{oc} = \frac{A}{1 + AB} V_{in}$$

$$\text{short circuit: } I_{sc} = A(V_{in} - 0)/R_o$$

$$Z_{out} = \frac{V_{oc}}{I_{sc}} = \frac{\frac{A}{1 + AB} V_{in}}{AV_{in}/R_o} = \frac{R_o}{1 + AB}$$

$$Z_{out} = \frac{R_o}{1 + GB/s}$$

$$b) \quad Z_{out} = \frac{R_o}{1 + GB/s} = \frac{1}{1/R_o + GB/s R_o} \quad \text{resistor in parallel with inductor}$$

$$L_{eff} = \frac{R_o}{GB}$$


$$B = \frac{R_1}{R_1 + R_2} = \frac{10k}{10k + 90k} = 0.1$$

$$L_{eff} = \frac{50}{10^6 \cdot 0.1} = 5 \times 10^{-4} = \underline{500 \mu H}$$

Question 4

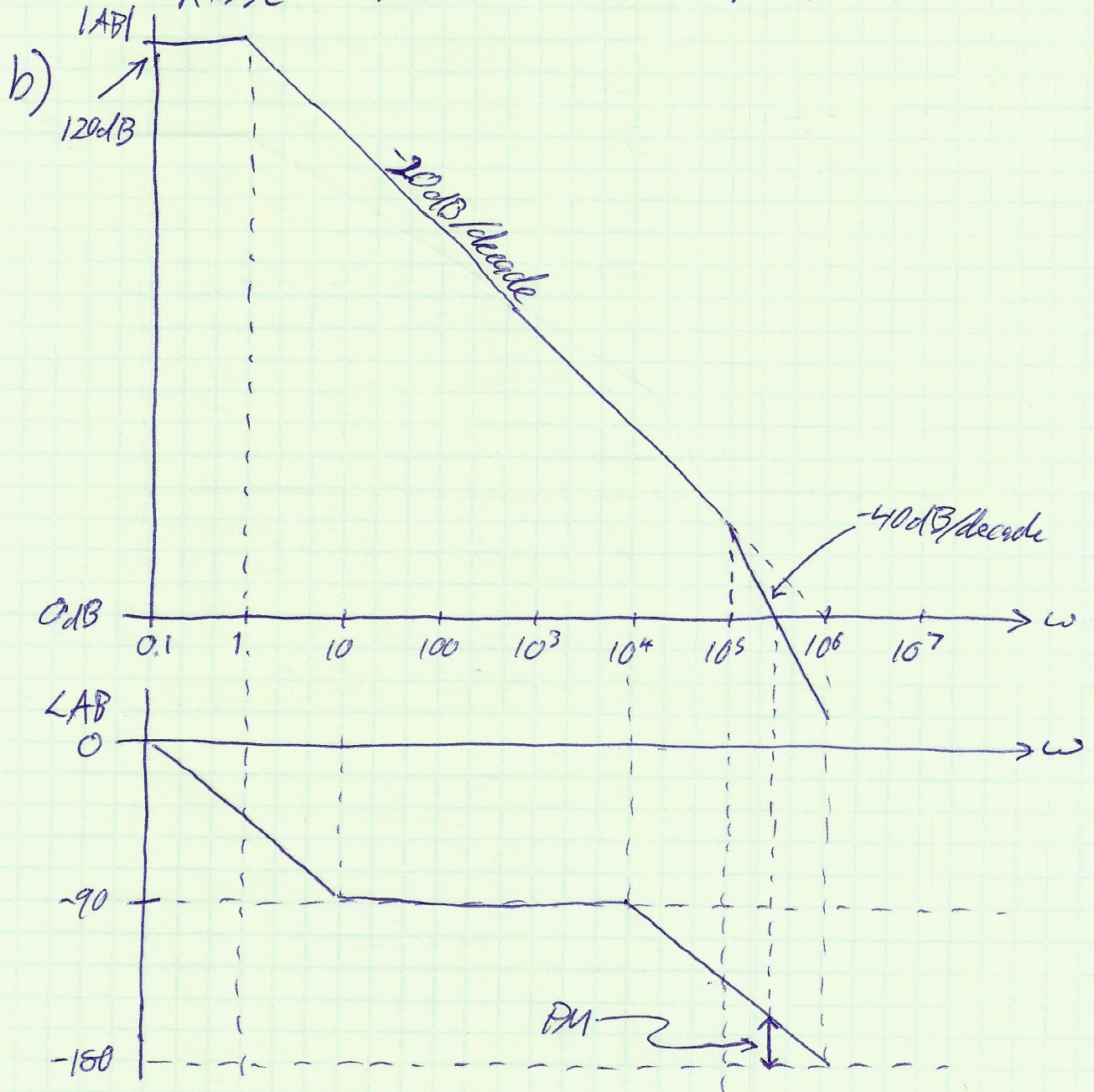a) $B = \frac{1/sC}{R + 1/sC} = \frac{1}{1 + sRC}$

$AB = \frac{A_0}{1 + s\tau_A} \cdot \frac{1}{1 + sRC}$



c) unity gain frequency $\approx 3 \times 10^5$ rad/sec

Phase margin $\approx 23^\circ$ (about half of 45°)

d) circuit is stable because phase margin > 0