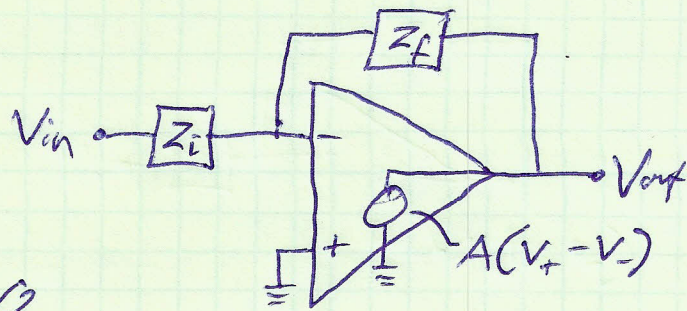


Question #1



$$a) \frac{V_- - V_{out}}{Z_f} + \frac{V_- - V_{in}}{Z_i} = 0$$

$$V_{out} = A(V_+ - V_-) = -AV_- \rightarrow V_- = -\frac{V_{out}}{A}$$

$$\frac{-\frac{V_{out}}{A} - V_{out}}{Z_f} + \frac{-\frac{V_{out}}{A} - V_{in}}{Z_i} = 0$$

$$V_{out}(Z_f + Z_i + AZ_i) = -AZ_f V_{in}$$


$$\frac{V_{out}}{V_{in}} = \frac{-Z_f}{Z_i} \cdot \frac{AZ_i}{Z_f + Z_i + AZ_i} = \frac{-Z_f}{Z_i} \cdot \frac{A \frac{Z_i}{Z_f + Z_i}}{1 + A \frac{Z_i}{Z_f + Z_i}} = \frac{-Z_f}{Z_i} \cdot \frac{AB}{1 + AB}$$

$$b) B = \frac{1/sC}{R + 1/sC} = \frac{1}{1 + sCR}, \quad A = G/s$$


$$H = -sCR \cdot \frac{\frac{G}{s} \cdot \frac{1}{1 + sCR}}{1 + \frac{G}{s} \cdot \frac{1}{1 + sCR}} = -sCR \cdot \frac{1}{\frac{s}{G}(1 + sCR) + 1}$$

$$= \frac{-sCR}{1 + \frac{s}{G} + \frac{s^2 CR}{G}} \rightarrow \text{second order response}$$

c)

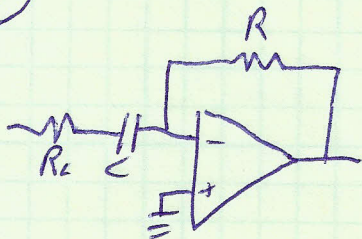


compensation resistor

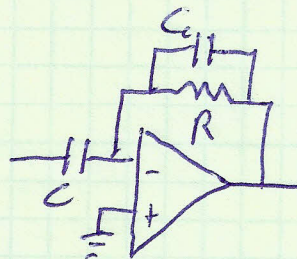

compensation capacitor

Both of these can be used to add a zero to the transfer function.

Question #2

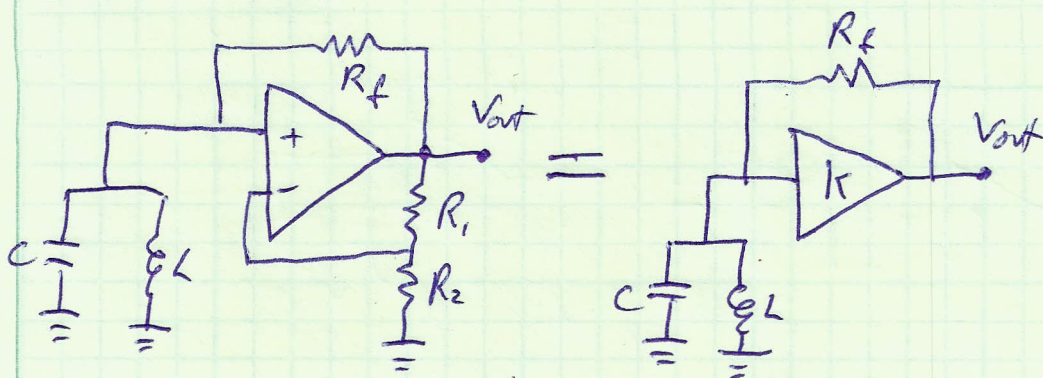


a) $V_{out} = A(V_+ - V_-)$ as $A \rightarrow \infty$

$$V_{out} = A(V_{in} - \frac{R_2}{R_1 + R_2} V_{out})$$

$$V_{out} (1 + A \frac{R_2}{R_1 + R_2}) = A V_{in}$$
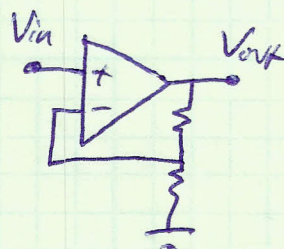
$$K = \frac{V_{out}}{V_{in}} = \frac{A}{1 + A \frac{R_2}{R_1 + R_2}} \text{ as } A \rightarrow \infty$$



$$K = \frac{R_1 + R_2}{R_2}$$

b)


$$A = K$$

$$B = -V_x / V_{out}$$

$$\frac{V_x}{Z_p} + \frac{V_x - V_{out}}{R_f} = 0$$

$$V_x (\frac{1}{Z_p} + \frac{1}{R_f}) = \frac{V_{out}}{R_f}$$
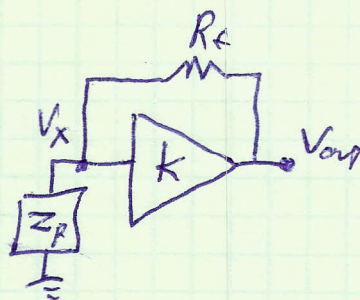
$$B = -\frac{V_x}{V_{out}} = \frac{-1}{R_f (\frac{1}{Z_p} + \frac{1}{R_f})} = \frac{-Z_p}{Z_p + R_f}$$




$$Z_p = \frac{1}{sL + 1/sL} = \frac{sL}{1 + s^2 LC}$$

$$AB = \frac{-K sL / (1 + s^2 LC)}{sL / (1 + s^2 LC) + R_f} = \frac{-K sL / R}{1 + sL/R + s^2 LC}$$

c) at $\omega = \omega_0 = \frac{1}{\sqrt{LC}}$, $AB = \frac{-j\omega_0 K L / R}{1 + j\omega_0 L / R - 1} = -K$

oscillator: $AB = -1$, $K = 1$, $R_1 = 0$ and $R_2 = \infty$ or any value

Question #3

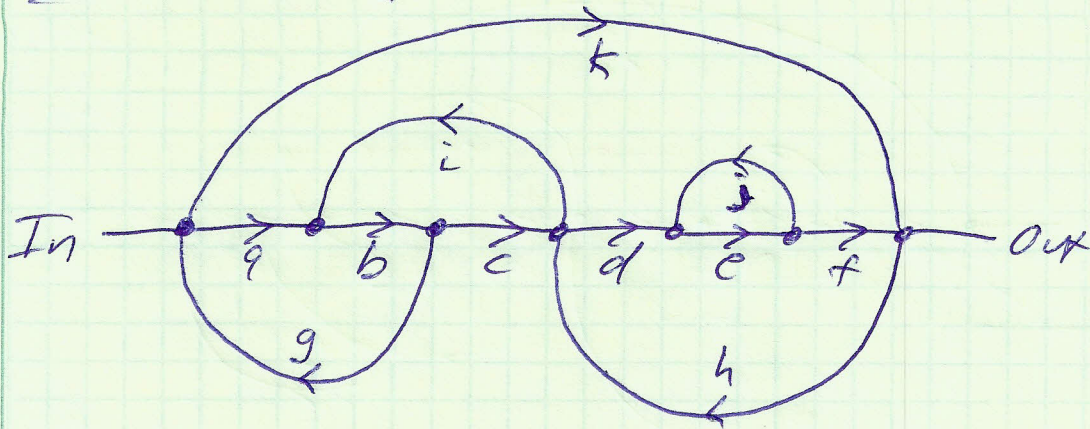

a) $\Delta = 1 - abg - bci - defh - ej - khig$
 $+ abgej + bciej + abgdefh + khigcej$


b) two forward paths = k and $abcdef$

c) $H = \frac{abcdef + k(1 - bci - ej + bciej)}{\Delta}$

$H = \frac{abcdef + k(1 - bci - ej + bciej)}{1 - abg - bci - defh - ej - khig + abgej + bciej + abgdefh + khigcej}$

Question #4

a)

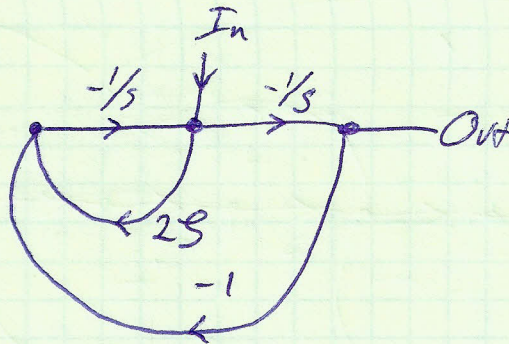

b) $\Delta = 1 + 2s/s + 1/s^2$

$$H = \frac{-1/s}{1 + 2s/s + 1/s^2} = \frac{-s}{1 + 2s + s^2} \rightarrow \text{band-pass response}$$

c)

