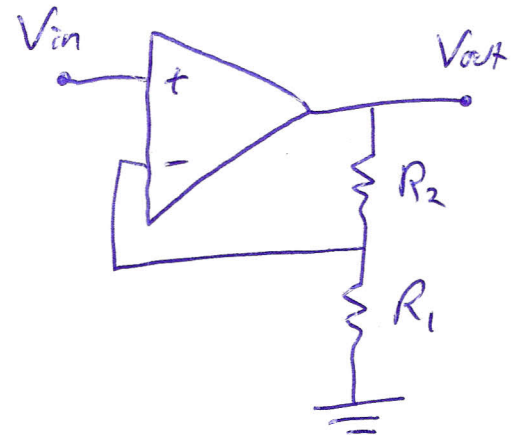


Question #1


- Sketch two non-trivially distinct ways to make a band-pass filter using a capacitor, an inductor and a resistor.
- Calculate its transfer function for both circuits. Identify ω_0 and ζ .
- Draw a Bode plot of the transfer function using a straight-line approximation. Identify all relevant features - slopes, phases, peak locations and values.

Question #2

- For the circuit shown at right, derive the transfer function for an op-amp with gain A .
- Now assuming $A=G/s$, and a differential input resistance of R_d , derive the capacitance seen at the input.
- Next, assuming $A=G/s$, and an output resistance of R_o , derive the inductance seen at the output.

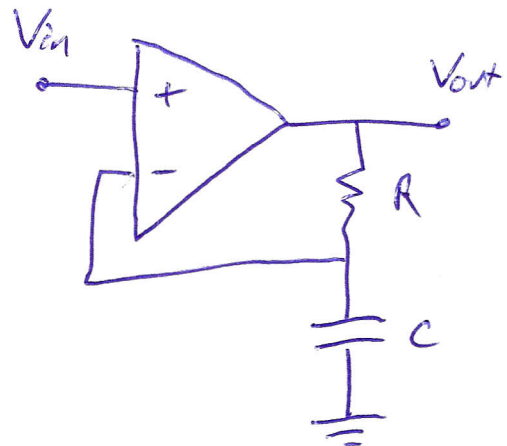
Question #3

- For the circuit shown at right, assuming $A = \frac{G}{s} \times \frac{1}{1+s\tau}$ find the loop gain.
- If $G=10^8$ rad/sec, $\tau=10^{-8}$ sec, $R=1\text{k}\Omega$, $C=100$ pF, draw a Bode plot of the loop gain using a straight line approximation, and estimate the phase margin.
- Where would you add a resistor to improve the phase margin, and why? What value of resistance would you choose?



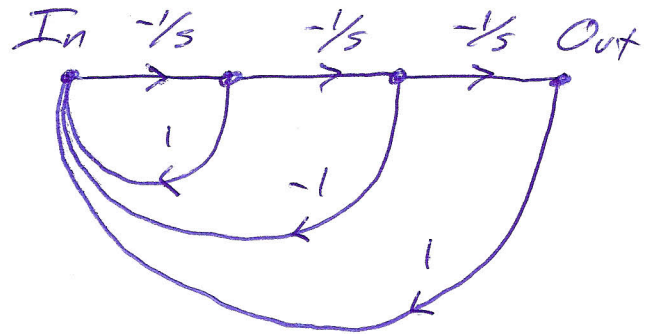
Question #4

- Use Mason's gain formula to calculate the transfer function of the signal flow diagram shown at right.
- Draw an alternative signal flow diagram that implements the identical transfer function.
- Draw a circuit that implements the signal flow diagram at right using op-amp integrators and summing circuits.



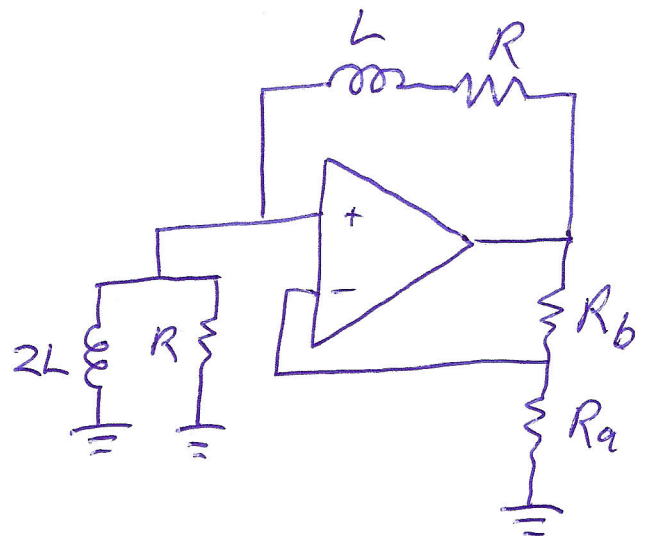Question #5

- Calculate the loop gain for the circuit shown at right for the non-inverting input to the op-amp.
- Find the condition for this circuit to work as an oscillator.
- For this condition, sketch a Nyquist plot of the loop gain.



Question #6

- For the circuit shown at right, assume that the op-amp outputs saturate at 10 volts. Find the relationship among the circuit components that will cause the output at node A to have an amplitude of 5 volts.
- Find the relationship among the circuit components that will cause this circuit to oscillate at a frequency of 1 MHz.
- For the conditions above, sketch the voltage at nodes A and B in the time domain.

