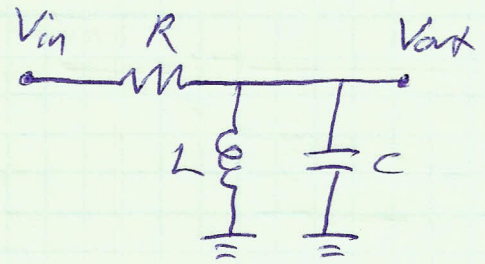
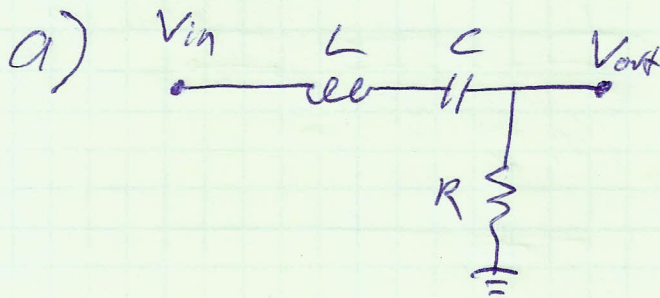


Question 1

or

$$b) \quad H(s) = \frac{R}{R + sL + \frac{1}{sC}}$$

$$H(s) = \frac{sCR}{1 + sCR + s^2LC}$$

$$\boxed{\omega_0 = \frac{1}{\sqrt{LC}}}$$

$$\frac{2\beta}{\omega_0} = CR \rightarrow \boxed{\beta = \frac{R}{2} \sqrt{\frac{C}{L}}}$$


$$H(s) = \frac{1}{sC + \frac{1}{sL} + R}$$

$$= \frac{1}{1 + sCR + \frac{R}{sL}}$$

$$H(s) = \frac{s \frac{L}{R}}{1 + s \frac{L}{R} + s^2 LC}$$

$$\boxed{\omega_0 = \frac{1}{\sqrt{LC}}}$$

$$\frac{2\beta}{\omega_0} = \frac{L}{R} \rightarrow \boxed{\beta = \frac{1}{2R} \sqrt{\frac{L}{C}}}$$

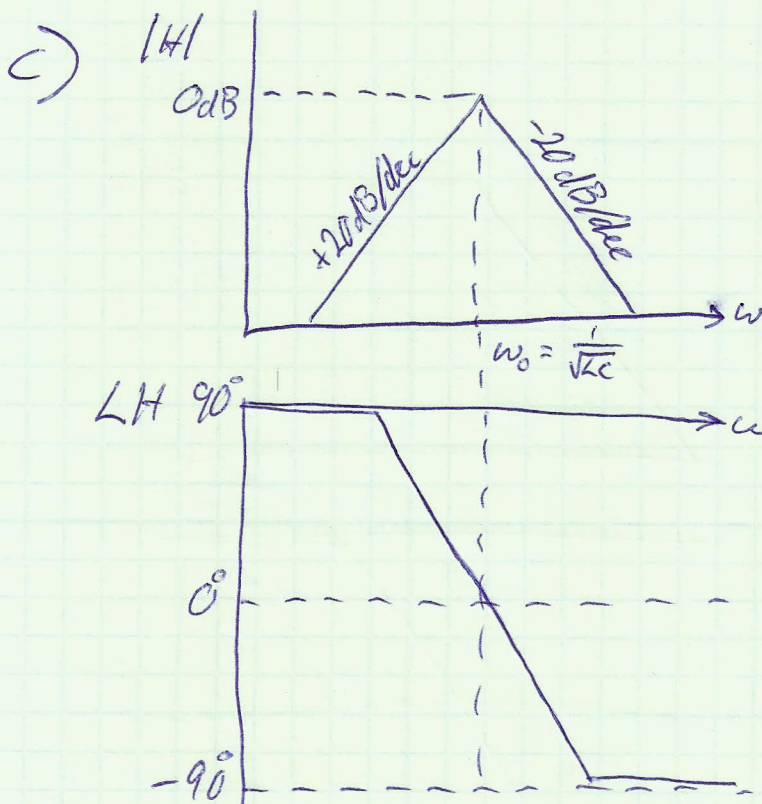

Question 2

$$a) V_- = B V_{out}, \quad B = \frac{R_1}{R_1 + R_2}$$

$$V_{out} = A(V_+ - V_-) = A(V_{in} - B V_{out})$$


$$V_{out}(1 + AB) = A V_{in}$$

$$\boxed{\frac{V_{out}}{V_{in}} = \frac{A}{1 + AB}}$$

$$\text{or } \frac{V_{out}}{V_{in}} = \frac{A}{1 + A \frac{R_1}{R_1 + R_2}}$$

$$b) I = \frac{V_{in} - B V_{out}}{R_d}$$
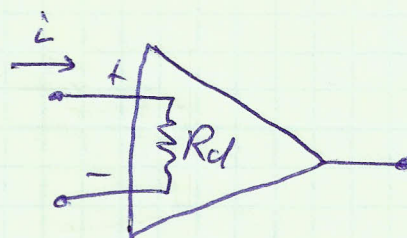
$$I = \frac{V_{in} - \frac{AB}{1+AB} V_{in}}{R_d}$$



$$\frac{V_{in}}{I} = R_d \cdot \frac{1}{1 - \frac{AB}{1+AB}} = R_d \frac{1+AB}{1+AB-AB} = R_d(1+AB)$$


$$Z_{in} = R_d \left(1 + \frac{GB}{s}\right) = R_d + \frac{1}{s C_{eff}}$$

$$\boxed{C_{eff} = \frac{1}{GB R_d}}$$

$$\text{or } \frac{1}{G R_d} \cdot \frac{R_1 + R_2}{R_1}$$

$$c) V_{oc} = V_{out} = \frac{A}{1+AB} V_{in}$$
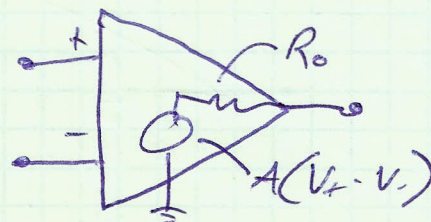
$$I_{sc} = A(V_+ - V_-) / R_o = A V_{in} / R_o$$



$$Z_{out} = \frac{V_{oc}}{I_{sc}} = \frac{\frac{A V_{in}}{1+AB}}{\frac{A V_{in}}{R_o}} = \frac{R_o}{1+AB} = \frac{1}{\frac{1}{R_o} + \frac{GB}{s}} = \frac{1}{\frac{1}{R_o} + \frac{1}{s L_{eff}}}$$


$$\boxed{L_{eff} = \frac{R_o}{GB}}$$

$$\text{or } \frac{R_o}{G} \cdot \frac{R_1 + R_2}{R_1}$$

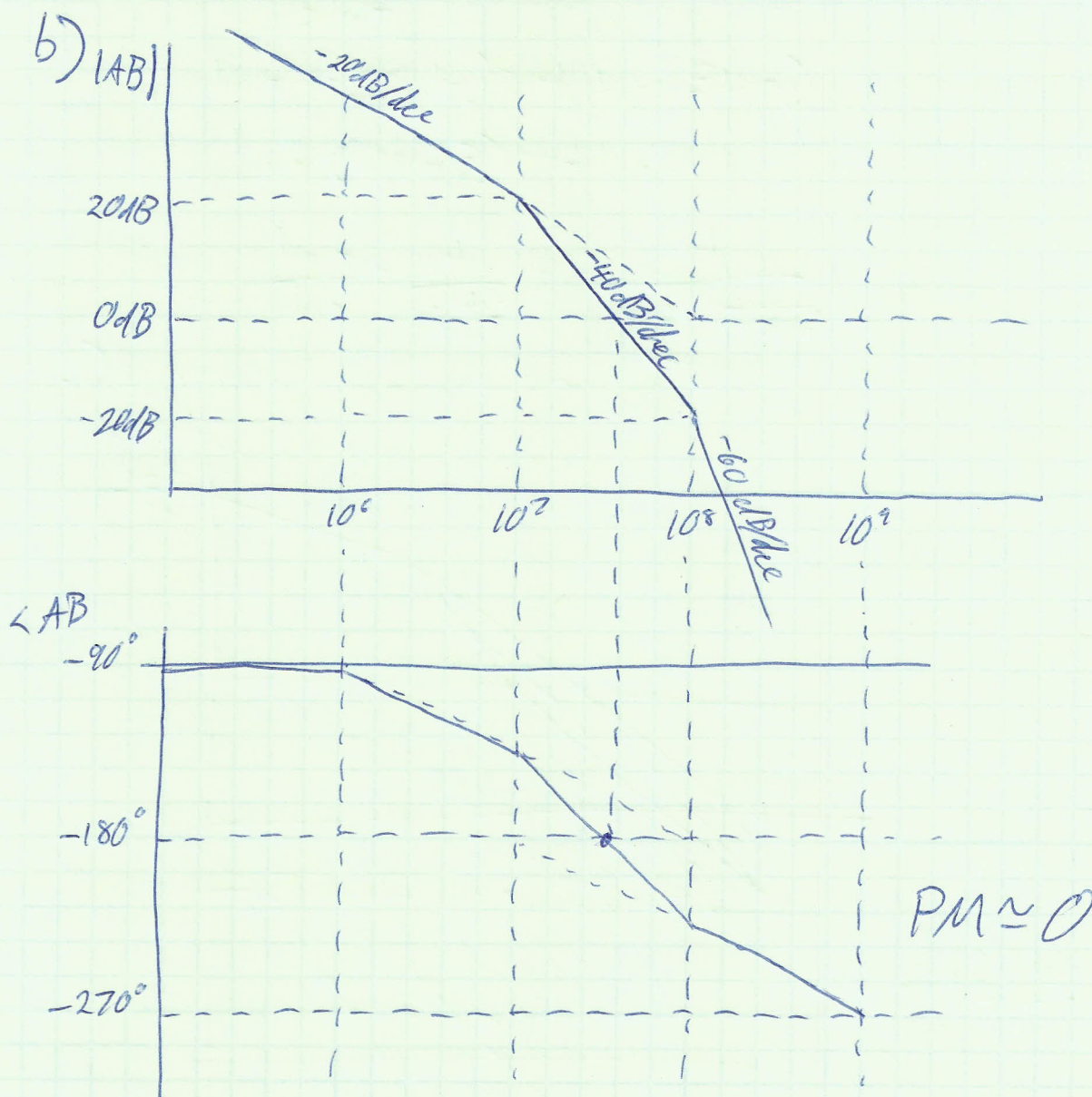
Question 3

$$a) B = \frac{1/sC}{R + 1/sC} = \frac{1}{1 + sCR}$$

$$AB = \frac{G}{s} \cdot \frac{1}{1 + sC} \cdot \frac{1}{1 + sCR}$$



c)

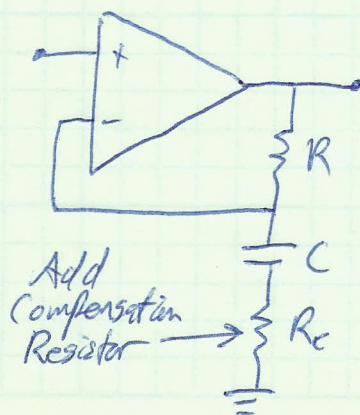

$$B = \frac{1/sC + R_c}{1/sC + R_c + R} = \frac{1 + sCR_c}{1 + sC(R_c + R)}$$

This adds a zero to the transfer function
at $\frac{1}{CR_c} \rightarrow$ choose near unity gain frequency

$$\frac{1}{CR_c} = 3 \times 10^7 \rightarrow R_c \approx \frac{1}{3 \times 10^7 \times 10^{-10}}$$

$$R_c \approx 300 \Omega$$

Question 4



a) forward path = $-\frac{1}{s^3}$

$$\Delta = 1 + \frac{1}{s} + \frac{1}{s^2} + \frac{1}{s^3}$$

$$H(s) = \frac{-\frac{1}{s^3}}{1 + \frac{1}{s} + \frac{1}{s^2} + \frac{1}{s^3}}$$

$$H(s) = \frac{-1}{1 + s + s^2 + s^3}$$

b) Using flow reversal theorem:

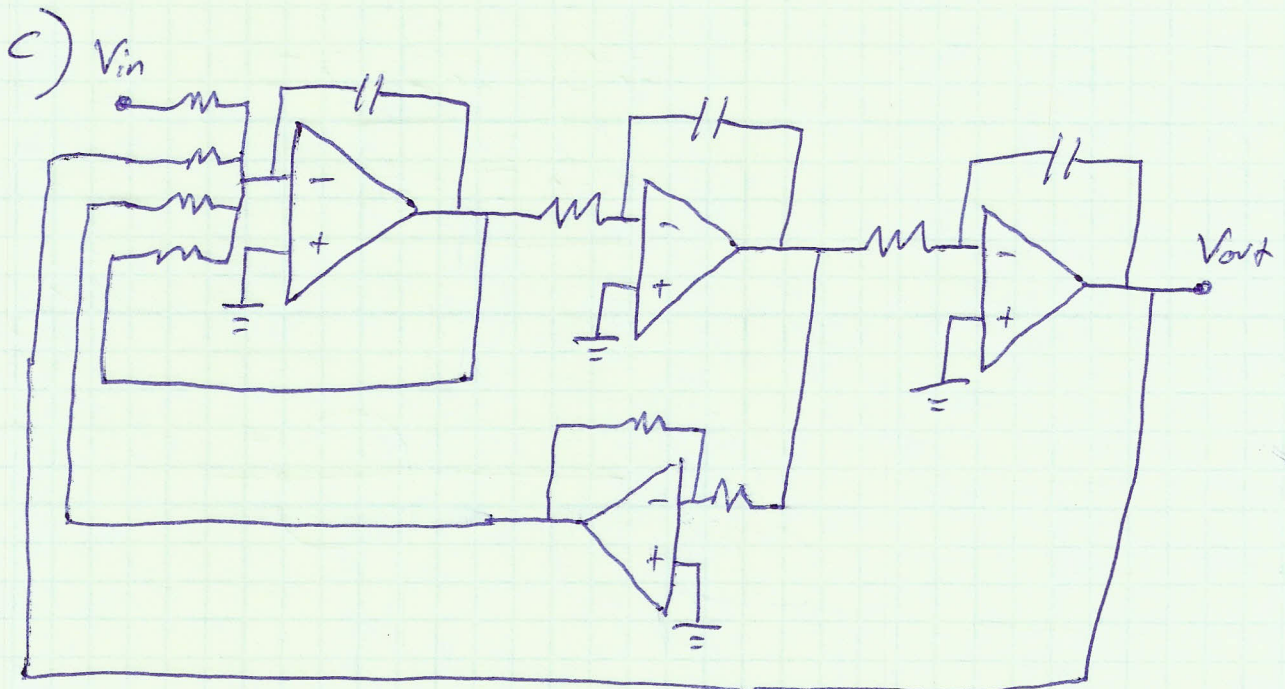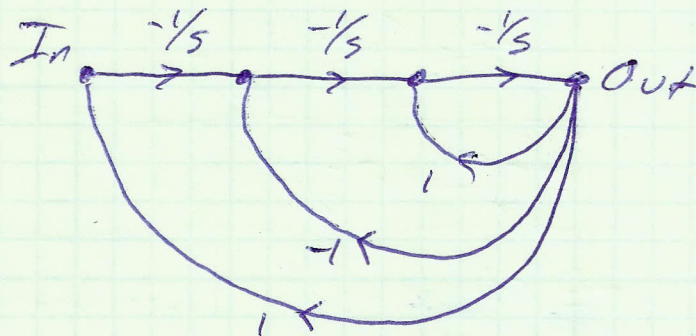

Question 5

a) gain $A = \frac{R_g + R_b}{R_g}$,

feedback term $B = \frac{1}{\frac{1}{s2L} + \frac{1}{R}}$

$$B = \frac{-1}{1 + \left(\frac{1}{s2L} + \frac{1}{R}\right)(sL + R)} = \frac{-1}{1 + \frac{1}{2} + \frac{sL}{R} + \frac{R}{s2L} + 1}$$


$$B = \frac{-\frac{s2L}{R}}{1 + \frac{s}{2} + \frac{s2L}{R} + \frac{s^2 2L^2}{R^2}}$$

$$AB = \frac{-\left(\frac{R_g + R_b}{R_g}\right) \frac{s2L}{R}}{1 + \frac{s}{2} + \frac{s2L}{R} + \frac{s^2 2L^2}{R^2}}$$

b) at resonance, $-\left(\frac{R_g + R_b}{R_g}\right) \frac{2L}{R} = -\frac{sL}{R}$

$$2R_g + 2R_b = sR_g$$

$$R_b = \frac{3}{2} R_g$$

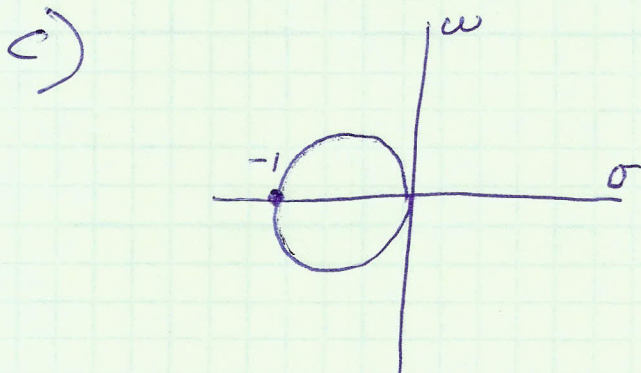

Question 6

a) Schmitt trigger switches when $V_+ = 0$

$$\frac{V_+ - V_A}{R_1} + \frac{V_+ - V_B}{R_2} = 0 \quad \frac{-V_A}{R_1} = \frac{V_B}{R_2}$$

$$V_A = -5V \quad V_B = 10V$$

$$\boxed{R_2 = 2R_1}$$

b) Integrator: $\frac{V_- - V_A}{1/C} + \frac{V_- - V_B}{R_3} = 0 \quad V_- = 0$

$$\frac{V_A}{1/C} = \frac{-V_B}{R_3} \quad \frac{V_A}{V_B} = \frac{-1}{sCR_3}$$

$$V_A(t) = \frac{-1}{R_3 C} \int_0^t V_B(z) dz + V_A(0)$$

$$\frac{1}{R_3 C} \times 10V \times 0.5 \times 10^{-6}s = 10V$$

$$\boxed{R_3 C = 0.5 \times 10^{-6} \text{ sec}}$$

