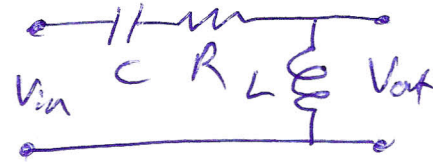


- For all numerical answers, be sure to include units
- For plots, use a straight-line approximation.
- Label all relevant values for frequency, magnitude, phase, slope, intercept, etc.

Question #1

For the circuit shown at right:


- Write an expression for the transfer function in terms of R , L , and C , and identify the type of filter.
- Assume the inductor has a value of $100 \mu\text{H}$. Choose values of R and C that produce a 2nd order Butterworth filter with a cutoff frequency of $\omega_0 = 10^6$ rad/sec.
- Sketch a Bode plot of this transfer function.

Question #2

The Sallen-Key filter shown at right has a transfer function of


$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + sC_1(R_1 + R_2) + s^2R_1R_2C_1C_2}$$

- Assuming that $R_1 = R_2$, and $C_1 = C_2$, find the cut-off frequency and damping coefficient.
- Now also assume that the op-amp has a finite output resistance R_o which is small compared to the other resistors. Derive an expression for the gain in the high-frequency limit.
- If $R_o = 100 \Omega$, what resistor values ensure a high-frequency gain of less than -40dB?

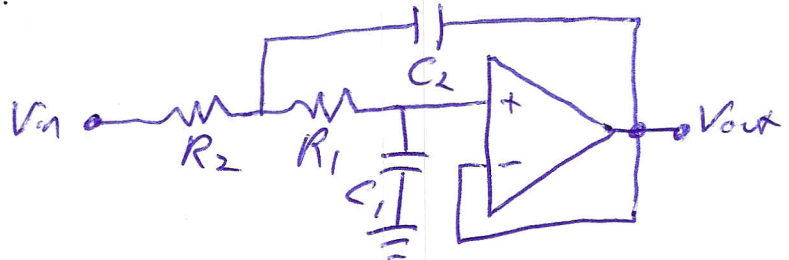Question #3

For the voltage follower circuit,

- Assuming the op-amp has finite gain, A , but is otherwise ideal, derive an expression for the transfer function of this circuit.
- Next, assuming that the op-amp has frequency-dependent gain $A(s) = G/s$ and finite differential input resistance R_d , derive an expression for the input impedance of the circuit.
- Describe the input impedance in terms of an effective circuit, and find the value of any effective circuit parameters for $R_d = 10\text{k}\Omega$, $G = 10^6$ rad/sec, $R_1 = 10\text{k}\Omega$, $R_2 = 90\text{k}\Omega$

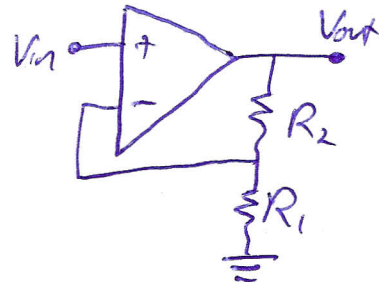Question #4

For the circuit shown at right, assume the op-amp gain is $A(s) = G/s$

- Write an expression for the loop gain, AB .
- Sketch a Bode plot of the loop gain for $R = 20 \Omega$, $L = 100 \mu\text{H}$, $C = 1 \mu\text{F}$, and $G = 10^6$ rad/sec.
- Sketch a Nyquist plot of the loop gain, and explain why it is stable or unstable.

