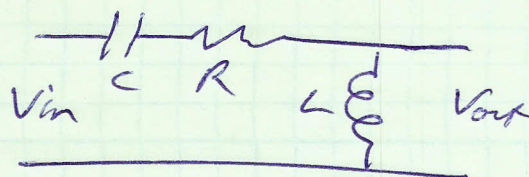


Question #1

$$a) \frac{V_{out}}{V_{in}} = \frac{sL}{sL + R + \frac{1}{sC}} = \frac{s^2 LC}{1 + sCR + s^2 LC} \quad \text{high-pass}$$

$$b) \omega_0 = \frac{1}{\sqrt{LC}} = 10^6$$


$$C = \frac{1}{L \cdot 10^{12}} = \frac{1}{10^{-4} \cdot 10^{12}} = 10^{-8} \quad \underline{C = 100 \mu F}$$

$$\text{Butterworth} \rightarrow \zeta = \frac{1}{\sqrt{2}}$$

$$\frac{2\zeta s}{\omega_0} = sCR$$

$$R = \frac{\sqrt{2}}{10^6 \cdot 10^{-8}} \approx 140$$

$$\underline{R = 140 \Omega}$$

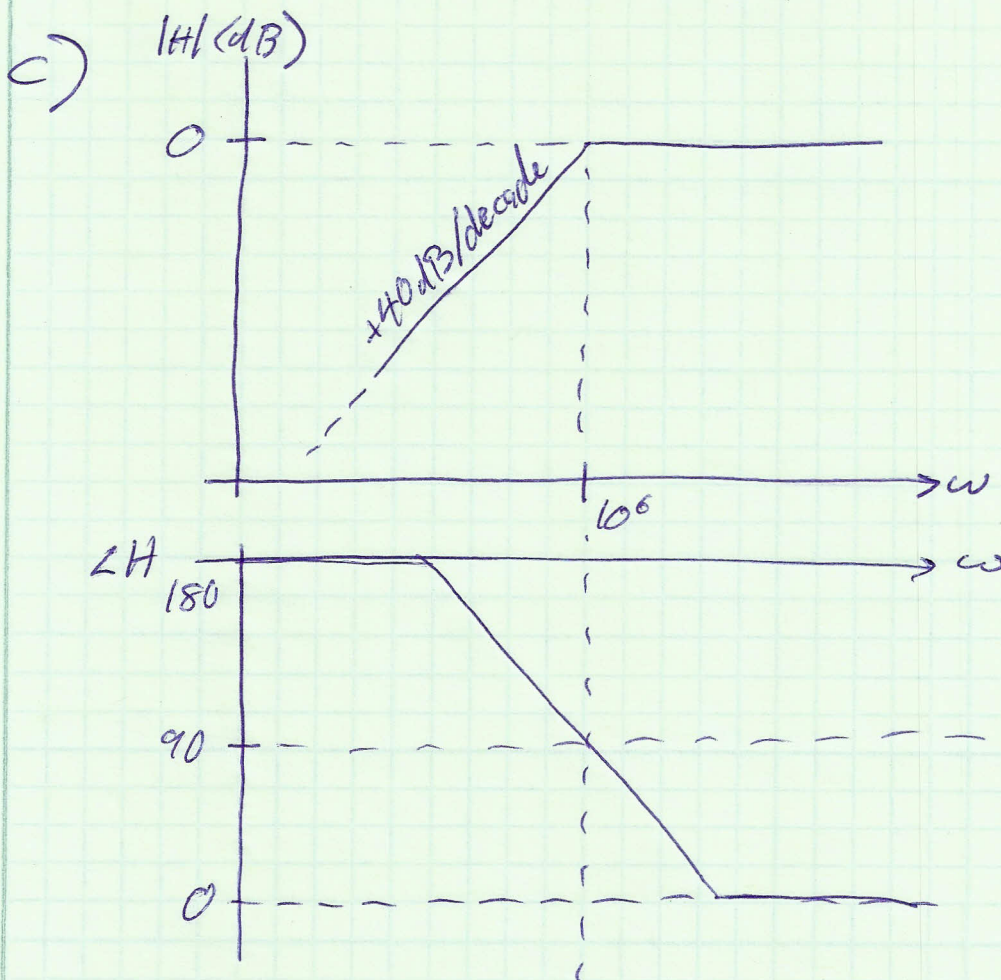


Question #2

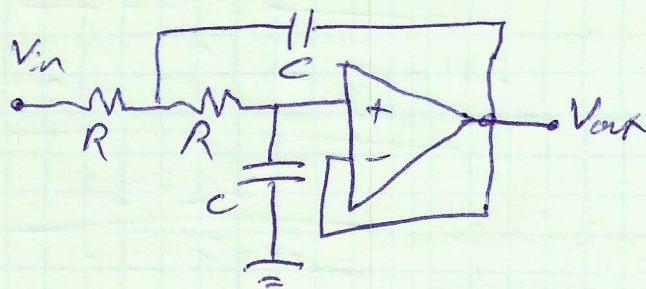a) $R_1 = R_2 = R$

$C_1 = C_2 = C$

$$\omega_0 = \frac{1}{\sqrt{R^2 C^2}} = \frac{1}{RC}$$




$$\frac{2\theta_s}{\omega_0} = \theta_s C (2R)$$

$$\theta_s = CR \cdot \frac{1}{RC}$$

$$\theta_s = 1, \omega_0 = \frac{1}{RC}$$

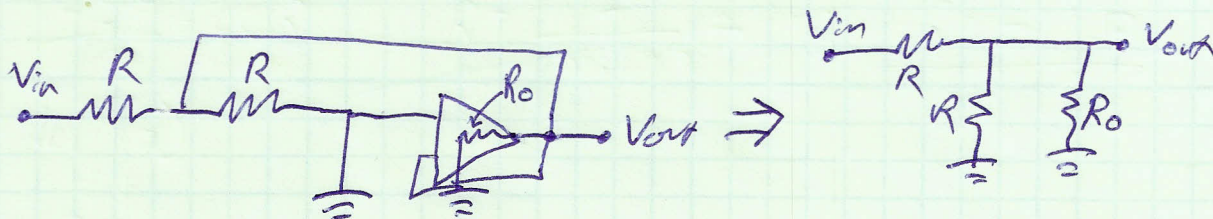b) $C \rightarrow$ short and $A \rightarrow 0$ for $\omega \rightarrow \infty$



$$\frac{V_{out}}{V_{in}} \approx \frac{R_o}{R_o + R} \approx \frac{R_o}{R}$$

c) $\left| \frac{V_{out}}{V_{in}} \right| \rightarrow -40\text{dB}$

$$\left| \frac{V_{out}}{V_{in}} \right|^2 = \left(\frac{R_o}{R} \right)^2 = 10^{-4}$$

$$\frac{R_o}{R} = 10^{-2}$$

$$R = 100 R_o = 10\text{k}\Omega$$

high frequency gain $\leq -40\text{dB}$ for $R \geq 10\text{k}\Omega$

Question #3

$$a) V_- = V_{out} \cdot \frac{R_1}{R_1 + R_2} = B V_{out}$$


$$B = \frac{R_1}{R_1 + R_2}$$

$$V_{out} = A(V_+ - V_-)$$

$$V_{out} = A(V_{in} - B V_{out})$$

$$V_{out}(1 + AB) = A V_{in}$$
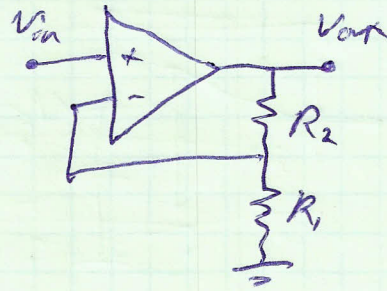
$$\frac{V_{out}}{V_{in}} = \frac{A}{1 + AB} \text{ where } B = \frac{R_1}{R_1 + R_2}$$




$$b) I_{in} = \frac{V_{in} - B V_{out}}{R_d}$$

$$= \frac{V_{in}}{R_d} \left(1 - \frac{AB}{1 + AB} \right)$$

$$= \frac{V_{in}}{R_d} \left(\frac{1}{1 + AB} \right)$$

$$Z_{in} = \frac{V_{in}}{I_{in}} = R_d(1 + AB)$$
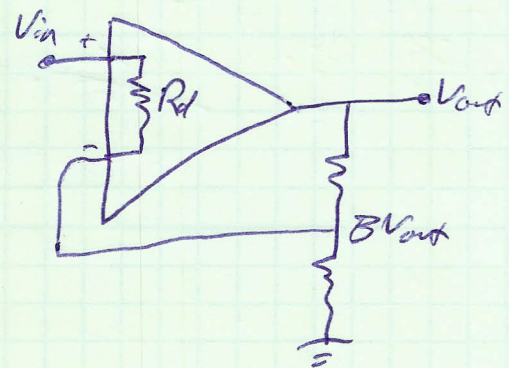
$$Z_{in} = R_d \left(1 + \frac{GB}{s} \right)$$



c) Input impedance is series RC circuit

$$Z_{in} = R_d + \frac{R_d GB}{s} = R_d + \frac{1}{s C_{eff}}$$

$$C_{eff} = \frac{1}{R_d GB}$$

$$C_{eff} = \frac{1}{10^4 \cdot 10^6 \cdot 10^{-1}} = 10^{-9}$$


$$\underline{C_{eff} = 1 \text{ nF}}$$

Question #4




$$a) B = \frac{1/sC}{1/sC + R + sL}$$

$$B = \frac{1}{1 + sRC + s^2LC}$$

$$AB = \frac{G}{s(1 + sRC + s^2LC)}$$

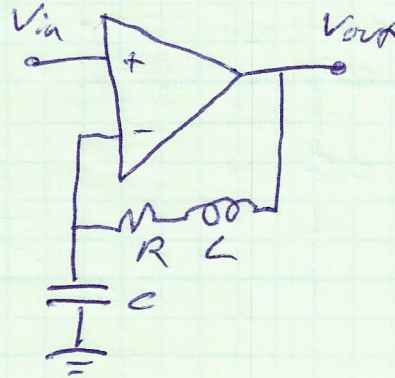
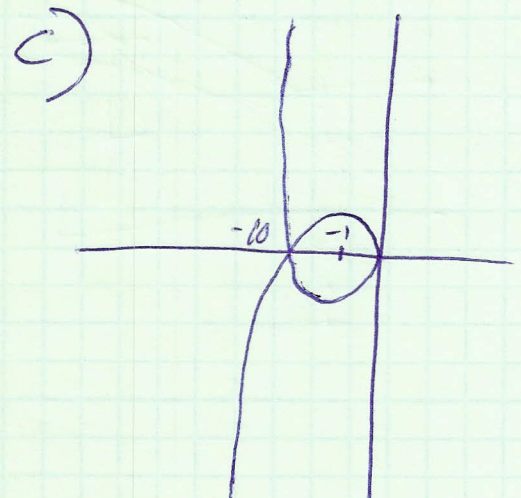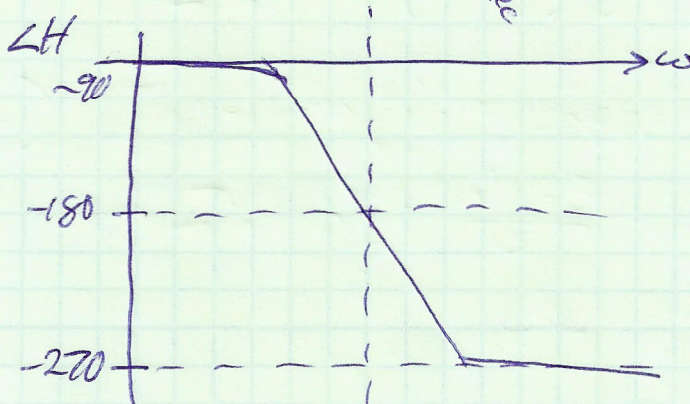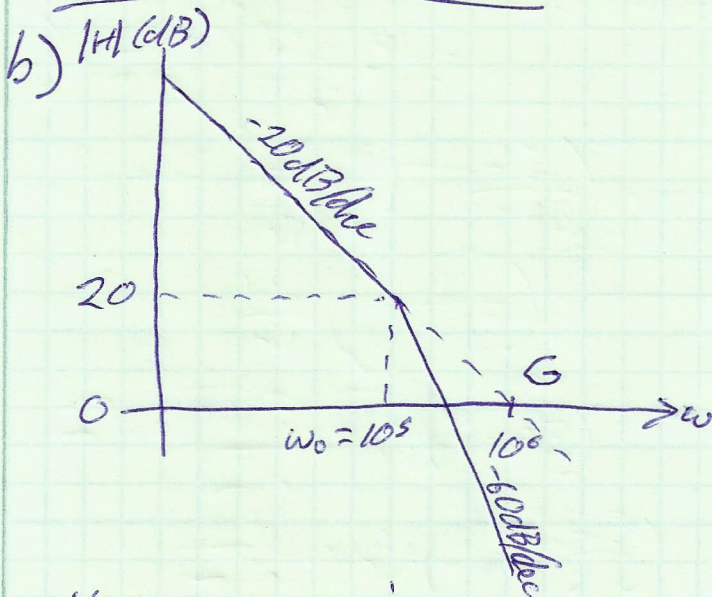
$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-4} \cdot 10^{-6}}} = 10^5$$



Nyquist plot encircles
-1 so circuit is
unstable