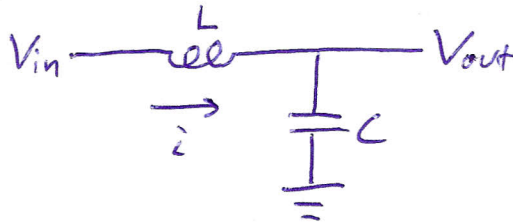


Question #1

- Sketch a differentiator circuit using an op-amp, a resistor, and an inductor.
- Assuming an ideal op-amp, derive the transfer function, and demonstrate that it is a differentiator.
- Now assuming the op-amp has gain $A=G/s$, show that the transfer function is second-order.


Question #2

- Write the current/voltage equations that govern the behavior of the circuit shown below.
- Express the equations as a signal flow diagram where currents and voltages appear as node values.
- Use Mason's gain equation to find the transfer function of the circuit from the signal flow diagram.

Question #3

The circuit below has a time delay of τ in the feedback path.

- Find the transfer function using a 1st order Pade approximation for the time delay.
- Now assuming that the op-amp has a gain of $A=G/s$, show that this is a second order system.
- If $G=10^5$ rad/sec, what is the shortest time delay τ that will cause the circuit to be unstable?

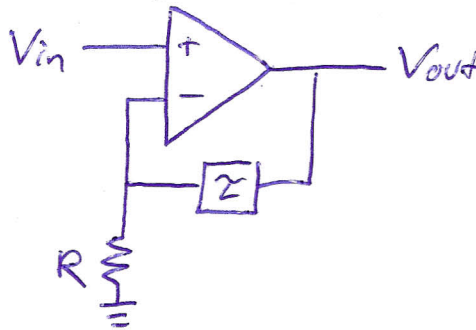Question #4

- Convert the circuit diagram shown below to that of a simple amplifier with positive feedback.
- Find an expression for the loop gain AB of your circuit as a function of circuit parameters.
- What is the relationship between the resistor values for this circuit to work as an oscillator?

