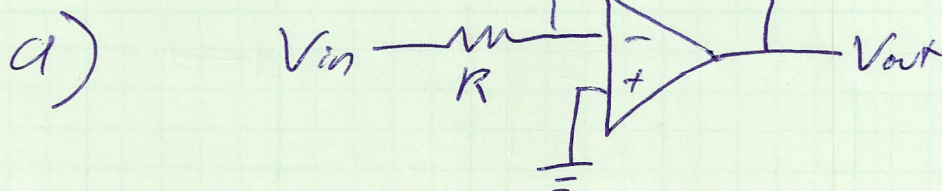


Question 1

b)

$$\frac{V_- - V_{in}}{R} + \frac{V_- - V_{out}}{sL} = 0 \quad V_- = V_+ = 0$$

$$-\frac{V_{in}}{R} = \frac{V_{out}}{sL} \rightarrow \boxed{\frac{V_{out}}{V_{in}} = -\frac{sL}{R}} \text{ differentiator}$$

note, $\frac{df(t)}{dt} \longleftrightarrow sF(s) - f(0)$

c)

$$\frac{V_- - V_{in}}{R} + \frac{V_- - V_{out}}{sL} = 0, \quad V_{out} = A(V_+ - V_-) \rightarrow V_- = -\frac{V_{out}}{A}$$

$$\frac{-\frac{V_{out}}{A} - V_{in}}{R} + \frac{-\frac{V_{out}}{A} - V_{out}}{sL} = 0$$

$$V_{out} \left(\frac{sL}{R} \right) + AV_{in} \left(\frac{sL}{R} \right) + V_{out} (1+A) = 0$$

$$V_{out} \left(1+A + \frac{sL}{R} \right) = -AV_{in} \left(\frac{sL}{R} \right)$$

$$\frac{V_{out}}{V_{in}} = -\frac{sL}{R} \left(\frac{A}{1+A + \frac{sL}{R}} \right) = -\frac{sL}{R} \left(\frac{G/s}{1+G/s + sL/R} \right)$$


$$\boxed{\frac{V_{out}}{V_{in}} = -\frac{sL}{R} \cdot \left(\frac{1}{1 + s/G + s^2L/GR} \right)}$$

Second order

Question 2

$$a) \quad i = \frac{V_{in} - V_{out}}{sL}$$

$$V_{out} = \frac{i}{sC}$$

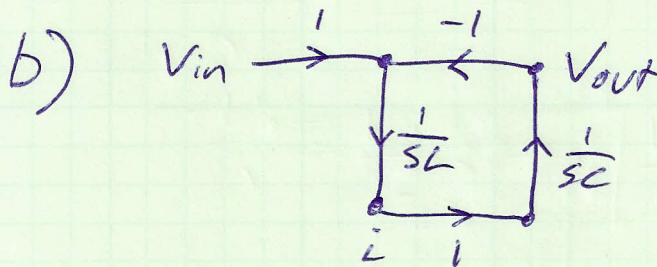

$$c) \quad \Delta = 1 + \frac{1}{s^2 LC}$$

forward path = $\frac{1}{s^2 LC}$

$$\frac{V_{out}}{V_{in}} = \frac{\frac{1}{s^2 LC}}{1 + \frac{1}{s^2 LC}}$$

$$\boxed{\frac{V_{out}}{V_{in}} = \frac{1}{1 + s^2 LC}}$$

Question 3

$$a) V_- = V_{out} \cdot \frac{1 - s\tau/2}{1 + s\tau/2}$$

$$V_{out} = A(V_+ - V_-) = A\left(V_{in} - V_{out} \frac{1 - s\tau/2}{1 + s\tau/2}\right)$$

$$V_{out} \left(1 + A \frac{1 - s\tau/2}{1 + s\tau/2}\right) = A V_{in}$$

$$\boxed{\frac{V_{out}}{V_{in}} = \frac{A}{1 + A \frac{1 - s\tau/2}{1 + s\tau/2}}}$$

$$\text{or } \frac{V_{out}}{V_{in}} = \frac{1 + s\tau/2}{1 - s\tau/2}$$

okay too (ideal opamp)

$$b) A = G/s \rightarrow \frac{V_{out}}{V_{in}} = \frac{G/s}{1 + \frac{G}{s} \cdot \frac{1 - s\tau/2}{1 + s\tau/2}}$$

$$\frac{V_{out}}{V_{in}} = \frac{1 + s\tau/2}{\frac{s}{G}(1 + s\tau/2) + 1 - s\tau/2}$$

$$\boxed{\frac{V_{out}}{V_{in}} = \frac{1 + s\tau/2}{1 + s\left(\frac{1}{G} - \frac{\tau}{2}\right) + \frac{s^2\tau}{2G}}}$$

second order

c) unstable when s is negative

$$\frac{1}{G} - \frac{\tau}{2} < 0$$


$$\tau > \frac{2}{G}$$

$$\text{for } G = 10^5 \text{ rad/sec}$$

$$\text{unstable when } \underline{\tau > 2 \times 10^{-5} \text{ sec}}$$

Question 4

a)

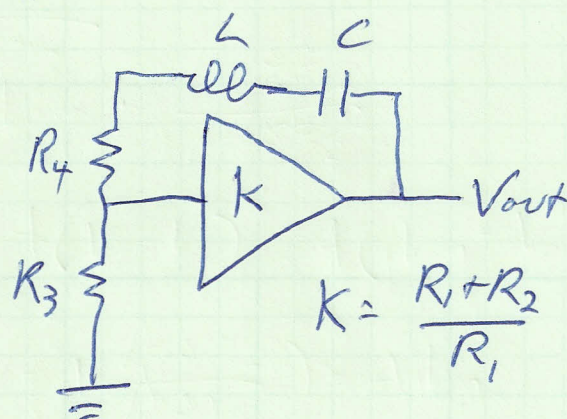

$$b) \quad V_{in} = V_{out} - \frac{R_3}{R_3 + R_4 + sL + 1/sC}$$

$$AB = \frac{-KR_3}{R_3 + R_4 + sL + 1/sC} = \frac{-(R_1 + R_2) \frac{R_3}{R_1}}{R_3 + R_4 + sL + 1/sC}$$

c) oscillator when $AB = -1$

$$AB = \frac{-sC(R_1 + R_2) \frac{R_3}{R_1}}{1 + sC(R_3 + R_4) + s^2LC}$$

resonant frequency $\omega_0 = \frac{1}{\sqrt{LC}}$ for $s = j\omega_0$

$$AB = \frac{-j\omega_0 C(R_1 + R_2) \frac{R_3}{R_1}}{1 + j\omega_0 C(R_3 + R_4) - 1}$$

$$\frac{-(R_1 + R_2) \frac{R_3}{R_1}}{R_3 + R_4} = -1 \quad \text{for oscillator}$$

$$\boxed{(R_1 + R_2)R_3 = (R_3 + R_4)R_1}$$