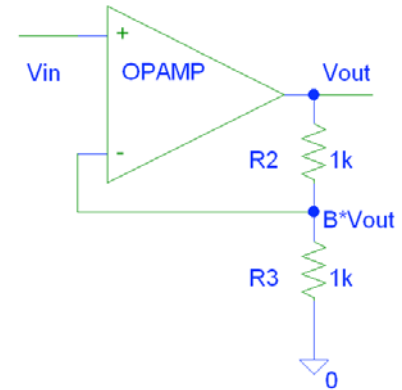


The objective of this assignment is to study the follower feedback circuit when implemented with real opamps. Ideal opamps have infinite gain, infinite input impedance, and zero output impedance. Real opamps are very complex, usually consisting of 10^3 's of transistors and many passive elements. However a first-order VCVS model captures much of the important behavior of a real opamp. In this model we define gain $A(s) = G/s$ or $A(\omega) = G/j\omega$ where G is called the unity-gain bandwidth. It is always greater than 1 MHz, and sometimes as high as 1 GHz. The input impedance is $R_D > 1 \text{ M}\Omega$ and the output impedance is $R_O < 100 \Omega$.

A. Analysis:

1. Unloaded: The normal follower-with-gain circuit is sketched to the right. Here we assume that $R_O \ll R_2 + R_3$ and $R_D \gg R_2$ in parallel with R_3 . If R_2 and R_3 are of the order of 10 K, this will be the case. With this simplification $B = R_3/(R_2+R_3)$ and it is easy to calculate: the transfer function $H(s) = A(s)/(1 + A(s)B)$; the input impedance $Z_{IN}(s) = R_D(1 + A(s)B)$; and the output impedance $Z_{OUT}(s) = R_O/(1 + A(s)B)$.



(a) Write rationalized polynomial expressions for $H(s)$, $Z_{IN}(s)$, and $Z_{OUT}(s)$ in terms of G , B , R_D and R_O .

(b) Show that $H(s)$ is the transfer function of a low-pass filter with a dc gain of $1/B$ and a -3dB bandwidth of $G*B$. Thus the product of the dc gain and the bandwidth is $(1/B)*G*B = G$. This is the origin of the useful rule “the gain-bandwidth product of a feedback amplifier is constant.” One must remember that this “rule” only applies to the first-order model of the opamp.

(c) Show that $Z_{IN}(s)$ can be modeled as a capacitor in series with R_D . So even when A is large, Z_{IN} is not resistive, it is capacitive.

(d) Show that $Z_{OUT}(s)$ can be modeled as an inductor in parallel with R_O . So even when A is large Z_{OUT} is not resistive, it is inductive.

2. With Capacitive Load: These results do not mean that the follower is not useful as a buffer, simply that it may behave in unexpected ways. For example when loaded by a large capacitance it may behave like a resonant circuit rather than the ideal voltage source that one might have expected.

(a) Write the transfer function of the circuit when a capacitor C_L is connected from the output to ground. Here R_O and C_L act like a low-pass filter. Put your expression in normalized form. You will find that the denominator of the transfer function is looks exactly like an RLC resonant circuit. Find ω_0 and ζ in terms of G , B , and $\tau = R_O C_L$.

(b) If the C_L is large, for example if the buffer is driving a long run of coaxial cable, the damping factor can be quite small and the step response will show a great deal of “ringing”. This is a common problem in both analog and digital integrated circuits. In large scale digital systems it can occur in the buffers which drive the system clock to the various logic components. It can be reduced or eliminated by putting a “compensation” resistor R_C in series with C_L . Find the transfer function of the modified circuit. Show that ζ can be adjusted by choosing R_C without making a significant change in the bandwidth ω_0 .

B. Simulations:

1. Unloaded Gain*Bandwidth Product:

(a) Simulate a follower with gain of 1, 3, 10, 30, and 100. For the opamp use a VCVS with a gain $A(s) = G/s$, where $G = 2 \pi 10^6$. The VCVS called ELAPLACE allows you to specify $A(s)$. Measure the -3dB bandwidth in each case. Confirm that the gain*bandwidth product is constant. You can do all the simulations at once using the Parameter property and a Parameter Sweep. Add a Parameter box to your schematic. Enter a parameter called “r” and give it a value of 1k. Then set $R_2 = 10\text{K}$ and $R_3 = \{r\}$. In the analysis setup menu add a Parameter Sweep with a value list. Enter the values of R_3 required to give the gains listed above. Pspice will then do an AC Sweep for each value of r in the list and overplot them all. Make a hard copy of the plot. You will still have to measure the -3dB frequency manually with the cursor.

(b) Repeat the simulation for a follower with gain of 1, 3, 10, 30, and 100 using the macromodel for an uA741 op amp. Remember to connect up the power supplies. Note that the -3dB bandwidth is defined with respect to the dc gain, not the maximum gain. You will see that the gain-bandwidth product is constant for the higher gains, but increases near unity gain. In fact the uA741 has several poles and a right half plane zero. It is the phase lag due to these high frequency “features” which causes the gain-bandwidth product to change. They have other interesting effects too - they can make the follower oscillate under certain conditions.

2. Effect of Capacitive Load: We can test this with a unity-gain follower.

(a) Use the uA741 macromodel in unity gain follower configuration to simulate the step response for load capacitances of 100pf 300pf 1nf 2nf 4nf 6nf and 10nf. Use the PARAM feature to get Pspice to run the entire list at one time and overplot the results. A time range of 0 to 2 μs should be sufficient. Make a hard copy of the plot. You will see that loads larger than 100pf can cause a lot of ringing. The typical capacitance of a coaxial cable is 30pf/ft. So it is easy to get a lot of ringing driving a cable incautiously.

(b) Put a $25\ \Omega$ resistor in series with the load capacitance and rerun the simulation. You will see that it seriously quenches the overshoot. In practice you would adjust the compensation resistor to be as small as possible, consistent with the desired overshoot, because larger resistors will cause a slower rise-time. Generally you would like the shortest feasible rise-time. What is the smallest resistor that will keep the overshoot $< 20\%$ for all loads?

C. Measurements:

1. Unloaded Gain*Bandwidth Product: In this section we will measure the gain bandwidth product of the follower under the same conditions as the simulation in Part 3. The measurements will require some care and the circuit will have to be laid out neatly because the bandwidth is large. Bypass both dc supplies to ground with a 0.1 μF capacitor placed close to the chip. Special care is needed for the feedback when $B=1$. You will not be able to use $R_2=10\text{K}$ and $R_3=\text{some large value}$, because the capacitance on the breadboard is about 6pf to ground and this will cause enough phase shift to greatly increase the ringing (or even make it oscillate). Set $R_2=\text{short circuit}$ and $R_3=\text{open circuit}$ instead. The exact values of the gain are not important – use the closest convenient resistors.

First check the calibration of your scope probe s and adjust if necessary. It will be necessary to respect the “slew-rate limit.” For the uA741 this is about 2 v/us. This means that $|dV_O/dt| < 2\ \text{v/us}$. If $V_O(t) = A \sin(2\pi ft)$ then $dV_O/dt = 2\pi f A \cos(2\pi ft)$. So we need $A < 2 \cdot 10^6 / 2\pi f$ or slew rate limiting will occur and mess up our measurements, e.g. at $f = 1\ \text{Mhz}$ the peak-to-peak $V_O < 0.6\ \text{v}$. If the gain = 100 that means that the input voltage will be only 6 mv. This is low to measure or trigger from and you may need to trigger from the output and use averaging to reduce the noise on the input. It will be necessary to use the 10X probe setting on the output because the 1X probe has considerable capacitance. You can use the 1X probe setting on the input though. Measure the gain-bandwidth product for each of the cases you simulated in Part 3(b). Remember that -3dB is with respect to the dc gain not the peak gain.

2. Capacitive Load: In this section we will measure the effect of a capacitive load on a unity-gain follower, as simulated in section 4. The same precautions against slew rate limiting apply. This means that the input step must be $<< 1\ \text{v}$, and you will need to use the 10X probe setting on the output. You might as well use it on both because both signals will be about the same amplitude. Remember to use $R_2=\text{short circuit}$ and $R_3=\text{open circuit}$ or you will see too much overshoot caused by the bread board.

(a) Measure the overshoot for (roughly) the same capacitances that you used in the simulation. Here the exact values are not important. You may find that the follower actually oscillates with some values of C_L . If it does oscillate the amplitude will be limited by the slew rate, so you won’t necessarily see a large signal. What you might see is a ringing that never dies away. If this happens make a hard copy for your report.

(b) In a practical situation you would have a certain load capacitance, say 3 nf, and you would want to compensate it to get the shortest rise-time consistent with some maximum overshoot, say 20%. Connect a 3 nf load and optimize the compensation resistor. What resistor works best? What was the optimal 10% to 90% rise time? Make a hard copy of the optimized step response.

Don’t forget to photograph your circuit, and include it with your lab report.