

ECE 100 - Electronic Systems Lab

website:Office hours: Tu. 2-4

web.eng.ucsd.edu/ece/groups/electromagnetics/
Classes/ECE100 Fall 2011/index.htm

Class builds on 35, 45, 65

Covers: Filters, feedback, oscillators, other related circuits7 labs: 2 matlab, 5 hardware (Reports ≤ 5 pages)Due at end of class each Thursday

2 midterms: October 20th, November 17th

Grades: 30% labs, 30% midterms, 40% final

Read Rules section of website

- No changes to midterm or final dates/times
- No late labs - after I leave the lecture hall, it's life!
- 24/7 access to labs (EBU2 rm 329 + 333A)
 - must photograph your circuit (instead of signoff sheet)
 - TAs available M 7-10^{Alex}, T 7-10^{Ansrum}, W 4-10 pm (not Friday)
- Note the section on integrity
 - Henry
 - Mahdi


Find a lab partner. One of you email me your names (PID).

Lab access code:

No Book Required, but Sedra & Smith Ch 10, 16, 17 will be useful.

Filters:

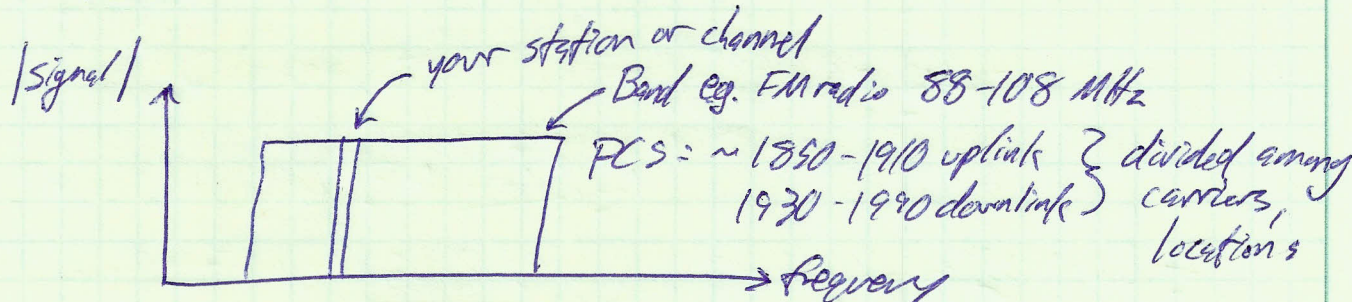- Reduce interference from signals not of interest
 - radio signals, mobile phones, transmit/receive channels, etc
- Reduce noise from outside the band of interest





- Other phones, stations, etc will interfere unless filtered out
 - Noise power is kTB ← Bandwidth
 - ↑ Noise temperature of receiver or antenna
 - ↑ Boltzmann Constant $1.38 \times 10^{-23} \text{ J/K}$
- Reducing bandwidth lowers noise!




$$G_{\text{gain}} = \frac{\text{out}}{\text{In}}$$

(V, I, ...)

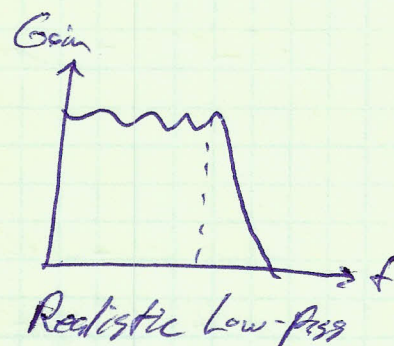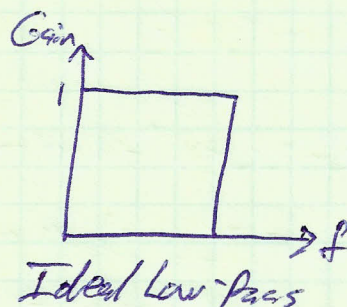


Passive Filter Building Blocks:

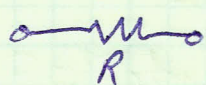


$$V = IR$$

$$Z = R$$

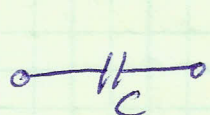

$$I = C \frac{dV}{dt} \rightarrow Z = C j\omega V$$


$$Z = \frac{1}{j\omega C}$$

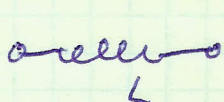

$$V = L \frac{dI}{dt} \quad V = L j\omega I$$

$$Z = j\omega L$$

Lab #1 RLC filters

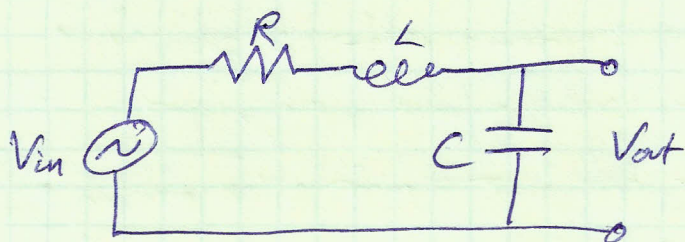

assume V_{in} is sinusoidal voltage, find steady-state response
 R, L, C are in series

$$i(\omega) = \frac{V_{in}(\omega)}{R + j\omega L + 1/j\omega C} = \frac{V_{in}(\omega) j\omega C}{1 + j\omega RC - \omega^2 LC}$$


$$V_{out}(\omega) = \frac{i(\omega)}{j\omega C} = \frac{V_{in}(\omega)}{1 + j\omega RC - \omega^2 LC}$$

$$\text{gain} = \frac{V_{out}(\omega)}{V_{in}(\omega)} = \frac{1}{1 + j\omega RC - \omega^2 LC}$$



Gain is complex. we typically want $|Gain|$

remember $|a + jb| = (a^2 + b^2)^{1/2}$



$$|Gain| = \left[\frac{1}{(1 - \omega^2 LC)^2 + (\omega RC)^2} \right]^{1/2}$$

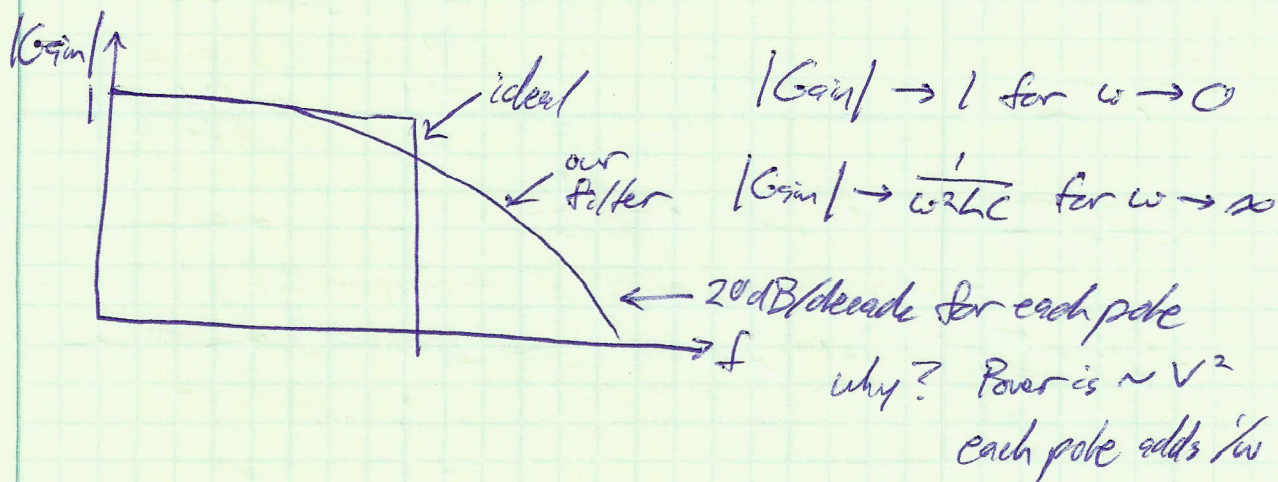

Other combinations of R, L, C :

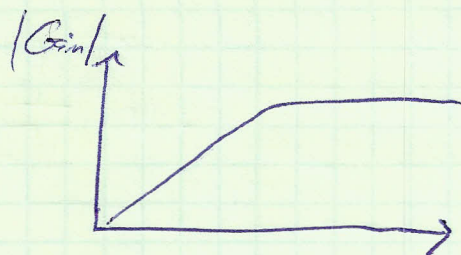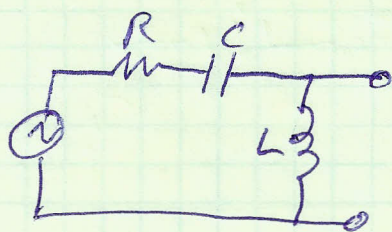


HPF

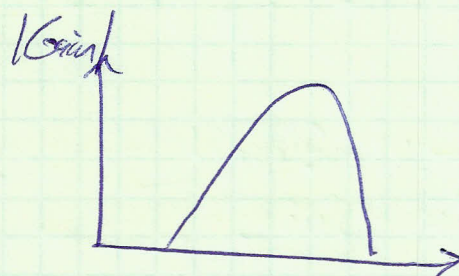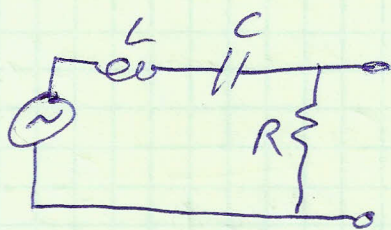

BPF

How can we make a band-reject or notch filter?

How to understand these intuitively:

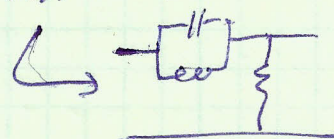

$$\text{voltage divider: } \frac{V_{out}}{V_{in}} = \frac{Z_2}{Z_1 + Z_2}$$

C is high impedance at low frequencies

L is high impedance at high frequencies

$\text{---} \text{---} \text{---} \text{---}$ is low impedance only at resonance $\omega = \frac{1}{\sqrt{LC}}$


$\text{---} \text{---} \text{---} \text{---}$ is high impedance only at resonance $\omega = \frac{1}{\sqrt{LC}}$

We define the transfer function $H(s)$, $s = \sigma + j\omega$


e.g. $H(\omega) = \frac{V_{out}(\omega)}{V_{in}(\omega)}$

- doesn't have to be voltage gain, but for us it typically is.
- we will talk more about complex variable s later

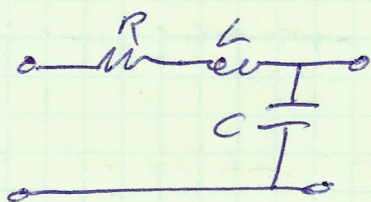
- poles, e.g. $H(s) = \frac{1}{s-p}$ describe natural modes of system
- pole at $\omega_0 \rightarrow$ system will oscillate at ω_0
- positive real part $\sigma \rightarrow$ oscillation grows with time
- negative real part $\sigma \rightarrow$ oscillation decays with time


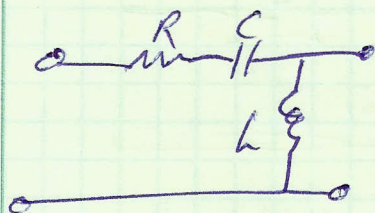
$$H(s) = \frac{1/sC}{R + sL + 1/sC} = \frac{1}{1 + sCR + s^2LC} \quad \text{LPF}$$


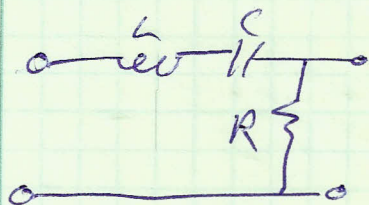
$$H(s) = \frac{sL}{R + 1/sC + sL} = \frac{s^2LC}{1 + sCR + s^2LC} \quad \text{HPF}$$



$$H(s) = \frac{R}{sL + 1/sC + R} = \frac{sRC}{1 + sCR + s^2LC} \quad \text{BPF}$$

All of these have a form of $\frac{1}{1 + 2\zeta (s/\omega_0) + s^2/\omega_0^2}$


$\omega_0 = \frac{1}{\sqrt{LC}}$ resonant frequency

$\zeta = \frac{R\sqrt{C}}{2\sqrt{L}}$ damping factor

$\zeta = 1$: critically damped

$\zeta = \frac{1}{\sqrt{2}}$: maximally flat

- more on this later

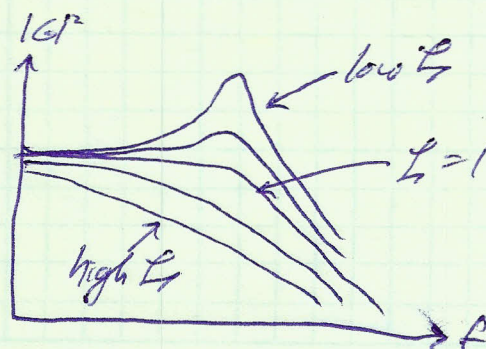

Let's explore LPF:

$$H(\omega) = \frac{1}{1 + j\omega RC - \omega^2 LC} = \frac{1}{1 + 2jL\frac{\omega}{\omega_0} - \frac{\omega^2}{\omega_0^2}}$$

set $\omega_0 = 1$ for simplicity (just scale it back in later)

$$|H(\omega)|^2 = \frac{1}{(1 - \omega^2)^2 + 4L^2\omega^2} \quad \text{where is the maximum?}$$

$$\frac{d}{d\omega} \left(\frac{1}{|H(\omega)|^2} \right) = 2(1 - \omega^2)(-2\omega) + 8L^2\omega = 0$$

one solution at $\omega = 0$

another solution at:

$$1 - \omega^2 = 2L^2$$

$$\omega = \sqrt{1 - 2L^2} \rightarrow \text{scale to } \omega_0 \sqrt{1 - 2L^2}$$

Substitute to get $|H(\omega_{peak})|^2 = \frac{1}{(1 - (1 - 2L^2))^2 + 4L^2(1 - 2L^2)}$

$$L = \frac{R}{2} \sqrt{\frac{C}{L}} \quad \text{what happens as } R \rightarrow 0? \quad = \frac{1}{4L^2(1 - L^2)}$$

Let's explore BPF: $H(\omega) = \frac{2jL\omega/\omega_0}{1 + 2jL\omega/\omega_0 - (\omega/\omega_0)^2}$, set $\omega_0 = 1$

$$|H(\omega)|^2 = \frac{4L^2\omega^2}{(1 - \omega^2)^2 + 4L^2\omega^2}$$

↪ half-power (-3dB) BW is when these are equal
(think about voltage divider)

$$(1 - \omega^2)^2 = 4L^2\omega^2 \rightarrow 1 - \omega^2 = \pm 2L\omega$$

$$\omega^2 \pm 2L\omega - 1 = 0 \rightarrow \omega = \pm L \pm \sqrt{L^2 + 1}$$

$$BW = 2L (\times \omega_0)$$

$$Q = \frac{\text{frequency}}{FWHM} = \frac{1}{2L}$$

