

Mason's Gain Formula

$$G = \frac{Out}{In} = \frac{\sum_{k=1}^N G_k \Delta_k}{\Delta}$$

$$\Delta = 1 - \sum L_i + \sum L_i L_j - \sum L_i L_j L_k + \dots$$

Δ = determinant of the graph

N = number of forward paths between In and Out

G_k = gain of k th forward path

L_i = loop gain of each closed loop


(no common nodes)
↓

$L_i L_j$ = product of loop gains of any non-touching loops

Δ_k = cofactor of Δ for the k th forward path

with loops touching the k th forward path removed

Example:

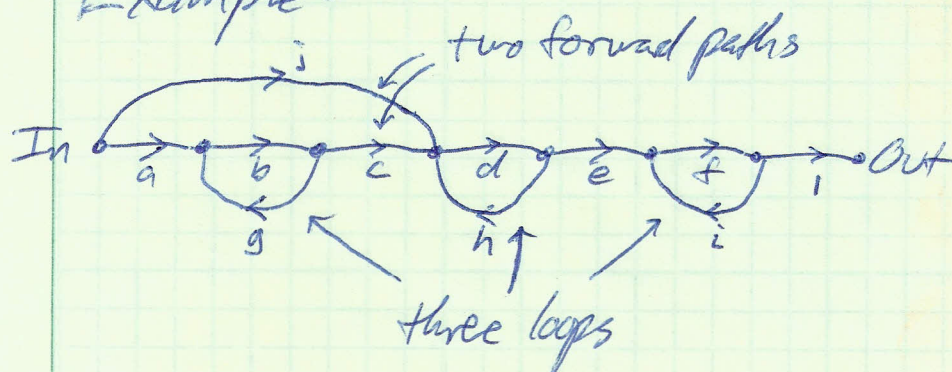


$$\Delta = 1 - bg - dh - fi + bgdh + bgfi + dhfi - bgd h fi$$

path 1: $G_1 = abcdefg$, $\Delta_1 = 1$ (touches all loops)

path 2: $G_2 = jdef$, $\Delta_2 = 1 - bg$ (this path does not touch loop bg)

$$G = \frac{abcdefg + jdef(1 - bg)}{\Delta}$$

Another example:

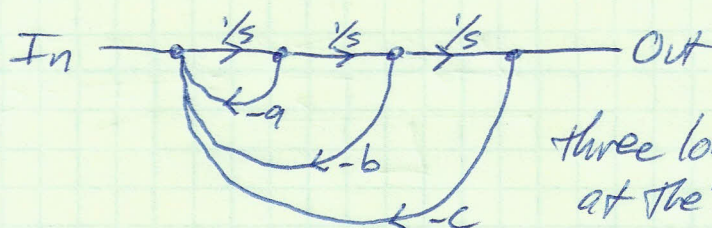

three loops, all touching at the first node

$$L_1 = -a/s$$

$$L_2 = -b/s^2$$

$$L_3 = -c/s^3$$


$$\Delta = 1 + a/s + b/s^2 + c/s^3$$

One forward path, $G_1 = 1/s^3$, that touches all loops

$$G = \frac{1/s^3}{1 + a/s + b/s^2 + c/s^3} = \frac{1}{s^3 + as^2 + bs + c}$$


We can add paths without adding complexity if the paths touch all loops $\rightarrow \Delta_i = 1$ for all i

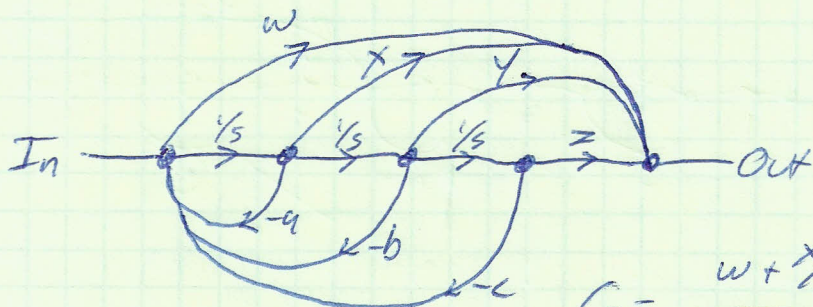Here, all loops touch the first summing node so all forward paths should go through that node.



$$G = \frac{w + x/s + y/s^2 + z/s^3}{1 + a/s + b/s^2 + c/s^3}$$

Dual form:

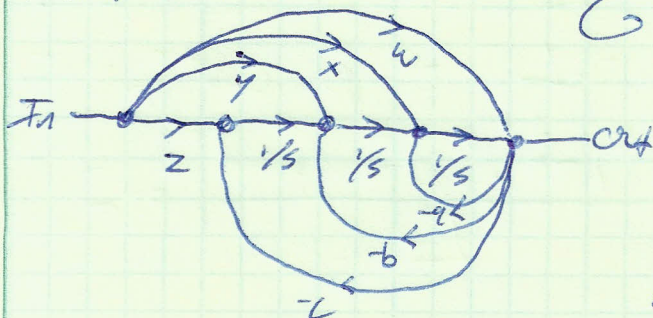


$$G = \frac{ws^3 + xs^2 + ys + z}{s^3 + as^2 + bs + c}$$

Flow reversal theorem:

Reverse direction of all branches and exchange In and Out, the transfer function is unchanged

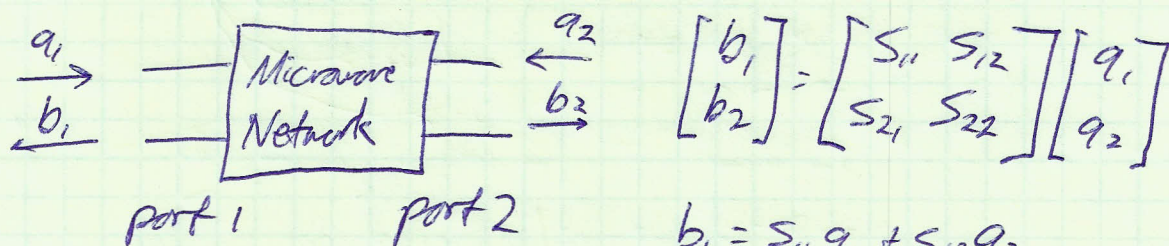Example: Microwave Circuits

Traveling waves instead of simple voltage and current




$$b_1 = S_{11} a_1 + S_{12} a_2$$


$$b_2 = S_{21} a_1 + S_{22} a_2$$

Ideal amplifier:


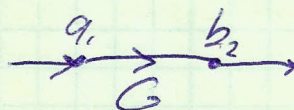
$$S_{11} = S_{22} = S_{12} = 0, S_{21} = G$$



General case:

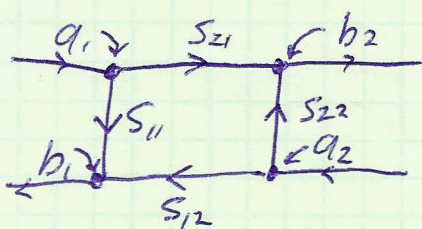

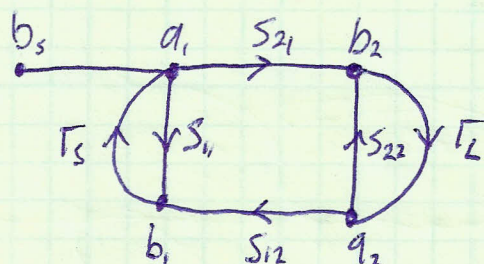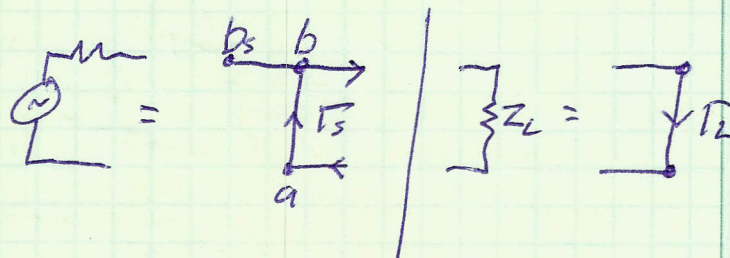Sources and loads have reflection coefficients:



3 loops

$$\Delta = 1 - S_{11}\Gamma_s - S_{22}\Gamma_L - S_{21}\Gamma_L S_{12}\Gamma_s + S_{11}\Gamma_s S_{22}\Gamma_L$$


$$\frac{b_2}{b_s} = \frac{S_{21}}{1 - S_{11}\Gamma_s - S_{22}\Gamma_L - (S_{21}S_{12} - S_{11}S_{22})\Gamma_L\Gamma_s}$$

← one forward path


↑
two non-touching loops

$$\frac{b_1}{b_s} = \frac{S_{11}(1 - S_{22}\Gamma_L) + S_{21}\Gamma_L S_{12}(1)}{1 - S_{11}\Gamma_s - S_{22}\Gamma_L - (S_{21}S_{12} - S_{11}S_{22})\Gamma_L\Gamma_s}$$

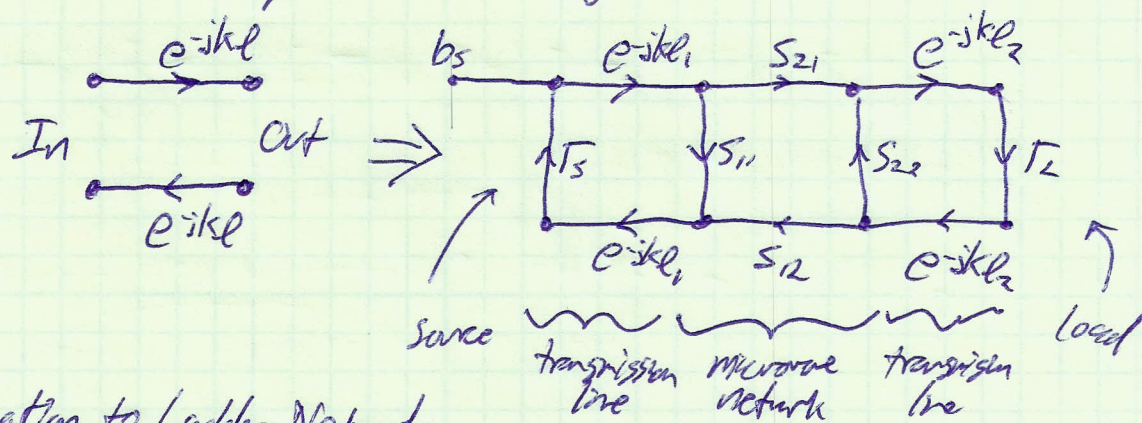We can also easily include a length of transmission line




Application to Ladder Networks

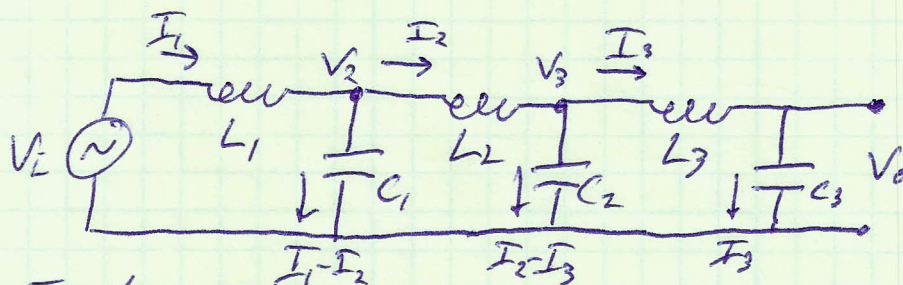

Equations:

$$I_1 = \frac{V_L - V_2}{sL_1}, \quad I_2 = \frac{V_2 - V_3}{sL_2}, \quad I_3 = \frac{V_3 - V_0}{sL_3}$$
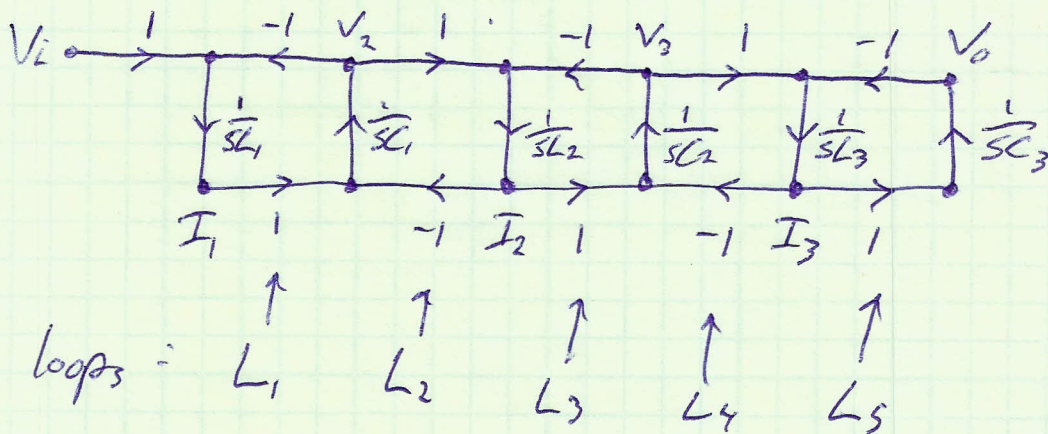
$$V_2 = \frac{I_1 - I_2}{sC_1}, \quad V_3 = \frac{I_2 - I_3}{sC_2}$$



$$L_1 = \frac{1}{s^2 L_1 C_1}, \quad L_2 = \frac{1}{s^2 L_2 C_2}, \quad \dots$$

Only one forward path touching all loops

$$G_1 = \frac{1}{sL_1} \frac{1}{sC_1} \frac{1}{sL_2} \frac{1}{sC_2} \frac{1}{sL_3} \frac{1}{sC_3} = -L_1 L_3 L_5$$

$$\Delta = 1 - L_1 - L_2 L_3 - L_4 - L_5 + L_3 L_4 + L_1 L_4 + L_2 L_5 + L_3 L_5 - L_1 L_3 L_5$$

↑
loop gains, not individual

$$H = \frac{-L_1 L_3 L_5}{\Delta}$$

Lab #6 System Analysis and Design

1. Dual-Integrator Analysis

find overshoot based on ζ (analytical)

find step response (numerical), blocks for $\frac{1}{s}$, ∇ , $\otimes \rightarrow$ in Simulink

2. Dual Integrator Realization


try minimizing the number of op-amps
by absorbing the sum function into the integrator where possible

3. Simulink is very good for nonlinear systems and mixed analog/digital systems, so it's good for oscillators

4. We discussed the effect of time delay but didn't try it.
Now is your chance

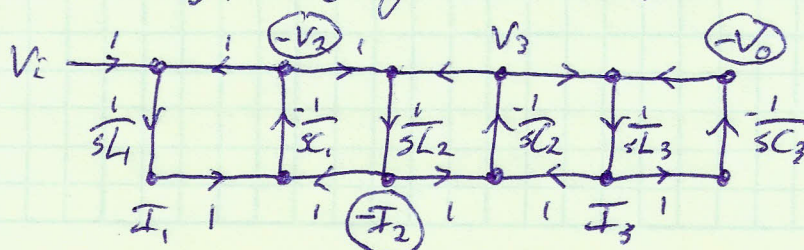5. Signal flow graph of ladder network

We can adjust the sign of variables to minimize # of inverters




Op-amps implementation of LC ladder network
 Called "Leapfrog ladder" circuit, used in IC filters

Realize the equations of a passive circuit so that the
 active circuit has the stability and sensitivity of passive circuit

Sensitivity : how accurately we must specify component values

example:

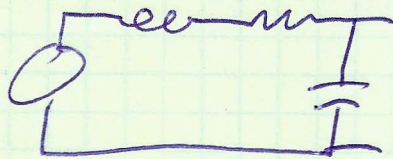

$$H(s) = \frac{1}{1 + sCR + s^2 LC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}, \quad \frac{2S}{\omega_0} = CR$$

$$\xi = \frac{1}{2} R \sqrt{\frac{C}{L}}$$

$$\frac{\delta \omega_0}{\omega_0} = S_L^{\omega_0} \frac{\delta L}{L} + S_C^{\omega_0} \frac{\delta C}{C}$$

$\uparrow$ $\uparrow$ $\uparrow$
 fractional fractional fractional
 error in ω_0 error in L error in C

We want $S_L^{\omega_0}$ and all others ≤ 1

Calculate S using logs,

$$\omega_0^2 = \frac{1}{LC} \rightarrow 2 \log \omega_0 = -\log L - \log C$$

take $\frac{\partial}{\partial L}$ of whole equation

$$\frac{2}{\omega_0} \frac{\partial \omega_0}{\partial L} = -\frac{1}{L}$$

$$\frac{\partial \omega_0}{\omega_0} = -\frac{1}{2} \frac{\partial L}{L} \quad \text{so } \underline{S_L^{\omega_0} = -\frac{1}{2}}$$