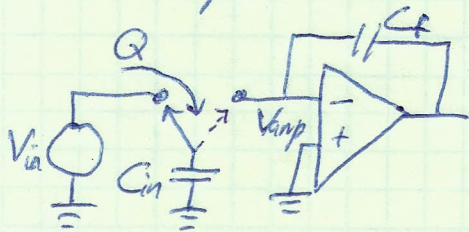


Switched capacitor circuits

Problem: large C can take a lot of chip area $\rightarrow$ use $C < 10\text{pF}$
 but need $RC \approx 10^{-3}$ so $R \approx 10^8$ which is also too large for a chip

Solution: replace R with switched C



$Q_{in} = C_{in} V_{in}$
 when switch to V_{in}

When switch to V_{amp} , Q_{in} goes to C_f , and C_{in} discharges completely because $V_{amp} = 0$.


$$I_{avg} = \Delta Q / \Delta t = Q_{in} f_{clock} = C_{in} V_{in} f_{clock}$$

$$\text{equivalent resistance } R_{eq} = \frac{1}{C_{in} f_{clock}}$$

note smaller $C_{in} \rightarrow$ larger R_{eq}

f_{clock} must be more than twice as high as any frequency in the signal

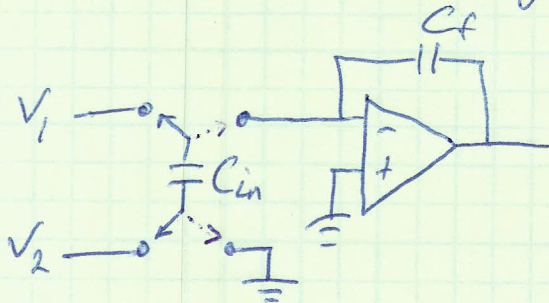- This is fine. We're talking about kHz signals, f_{clock} can be MHz or GHz




$$Q_{in} = (V_1 - V_2) C_{in}$$

R_{eq} is the same, but now we have both positive and negative integrators

This is useful for biquads and ladder simulators
 where we need both positive and negative integrators

The details of the switches are also important:

continued $\rightarrow$

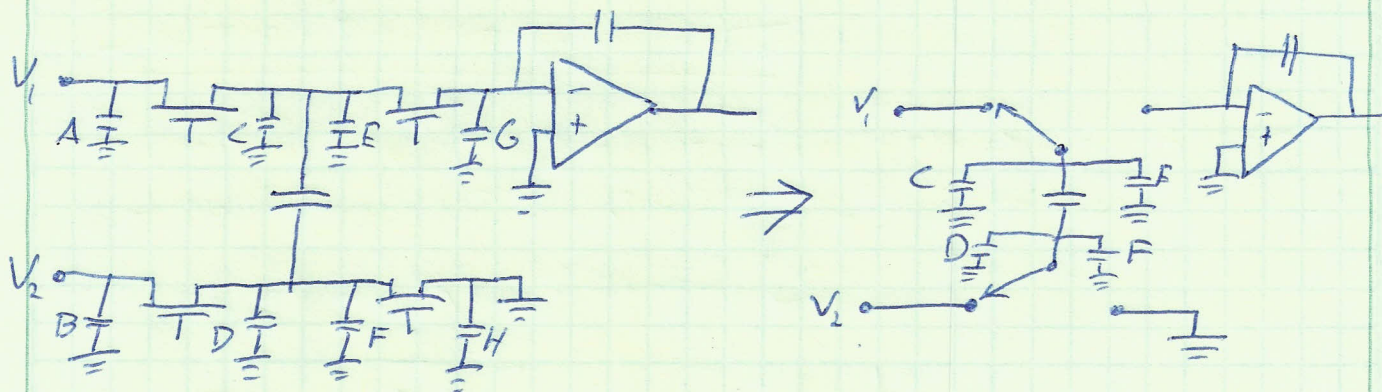


Caps A, B are connected to V_1, V_2 and don't transfer any Q through switches

Caps G, H are always at 0 volts, with no charge

Caps D, F charge up to V_2 and transfer $Q_2 = V_2(C_D + C_F)$ to ground each cycle


Caps C, E are problems. They transfer $Q_1 = V_1(C_C + C_E)$ to the op-amp each cycle, so they look like extra resistors to V_1 .

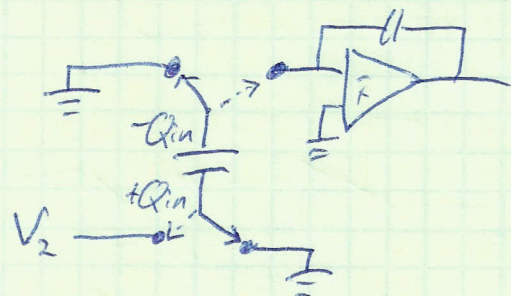We set $V_1 = 0$, and V_2 works well as a positive integrator circuit
What about a negative integrator?



run the switches with opposite phase.

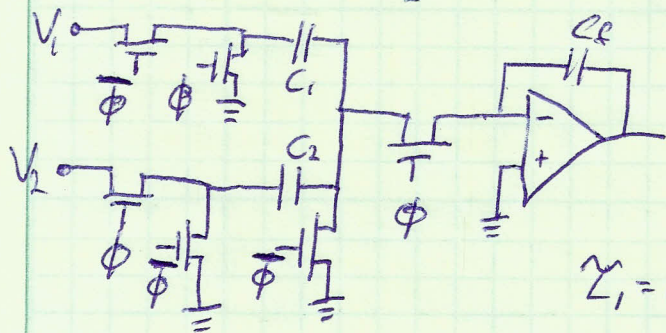
Think about which direction current flows in each case.



$$V_o(s) = \frac{V_1}{s\tau_1} - \frac{V_2}{s\tau_2}$$

$$\tau_1 = C_f R_{eq1} = \frac{C_f}{C_1 f_{clock}} = \frac{C_f}{C_1} T_{clock}$$


we want $\tau \gg T_{clock}$ so $C_f \gg C_1, C_2$

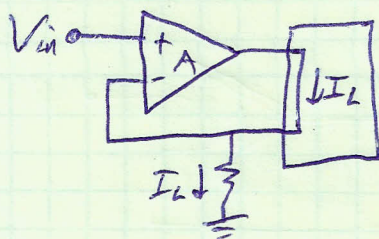Current Driver

$$V_{oc} = V_{in} A$$

$$I_{sc} = \frac{A(V_{in} - I_{sc}R)}{R} = \frac{1}{R} \frac{AV_{in}}{1+A}$$

$$Z_{out} = \frac{V_{oc}}{I_{sc}} = R(1+A) \rightarrow \infty$$

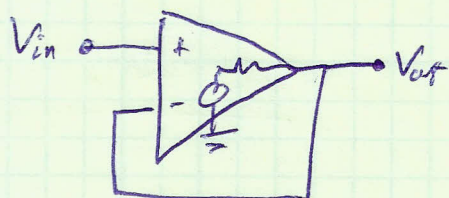Voltage Follower

$$V_{oc} = A(V_{in} - V_{oc})$$


$$V_{oc}(1+A) = A V_{in}$$

$$V_{oc} = \frac{A}{1+A} V_{in}$$

$$I_{sc} = \frac{AV_{in}}{R_0}$$

$$Z_{out} = \frac{V_{oc}}{I_{sc}} = \frac{R_0}{1+A} \rightarrow 0$$

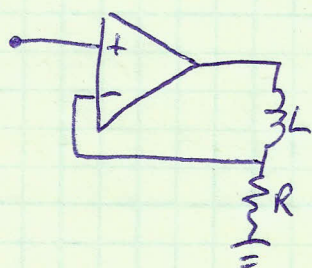
Feedback makes either supply more constant (independent of load)
 Current source wants high Z_{out} , Voltage Source wants low Z_{out}
 Note that stability depends on Z_{load} , e.g. magnetic coil driver



$$B = \frac{R}{R + sL} = \frac{1}{1 + sL/R} \rightarrow \text{low pass filter with } \tau = R/L$$


This pole in transfer function reduces phase margin, could lead to instability.

Compensate by adding a zero

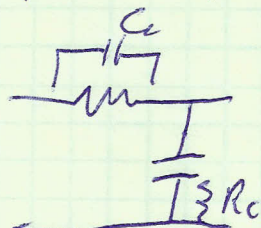

either C_c or R_c works
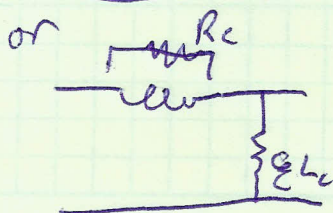
$$B = \frac{R + sL C_c}{R + sL C_c + sL}$$



either R_c or L_c works

$$= \frac{1 + sL C_c / R}{1 + s(L + L_c) / R}$$

Power Supplies

Standby power in residential appliances costs $\sim \$3\text{B}/\text{year}$
in the USA alone, or $64 \times 10^6 \text{ MWh/yr}$
or 18-400MW power stations running full time

Converting to high efficiency power supplies would reduce by factor of 10.
Equivalent to 18 M cars worth of CO_2

Power supplies convert power from one source to another, e.g. 120VAC to 5VDC


Needs low output resistance so V_{out} independent of I_{out}

Also needs V_{out} independent of V_{in}


AC distribution: $P = VI$, but $\text{loss} = I^2 R$, so usually use high V

It is easy to change AC voltages with transformers

AC $\rightarrow$ DC rectification:

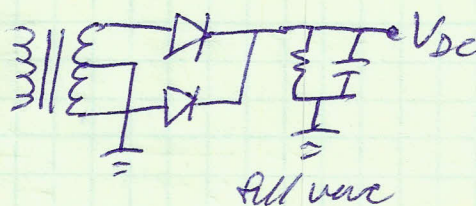


Voltage reference:

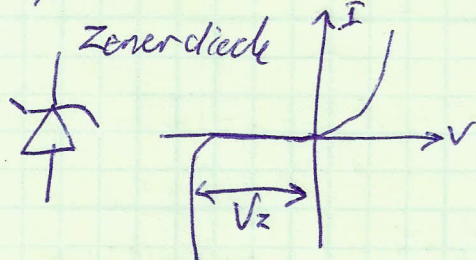

Zener diode provides a good reference voltage

However, power is drawn from the source regardless of the load

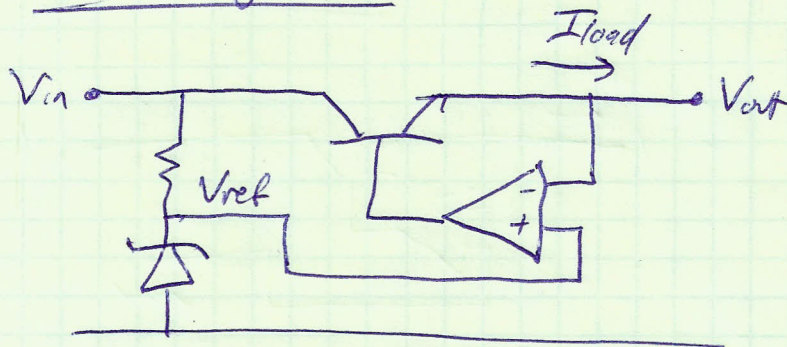
Series regulator

$$P_{in} = I_{load} V_{in}$$



$$P_{out} = I_{load} V_{out}$$

$$\epsilon = \frac{P_{out}}{P_{in}} = \frac{V_{out}}{V_{in}}$$


Feedback circuit looks like this:

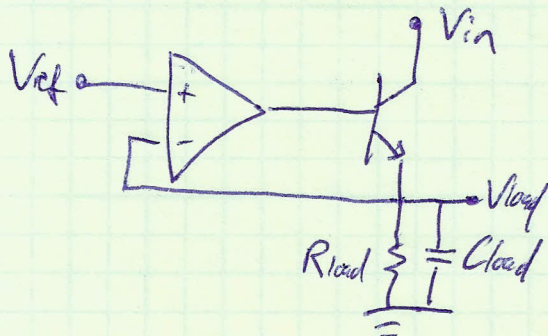

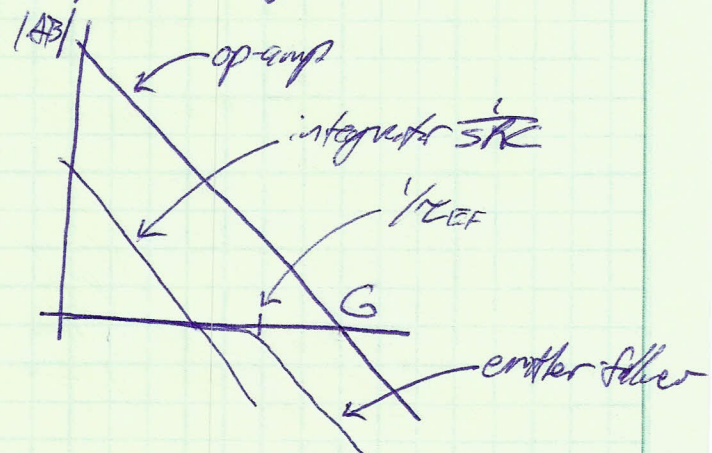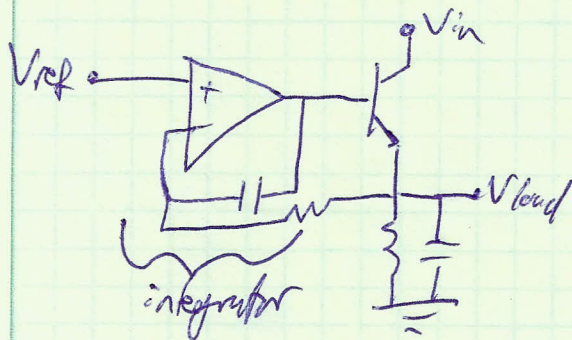Emitter follower will have time constant due to load capacitance. This may affect phase margin.




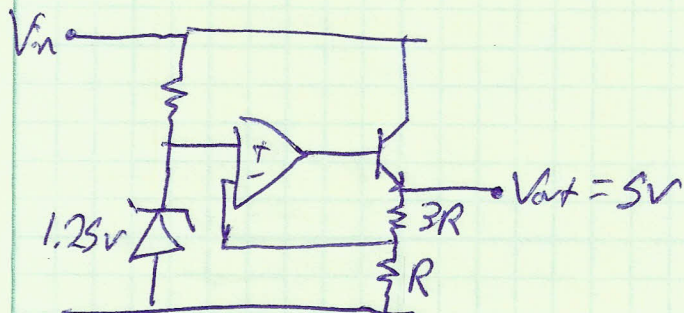Voltage reference would likely be "bandgap reference" which compensates for temperature variations, gives $V_{ref} \approx 1.25$ near bandgap of silicon





we generate 5V by dividing V_{out} by 4 before comparing with V_{ref}


How do we handle $V_{in} \gg V_{load}$?

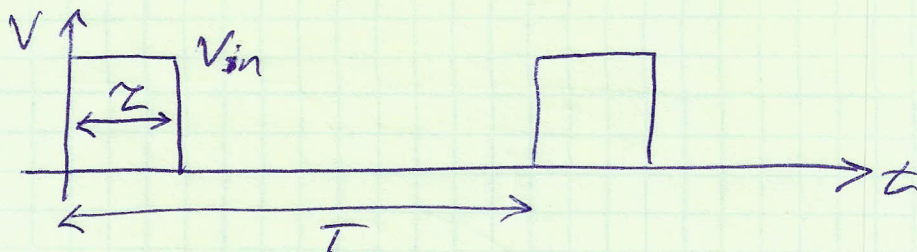

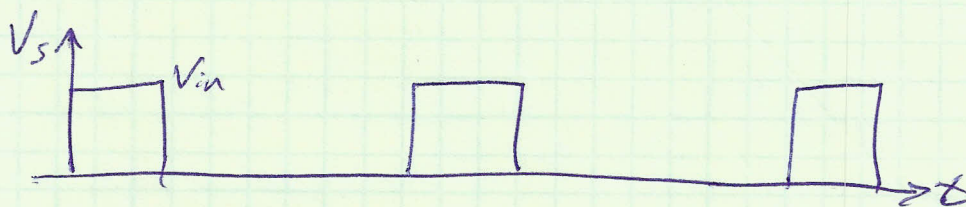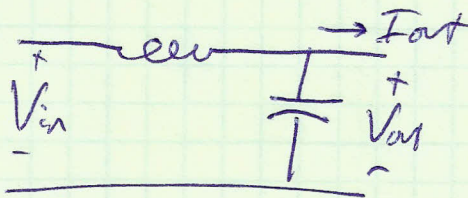Average voltage $V_{avg} = V_{in} \frac{\tau}{T}$ can be $\ll V_{in}$
 Store energy in a reactance in between pulses
 need a reactive low-pass filter



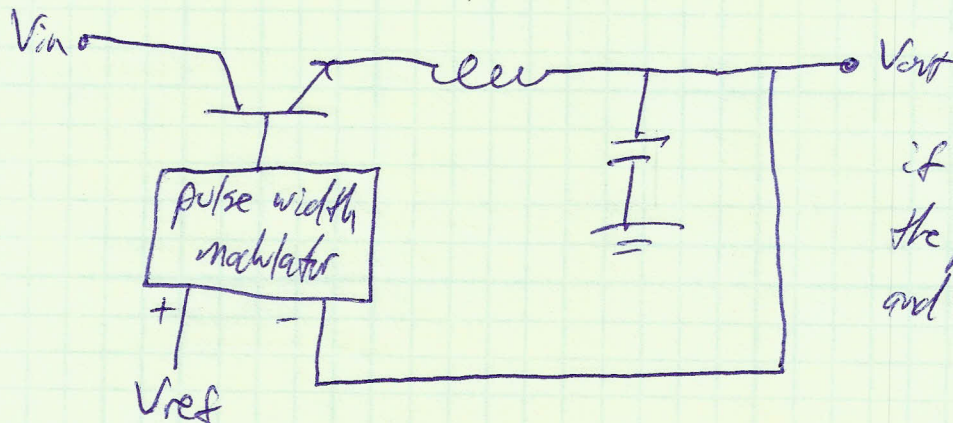The larger the inductor, the smaller the current ripple



if $V_{out} < V_{ref}$,
 the pulse width increases
 and V_{out} starts to rise