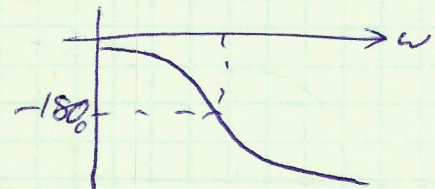
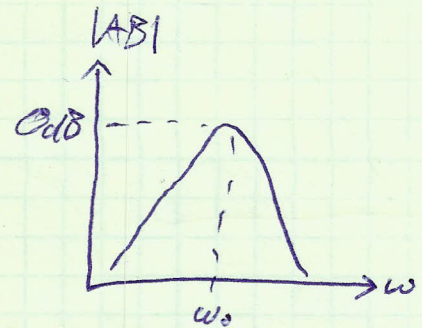
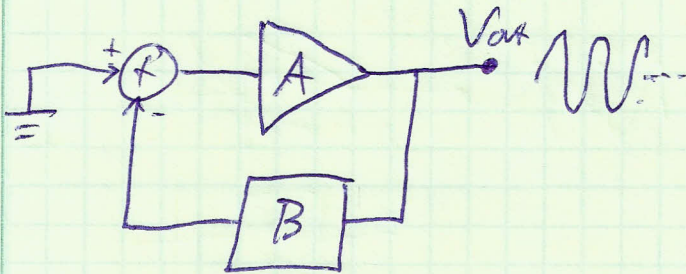
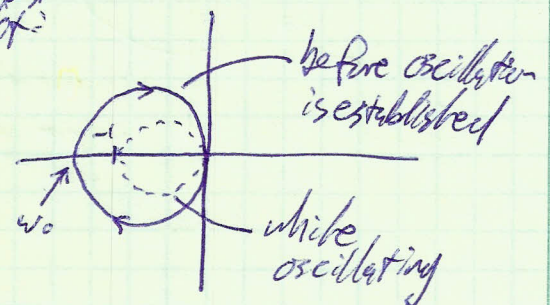
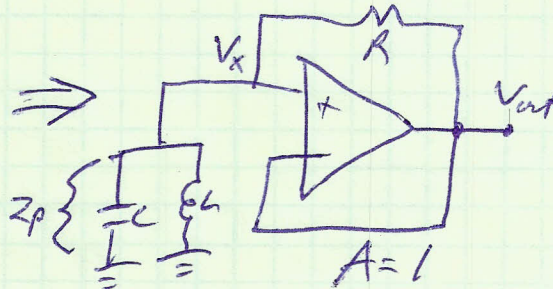
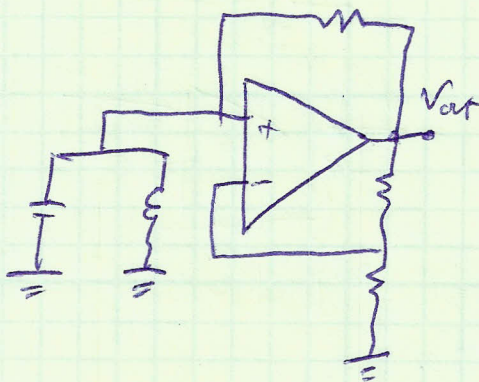


First, review midterm #2Oscillators:

Nyquist plot:

Example oscillators:



$$B = \frac{-V_x}{V_{out}}$$

$$Z_p = \frac{1}{\frac{1}{sL} + sC} = \frac{sL}{1 + s^2LC}$$


$$B = \frac{-sL / (1 + s^2LC)}{R + sL / (1 + s^2LC)}$$

$$B = \frac{-sL/R}{1 + \frac{sL}{R} + s^2LC}$$
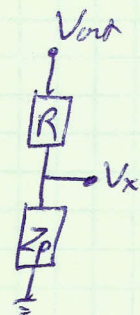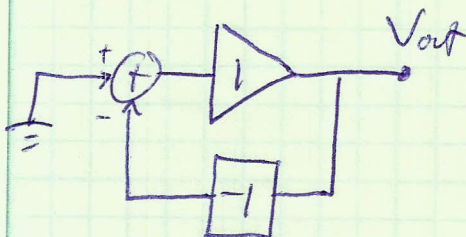
$$\omega_0 = \frac{1}{\sqrt{LC}}, \text{ at } \omega_0 \Rightarrow B = -1$$



Another oscillator:

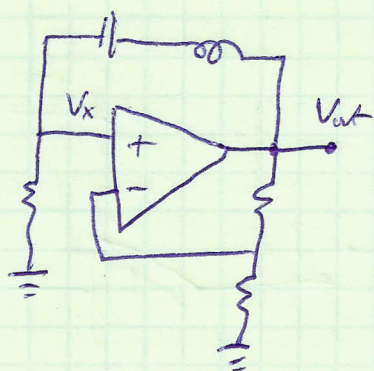


$$B = \frac{-V_x}{V_{out}} = \frac{-R}{R + sR + \frac{1}{sC}}$$


$$B = \frac{-sCR}{1 + sCR + s^2 LC}$$

at $\omega = \frac{1}{\sqrt{LC}}$, $B = -1$ same as last case

Phase shift oscillator:

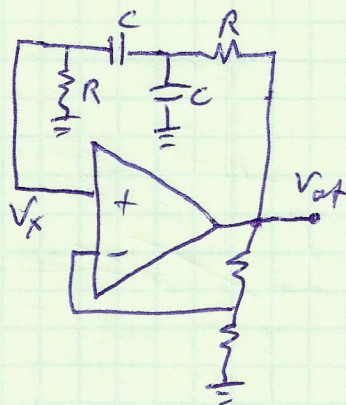

Ladder network:

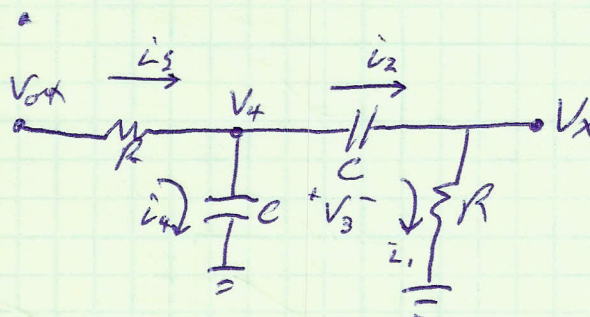

start at the output, and work backward to input

$$\frac{V_{out}}{V_x} = \frac{(1 + sCR) + (2 + sCR)(sCR)}{sCR}$$

$$B = \frac{-V_x}{V_{out}} = \frac{-sCR}{1 + 3sCR + s^2 C^2 R^2}$$

$$\omega_0 = \frac{1}{RC}$$

$$\text{at } \omega_0, B = -\frac{1}{3}$$

want AB to be -1

$$\text{so } A = 3$$

• assume V_x

$$\bullet i_1 = V_x / R$$

$$\bullet i_2 = V_x / R$$

$$\bullet V_3 = i_2 / sC = \frac{V_x}{sCR}$$


$$\bullet V_4 = V_x + V_3 = V_x + \frac{V_x}{sCR} = \left(\frac{1 + sCR}{sCR} \right) V_x$$

$$\bullet i_4 = V_4 sC = \left(\frac{1 + sCR}{R} \right) V_x$$


$$\bullet i_5 = i_4 + i_2 = \frac{V_x}{R} + \frac{V_x (1 + sCR)}{R} = \frac{V_x (2 + sCR)}{R}$$

$$\bullet V_{out} = V_4 + i_5 R = V_x \left(\frac{1 + sCR}{sCR} \right) + \frac{V_x (2 + sCR) R}{R}$$



Ring Oscillator:

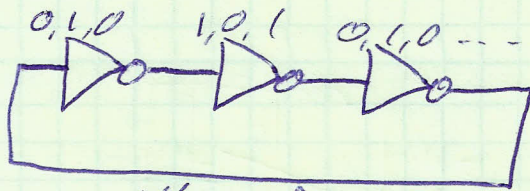

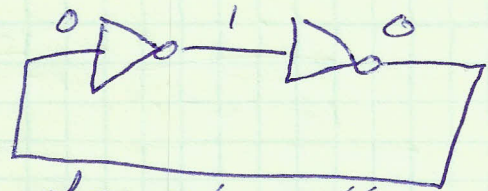Oscillates forever
 $0 \rightarrow 1 \rightarrow 0 \rightarrow \dots$



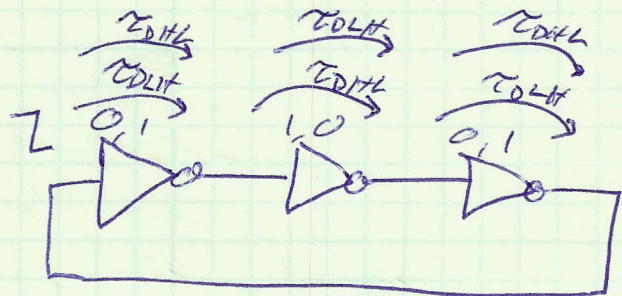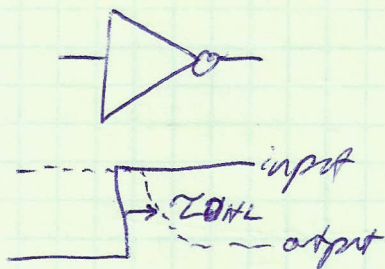does not oscillate
 need odd number
 of inverters



Period of square wave is

$$3\tau_{DHL} + 3\tau_{DLH} = 6\tau_D \quad \text{if } \tau_{DLH} \approx \tau_{DHL}$$

we can also define average $\tau_D = \frac{1}{2}(\tau_{DLH} + \tau_{DHL})$

$$\text{frequency} = \frac{1}{6\tau_D} = \frac{1}{2n\tau_D} \quad \text{for } n\text{-stage oscillator}$$

More accurate model of inverter

