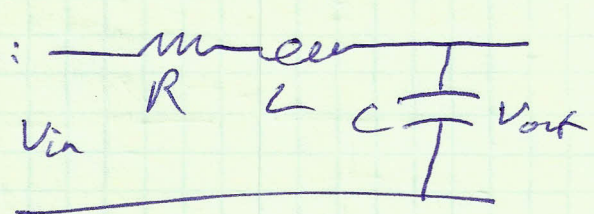


Recall the low-pass filter: 

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + sRC + s^2LC} = \frac{1}{1 + j\omega RC - \omega^2 LC}$$

General form:

$$H(s) = \frac{1}{1 + 2\zeta \frac{s}{\omega_0} + \left(\frac{s}{\omega_0}\right)^2} \quad \omega_0 = \frac{1}{\sqrt{LC}}, \quad \zeta = \frac{R}{2} \sqrt{\frac{C}{L}}$$

note on units: $V = L \frac{di}{dt} \rightarrow [L] = V \cdot \frac{s}{A}$

$i = C \frac{dv}{dt} \rightarrow [C] = A \cdot \frac{s}{V}$


$\left[\frac{1}{\sqrt{LC}}\right] = \frac{1}{s} \rightarrow \text{frequency}$

$\left[\sqrt{\frac{L}{C}}\right] = \frac{V}{A} = \text{Ohms}$

so ζ is dimensionless

Filter design:

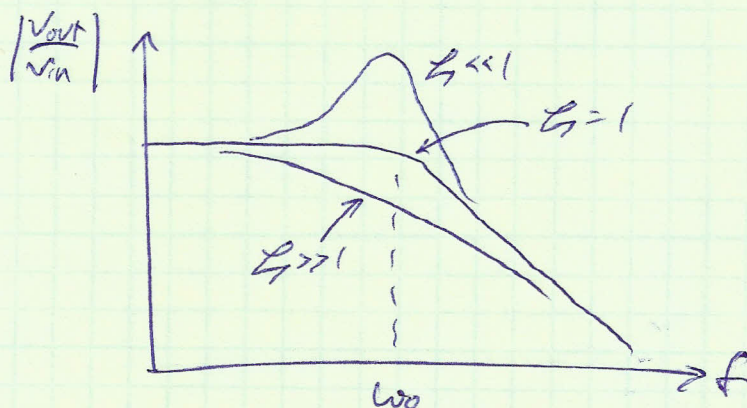1. Choose L, C to get desired ω_0
2. Choose R to get desired ζ



Bode Plots (Hendrik Wade Bode - Bell Labs)


$$G_{\text{ain}} = \left| \frac{V_{\text{out}}}{V_{\text{in}}} \right| \dots \text{remember } |a+jb| = (a^2+b^2)^{1/2}, \left| \frac{1}{a+jb} \right| = \frac{1}{(a^2+b^2)^{1/2}}$$

we often care about $G_{\text{ain}}^2 \rightarrow \text{power}$

$$\text{LPF: } |H(\omega)|^2 = \left| \frac{V_{\text{out}}}{V_{\text{in}}} \right|^2 = \frac{1}{(1-\omega^2 LC)^2 + (\omega RC)^2}$$

however, gain is complex - it also has phase

$$a+jb = |a+jb| e^{j\theta}, \theta = \tan^{-1}\left(\frac{b}{a}\right)$$

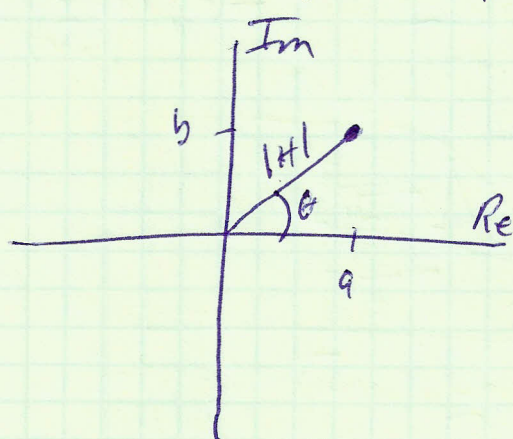


$$= \frac{1}{\left(1 - \left(\frac{\omega}{\omega_0}\right)^2\right)^2 + \left(\frac{\omega 2L}{\omega_0}\right)^2}$$




phase of $\left(\frac{1}{a+jb}\right)$ is $-\tan^{-1}\left(\frac{b}{a}\right)$

phase of $H(\omega)$ is $-\tan^{-1}\left(\frac{\omega RC}{1-\omega^2 LC}\right)$

$$= -\tan^{-1}\left(\frac{\omega 2L/\omega_0}{1 - (\omega/\omega_0)^2}\right)$$

Bode Plot:

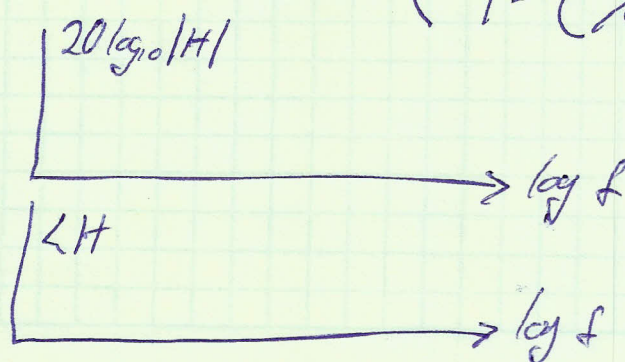

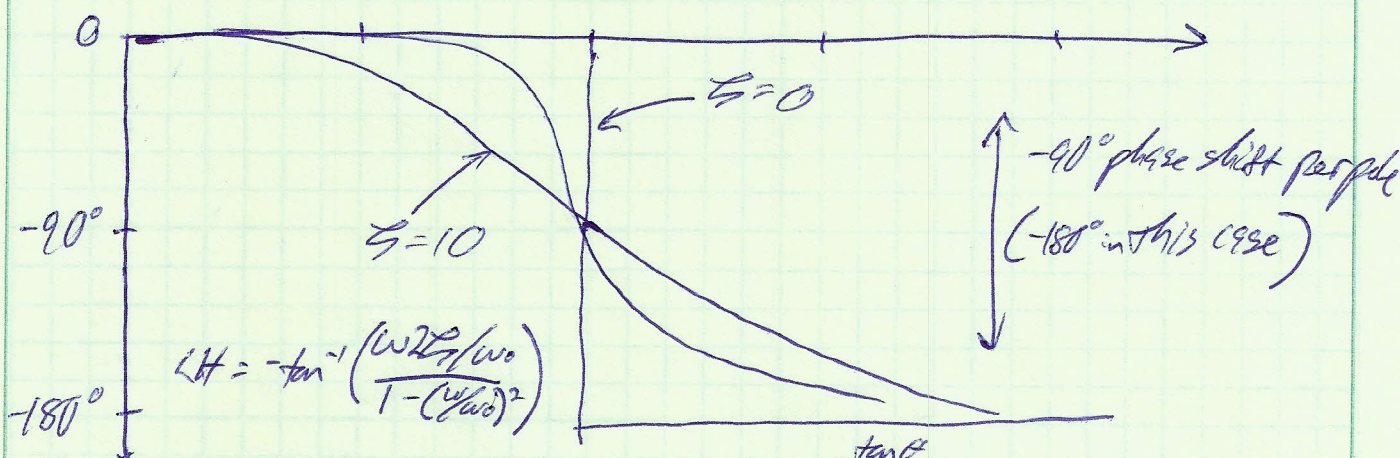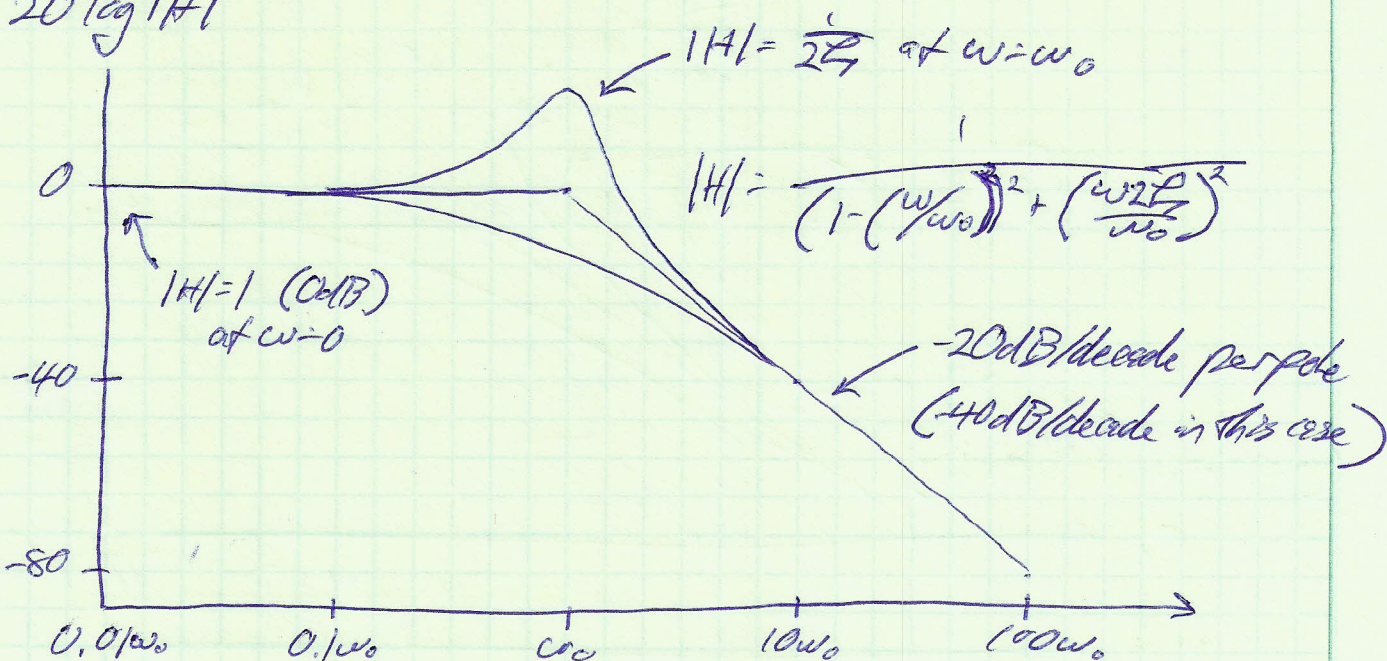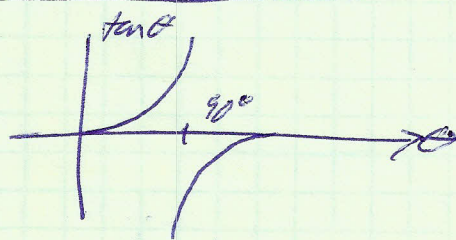$20 \log |H|$ Note $\tan^{-1}(\infty) = 90^\circ$ 

General transfer function:

$$H(s) = A \frac{(s+z_1)(s+z_2) \dots}{(s+p_1)(s+p_2) \dots}$$

← zeros
← poles


$$s = \sigma + j\omega$$

Our case:

$$H(s) = \frac{1}{1 + 2\zeta \frac{s}{\omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$

poles are roots of denominator


$$s = (-\zeta \pm \sqrt{\zeta^2 - 1}) \omega_0$$

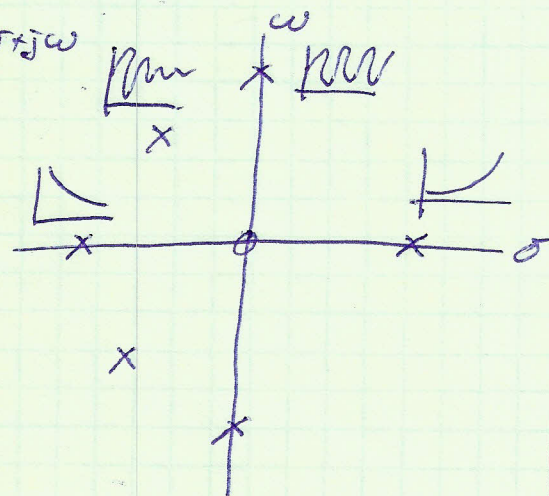if $\zeta = 0$, poles at $\pm j\omega_0$ if ζ positive, poles have negative real part

How to make hand-drawn Bode plots:

1. Get $H(s)$ into form of $H(s) = A \frac{(s+z_1)(s+z_2)\dots}{(s+p_1)(s+p_2)\dots}$
2. Determine low frequency asymptote (value at $\omega=0$ or $\omega=1$)
3. Every pole changes slope by -20dB/decade
Every zero changes slope by $+20\text{dB/decade}$
(Including poles or zeros at $\omega=0$)
4. Actual curve deviates from asymptotic curve by 3dB at break points (for first order)
or has value of $\frac{1}{2\pi}$ (for second order)
5. Determine low frequency asymptote of phase ($\phi = n \times 90^\circ$)
6. Phase changes by $+90^\circ$ at each zero, -90° at each pole
7. Real phase curve changes by $\pm 45^\circ$ per decade, per order
(i.e. it is asymptotic value at $0.1\omega_0$ or $10\omega_0$)
For Second order, can be more accurate using $\frac{1}{2\pi}$

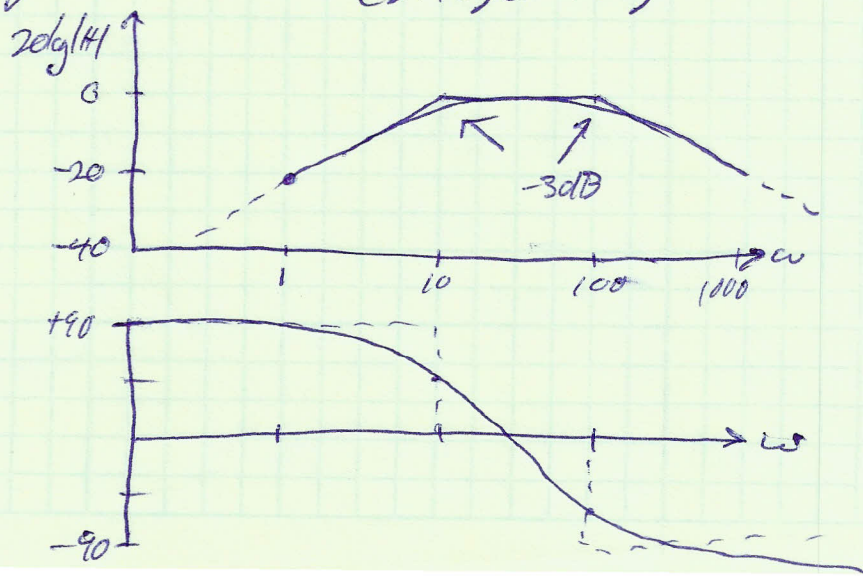Example: $H(s) = \frac{100s}{(s+10)(s+100)}$ as $s \rightarrow 0$, $H(s) \rightarrow 0.1s$



Butterworth Filters (maximally flat)

Goal is to make gain as flat as possible in the pass band

$$|H(\omega)|^2 = \frac{1}{(1 - (\frac{\omega}{\omega_0})^2)^2 + (\frac{2\zeta\omega}{\omega_0})^2}$$

$\frac{\partial |H(\omega)|^2}{\partial \omega}$ is difficult to solve, but $\frac{\partial \frac{1}{|H(\omega)|^2}}{\partial \omega}$ is fine

$$\frac{\partial}{\partial \omega} \left[(1 - (\frac{\omega}{\omega_0})^2)^2 + (\frac{2\zeta\omega}{\omega_0})^2 \right] = 0 \quad \text{set } \omega_0 = 1$$

$$\frac{\partial}{\partial \omega} \left[(1 - \omega^2)^2 + (2\zeta\omega)^2 \right] = 0$$

$$2(1 - \omega^2)(-2\omega) + 8\zeta^2\omega = 0$$

One solution: slope is 0 at $\omega = 0$

another solution at

$$4\omega(1 - \omega^2) = 8\zeta^2$$

$$\omega^2 = 1 - 2\zeta^2$$

no ripple if we set this frequency to zero


so $\zeta = \frac{1}{\sqrt{2}}$ plug this back into gain

$$|H(\omega)|^2 = \frac{1}{(1 - (\frac{\omega}{\omega_0})^2)^2 + (\frac{\sqrt{2}\omega}{\omega_0})^2} \quad \text{or for } \omega_0 = 1, |H(\omega)|^2 = \frac{1}{(1 - \omega^2)^2 + 2\omega^2}$$

$$|H(\omega)|^2 = \frac{1}{1 - 2\omega^2 + \omega^4 + 2\omega^2} = \frac{1}{1 + \omega^4}$$

$$\text{un-normalized: } |H(\omega)|^2 = \frac{1}{1 + (\frac{\omega}{\omega_0})^4}$$

2nd order Butterworth filter


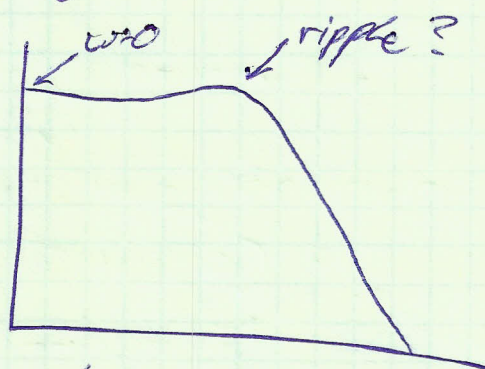


Higher order Butterworth filters:

$$2: H(s) = \frac{1}{1 + \frac{\sqrt{2}s}{\omega_0} + \frac{s^2}{\omega_0^2}} \quad |H(\omega)|^2 = \frac{1}{1 + \left(\frac{\omega}{\omega_0}\right)^4}$$



$$3: H(s) = \frac{1}{1 + \frac{2s}{\omega_0} + \frac{2s^2}{\omega_0^2} + \frac{s^3}{\omega_0^3}} \quad |H(\omega)|^2 = \frac{1}{1 + \left(\frac{\omega}{\omega_0}\right)^6}$$

$$4: |H(\omega)|^2 = \frac{1}{1 + \left(\frac{\omega}{\omega_0}\right)^8} \dots$$

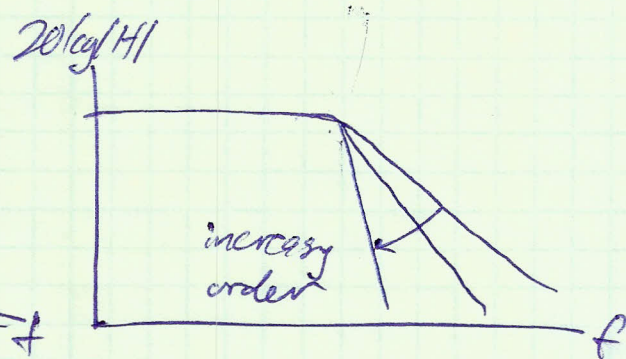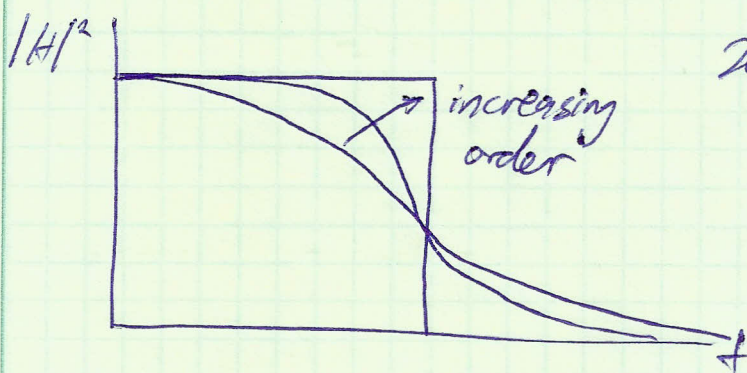

Other types of filters:

Chebyshev:

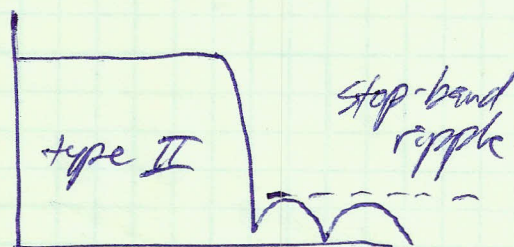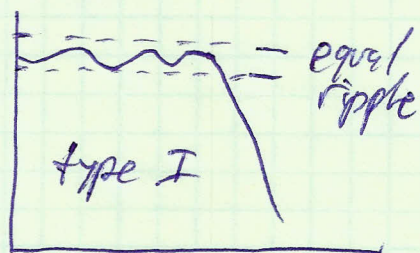

Elliptic:

