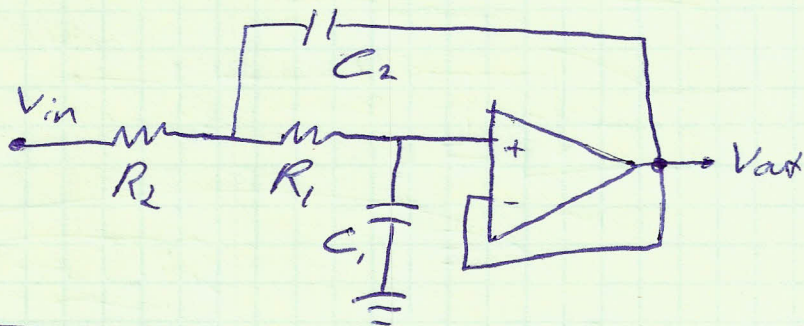


More on lab #2



last time we found:

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + sC_1(R_1 + R_2) + s^2C_1C_2R_1R_2}$$

How do we choose these 4 values? Start with $R_1 = R_2 = R$

$$\frac{1}{1 + 2sC_1R + s^2C_1C_2R^2} = \frac{1}{1 + \frac{2\zeta s}{\omega_0} + \frac{s^2}{\omega_0^2}}$$

$$\omega_0^2 = \frac{1}{C_1C_2R^2}, \quad \zeta = C_1R\omega_0 = \frac{C_1R}{\sqrt{C_1C_2R^2}} = \sqrt{\frac{C_1}{C_2}}$$

set $C_1 = \zeta C$ and $C_2 = C/\zeta \leftarrow$ arbitrary choice


$$\underline{\underline{\zeta = \sqrt{\frac{C_1}{C_2}} = \sqrt{\frac{\zeta C}{C/\zeta}} = \zeta}} \quad \text{and} \quad \underline{\underline{\omega_0 = \frac{1}{RC}}}$$

Now we only have 2 variables = R and C What R should we choose?



Filter is non-ideal at high frequencies, due to

- Finite output resistance
- Reduced gain

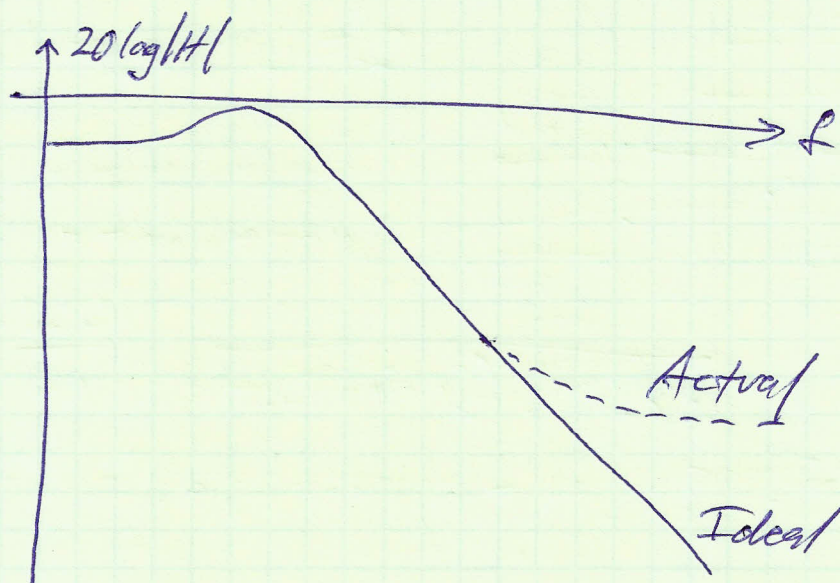Choose R to minimize this effect and meet -55dB gain spec at 180kHz



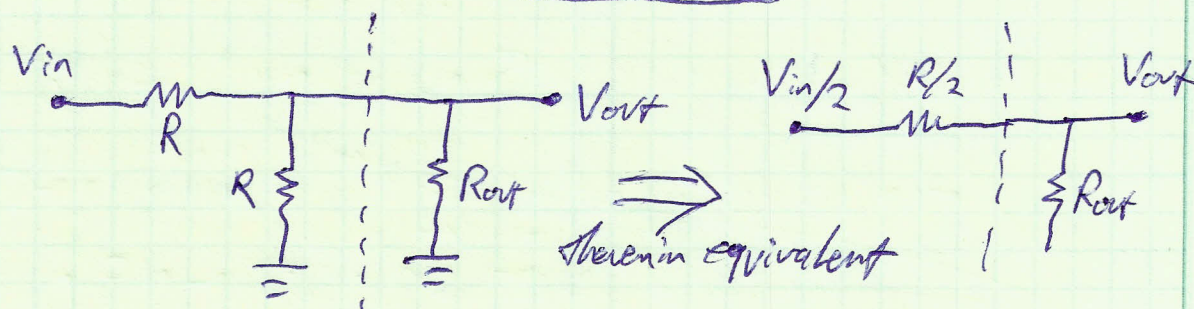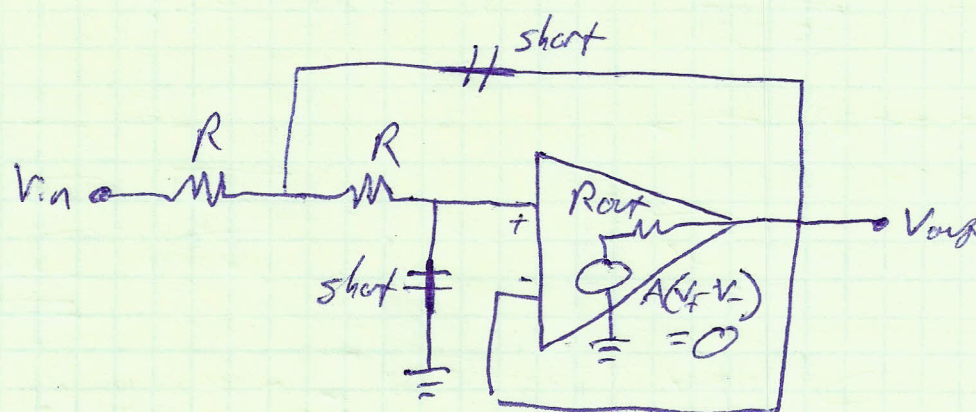Assume as $\omega \rightarrow \infty$, op-amp gain $A \rightarrow 0$
and capacitors $\rightarrow$ short circuits



$$\frac{V_{out}}{V_{in}/2} = \frac{R_{out}}{R/2 + R_{out}} \approx \frac{2R_{out}}{R}$$


$$\frac{V_{out}}{V_{in}} = \frac{R_{out}}{R} \quad \text{we need } \left| \frac{V_{out}}{V_{in}} \right|^2 \leq -55 \text{ dB}$$

$$\frac{R_{out}}{R} < 0.0018 \quad \text{If } R_{out} = 50 \Omega, R > 28 \text{ k}\Omega$$

Laplace Transform

Why do we use it? Replace complicated differential equations with simple algebra and a "look-up table"

Example:

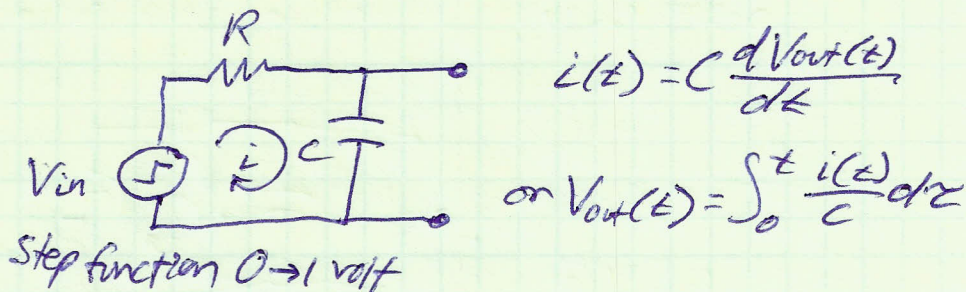

2 options:

$$\left. \begin{aligned} 1 - Ri - \int_0^t \frac{i}{C} d\tau &= 0 \\ 1 - RC \frac{d}{dt} V_{out} - V_{out} &= 0 \end{aligned} \right\} \begin{array}{l} \text{neither of} \\ \text{these are} \\ \text{trivial} \end{array}$$

we usually guess the solution, e.g. $V_{out} = A - Be^{-t/RC}$
and plug it in to solve for the unknown coefficients

In this case we know the answer is $V_{out} = 1 - e^{-t/RC}$ (starting at zero)

Easier way: $H(s) = \frac{V_{out}}{V_{in}} = \frac{1/sC}{R + 1/sC} = \frac{1/RC}{s + 1/RC}$

$$V_{out}(s) = H(s)V_{in}(s)$$

$$V_{in}(t) = U(t) \rightarrow V_{in}(s) = \frac{1}{s}$$

$$V_{out}(s) = \frac{1/RC}{s(s + 1/RC)}$$

look this up in a table of Laplace transforms $\frac{\alpha}{s(s+\alpha)} \rightarrow (1 - e^{-\alpha t})U(t)$

$$V_{out}(t) = (1 - e^{-t/RC})U(t)$$

This is a very simple example. Imagine how much easier the Laplace Transform method is for complicated circuits!

Definition of Laplace Transform:

$$\mathcal{L}[f(t)] = \int_0^{\infty} e^{-st} f(t) dt = F(s)$$

Note: there is an Inverse Laplace Transform:

$$\mathcal{L}^{-1}[F(s)] = \frac{1}{2\pi j} \lim_{T \rightarrow \infty} \int_{\gamma - jT}^{\gamma + jT} e^{st} F(s) ds$$

where $\gamma >$ all poles in $F(s)$, usually solved with Cauchy residue theorem. This is beyond the scope of this class.


Simple example: $f(t) = e^{-t}$

$$\mathcal{L}[e^{-t}] = \int_0^{\infty} e^{-st} e^{-t} dt = \left. \frac{-e^{-(s+1)t}}{s+1} \right|_0^{\infty} = \frac{1}{s+1}$$

Some important Laplace transforms:


$f(t)$	$F(s)$	name
$\star \rightarrow \delta(t)$	1	unit impulse
$u(t)$	$\frac{1}{s}$	unit step
$e^{-\alpha t} u(t)$	$\frac{1}{s+\alpha}$	exponential decay
$(1 - e^{-\alpha t}) u(t)$	$\frac{\alpha}{s(s+\alpha)}$	exponential approach
$\sin(\omega t) u(t)$	$\frac{\omega}{s^2 + \omega^2}$	sine
$\cos(\omega t) u(t)$	$\frac{s}{s^2 + \omega^2}$	cosine
$e^{-\alpha t} \sin(\omega t) u(t)$	$\frac{\omega}{(s+\alpha)^2 + \omega^2}$	decaying sine wave
$e^{-\alpha t} \cos(\omega t) u(t)$	$\frac{s+\alpha}{(s+\alpha)^2 + \omega^2}$	decaying cosine wave
$f'(t)$	$sF(s) - f(0)$	differentiation
$\int_0^t f(\tau) d\tau$	$\frac{1}{s} F(s)$	integration
$\star \rightarrow \int_0^t f(\tau) g(t-\tau) d\tau$	$F(s) \cdot G(s)$	convolution

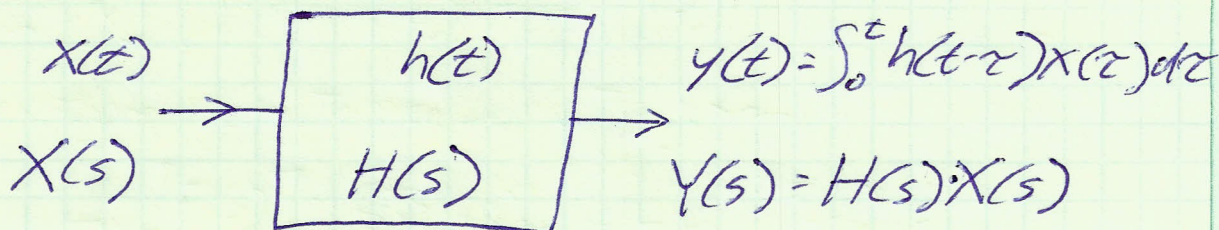Importance of delta function and convolution:




Which would you rather solve: convolution $y(t)$ or multiplication $Y(s)$?

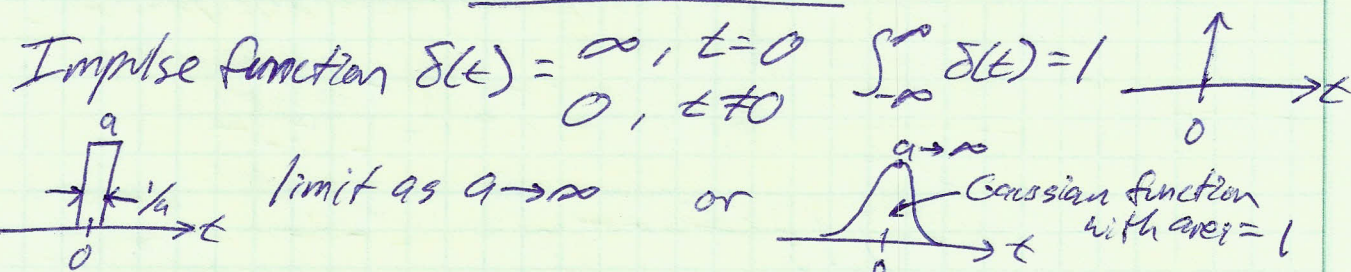$h(t)$ is also called the impulse response function




$h(t)$ is the response of the system to a "ping"

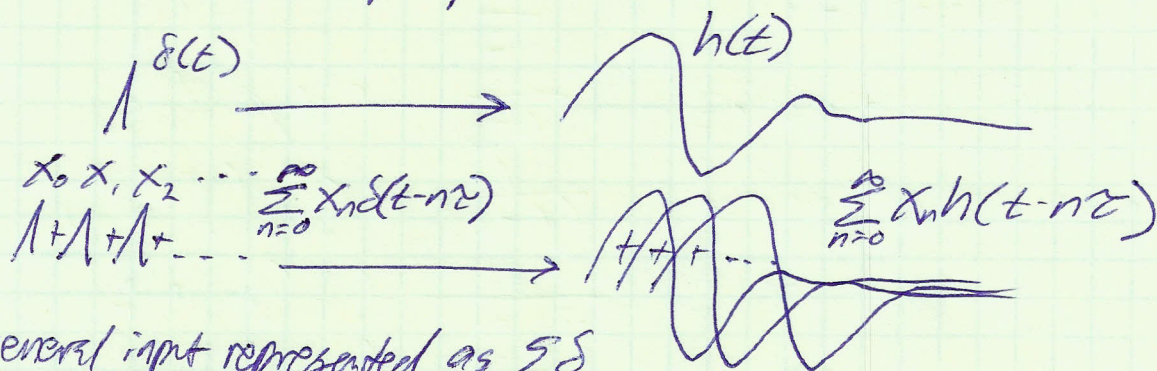- think of a hammer tapping a mechanical system
or a small voltage spike in an electrical system



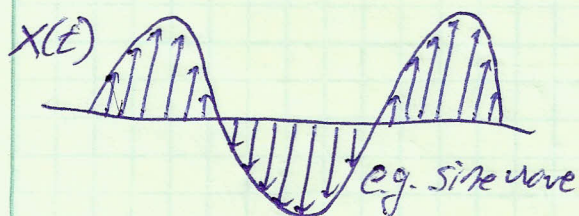general input represented as $\sum \delta$



output: $y(t) = \int_0^t h(t-\tau) x(\tau) d\tau$

integral form of
sum of response to
all previous impulses

Poles and Zeros




$$H(s) = \frac{\sum_{i=0}^m a_i s^i}{\sum_{k=0}^n b_k s^k} = K \frac{\prod_{i=1}^m (s - z_i) \leftarrow \text{zeros } z_i}{\prod_{k=1}^n (s - p_k) \leftarrow \text{poles } p_k}$$

a_i, b_k are real $\rightarrow z_i, p_k$ either real, or complex conjugate pairs

e.g. $s^2 + 2\zeta s + 1 = 0$ has roots at $-\zeta \pm \sqrt{\zeta^2 - 1}$

if $\zeta > 1$, the roots are both real

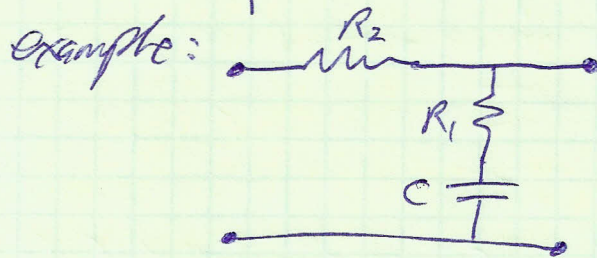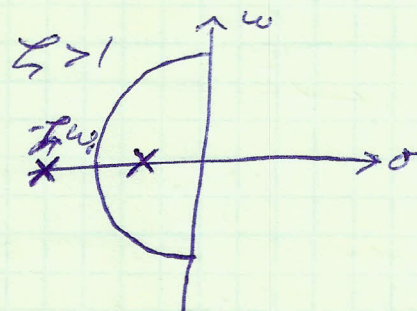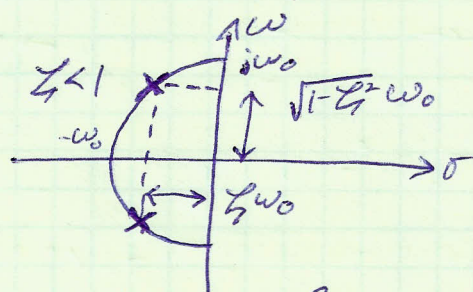if $\zeta < 1$, they are $-\zeta \pm j\sqrt{1 - \zeta^2}$ i.e. conjugate pairs



$$H(s) = \frac{R_1 + 1/sC}{R_1 + R_2 + 1/sC} = \frac{1 + sCR_1}{1 + sC(R_1 + R_2)}$$

pole at $s = -\frac{1}{C(R_1 + R_2)}$

zero at $s = -\frac{1}{CR_1}$

Constraints:

- number of zeros $\leq$ number of poles due to causality

e.g. $H(s) = s \rightarrow$ derivative function would need to know future value of input

- all poles in left half plane $\rightarrow$ stable
- any poles in right half plane $\rightarrow$ unstable

e.g. $\frac{1}{s - \alpha} \rightarrow e^{+\alpha t} u(t)$ pole at $s = +\alpha$
exponential increase

