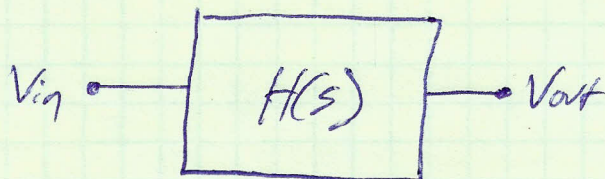


Impulse Response of Some Systems We Have Studied:




$$\delta(t) \rightarrow V_{in}(s) = 1 \longrightarrow V_{out}(s) = H(s)$$

$$\text{arbitrary } V_{in}(s) \longrightarrow V_{out}(s) = H(s) \cdot V_{in}(s)$$


Perform the inverse transform $V_{out}(s) \rightarrow V_{out}(t)$ using tables

Low Pass Filter

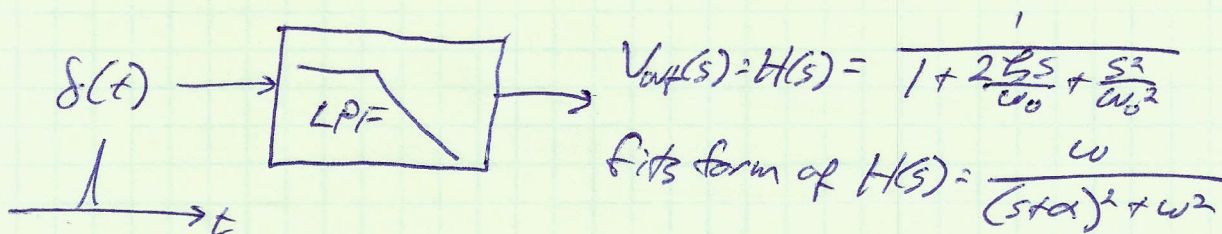

$$H(s) = \frac{\omega_0^2}{s^2 + 2\zeta s \omega_0 + \omega_0^2}$$
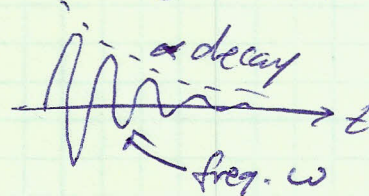
$$V_{out}(t) = e^{-\alpha t} \sin \omega t$$



$$= \frac{\omega_0^2}{(s^2 + 2\zeta s \omega_0 + \zeta^2 \omega_0^2) + \omega_0^2 - \zeta^2 \omega_0^2}$$

complete square

$$= \frac{\omega_0^2}{(s + \zeta \omega_0)^2 + \omega_0^2(1 - \zeta^2)} \times \left[\frac{\omega_0^2(1 - \zeta^2)}{\omega_0^2(1 - \zeta^2)} \right]^{1/2}$$

$$= \frac{\omega_0^2}{[\omega_0^2(1 - \zeta^2)]^{1/2}} \cdot \frac{[\omega_0^2(1 - \zeta^2)]^{1/2}}{(s + \zeta \omega_0)^2 + \omega_0^2(1 - \zeta^2)} = K \frac{\omega}{(s + \alpha)^2 + \omega^2}$$

$\uparrow$ constant (scale factor)

$$V_{out}(t) = \frac{\omega_0}{(1 - \zeta^2)^{1/2}} e^{-\zeta \omega_0 t} \sin[\omega_0(1 - \zeta^2)^{1/2} t]$$

Band Pass Filter

$$H(s) = \frac{2\zeta s/\omega_0}{1 + \frac{2\zeta s}{\omega_0} + \frac{s^2}{\omega_0^2}}$$

we can solve this with:

$$\frac{(s+\alpha)}{(s+\alpha)^2 + \omega^2} \rightarrow e^{-\alpha t} \cos \omega t$$

and

$$\frac{\omega}{(s+\alpha)^2 + \omega^2} \rightarrow e^{-\alpha t} \sin \omega t$$

Why? Force $H(s)$ into this form

$$\frac{K_1(s+\alpha) + K_2\omega}{(s+\alpha)^2 + \omega^2}$$

This term is whatever is left after finding $(s+\alpha)$ term.

$$H(s) = \frac{2\zeta s/\omega_0}{1 + \frac{2\zeta s}{\omega_0} + \frac{s^2}{\omega_0^2}} \cdot \frac{\omega_0^2}{\omega_0^2} = \frac{2\zeta \omega_0 s}{(s + \zeta \omega_0)^2 + \omega_0^2(1 - \zeta^2)} \quad \text{see LPF solution}$$

$$= \frac{2\zeta \omega_0 (s + \zeta \omega_0)}{(s + \zeta \omega_0)^2 + \omega_0^2(1 - \zeta^2)} - \frac{2\zeta^2 \omega_0^2}{(s + \zeta \omega_0)^2 + \omega_0^2(1 - \zeta^2)}$$


$$h(t) = 2\zeta \omega_0 e^{-\zeta \omega_0 t} \cos[\omega_0(1 - \zeta^2)^{1/2} t]$$

$$- \frac{2\zeta^2 \omega_0^2}{\omega_0(1 - \zeta^2)^{1/2}} e^{-\zeta \omega_0 t} \sin[\omega_0(1 - \zeta^2)^{1/2} t]$$



$$\text{at } s=0, |H(s)| = \frac{0}{1} = 0$$

$$\text{at } s=\infty, |H(s)| = \frac{2\zeta s/\omega_0}{s^2/\omega_0^2} = 0$$


$$\text{at } s=j\omega_0, |H(s)| = \frac{2\zeta s/\omega_0}{\frac{s^2}{\omega_0^2}} = 1$$

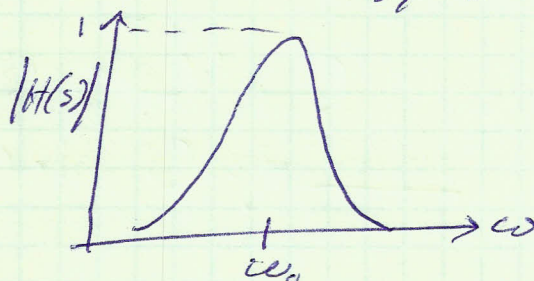

Lab #3 - Voltage Follower Circuit

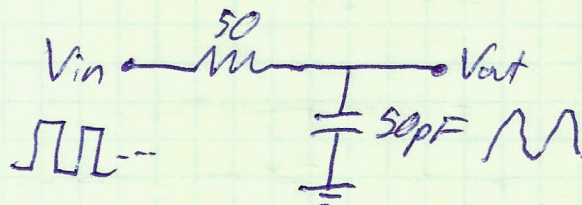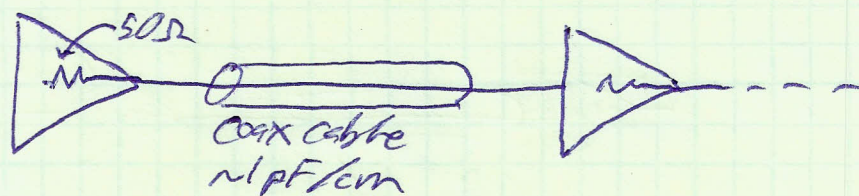

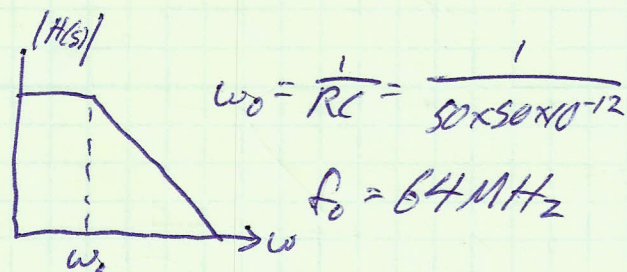
$$H(s) = \frac{1/sC}{R + 1/sC} = \frac{1}{1 + sRC} = \frac{1}{1 + s/\omega_0}$$



Data Rate limited to < 64 Mb/s
How do we send 10 Gb/s?

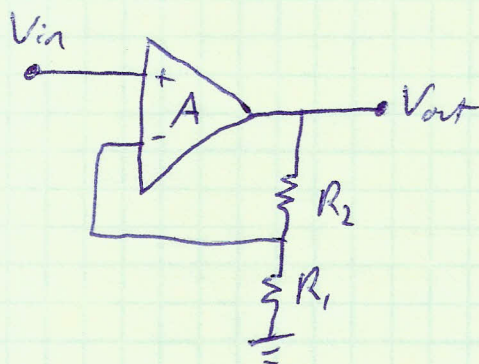Lower Capacitance? - use optical fiber → expensive!
Lower Rout? $50\Omega \rightarrow 0.5\Omega$ Use Feedback!




$$V_- = V_{out} \frac{R_1}{R_1 + R_2} = \underline{\underline{B V_{out}}}$$

$$V_{out} = A(V_+ - V_-) = A(V_{in} - B V_{out})$$

$$\underline{\underline{\frac{V_{out}}{V_{in}} = \frac{A}{1 + AB}}}$$

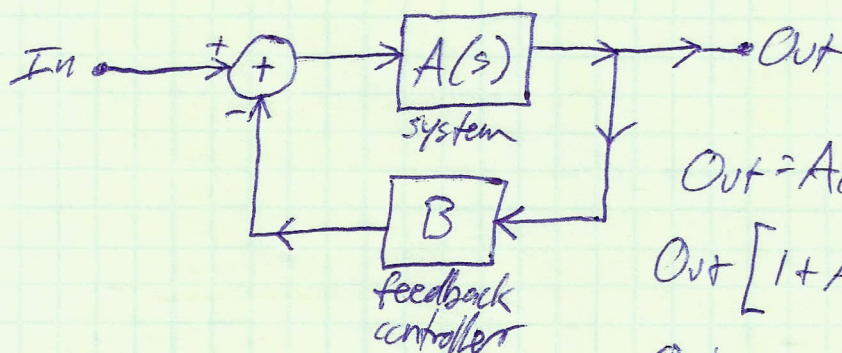This is the general form for feedback systems:




$$Out = A(s) [In - B \cdot Out]$$

$$Out [1 + A(s) \cdot B] = In \cdot A(s)$$

$$\underline{\underline{\frac{Out}{In} = \frac{A(s)}{1 + A(s) \cdot B}}}$$


Real Op-Amp Behavior

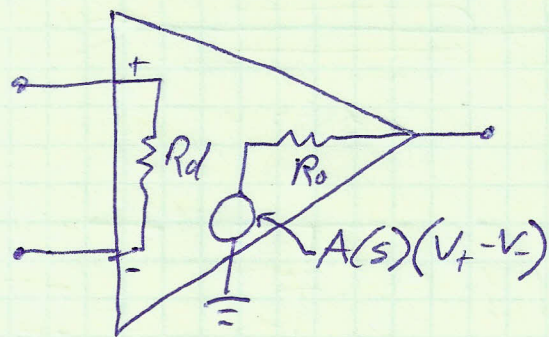

$$R_d \approx 10^7 \text{ (ideally } \infty)$$

$$R_o \approx 100 \text{ (ideally } 0)$$

$$A = \text{ideally } \infty$$

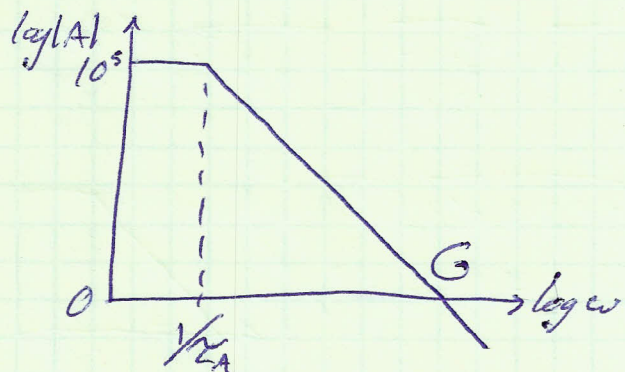

$A(s)$ actually has a pole near zero on the negative real axis

Consider case of $B=1$

$$H(s) = \frac{A(s)}{1+A(s)} = \frac{1}{1+1/A(s)}$$

$$= \frac{1}{1 + \frac{1+s\tau}{A_0}} = \frac{1}{1 + \frac{1}{A_0} + \frac{s\tau}{A_0}} \approx \frac{1}{1 + \frac{s\tau}{A_0}} = \frac{1}{1 + s/G}$$

we can usually ignore this term

Usually $A(s) = G/s$ is a good approximation for op-amp gain

For general B ,


$$H(s) = \frac{A}{1+AB} = \frac{1}{B} \cdot \frac{AB}{1+AB} = \frac{1}{B} \cdot \frac{1}{1+\frac{1}{AB}} = \frac{1}{B} \left(\frac{1}{1 + \frac{s}{GB}} \right)$$

$$\text{DC gain} = 1/B$$


$$\text{Bandwidth (3dB)} = GB$$

Gain-Bandwidth Product
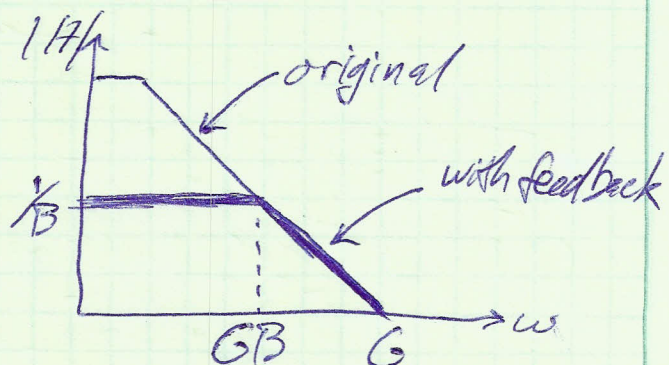
$$\frac{1}{B} \cdot GB = G \rightarrow \text{constant}$$



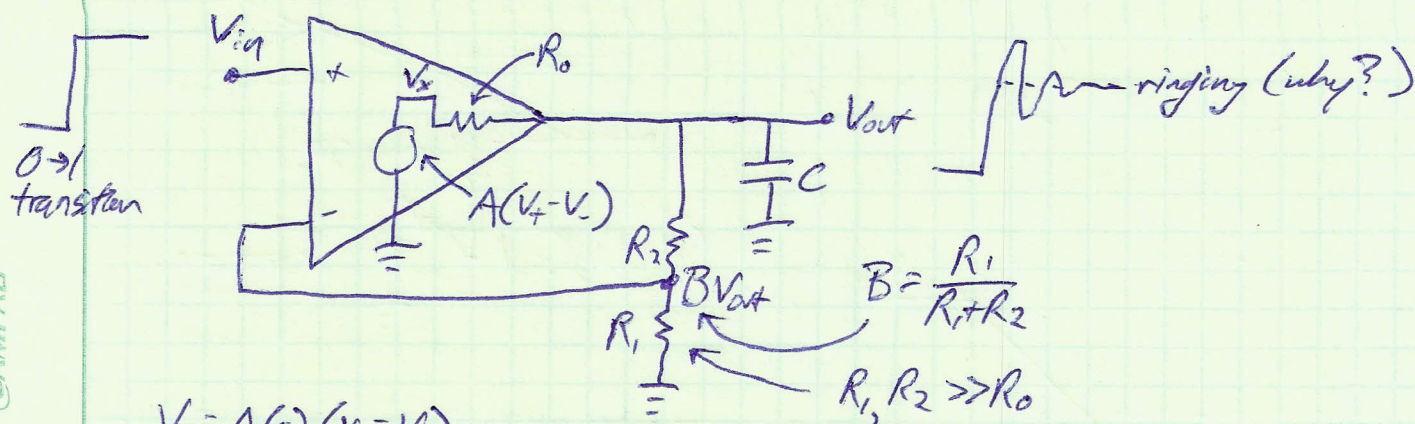Apply voltage follower to capacitive load



$$V_x = A(s)(V_+ - V_-)$$

$$V_x = A(s)(V_{in} - BV_{out}) \quad V_{out} = \frac{V_x}{1 + sR_oC} \quad \text{low pass filter}$$

$$V_x = A(s) \left(V_{in} - \frac{BV_x}{1 + sR_oC} \right)$$

$$V_x \left(1 + \frac{A(s)B}{1 + sR_oC} \right) = A(s)V_{in}$$

$$\frac{V_x}{V_{in}} = \frac{A(s)}{1 + \frac{A(s)B}{1 + sR_oC}} = \frac{A(s)(1 + sR_oC)}{1 + sR_oC + A(s)B} \quad \tau = R_oC$$

$$\frac{V_{out}}{V_{in}} = \frac{A(s)}{1 + s\tau + A(s)B} = \frac{1}{B} \left[\frac{1}{1 + \frac{(1 + s\tau)}{A(s)B}} \right] = \frac{1}{B} \left[\frac{1}{1 + \frac{s(1 + s\tau)}{GB}} \right]$$

$\uparrow A(s) = G/s$

$$\frac{V_{out}}{V_{in}} = \frac{1}{B} \left[\frac{1}{1 + \frac{s}{GB} + \frac{s^2\tau}{GB}} \right] \rightarrow H(s)_{LPF} = \frac{1}{1 + \frac{2\zeta s}{\omega_0} + \frac{s^2}{\omega_0^2}}$$

$$\omega_0 = \sqrt{\frac{GB}{\tau}}, \quad \zeta = \frac{1}{2\sqrt{GB\tau}}$$

make $\zeta \geq 1$ to stop ringing $\rightarrow \tau \geq \frac{1}{4GB}$

Example: $|A| > 1$ at 1 MHz $\rightarrow G = 2\pi \times 10^6$

$B = 0.1 \rightarrow$ DC gain of 10


$R_o = 100$

$$\tau = \frac{1}{4GB} = \frac{1}{8\pi \times 10^5} \approx 4 \times 10^{-7} = R_oC$$

$C = 4 \times 10^{-9}$ or 4 nF

Circuit will ring if C is larger than this

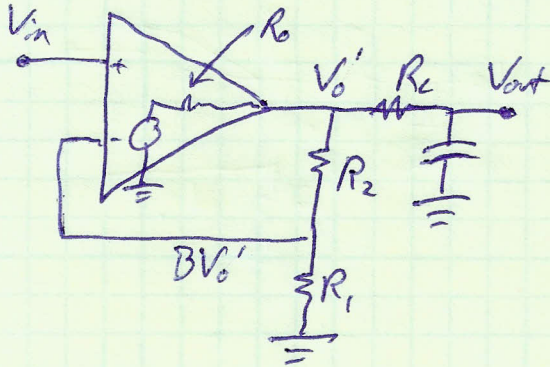Add compensation Resistor to reduce ringing



$$V_o' = A(V_{in} - BV_o') \left[\frac{R_c + 1/sC_c}{R_o + R_c + 1/sC_c} \right]$$

$$\frac{1 + sC_c R_c}{1 + sC_c(R_o + R_c)} = \frac{1 + s\zeta_c}{1 + s(\zeta_L + \zeta_c)}$$

load compensation

$$\frac{V_o'}{V_{in}} = \frac{1}{B} \cdot \frac{1}{1 + \frac{s}{GB} \cdot \frac{1 + s(\zeta_L + \zeta_c)}{1 + s\zeta_c}} = \frac{1}{B} \cdot \frac{1 + s\zeta_c}{1 + s(\zeta_L + \frac{1}{GB}) + s^2 \left(\frac{\zeta_L + \zeta_c}{GB} \right)}$$

$$\frac{V_{out}}{V_o'} = \frac{1}{1 + s\zeta_c} \quad \text{so} \quad \frac{V_{out}}{V_{in}} = \frac{1}{B} \cdot \frac{1}{1 + s(\zeta_L + \frac{1}{GB}) + s^2 \left(\frac{\zeta_L + \zeta_c}{GB} \right)}$$

$$\omega_0 = \sqrt{\frac{GB}{\zeta_L + \zeta_c}} \quad \text{slightly lower}$$

$$\zeta_c = \frac{1}{2} \left(\zeta_L + \frac{1}{GB} \right) \sqrt{\frac{GB}{\zeta_L + \zeta_c}}$$

Using R_c we can adjust ζ_c to ≈ 1 to remove ringing.