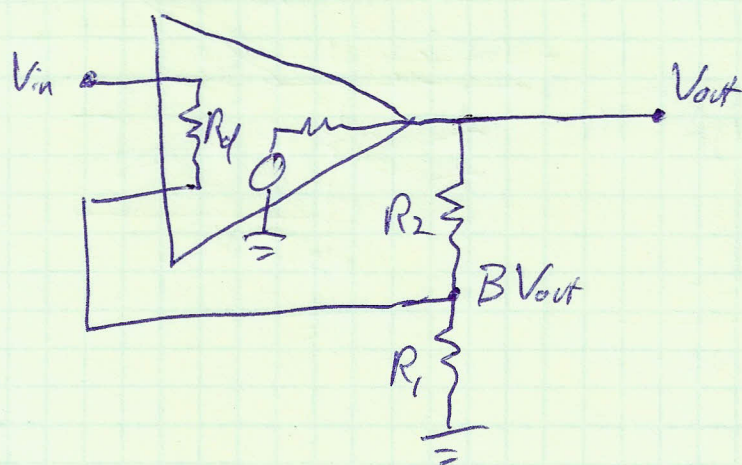


Input Impedance

$$B = \frac{R_1}{R_1 + R_2}$$

$$I_{in} = \frac{V_{in} - BV_{out}}{R_d} = \frac{V_{in}}{R_d} (1 - BH) = \frac{V_{in}}{R_d} \left(1 - \frac{AB}{1+AB}\right) = \frac{V_{in}}{R_d} \frac{1}{1+AB}$$

$$I_{in} = \frac{V_{in}}{R_d} \frac{1}{1 + \frac{GB}{s}}$$

$$A = \frac{G}{s}$$

$$Z_{in} = \frac{V_{in}}{I_{in}} = R_d \left(1 + \frac{GB}{s}\right) = R_d + \frac{1}{sC_{eff}} \leftarrow C_{eff} = \frac{1}{GBR_d}$$

Input impedance is R_d in series with small capacitor.


e.g. $G = 2\pi \times 10^6$, $B = 0.1$, $R_d = 10^7 \rightarrow \underline{0.16 \text{ pF}}$




$$Z = R + jX$$

at $\omega = GB$, $X_{eff} = \frac{GBR_d}{GB} = R_d$

for $\omega < GB$, $X_{eff} > R_d \rightarrow$ input is capacitive

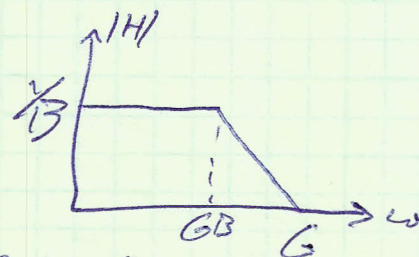for $\omega > GB$, $X_{eff} < R_d \rightarrow$ input is resistive



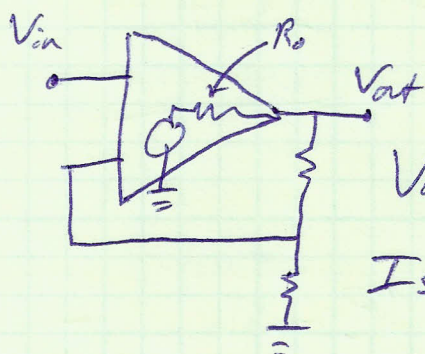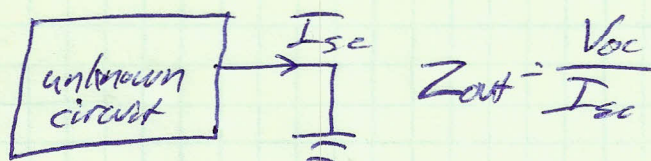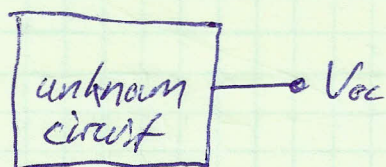Output Impedance

note: $I_{sc} = V_{out}/R_{out}$
 $V_{oc} = V_{out}$

$$V_{out} = H V_{in} = V_{in} \frac{A}{1+AB}$$

$$I_{sc} = A V_{in} / R_o$$

$$Z_{out} = \frac{V_{in} \frac{A}{1+AB}}{A V_{in} / R_o} = \frac{R_o}{1+AB} \quad A = G/s$$

$$Z_{out} = \frac{R_o}{1+GB/s} = \frac{1}{\frac{1}{R_o} + \frac{GB}{R_o s}}$$

Output impedance is R_o in parallel with inductor $X_{eff} = \frac{R_o}{GB}$

for $\omega = GB$, $X_{eff} = R_o$

for $\omega < GB$, $X_{eff} < R_o \rightarrow$ output is inductive

for $\omega > GB$, $X_{eff} > R_o \rightarrow$ output is resistive

3 effects of feedback

1. Reduces and stabilizes gain, increasing bandwidth
2. Increases Z_{in} , but makes it capacitive
3. Reduces Z_{out} , but makes it inductive

Slew Rate Limiting

$$i = C \frac{dV_{out}}{dt}$$




$$V_{out} = A \sin \omega t$$

$$i = AC\omega \cos \omega t$$

$$|i| = AC\omega \rightarrow \text{current scales with:}$$

- Signal amplitude
- Capacitance
- Frequency

$$\left. \frac{dV_{out}}{dt} \right|_{\max} = \frac{i_{\max}}{C}$$

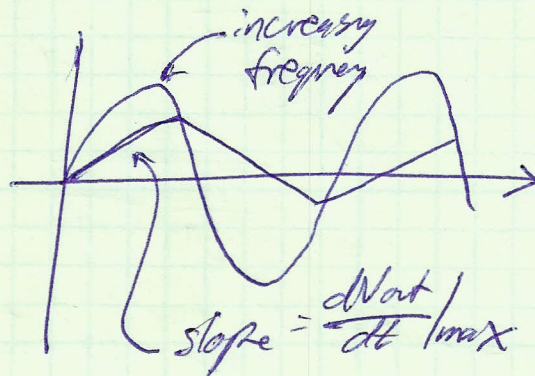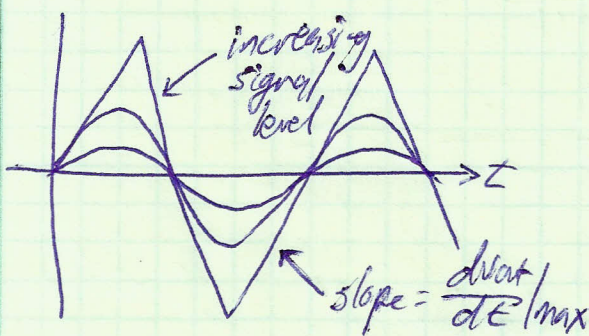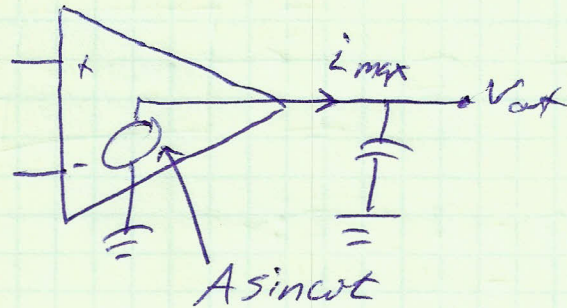

Overshoot and Rise Time



$$\% \text{ overshoot} = \left(\frac{y}{x} - 1 \right) \times 100$$


10% to 90% rise time

Stability Theory

Transfer function always has form of $\sim H(s) = \frac{1}{B} \left(\frac{AB}{1+AB} \right) = \frac{A}{1+AB}$

Always has $1+AB$ in denominator

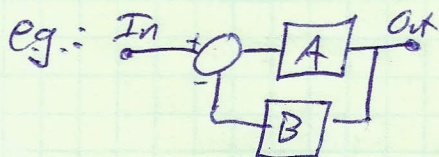Numerator depends on how the input enters the circuit




$$A(In - BOut) = Out$$

$$AIn - ABOut = Out$$

$$AIn = Out(1+AB)$$

$$\frac{Out}{In} = \frac{A}{1+AB}$$

another common form:

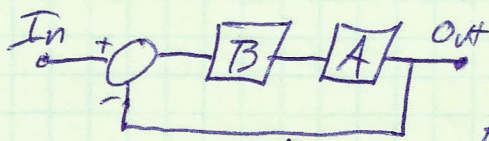

$$AB(In - Out) = Out$$

$$ABIn - ABOut = Out$$

$$ABIn = Out(1+AB)$$

$$\frac{Out}{In} = \frac{AB}{1+AB}$$

If we cut the feedback loop here

then we have $Out = \underline{AB} In$ where AB is the open-loop transfer func.

We can analyze AB to determine stability of the closed loop system

Circuit cannot be stable if any subcircuit (A, B) is unstable

How to determine stability:

Does $1+AB$ have any zeros in right half plane?

Is $AB = -1$ for any s ?

Remember $-1 = 1 \angle -180^\circ$

Point of neutral stability (just barely stable/unstable):


$$|AB| = 1 \text{ and } \angle AB = \pm 180^\circ$$

Gain and Phase Margin

Gain Margin = $-20 \log_{10} |AB|$ at ω where $\angle AB = -180^\circ$


Phase Margin = $\angle AB + 180^\circ$ at ω where $|AB| = 1$ (0dB)

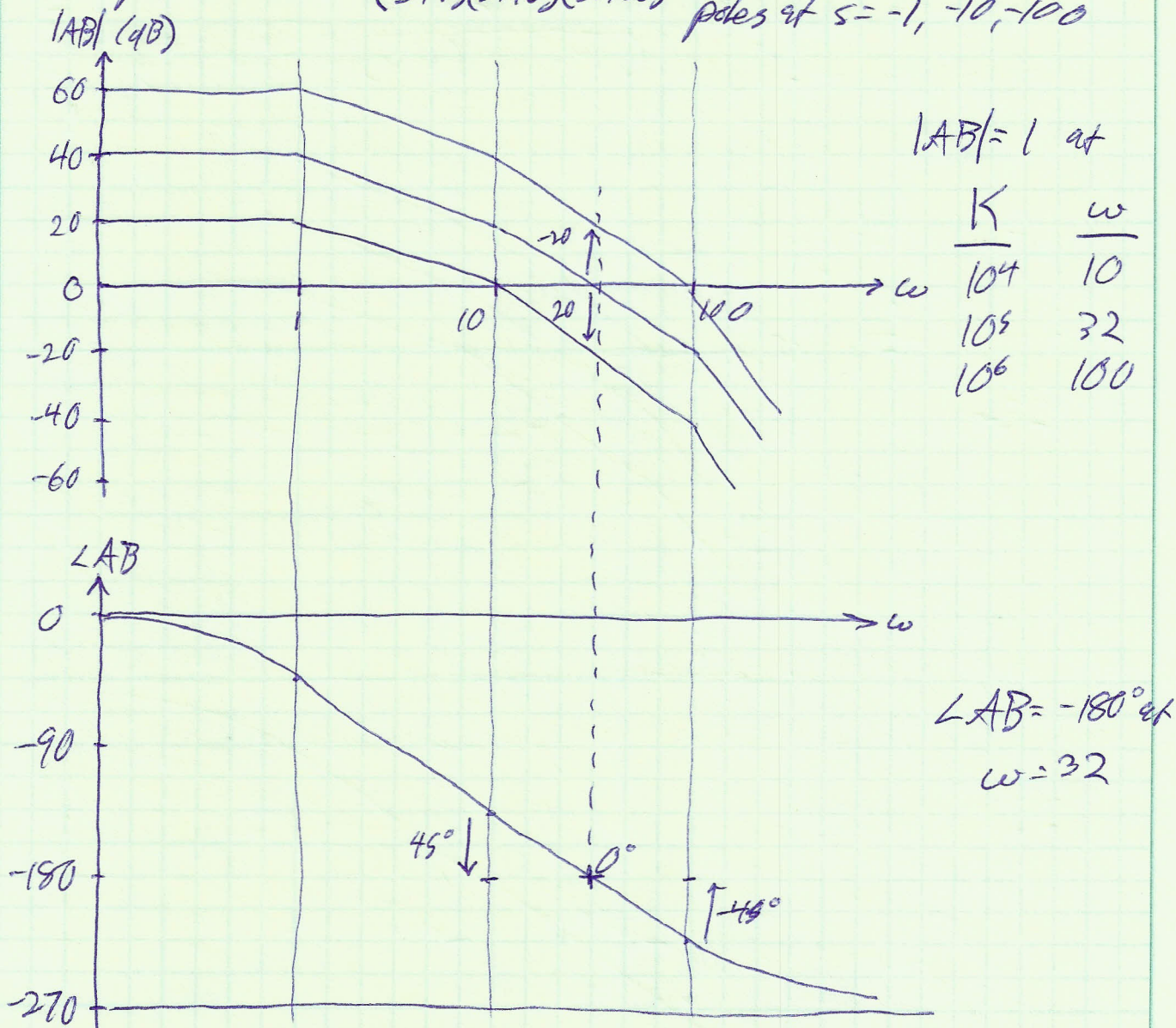Example: $AB = \frac{K}{(s+1)(s+10)(s+100)}$ for $K = 10^4, 10^5, 10^6$
poles at $s = -1, -10, -100$



K	G.M	P.M	stability	Roots of $(s+1)(s+10)(s+100)+K=0$?
10^4	20dB	45°	stable	$-101, -5 \pm 9j$
10^5	0dB	0°	marginally stable	$-109, -0.8 \pm 30j$
10^6	-20dB	45°	unstable	$-148, 18 \pm 80j$ ↑ in RHP!

Nyquist Stability Criterion

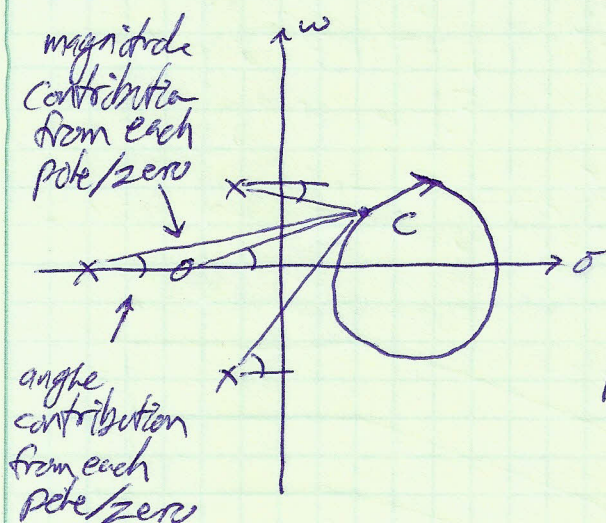


Consider a contour C in the s plane
If C does not enclose any poles or zeros, it will not go through a full 360° of phase

$$1+AB = \frac{\prod (s-z_i)}{\prod (s-p_j)} = \text{Mag} e^{i\text{Ph}}$$

$$\text{Mag} = \frac{\prod \text{magnitude from zeros}}{\prod \text{magnitude from poles}}$$
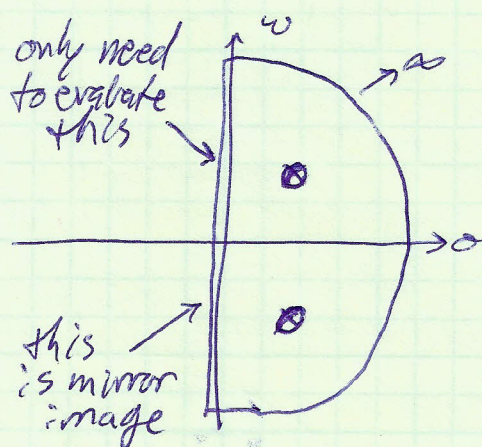
$$\text{Ph} = \sum \text{phase from zeros} - \sum \text{phase from poles}$$



We take a contour along imaginary axis and extending to ∞ on positive real side

total number of times contour of $1+AB$ encircles origin: $N = Z - P$ (clockwise)

$Z = \# \text{Zeros of } 1+AB \text{ in RHP}$

$P = \# \text{Poles of } 1+AB \text{ in RHP}$

but poles of $1+AB = \text{poles of } AB$

we know these have no poles in RHP if A and B are stable

If contour of $1+AB$ encircles origin clockwise, system is unstable

We actually look for encirclements of -1 in plot of AB

If $AB = -1$, there is a pole right on the ω axis.