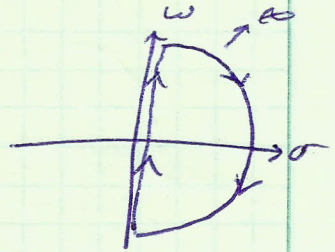


Nyquist Stability Criterion (continued)


- A contour evaluation of a complex function will only encircle the origin if the contour contains a singularity of the function.
- Number of clockwise encirclements $N = Z - P$
 - Z = number of zeros within contour
 - P = number of poles within contour
- Contour is taken to be the entire RHP
 - Negative ω axis is just mirror image of positive ω axis
 - Contour at $s \rightarrow \infty$ contributes nothing if number of poles in AB is greater than number of zeros (which must be true!)
 - $\rightarrow$ transfer function cannot go to ∞ as s (or ω) go to ∞
- If A and B are stable individually, they have no poles in RHP
 - Subcircuits must all be stable for whole circuit to be stable
 - Poles of $1 + AB$ are the same as poles of AB
 - We are now only concerned with Zeros of $1 + AB$ in RHP
- We typically plot AB, look for clockwise encirclements of -1
- Procedure for drawing simple Nyquist plots:
 1. Draw a Bode plot of open-loop transfer function AB
 2. Look for points where phase crosses $0, -90, -180, \dots$
 3. Plot these intercept points based on magnitude plot
 4. Connect the dots, based on shape of magnitude + phase functions

Be sure to include where magnitude may approach 0 or ∞




Revisit our previous example
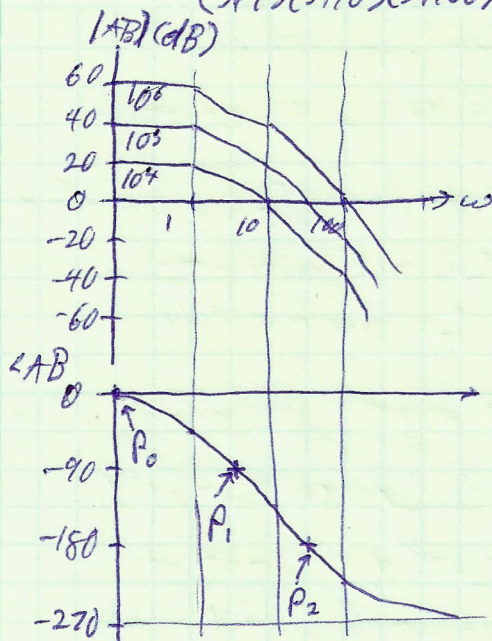
$$AB = \frac{K}{(s+1)(s+10)(s+100)} \quad \text{for } K = 10^4, 10^5, 10^6$$



$$K = 10^4:$$

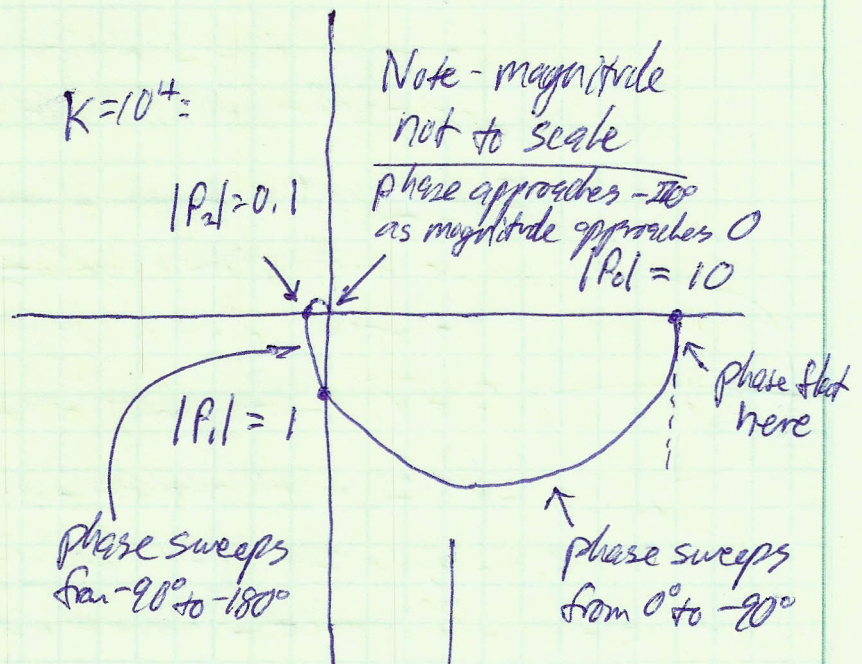

Does the plot encircle -1?

Depends on the value of K .

$K = 10^4 \rightarrow$ no



$K = 10^5 \rightarrow$ just barely


$K = 10^6 \rightarrow$ yes

Same result as our previous mag/phase margin analysis!

We can also get mag/phase margin from Nyquist plots:

Complete Nyquist plot (all cases)

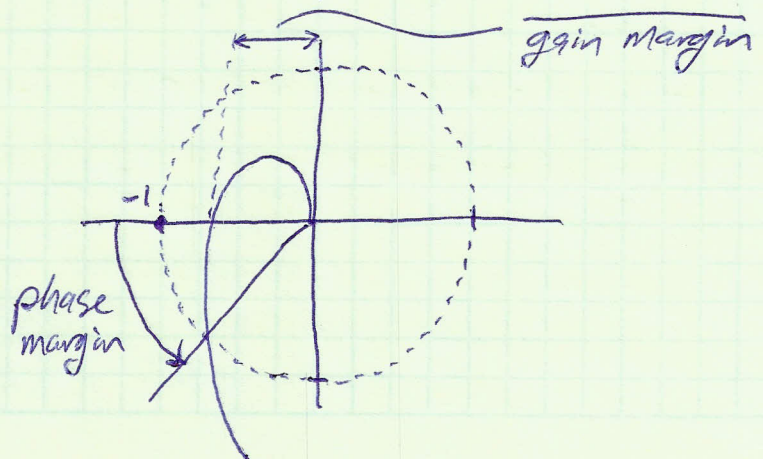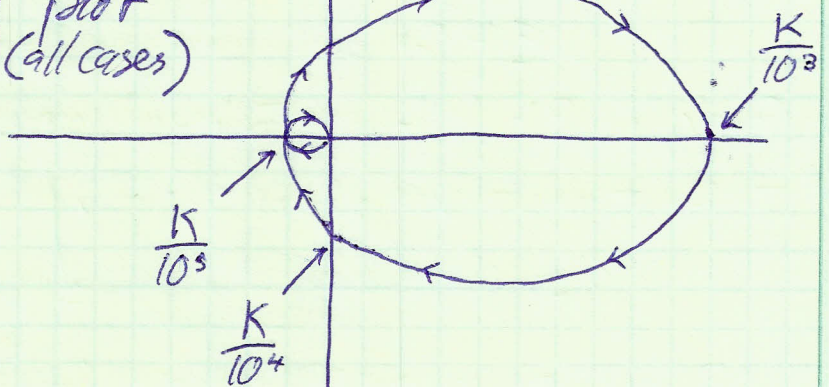


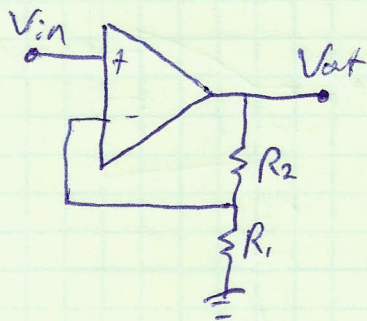Example: Voltage follower circuit


$$A = \frac{A_0}{1 + s\tau_A}$$

$$B = \frac{R_1}{R_1 + R_2}$$

(constant)

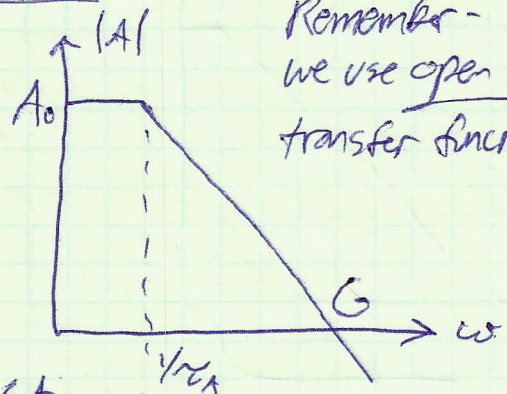


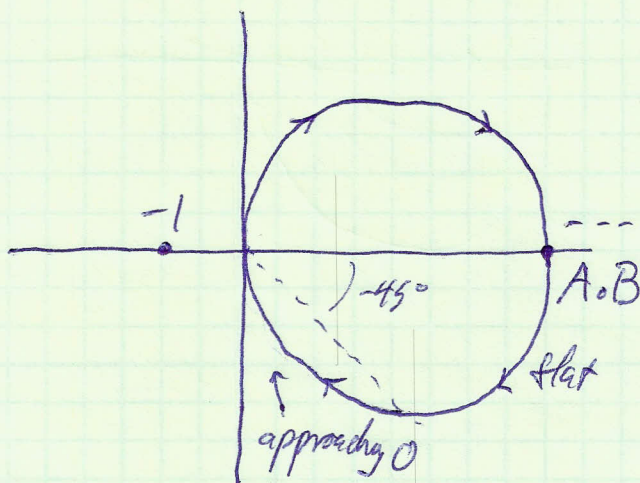Remember -
we use open loop
transfer function: AB



--- $\rightarrow \infty$ if we use $A = G/s$ model

Does not encircle -1
Unconditionally stable

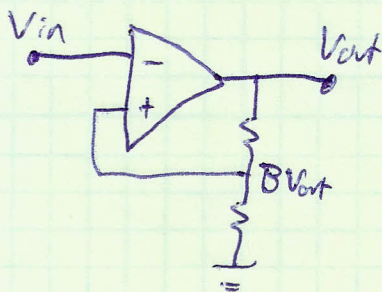
Example: Schmitt trigger

$$V_{out} = A(BV_{out} - V_{in})$$

$$A V_{in} = AB V_{out} - V_{out}$$

$$\frac{V_{out}}{V_{in}} = \frac{-A}{1 - AB} = \frac{-A}{1 + T}$$
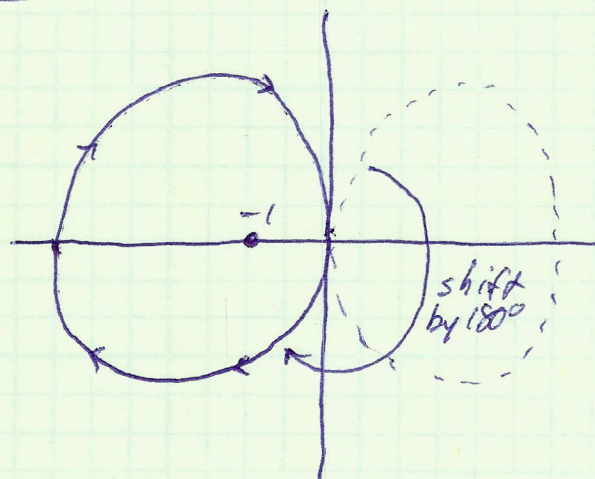
$$T = -AB \rightarrow \text{shifted by } 180^\circ$$




Encircles -1 one time, clockwise
closed loop transfer function
has one pole in RHP

Schmitt trigger (continued)

Assume $\pm 15V$ bias, and amplifier saturates at $\pm 13V$

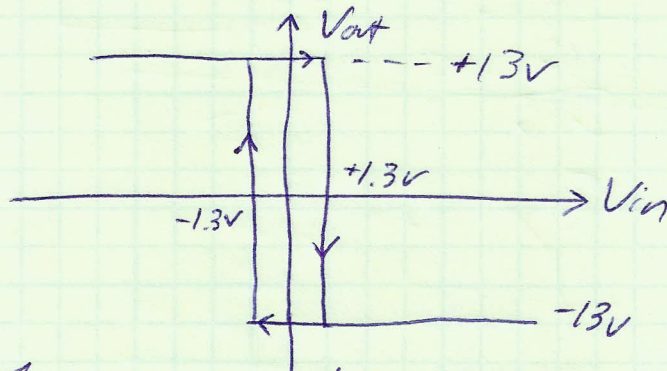Assume $B=0.1$, let $V_{in} = -15V \rightarrow +15V$




When $V_{in} > 1.3V$
output switches to $-13V$

The circuit is bistable, with hysteresis
Used in many digital circuits

$$H(s) = \frac{-A}{1-AB} = \frac{1}{B} \cdot \frac{1}{1-AB} = \frac{1}{B} \cdot \frac{1}{1-\frac{s}{GB}} = -G \cdot \frac{1}{s-GB}$$

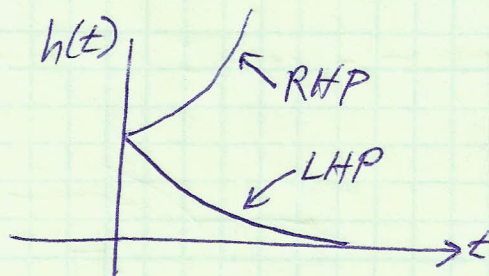
recall Laplace transform $\frac{1}{1+\alpha} \leftrightarrow e^{-\alpha t} u(t)$ ↖ pole in RHP



pole in LHP: exponential decay: e^{-tGB}
pole in RHP: exponential growth: e^{+tGB}

The circuit switches very quickly because
the feedback increases the drive to change state.

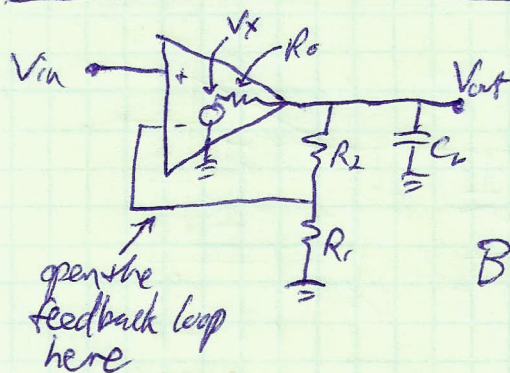Example: Voltage follower with Capacitive Load (Lab#3)



$$B = \frac{R_1}{R_1 + R_2}$$



$$\frac{V_x}{V_{in}} = \frac{A_o}{1 + s\tau_A}, \quad \frac{V_{out}}{V_x} = \frac{1/sC_L}{R_1 + 1/sC_L} = \frac{1}{1 + sR_1C_L}$$

$$AB = \frac{A_o}{1 + s\tau_A} \cdot \frac{1}{1 + sR_1C_L} \cdot \frac{R_1}{R_1 + R_2}$$



Phase gets close to -180° , but never exceeds it.

However, real op-amps have a second pole near $\sim 2G$
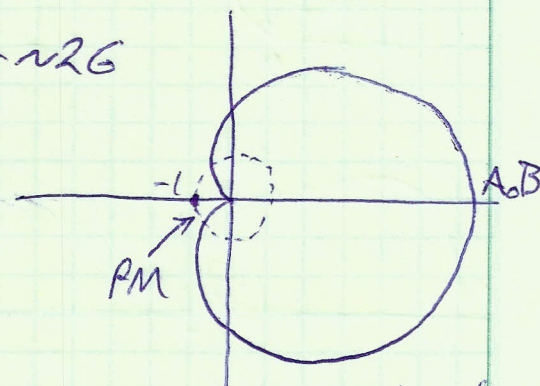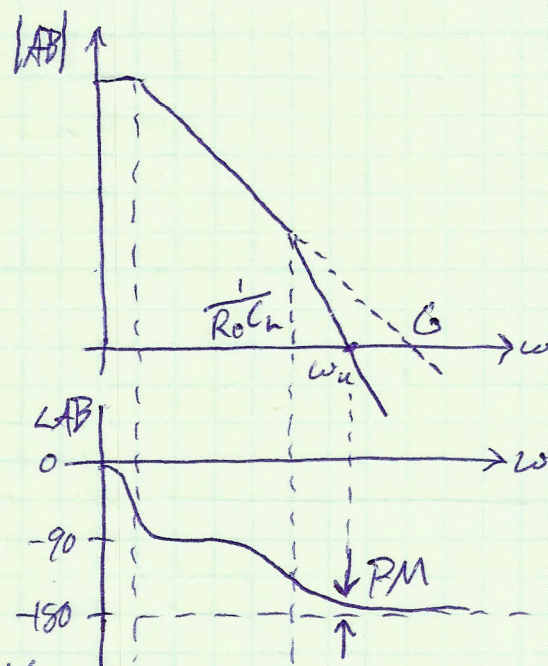
$$AB = \frac{A_o}{1 + s\tau_A} \cdot \frac{1}{1 + s/2G} \cdot \frac{1}{1 + sR_1C_L} \cdot \frac{R_1}{R_1 + R_2}$$




with extra pole

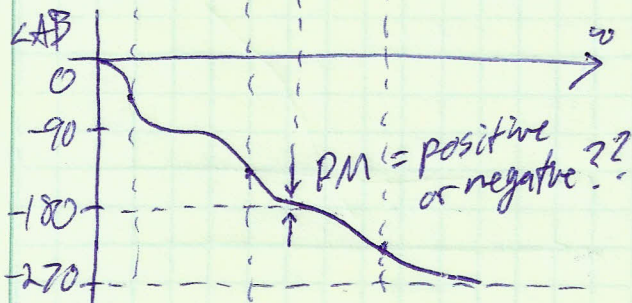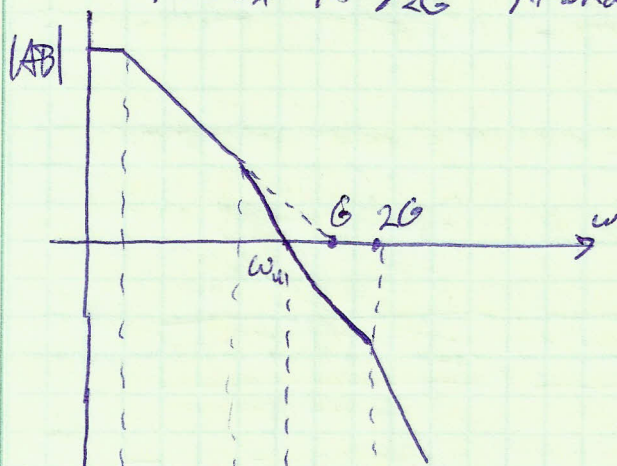


Phase Margin may be positive (stable) or negative (unstable) depending on the relative frequencies of the various poles

Effect of Compensation



Change this:

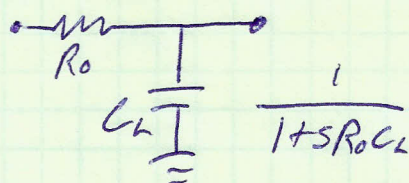

to this:

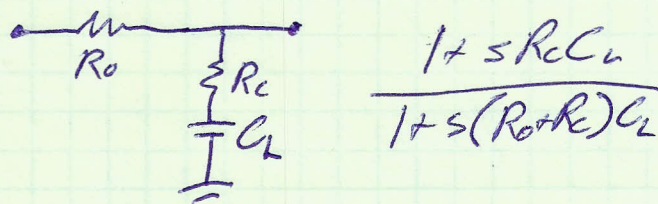

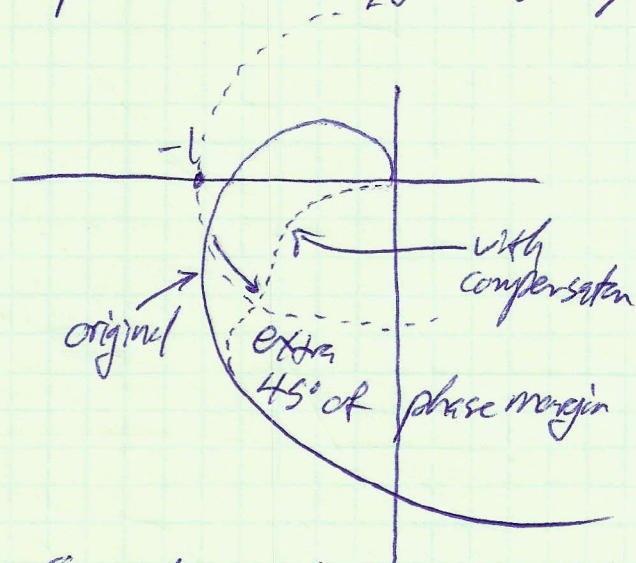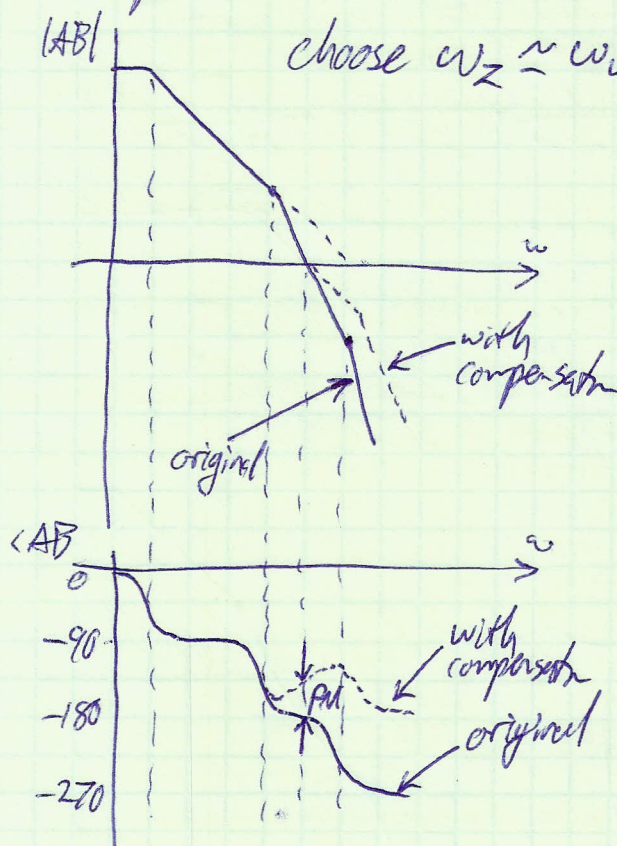Compensation resistor adds a zero to the transfer function
choose $\omega_z \approx \omega_u \rightarrow$ put zero near unity gain frequency



General approach to compensation:

Look for a way to add a zero to the feedback path or transfer function

Effect of Delay

$$f(t-a)U(t-a) \longleftrightarrow e^{-as} F(s)$$

causes a phase lag, but does not reduce gain
(compare this to a pole, which does both)
tends to cause instability

Examples:

- loudspeaker to microphone feedback
- attempt to control water temperature in a shower
- psycho-acoustic effect of delay between speaking and hearing