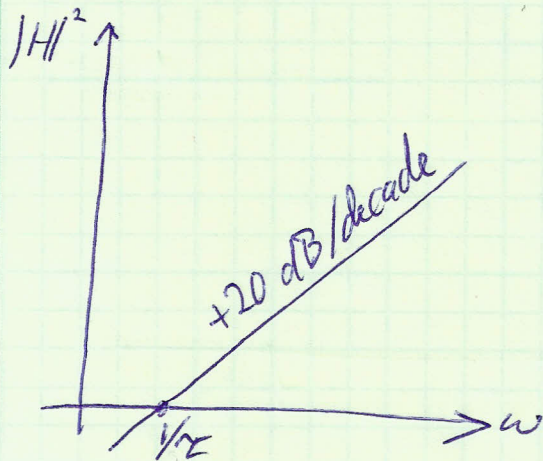


Lab #4: Design of a Differentiator

Laplace transform: $f'(t) \leftrightarrow sF(s) - f(0) \leftarrow$ initial value

We need a system where $H(s) = s \leftarrow$ scale factor



phase = $+90^\circ$ at all ω .

problems with this system:

- Non causal: can't anticipate phase of incoming signal at all frequencies
- Can't have Gain $\rightarrow \infty$ for $\omega \rightarrow \infty$ (can't have more zeros than poles)

Consider this circuit:

Simple model: $V_- = 0$

$$\frac{0 - V_{in}}{Z_i} + \frac{0 - V_{out}}{Z_f} = 0$$

$$\frac{V_{out}}{V_{in}} = -\frac{Z_f}{Z_i}$$



$$\frac{V_{out}}{V_{in}} = -sCR$$

or $V_{out}(s) = -s\tau V_{in}(s)$

$$V_{out}(t) = -\tau \frac{dV_{in}(t)}{dt}$$

$$\tau = RC$$


note RC has units of time

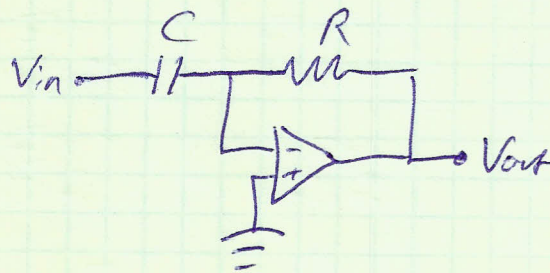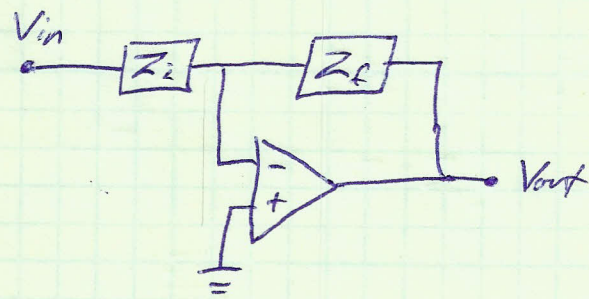

$V_{in}(t)$:




$V_{out}(t)$:

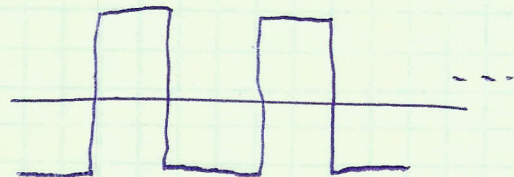

what about $\tau = RC$ factor?


example: $RC = 10^{-3}$

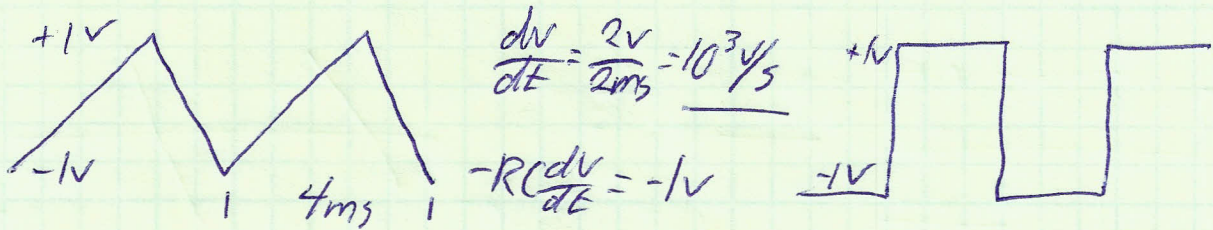

however, what you actually see in the lab is:

This must be a second-order system.

More detailed analysis:

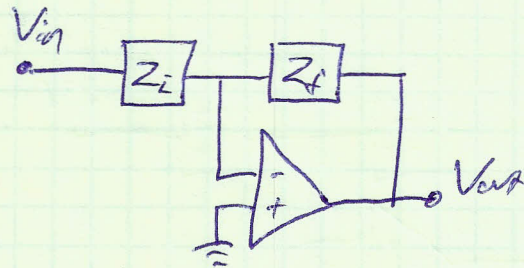

$$V_{out} = -A V_-$$

$$\frac{V_- - V_{out}}{Z_f} + \frac{V_- - V_{in}}{Z_i} = 0$$

$$V_- \left(\frac{1}{Z_f} + \frac{1}{Z_i} \right) = \frac{V_{out}}{Z_f} + \frac{V_{in}}{Z_i}$$

$$V_- (Z_i + Z_f) = V_{out} Z_i + V_{in} Z_f$$



$$V_- = V_{out} \frac{Z_i}{Z_i + Z_f} + V_{in} \frac{Z_f}{Z_i + Z_f}$$

$$V_{out} = -A V_- = -A \left(V_{out} \frac{Z_i}{Z_i + Z_f} + V_{in} \frac{Z_f}{Z_i + Z_f} \right)$$

$$V_{out} \left(1 + A \frac{Z_i}{Z_i + Z_f} \right) = -A V_{in} \frac{Z_f}{Z_i + Z_f}$$

$$\frac{V_{out}}{V_{in}} = \frac{-Z_f}{Z_i} \cdot \frac{AB}{1+AB} \quad \text{where } B = \frac{Z_i}{Z_i + Z_f}$$

$$H_{ideal} = \frac{-Z_f}{Z_i} \quad \text{and} \quad H_{real} = H_{ideal} \cdot \frac{AB}{1+AB}$$

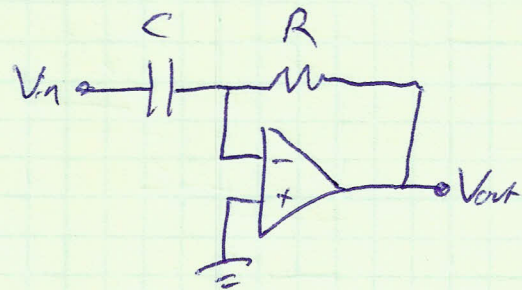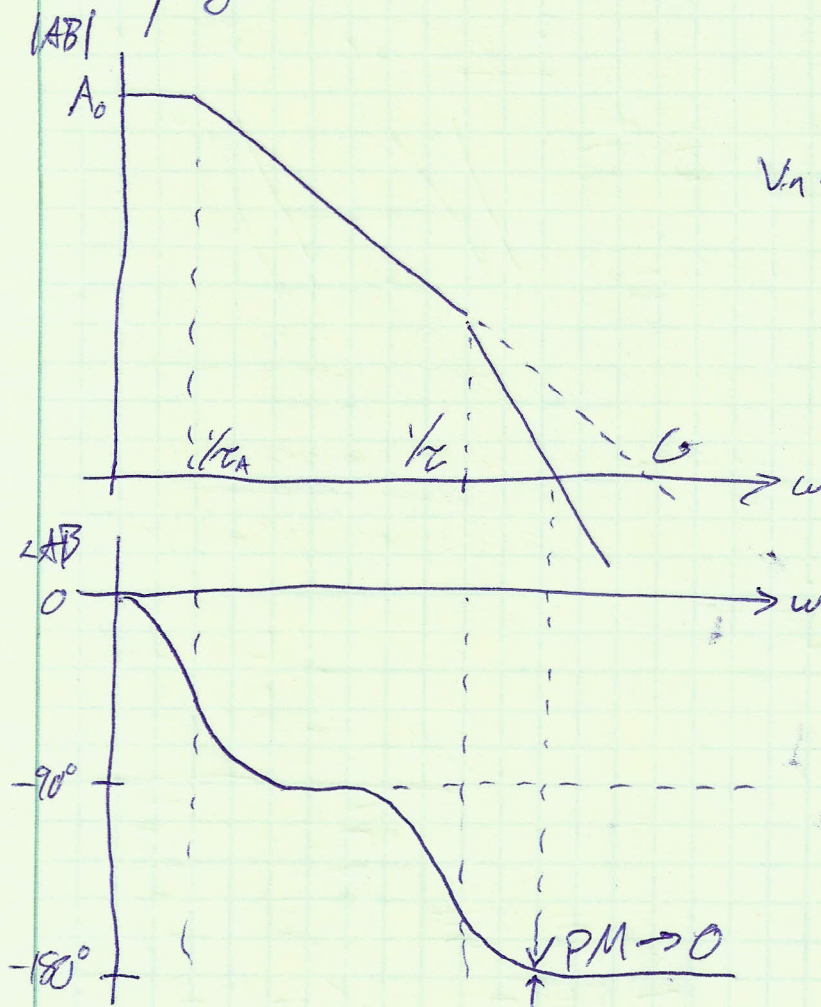Loop gain AB for Differentiator

Phase margin approaches zero

- response will be \int with overshoot and oscillations
- may even be unstable (considering higher op-amp poles)

How do we eliminate this? - Compensation (next lecture)

Remainder of this lecture - review for Midterm #1