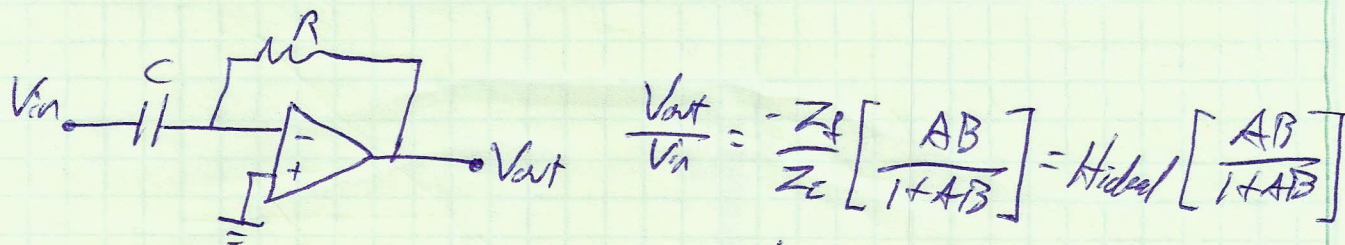


More on Lab #4 - Design of a Differentiator

$$Z_i = \frac{1}{sC}, Z_f = R, B = \frac{Z_i}{Z_i + Z_f} \quad B = \frac{1}{1+sCR} \quad A = G/s$$

Check last lecture for derivation and other details

$$\frac{AB}{1+AB} = \frac{1}{1+1/AB} = \frac{1}{1+\frac{s}{G}(1+sCR)} = \frac{1}{1+\frac{s}{G} + \frac{s^2 CR}{G}}$$

This is a 2nd order Low pass filter. Define $\tau \equiv RC$

$$\frac{1}{1+\frac{s}{G} + \frac{s^2 \tau}{G}} = \frac{1}{1+\frac{2\zeta s}{\omega_0} + \frac{s^2}{\omega_0^2}}$$

$$\frac{\tau}{G} = \frac{1}{\omega_0^2} \rightarrow \omega_0 = \sqrt{\frac{G}{\tau}}$$

$$\frac{2\zeta}{\omega_0} = \frac{1}{G} \rightarrow \zeta = \frac{\omega_0}{2G} = \sqrt{\frac{G}{\tau}} \cdot \frac{1}{2G} = \frac{1}{\sqrt{4G\tau}}$$


$$\text{for } RC = 25 \times 10^{-4}$$

$$\text{and } G = 2 \times 10^6 \text{ (1 MHz unity gain frequency)}$$

$$\zeta = \frac{1}{\sqrt{4 \times 2 \times 10^6 \times 25 \times 10^{-4}}} \approx \frac{1}{80} \rightarrow \text{very small damping}$$

$$\text{Compare to Butterworth, } \zeta = \frac{1}{\sqrt{2}} = 0.707$$

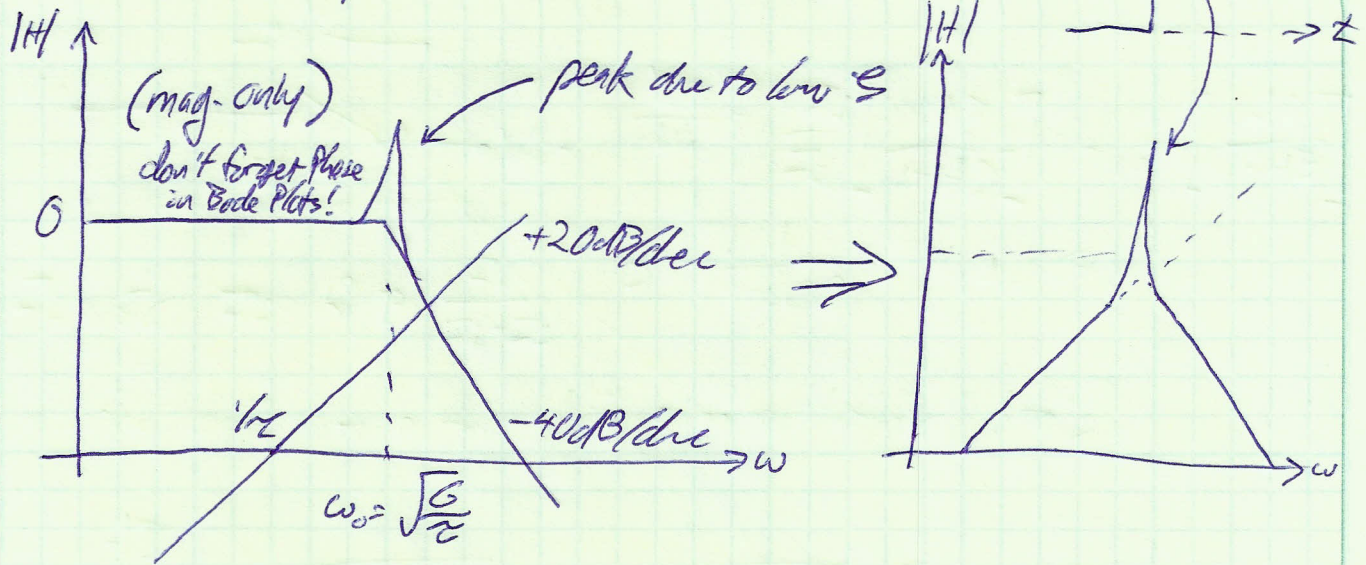
Bode plot is composite of $\frac{Z_f}{Z_i}$ and $\frac{AB}{1+AB}$



Low ξ causes: (1) Ringing and overshoot in time domain
(2) Peaking in frequency domain


We can also see the problem in the loop gain:
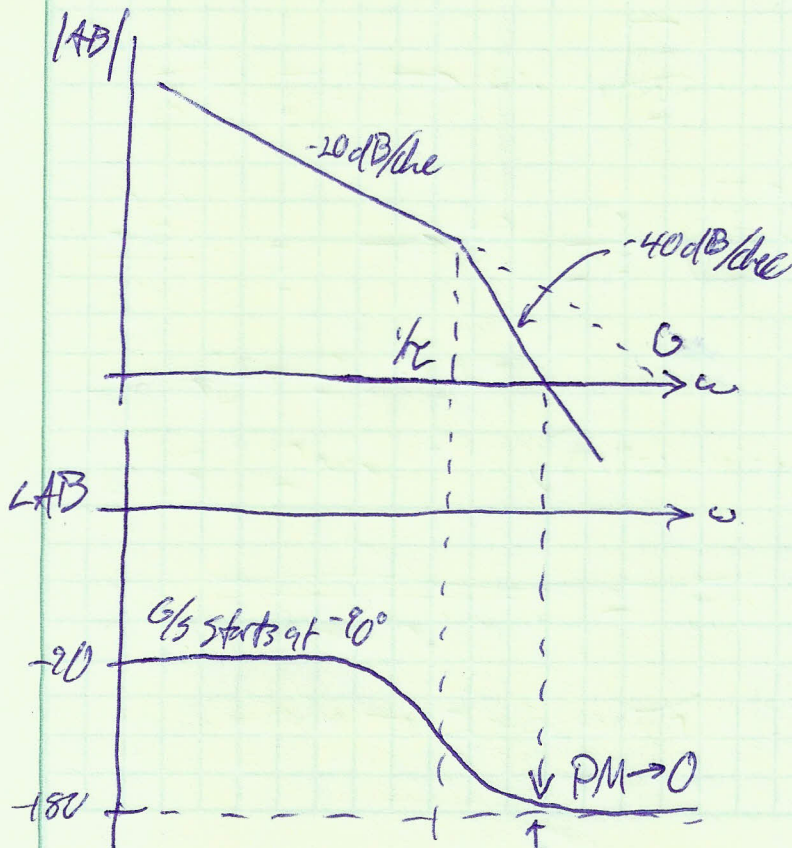
$$AB = \frac{G}{s} \cdot \frac{1}{1+s\tau}$$



Phase Margin approaches 0

Fixing the problem with Compensation

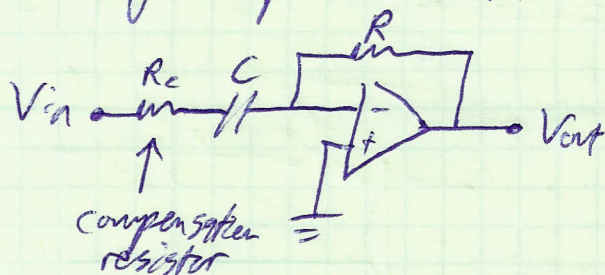

(add a zero to the transfer function)

$$\frac{AB}{1+AB} = \frac{1}{1+\frac{1}{AB}}, \quad B = \frac{Z_i}{Z_f + Z_i} = \frac{R_c + 1/sC}{R + R_c + 1/sC}$$

$$B = \frac{1 + sCR_c}{1 + sC(R + R_c)} \quad \leftarrow \text{added a zero (old } B = \frac{1}{1 + sCR} \right)$$


$$\text{for } A = \frac{G}{s}, \quad \frac{1}{1 + \frac{1}{AB}} = \frac{1}{1 + \frac{s}{G} \frac{1 + s(\tau + \tau_c)}{1 + s\tau_c}} \quad \begin{matrix} \tau = RC \\ \tau_c = R_c C \end{matrix}$$

$$\frac{1}{1 + \frac{1}{AB}} = \frac{1 + s\tau_c}{1 + s\tau_c + \frac{s}{G} + \frac{s^2(\tau + \tau_c)}{G}}$$

$$\omega_0 = \sqrt{\frac{G}{\tau + \tau_c}} \quad \zeta = \frac{1}{2} \sqrt{\frac{c}{\tau + \tau_c}} \left(\tau_c + \frac{1}{G} \right)$$

allows good control over ζ

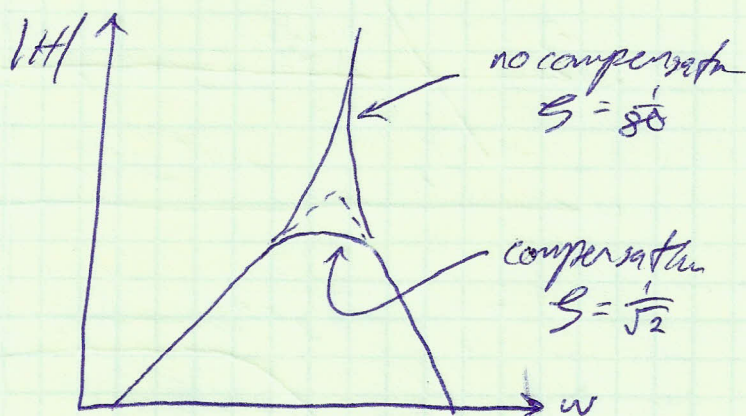making $\zeta = \frac{1}{\sqrt{2}}$ gives Butterworth response



Relationship between ζ and phase margin
(only valid for 2nd order systems)

using example of differentiator

$$A = \frac{G}{s} \quad B = \frac{1}{1+s\tau}$$

$$|AB| = \left| \frac{G}{s} \cdot \frac{1}{1+s\tau} \right| = 1 \rightarrow \left| \frac{G}{s} \right|^2 = |1+s\tau|^2$$

$$\frac{G^2}{\omega^2} = 1 + \omega^2 \tau^2 \quad \text{usually } \omega^2 \tau^2 \gg 1$$

$$\frac{G^2}{\omega^2} \approx \omega^2 \tau^2 \quad \text{or } \omega_u \approx \sqrt{\frac{G}{\tau}} \leftarrow \text{frequency where } |AB|=1$$

calculate the phase at this frequency

$$PM = 180 + \angle AB \text{ at } \omega_u$$

$$= 180 + \angle A + \angle B \quad \text{but } \angle A \text{ is } -90 \text{ always (A = } G/s \text{)}$$

$$PM = 90 + \angle B$$

$$B = \frac{1}{1+s\tau} \rightarrow \angle B = -\tan^{-1} \omega_u \tau$$


$$B = -\tan^{-1} \sqrt{\frac{G}{\tau}} \tau = -\tan^{-1} \sqrt{G\tau}$$

$$PM = 90 - \tan^{-1} \sqrt{G\tau}$$


$$\text{remember } \zeta = \frac{1}{2\sqrt{G\tau}}$$

$$PM = 90 - \tan^{-1} \left(\frac{1}{2\zeta} \right)$$


general equation for
2nd order systems

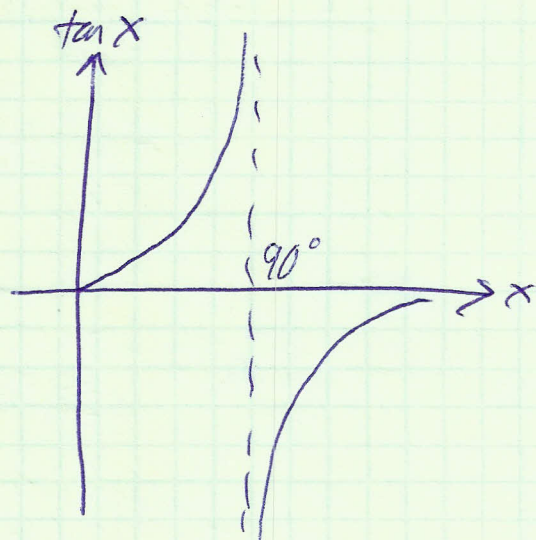

Another similar example - Integrator

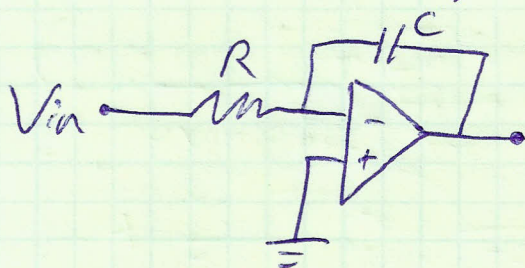
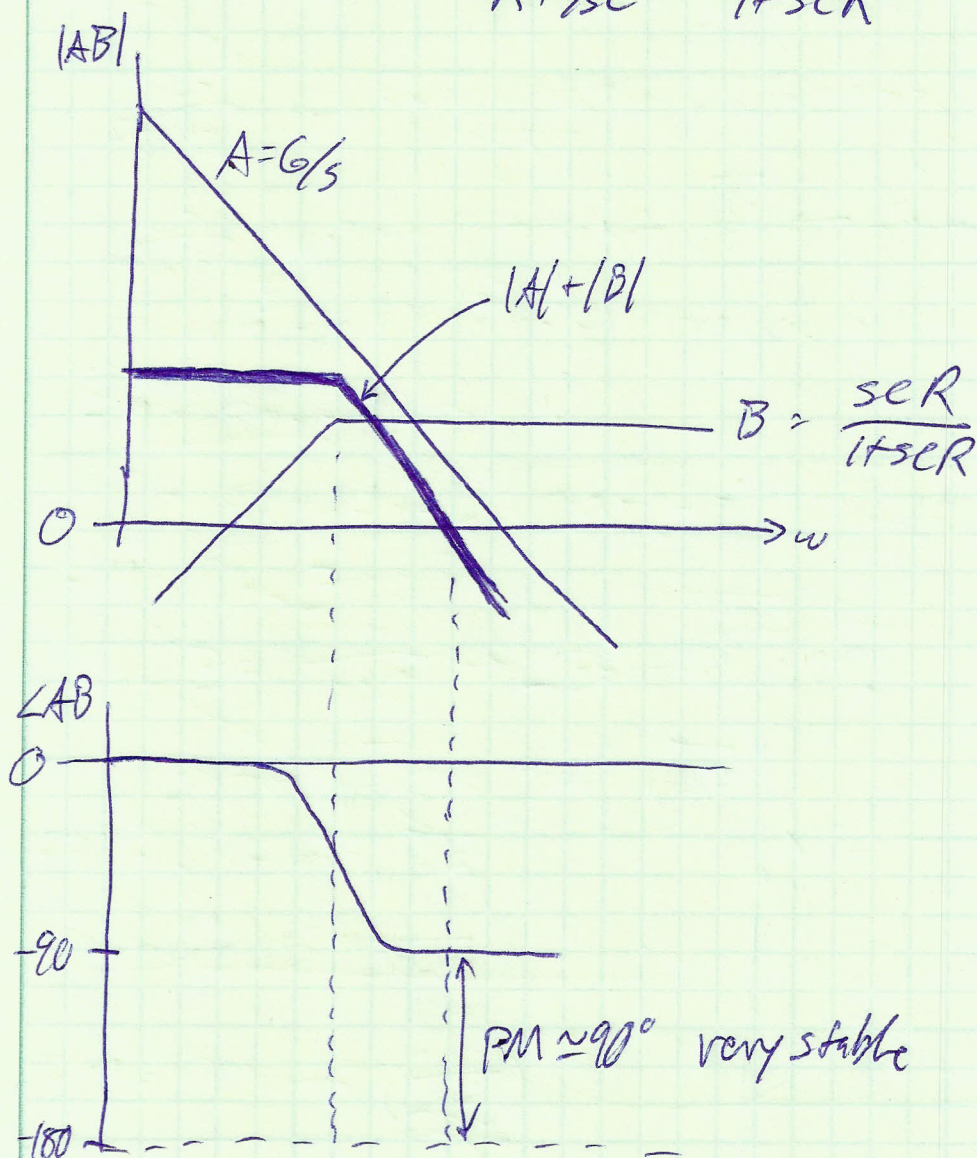
$$A = G/s, \quad B = \frac{R}{R + 1/sC} = \frac{sCR}{1 + sCR}$$



Rest of lecture: review mid-term