

ECE 167, HW2 Solutions

① 2.36

We need $Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)} = 40j \Omega$

$$Z_0 = 50 \Omega$$

$$Z_L = 0 \quad (\text{short circuit})$$

$$\beta = \frac{2\pi}{\lambda} = \frac{2\pi f}{c} = 2\pi \frac{300 \times 10^6 \text{ Hz}}{.75 \times (3 \times 10^8 \text{ m/s})} = 8.34 \text{ m}^{-1}$$

$$\text{So } Z_{in} = jZ_0 \tan(\beta l) = 40j$$

$$l = \frac{1}{\beta} \tan^{-1}\left(\frac{40}{Z_0}\right)$$

The smallest positive solution corresponds to

$$0 < \tan^{-1}\left(\frac{40}{50}\right) < \frac{\pi}{2}$$

$$= 8.05 \text{ cm}$$

② 2.40

$$(a) \text{ Electrical length} = \beta l = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{4} = \pi/2$$

$$\text{For matching, we need } Z_{in}(-l) = \frac{Z_0^2}{Z_L} = Z_{01}$$

$$\begin{aligned} Z_{02} &= \sqrt{Z_L Z_{01}} \\ &= \sqrt{73 \Omega \cdot 300 \Omega} \\ &= 148 \Omega \end{aligned}$$


$$(b) \quad l = \frac{\lambda}{4} = \frac{c}{4f\sqrt{\epsilon_r}} = \frac{3 \times 10^8 \text{ m/s}}{4 \cdot (100 \times 10^6 \text{ Hz}) \sqrt{2.6}} = 46.5 \text{ cm}$$

$$Z_{02} = \frac{120\sqrt{\epsilon_r}}{\ln\left(\frac{D}{d} + \sqrt{\left(\frac{D}{d}\right)^2 - 1}\right)}$$

$$\left(\frac{D}{d} - e^{\frac{Z_{02}\sqrt{\epsilon_r}}{120}}\right)^2 = \left(\frac{D}{d}\right)^2 - 1 \Rightarrow \frac{D}{d} = \frac{e^{\frac{Z_{02}\sqrt{\epsilon_r}}{120}} + 1}{2e^{\frac{Z_{02}\sqrt{\epsilon_r}}{120}}} \Rightarrow d = 0.67 \text{ cm}$$

3 2.44

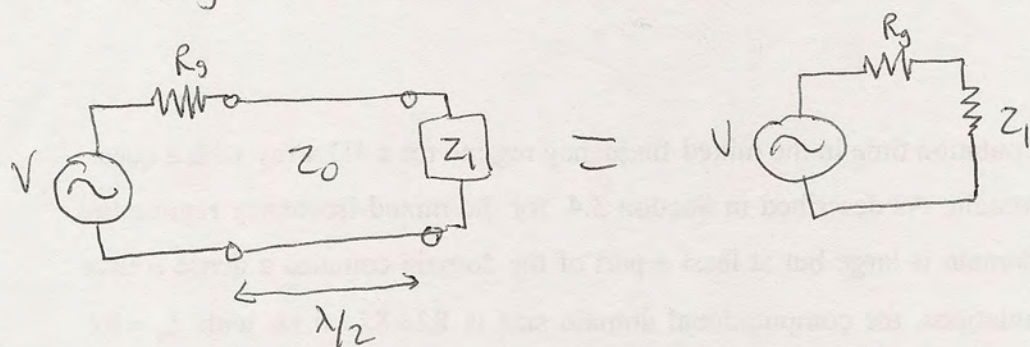Taking into account input impedance, the setup becomes



because $\frac{\lambda}{2}$ sections contribute nothing to input impedance

$$\Gamma = \frac{Z_1 - Z_0}{Z_1 + Z_0} = \frac{100\Omega - 50\Omega}{100\Omega + 50\Omega} = \frac{1}{3}$$

In the circuit representation, the voltage across the load is

$$V_L = V \frac{Z_1}{R_g + Z_1}, \quad I_L = \frac{V}{R_g + Z_1}$$

The power dissipated by the load in the circuit representation equals the power transmitted into the infinite transmission line

$$\text{Transmitted power } P_{av}^+ = \frac{V_L I_L}{2} = \frac{V^2}{2(R_g + Z_1)^2} Z_1 = \frac{2V^2 \cdot 100\Omega}{2(50\Omega + 100\Omega)^2} = \boxed{8.89 \text{ mW}}$$

$$= \frac{|V_0^+|^2}{2Z_0} (1 - |\Gamma|^2)$$

$$P_{av}^i = \frac{|V_0^+|^2}{2Z_0} = \frac{P_{av}^+}{1 - |\Gamma|^2} = \frac{8.89 \text{ mW}}{1 - (\frac{1}{3})^2} = \boxed{10 \text{ mW}}$$

$$P_{av}^r = -|\Gamma|^2 P_{av}^i = -(\frac{1}{3})^2 \cdot 10 \text{ mW} = \boxed{-1.1 \text{ mW}}$$


Note that the input impedance of an infinite line is always equal to its input impedance, even if there is no loss. (The book is wrong)

$$\text{Remember, } Z_{in}(z) = \frac{\tilde{V}(z)}{\tilde{I}(z)} = \frac{V_0^+ e^{-\gamma z}}{\frac{V_0^+}{Z_0} e^{-\gamma z}} \quad (\text{because there can be no reflected wave})$$

$$= Z_0$$


4 2.46

Under matched conditions, meaning

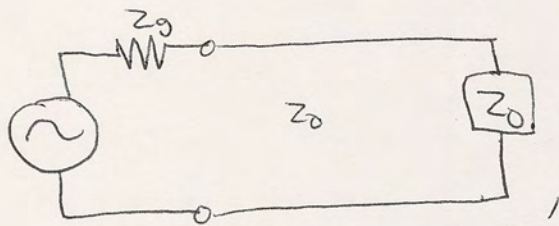

20W is delivered to the load. Because there is no reflected power, $P_{av}^i = 20W$.

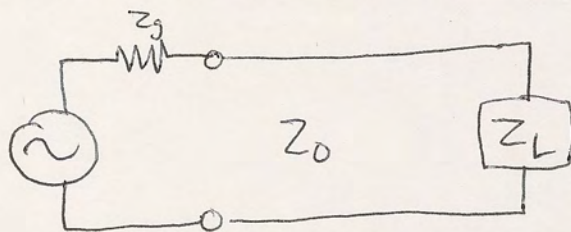When the transmitter is connected to the antenna,



the incident power is still 20W, but some power is reflected. The power delivered to the load is

$$P_{av} = P_{av}^i - |\Gamma|^2 P_{av}^i$$
$$= P_{av}^i (1 - |\Gamma|^2)$$

Note that $Z_g = Z_0$ in this case, so there are no multiple reflections from the generator

$$\text{where } \Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{25 + 25j \Omega}{125 + 25j \Omega} = \frac{1 + j}{5 + j}$$

$$|\Gamma| = \frac{|1 + j|}{|5 + j|}$$

$$|\Gamma| = \sqrt{\frac{2}{26}}$$

$$\text{so } P_{av} = \left(1 - \frac{1}{13}\right) 20W = 18.5W$$

(5.)

$$\Gamma_L + jX_L = \frac{1 + \Gamma_r + j\Gamma_i}{1 - \Gamma_r + j\Gamma_i} \cdot \frac{1 - \Gamma_r + j\Gamma_i}{1 - \Gamma_r + j\Gamma_i}$$

$$= \frac{1 - \Gamma_r^2 - \Gamma_i^2 + 2j\Gamma_i}{(1 - \Gamma_r)^2 + \Gamma_i^2}$$

$$\text{So } X_L = \frac{2\Gamma_i}{(1 - \Gamma_r)^2 + \Gamma_i^2}$$

$$(1 - \Gamma_r)^2 X_L + \Gamma_i^2 X_L = 2\Gamma_i$$

$$(1 - \Gamma_r)^2 + \Gamma_i^2 - \frac{2}{X_L} \Gamma_i = 0$$


$$\text{but } \Gamma_i^2 - \frac{2}{X_L} \Gamma_i = \left(\Gamma_i - \frac{1}{X_L}\right)^2 - \left(\frac{1}{X_L}\right)^2$$

$$\text{So } (1 - \Gamma_r)^2 + \left(\Gamma_i - \frac{1}{X_L}\right)^2 = \frac{1}{X_L^2}$$

6 and 7

The Complete Smith Chart

Black Magic Design

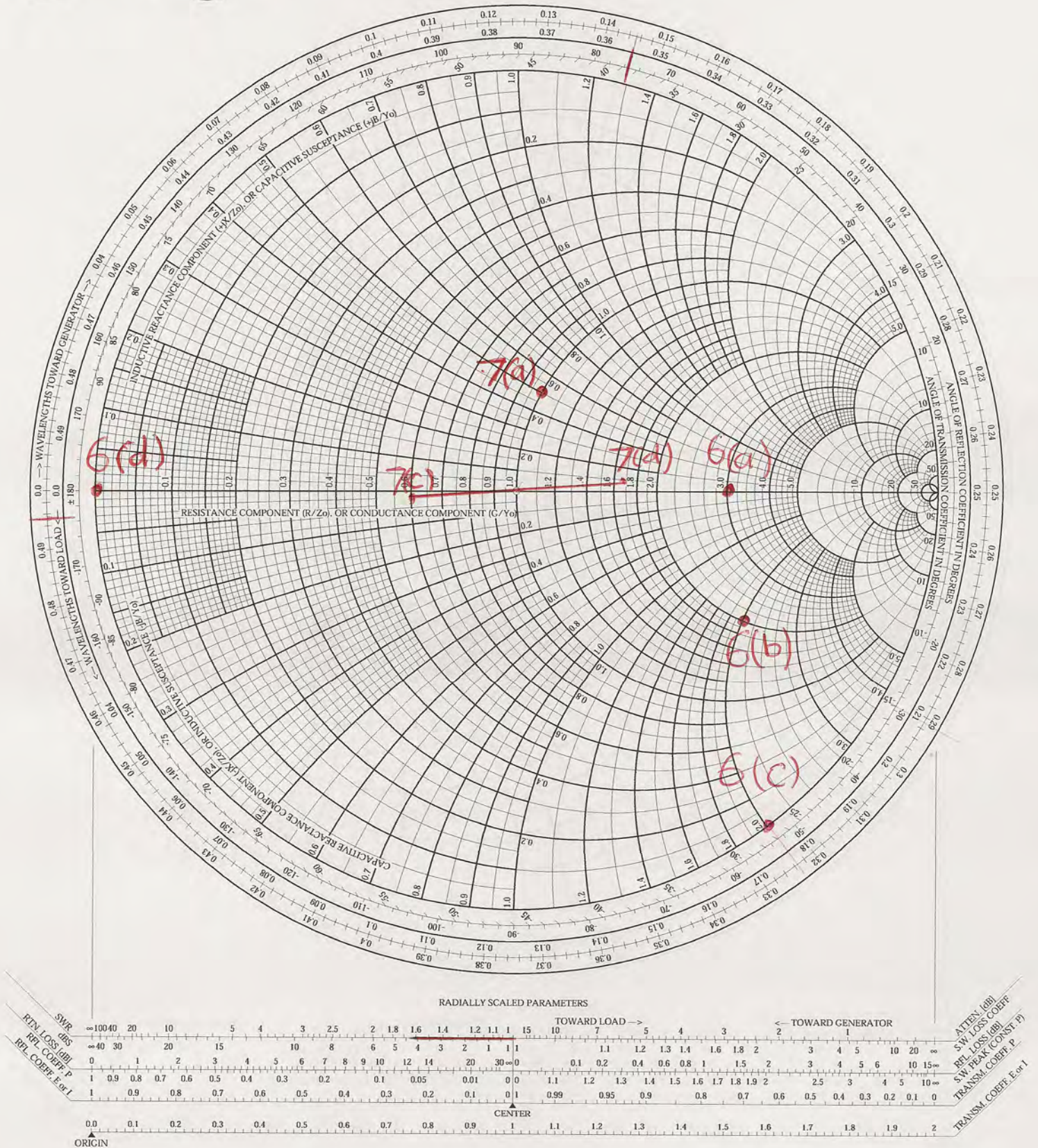

⑥ 2.47

For the smith chart given in class, there is a distance of 8cm from the origin ($\Gamma=0$) to the outer circle ($|\Gamma|=1$). Therefore, $|\Gamma|$ is measured from the formula $|\Gamma| = \frac{\text{distance from origin (cm)}}{8\text{cm}}$

and the angle of Γ is read off from the outer scale.

$$(a) |\Gamma| = \frac{4\text{cm}}{8\text{cm}} = \frac{1}{2}, \quad \theta_r = 0$$

$$\Gamma = \frac{1}{2}$$

$$(b) |\Gamma| = \frac{5\text{cm}}{8\text{cm}} = 0.625, \quad \theta_r \approx -30^\circ$$

$$\Gamma = .625 e^{-j\pi/6} = .54 - .31j$$

$$(c) |\Gamma| = \frac{8\text{cm}}{8\text{cm}} = 1, \quad \theta_r = -53^\circ$$

$$\Gamma = e^{-j0.93} = .60 - .80j$$

$$(d) |\Gamma| = \frac{8\text{cm}}{8\text{cm}} = 1, \quad \theta_r = 180^\circ$$

$$\Gamma = 1e^{+j\pi} = -1$$

⑦ (a) $|\Gamma| = \frac{2\text{cm}}{8\text{cm}} = \frac{1}{4}, \quad \theta_r \approx 75.5^\circ$

$$\Gamma = \frac{1}{4} e^{j\theta_r} = 0.063 + 0.24j$$

(b) Measuring 2cm on the SWR scale gives

$$\text{SWR} \approx 1.65$$

⑦(c) Using the outer scale, $.145 + .35 =$

This gives a normalized input impedance of

$$\frac{Z_{in}(-.35\lambda)}{Z_0} = .60 - .02j$$

$$Z_{in}(-.35\lambda) = 30 - j\Omega$$

(d) Inverting the input impedance gives the normalized input admittance:

$$\frac{Y_{in}(-.35\lambda)}{Y_0} = 1.7 + .05j \quad Y_0 = \frac{1}{Z_0}$$

$$Y_{in} = .034 + .001j \Omega^{-1}$$

(e) Using the outer scale, it requires a length

$$l = .25\lambda - .145\lambda$$

$$= .105\lambda$$

to get to the real axis, where Z_{in} is purely real

(f) The first voltage maximum coincides with the first point where Z_{in} is purely real, so the answer is

$$l = .105\lambda$$

8) 2.66

$$Z_L = 50 - 25j \Omega$$

$$Y_L = \frac{1}{Z_L} = .016 + .008j \Omega^{-1}$$

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{50 - 25j - 200}{50 - 25j + 200} = -.584 - .158j$$

$$\Gamma = .605 e^{-2.88j}$$

need to solve for d :

$$\cos(\theta_r - 2\beta d) = -|\Gamma|$$

$$\theta_r - 2\beta d = \pm \cos^{-1}(-|\Gamma|)$$

$$d = \frac{\theta_r \mp \cos^{-1}(-|\Gamma|)}{2\beta}$$

$$|\Gamma| = .605$$

$$\theta_r = -2.88$$

$$\beta = \frac{2\pi f}{c/\epsilon_r} = \frac{2\pi \cdot 8 \cdot 10^8 \text{ Hz}}{3 \cdot 10^8 \text{ m/s} \cdot \frac{1}{2}} = 33.5$$

Two solutions exist:

$$d_1 = 1.77 \text{ cm} \quad \text{where } \cos^{-1}(-|\Gamma|) \text{ is chosen so that } d$$
$$d_2 = 8.40 \text{ cm} \quad \text{is the smallest possible positive value}$$

These are the two positions at which $\text{Re}\{Y_{in}\} = Y_0$

a) Now, for each case, the imaginary part must be matched

for $d = d_1$ the shunt reactive component has impedance

$$Z_{s1} = \frac{Z_0}{j b_{s1}} = \frac{200 \Omega}{j} \frac{1 + |\Gamma|^2 + 2|\Gamma| \cos(\theta_r - 2\beta d_1)}{2|\Gamma| \sin(\theta_r - 2\beta d_1)}$$

$$= -131.5j \Omega$$

In this case use a capacitor with capacitance satisfying

$$\frac{1}{j\omega C} = -131.5j \Omega$$

$$C = \frac{1}{2\pi \cdot 8 \times 10^8 \text{ Hz} \cdot 131.5} = \boxed{1.51 \text{ pF}}$$

b) for $d = d_2$ the matching element has impedance

$$Z_{s2} = 131.5j \Omega$$

Use an inductor with inductance

$$j\omega L = 131.5j$$

$$L = \frac{131.5}{2\pi \cdot 8 \cdot 10^8 \text{ Hz}} = \boxed{26.2 \text{ nH}}$$

9. $Z_L = \frac{Z_L}{Z_0} = .25 - .125j$

Using the Smith chart, the normalized admittance is

$$y_L = 3.2 + 1.7j$$


Tracing the arc to the point where $\text{Re}\{y_{in}\} = y_0$ yields two possible solutions

(a) at a distance from the load (given by the outer scale)

$$\begin{aligned} d_1 &= .322\lambda - .228\lambda & \lambda &= \frac{2\pi}{\beta} = 18.75 \text{ cm} \\ &= 1.76 \text{ cm} \end{aligned}$$

The Complete Smith Chart

Black Magic Design

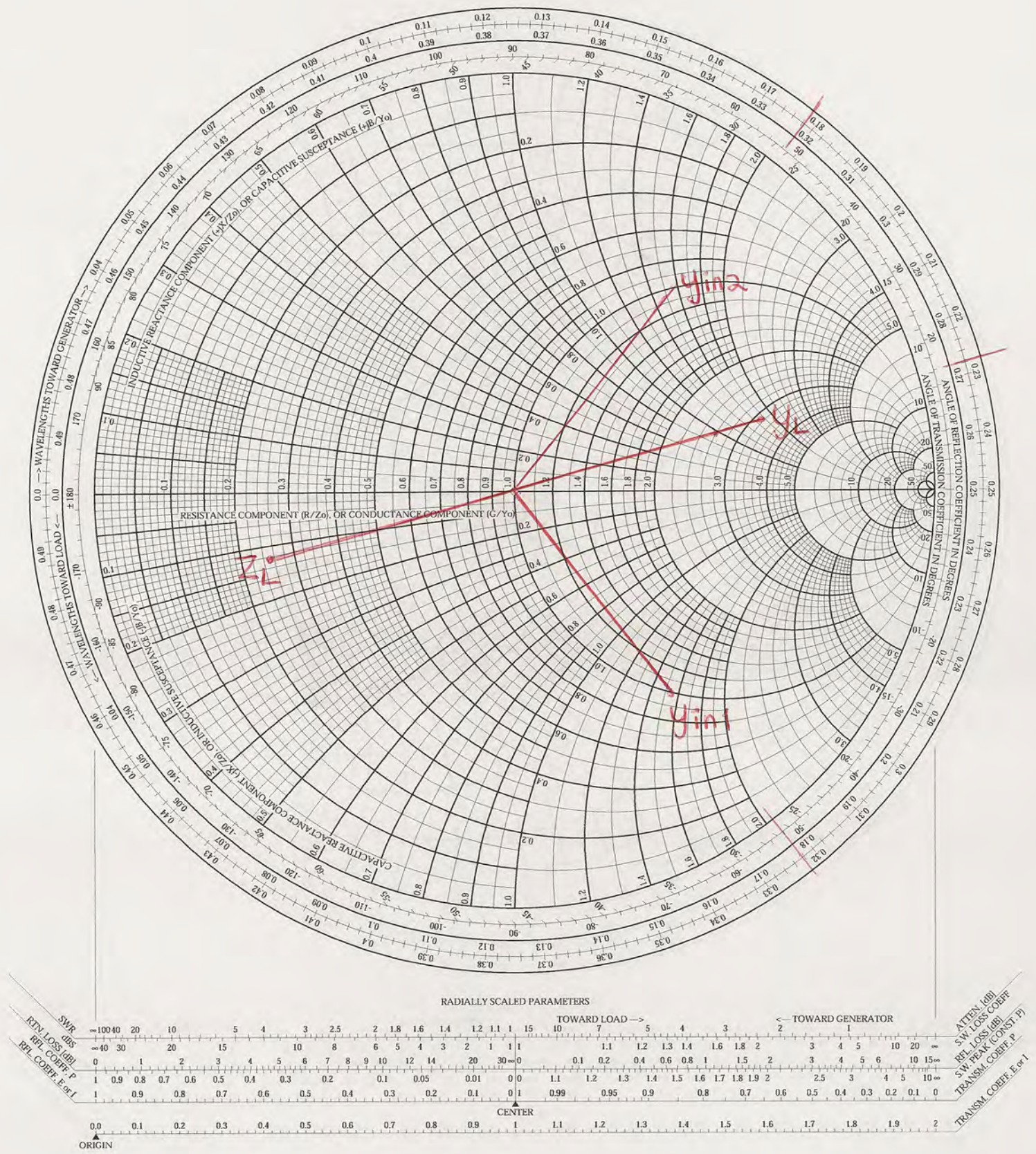

(9)

at this position the normalized input admittance is

$$Y_{in1} = 1 - 1.55j$$

so the shunt element must have normalized susceptance

$$b_{s1} = 1.55$$

and impedance

$$Z_{s1} = \frac{Z_0}{j b_{s1}} = -129j \Omega$$

Using a capacitor,

$$C = \frac{1}{j\omega Z_s} = \boxed{1.54 \text{ pF}}$$

The other solution is found a distance

$$d_2 = \underbrace{\frac{\lambda}{2}}_{\text{full circle}} - \underbrace{(-.228 - .178)\lambda}_{\text{"wedge"}} = 8.44 \text{ cm}$$

at this point $Y_{s2} = 1 + 1.55j$

$$b_{s2} = -1.55j$$

$$Z_{s2} = \frac{Z_0}{j b_{s2}} = +129j \Omega$$

use an inductor

$$L = \frac{Z_{s2}}{j\omega} = \boxed{25.7 \text{ nH}}$$

2-74
(10)

I will use a reactive shunt impedance, and solve using the smith chart

$$Z_L = \frac{Z_L}{Z_0} = \frac{25\Omega}{75\Omega} = \frac{1}{3}$$

$$\text{so } y_L = \frac{1}{Z_L} = 3$$

tracing the arc (with radius 4cm), the closest matching admittance is

$$y_{in} = 1 - 1.15j \Rightarrow b_s = +1.15 = \text{susceptance of shunt element}$$

It is found a distance

$$\begin{aligned} l &= (.334 - .25)\lambda \\ &= 0.084\lambda \text{ from the load} \end{aligned}$$

$$\text{so } Z = \frac{Z_0}{jb_s} = \frac{75\Omega}{j1.15} = \boxed{-65.2j}$$

This would require a capacitor

Another option is to place the shunt element a distance

$$l = \frac{\lambda}{2} - .084\lambda = .416\lambda \text{ from the load}$$

In this case

$$\boxed{Z = +65.2j} \text{ and an inductor is required}$$

The Complete Smith Chart

Black Magic Design

