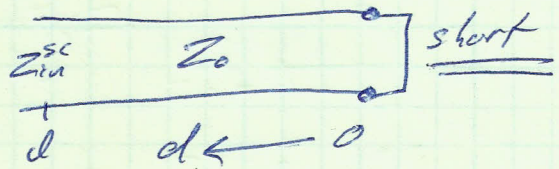


Special Cases of Lossless Line

From Last lectures:

$$\tilde{V}(z) = V_0^+ (e^{-j\beta z} + \Gamma e^{j\beta z})$$

$$\tilde{I}(z) = \frac{V_0^+}{Z_0} (e^{-j\beta z} - \Gamma e^{j\beta z})$$



- at $z = -d$ (remember, book uses d as substitute variable, not line length)
- assume short circuit $Z_L = 0$

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = -1$$



$$\tilde{V}_{sc}(d) = V_0^+ [e^{j\beta d} - e^{-j\beta d}] = 2j V_0^+ \sin \beta d$$

$$\tilde{I}_{sc}(d) = \frac{V_0^+}{Z_0} [e^{j\beta d} + e^{-j\beta d}] = \frac{2V_0^+}{Z_0} \cos \beta d$$

$$Z_{sc}(d) = \frac{\tilde{V}_{sc}(d)}{\tilde{I}_{sc}(d)} = j Z_0 \tan \beta d$$

for line of length l
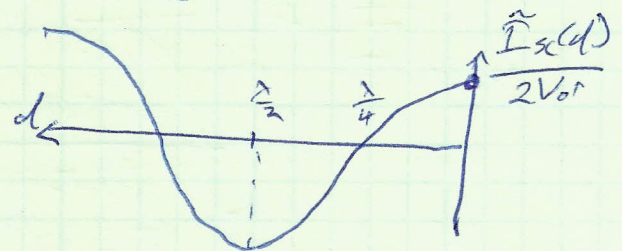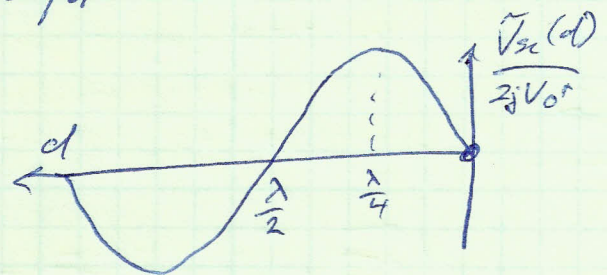
$$\boxed{Z_{in}^{sc} = j Z_0 \tan \beta l}$$



- Equivalent Inductance

$$L_{eq} = \frac{Z_0 \tan \beta l}{\omega} \leftarrow \text{use}$$

$$l = \frac{1}{\beta} \tan^{-1} \left(\frac{\omega L_{eq}}{Z_0} \right)$$

$$Z = R + jX = Z_{in}^{sc}$$

$$j\omega L_{eq} = j Z_0 \tan \beta l$$


- Equivalent Capacitance
(for lines longer than $\lambda/4$)

$$\frac{1}{j\omega L_{eq}} = -j Z_0 \tan \beta l$$

$$C_{eq} = \frac{-1}{Z_0 \omega \tan \beta l}$$

π comes from equivalence of these 2 points

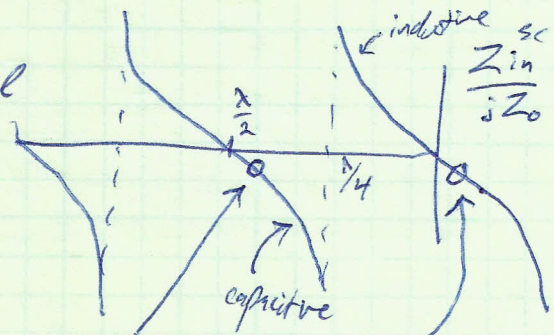
$$l = \frac{1}{\beta} \left[\pi - \tan^{-1} \left(\frac{1}{\omega C_{eq} Z_0} \right) \right]$$



$\tan^{-1}$ usually defined over this range

$$\left[-\frac{\pi}{2}, \frac{\pi}{2} \right]$$


For open-circuited line

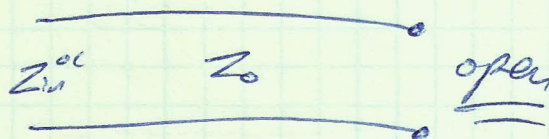

$$\tilde{V}_{oc}(d) = V_0^+ [e^{j\beta d} + e^{-j\beta d}] = 2V_0^+ \cos \beta d$$

$$\tilde{I}_{oc}(d) = \frac{V_0^+}{Z_0} [e^{j\beta d} - e^{-j\beta d}] = \frac{2jV_0^+}{Z_0} \sin \beta d$$
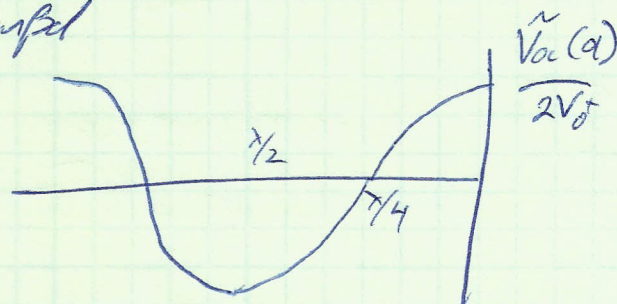
$$Z_{in}^{oc} = \frac{\tilde{V}_{oc}(d)}{\tilde{I}_{oc}(d)} = -jZ_0 \cot \beta l$$





Note about Short/Open Circuits:

$$Z_0 = \sqrt{Z_{in}^{sc} Z_{in}^{oc}}$$

$$\tan \beta l = \sqrt{\frac{-Z_{in}^{sc}}{Z_{in}^{oc}}}$$

This method can be used to measure Z_0 and β

for an unknown transmission line

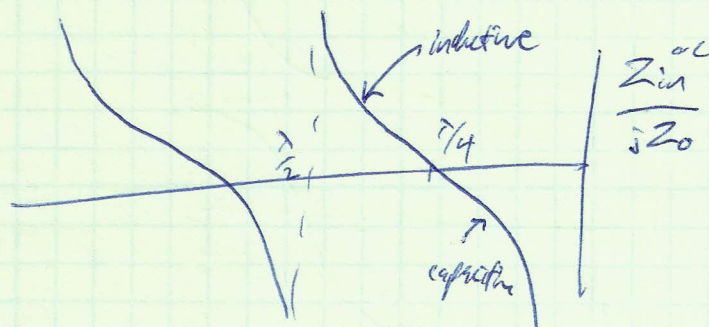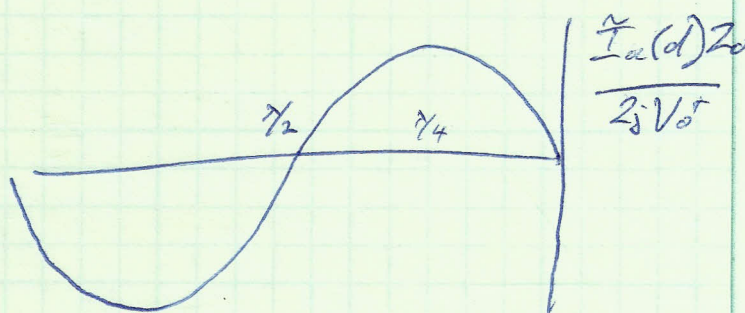

~~half-wavelength line~~


$$\tan \beta l = \tan \left(\frac{2\pi}{\lambda} \cdot \frac{\lambda}{2} \right) = \tan \pi = 0$$

note the top graphs do not divide to get the bottom one because of the factor of j

- Half-wavelength (or multiples) transmission line

Remember,
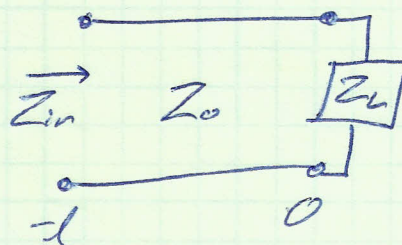
$$Z_{in} = Z_0 \left(\frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \right)$$



when $l = \frac{n\lambda}{2}$ ($n = \text{integer}$)

$$\tan \beta l = \tan \left(\frac{2\pi}{\lambda} \cdot \frac{n\lambda}{2} \right) = \tan n\pi = 0$$


$Z_{in} = Z_L \rightarrow$ transmission line has no effect on impedance

- Quarter-wavelength transformer

when $l = \frac{\lambda}{4}$ (or $\frac{\lambda}{4} + \frac{n\lambda}{2}$)

$$\tan \beta l = \tan \left(\frac{2\pi}{\lambda} \cdot \frac{\lambda}{4} \right) = \tan \frac{\pi}{2} = \infty$$

$$Z_{in} = \frac{Z_0^2}{Z_L}$$

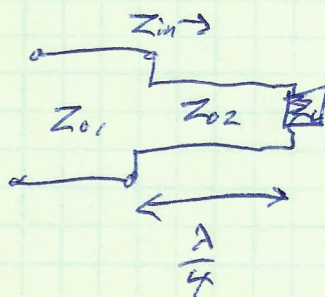

To cancel reflections,

$$\frac{Z_{02}^2}{Z_L} = Z_{01}$$

$$Z_{02} = \sqrt{Z_L Z_{01}^2}$$

Power Flow on Lossless Transmission Line

$$\tilde{V}(d) = V_0^+ (e^{j\beta d} + \Gamma e^{-j\beta d})$$

$$\tilde{I}(d) = \frac{V_0^+}{Z_0} (e^{j\beta d} - \Gamma e^{-j\beta d})$$

$$v(d,t) = \text{Re}[\tilde{V}e^{j\omega t}] = \text{Re}[|V_0^+|e^{j\phi^+}(e^{j\beta d} + |\Gamma|e^{j\theta_r}e^{-j\beta d})e^{j\omega t}]$$

$$= |V_0^+| [\cos(\omega t + \beta d + \phi^+) + |\Gamma| \cos(\omega t - \beta d + \phi^+ + \theta_r)]$$

$$i(d,t) = \frac{|V_0^+|}{Z_0} [\cos(\omega t + \beta d + \phi^+) - |\Gamma| \cos(\omega t - \beta d + \phi^+ + \theta_r)]$$

$$P(d,t) = v(d,t) i(d,t)$$

$$= \frac{|V_0^+|^2}{Z_0} [\cos^2(\omega t + \beta d + \phi^+) - |\Gamma|^2 \cos^2(\omega t - \beta d + \phi^+ + \theta_r)]$$

instantaneous incident power instantaneous reflected power

Use $\cos^2 x = \frac{1}{2}(1 + \cos 2x)$

$$P^i(d,t) = \frac{|V_0^+|^2}{2Z_0} [1 + \cos(2\omega t + 2\beta d + 2\phi^+)]$$

and similar expression for $P^r(d,t)$

note: power oscillates
at twice the ~~rate~~ frequency
of the wave.

• Time average power

$$P_{av}^i(d) = \frac{1}{T} \int_0^T P^i(d,t) dt = \frac{\omega}{2\pi} \int_0^{\frac{2\pi}{\omega}} P^i(d,t) dt$$

Integral over cosine term is 0

We are left with

$$P_{av}^i = \frac{|V_0^+|^2}{2Z_0}$$

$$P_{av}^r = -|\Gamma|^2 P_{av}^i$$

Power flowing toward load (and absorbed)

$$P_{av} = P_{av}^i + P_{av}^r$$

$$= \frac{|V_0^+|^2}{2Z_0} [1 - |\Gamma|^2]$$

note convention that both power terms
are for power flowing in forward direction