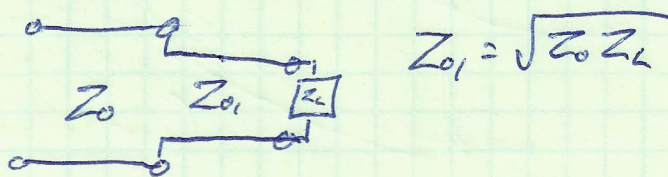


Impedance Matching


- Length of transmission line, or lumped element that is added to a circuit to eliminate reflections from propagating back toward generator
- There can be internal reflections in matching circuit, but the net reflected power toward generator is canceled




- If Z_L is real, we can use quarter wave transformer



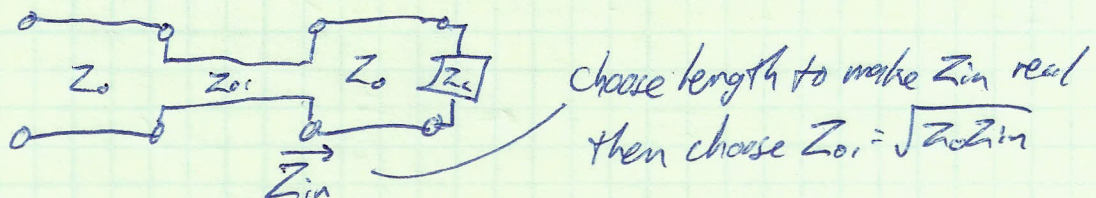- If Z_L is complex, we can still use quarter wave transformer, but offset



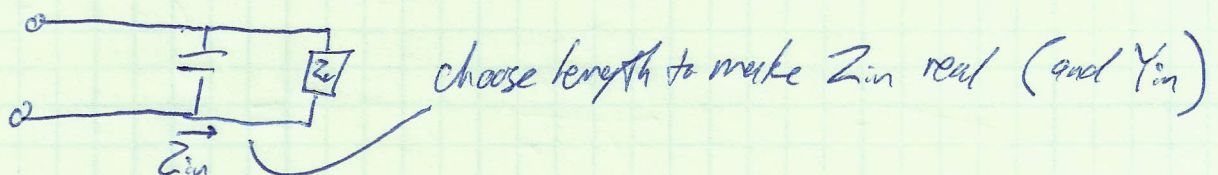- Can also use lumped elements in shunt with transmission line



With shunt elements, it is easiest to work in admittance

$$Y_{in} = Y_0 + Y_s \leftarrow \text{admittances add in shunt}$$

Admittance $Y = G + jB \leftarrow$ Susceptance
 $\uparrow$
 Conductance


$$Y_{in} = (G_d + jB_d) + jB_s$$

$\uparrow$ (load + line) $\uparrow$ shunt element or stub


normalized quantities $y_{in} = g_d + j(b_d + b_s)$

matching condition: $g_d = 1, b_d = -b_s$

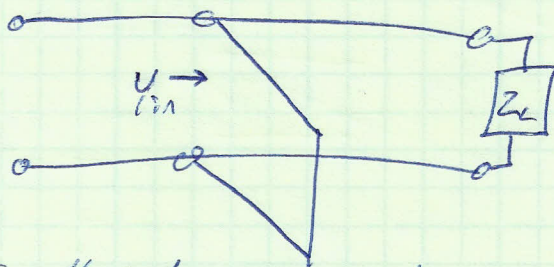- Can also realize shunt susceptance using length of open or short transmission line



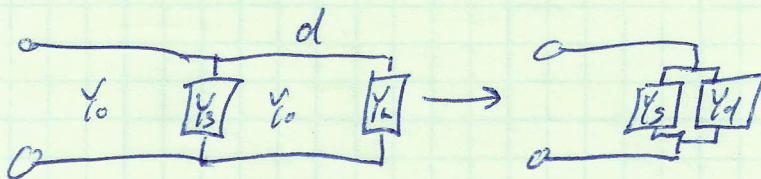- In all of these cases, take equivalent admittance of line and load and treat in parallel with lumped element or stub



Design procedures for matching circuits using smith chart

- Quarter wave transformer at distance d from load
 - locate point Z_L normalized ~~load~~ load impedance on chart
 - draw circle of constant $|r|$ around origin
 - rotate from Z_L to a point on the real axis (clockwise!)
 - read distance in wavelengths from chart
 - get Z_d from real axis on chart
 - design $\lambda/4$ transmission line with $Z_1 = \sqrt{Z_0 Z_d}$
- Shunt stub (or lumped element)
 - locate point Z_L normalized load impedance on chart
 - draw circle of constant $|r|$ around origin
 - locate point Y_L on opposite point on constant $|r|$ circle
 - rotate from Y_L to the $g=1$ circle (clockwise!)
 - read distance in wavelength from the chart
 - read value of b_d from the chart
 - for lumped element matching:
 - $B_d = b_d Y_0$
 - $B_s = -B_d = \omega C$ for capacitor
 - $-B_d = \frac{1}{\omega L}$ for inductor
 - for stub matching:
 - Choose open or short (remember Y is at opposite side from Z) that is closest to $-b_d$ (remember you will be rotating clockwise)
 - read length in wavelengths from the chart

Quarter Wave transformer Design (with offset d)

The Complete Smith Chart



Black Magic Design

$$Z_L = (0.4 + 0.6j) Z_0$$

$$Z_d = 3.5 Z_0$$

$$d = (0.25 - 0.0995) \lambda$$

$$Z_1 = \sqrt{Z_0 Z_d}$$

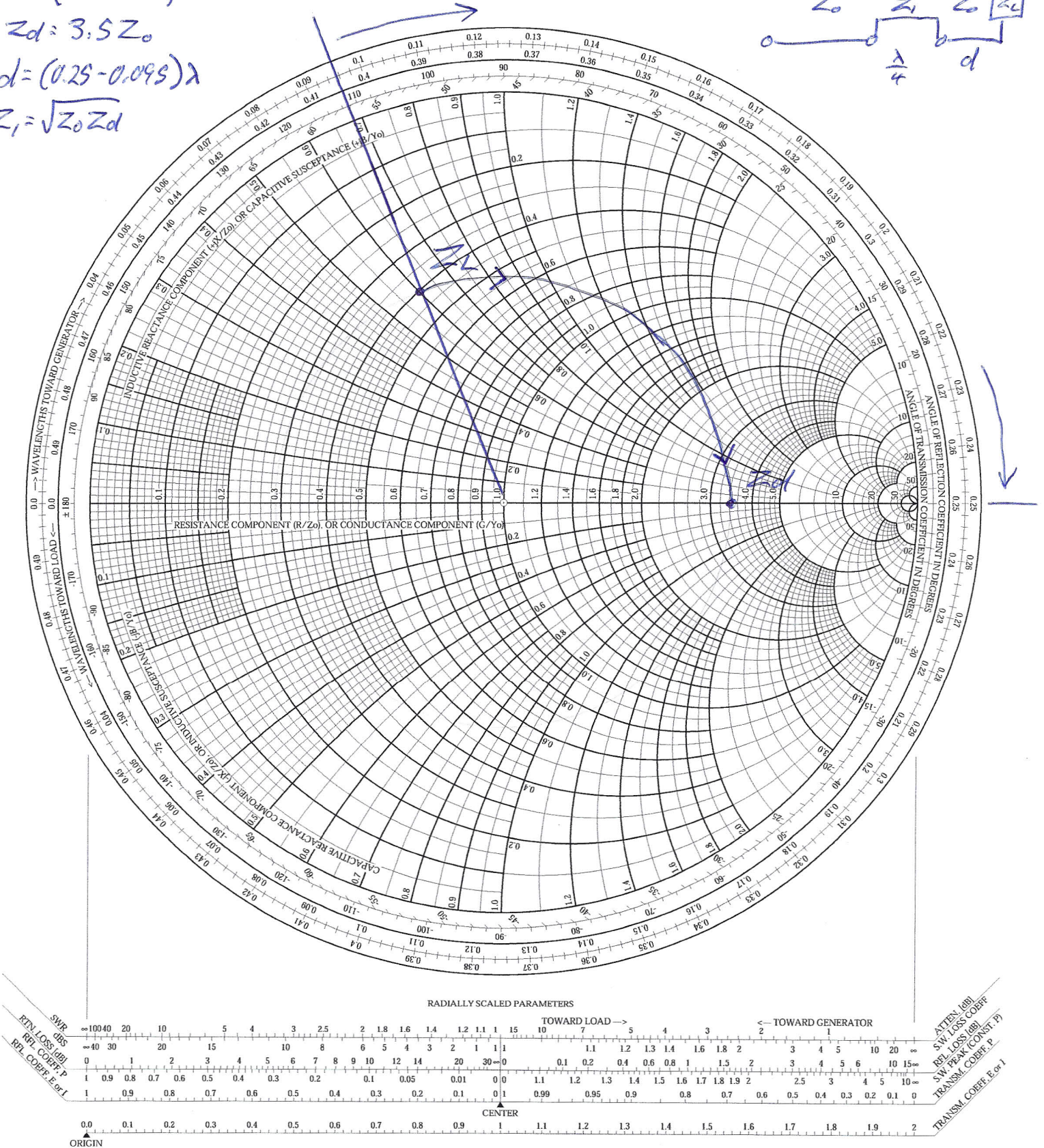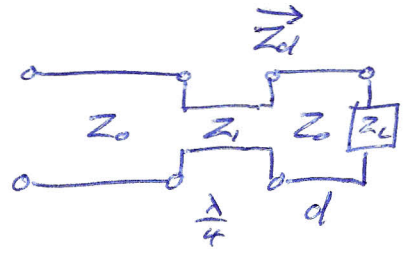

Single stub (or lumped element) Design

The Complete Smith Chart

Black Magic Design



$$Z_L = 0.4 + j0.8$$

$$Y_L = 0.8 + j1.0$$

$$d = [(0.5 - 0.25 \times 2) + 0.17] \lambda$$

$$Y_d = 1.3$$
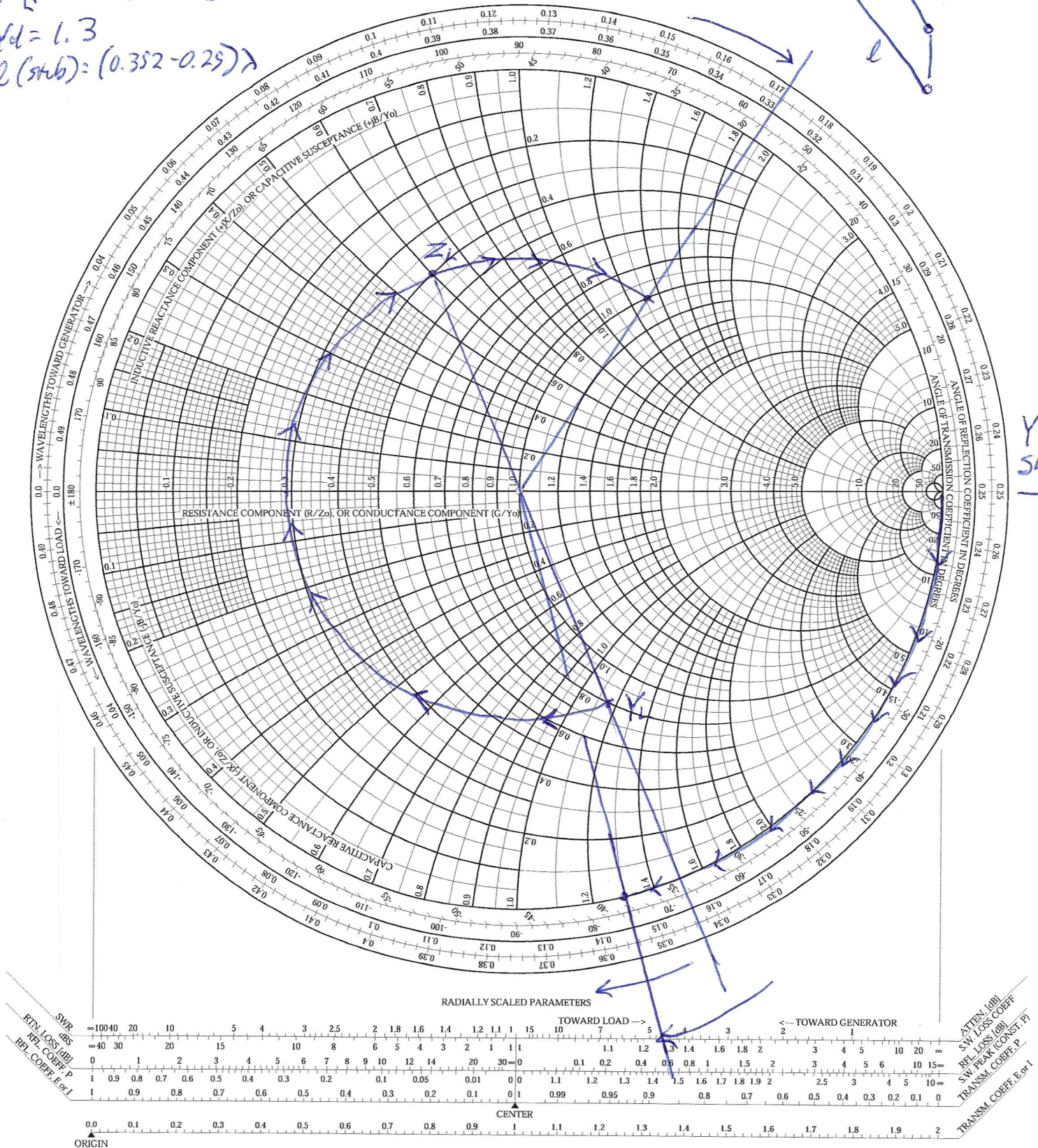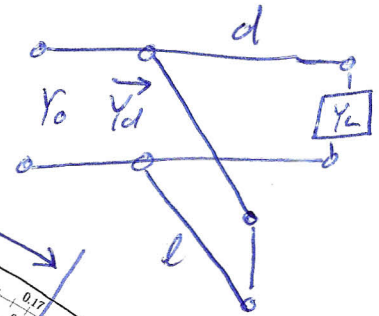
$$l(\text{stub}) = (0.352 - 0.25) \lambda$$



Y_d of short