

Example. Find i & v

AC Circuit

17

$$\omega = 1000$$

$$4 \cos(1000t) \rightarrow 4$$

$$0.1 \text{ H} \rightarrow j\omega L = j(1000)(0.1) = j100$$



$$0.2 \text{ H} \rightarrow j200$$

$$0.4 \text{ H} \rightarrow j400$$

$$1.25 \mu\text{F} \rightarrow \frac{-j}{\omega C} = \frac{-j}{1000 \times 1.25 \times 10^{-6}} = -j800$$

$$5 \mu\text{F} \rightarrow -j200$$

$$4 \cos(1000t)$$

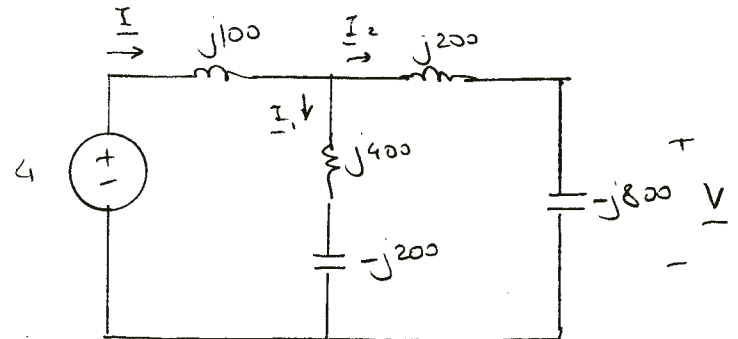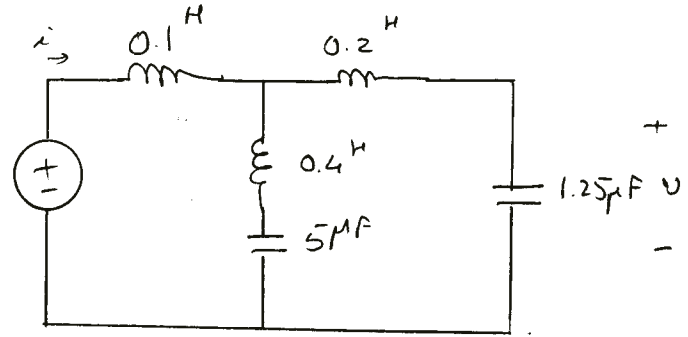

$$\text{KCL : } \underline{I} = \underline{I}_1 + \underline{I}_2$$

$$\text{KVL : } \underline{I}(j100) + \underline{I}_1(j400 - j200) - 4 = 0$$

$$\text{KVL : } \underline{I}_2(j200 - j800) - \underline{I}_1(j400 - j200) = 0$$

$$\begin{cases} \underline{I} = \underline{I}_1 + \underline{I}_2 \\ j100 \underline{I} + j200 \underline{I}_1 = 4 \\ -j600 \underline{I}_2 - j200 \underline{I}_1 = 0 \end{cases} \Rightarrow \underline{I}_1 = -3 \underline{I}_2$$

$$\begin{cases} \underline{I} = -3 \underline{I}_2 + \underline{I}_2 = -2 \underline{I}_2 \\ j100 \underline{I} - j600 \underline{I}_2 = 4 \end{cases} \Rightarrow \begin{aligned} -j200 \underline{I}_2 - j600 \underline{I}_2 &= 4 \\ -j800 \underline{I}_2 &= 4 \end{aligned}$$

$$\begin{cases} \underline{I}_2 = \frac{4}{-j800} = j \frac{1}{200} = 0.005j = 0.005 \angle 90^\circ \\ \underline{I} = -2 \underline{I}_2 = -0.01j = 0.01 \angle -90^\circ \\ \underline{V} = -j800 \underline{I}_2 = -j800(0.005j) = 4 = 4 \angle 0^\circ \end{cases} \Rightarrow \begin{cases} i_2 = 0.005 \cos(1000t + 90^\circ) \\ i = 0.01 \cos(1000t - 90^\circ) \\ v = 4 \cos(1000t) \end{cases}$$

Thevenin / Norton Transformation

$$Z_T = Z_N$$


$$V_T = Z_N I_N$$

Also

$$V_T = V_{oc}$$

$$I_N = I_{sc}$$

$$Z_T = Z_N = \frac{V_{oc}}{I_{sc}}$$

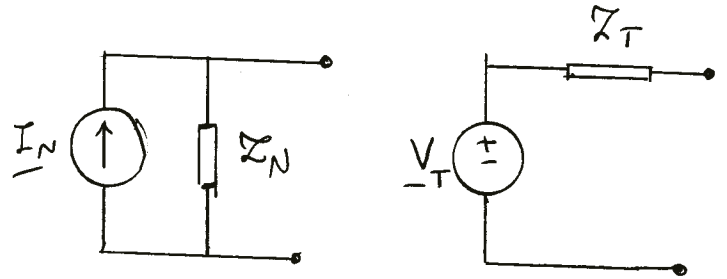

Example:

$$\omega = 2$$




$$8G_0(2\omega) \rightarrow 8$$

$$\frac{1}{4}F \rightarrow \frac{-j}{2 \times (\frac{1}{4})} = -j2$$

$$2H \rightarrow j\omega(2) = j4$$

$$3H \rightarrow j6$$

$$Z_1 = 2 + j6$$

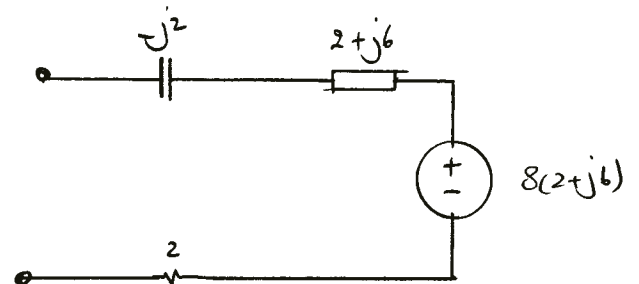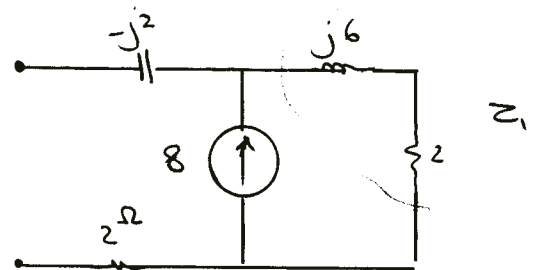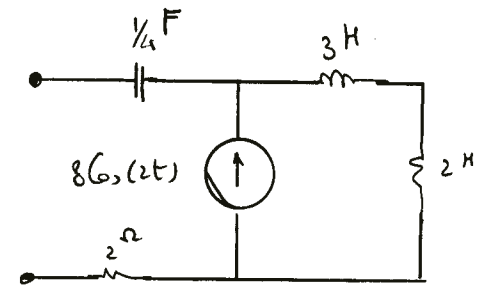



$$Z_T = 4 + j4, \quad V_T = 16 + j48$$

$$Z_N = 4 + j4$$

$$I_N = \frac{V_T}{Z_N} = \frac{16 + j48}{4 + j4}$$

$$= \frac{4 + j12}{1 + j} = \frac{(4 + j12)(-j)}{2}$$

$$= 8 + j4$$

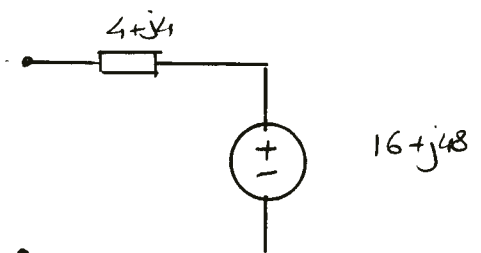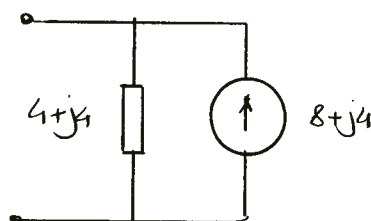


Method 2:

$$\textcircled{1} \underline{V} = \underline{V}_{oc}, \quad \underline{I} = 0$$

$$\text{KCL} \rightarrow \underline{I}_1 = 8$$

$$\text{KVL: } -\underline{I}(j^2) + \underline{I}_1(j6+2) - 2\underline{I} - \underline{V}_{oc} = 0$$
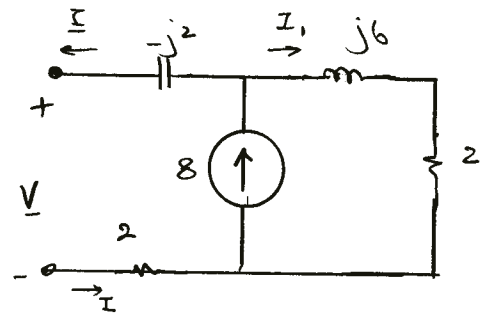
$$\underline{V}_{oc} = \underline{I}_1(j6+2) = 8(j6+2) = 16 + j48 \quad \leftarrow$$



$$\textcircled{2} \underline{V} = 0, \quad \underline{I} = \underline{I}_{sc}$$

using current divider formula


$$\underline{I}_{sc} = \frac{\underline{V}}{-j^2} = \frac{\underline{I}(\underline{X}_{eq})}{-j^2 + 2} = \frac{\frac{1}{-j^2 + 2} \underline{I}}{\underline{V}_{eq}}$$

$$\underline{I}_{sc} = \frac{\frac{1}{2-j^2}}{\frac{1}{2-j^2} + \frac{1}{2+j6}} 8 = \frac{2+j6}{2+j6+2-j^2} \times 8 = \frac{8(2+j6)}{4+j4} = \frac{4+j12}{1+j} = 8+j4$$

$$\underline{I}_{sc} = 8+j4 \quad \leftarrow$$

$$\textcircled{3} \underline{Z}_T \quad (\text{kill all independent source})$$
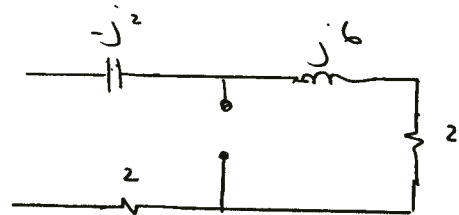
$$\underline{Z}_T = -j2 + j6 + 2 + 2 = 4 + j4$$




Conversion to time domain

$$\underline{V}_T = 16 + j48 = 50.60 \angle 71.57^\circ$$


$$\underline{I}_{sc} = 8 + j4 = 8.94 \angle 26.57^\circ$$
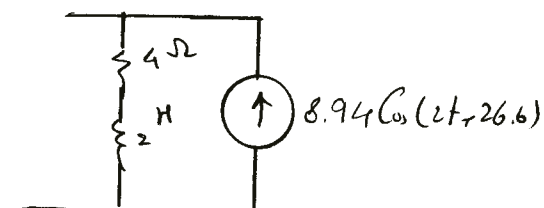
$$\underline{Z}_T = 4 + j4 = \underbrace{4}_{R} + \underbrace{j\omega 2}_{L}$$



$$v_T = 50.60 \cos(2t + 71.57^\circ)$$

$$i_{sc} = 8.94 \cos(2t + 26.57^\circ)$$

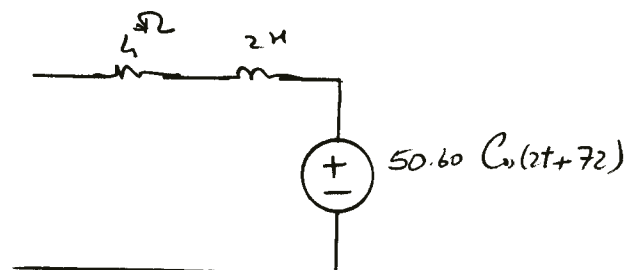

★ Norton / Thevenin Transformation is frequency dependent

Dependent sources


Ex-ple Find v_1

$$\omega = 2$$

$$2 \cos 2t \rightarrow 2$$

$$\frac{1}{8} F \rightarrow \frac{-j}{\omega C} = \frac{-j}{2 \cdot 1/8} = -j4$$
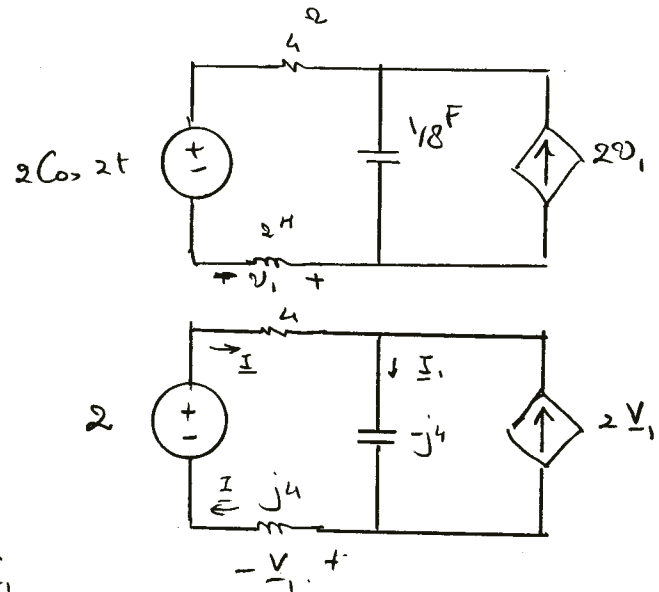
$$2H \rightarrow j\omega L = j(2)(2) = j4$$



$$\text{KCL: } -I + 2V_1 + I_1 = 0 \Rightarrow I_1 = I + 2V_1$$

$$\text{KVL: } 4I + I_1(-j4) + V_1 - 2 = 0 \Rightarrow 4I - j4(I + 2V_1) + V_1 = 2$$

$$\text{Ans: } V_1 = +j4 I$$

$$\begin{cases} I_1 = I + 2V_1 \\ I(4 - j4) + V_1(1 - j8) = 2 \\ V_1 = +j4 I \end{cases}$$

$$I(4 - j4 + j4(1 + j8)) = 2 \Rightarrow I = \frac{2}{36} A$$

$$V_1 = j4 I = \frac{j8}{36} A$$

$$\begin{cases} I = 0.0556 A = 56.6 \angle 0^\circ \text{ mA} \\ V_1 = j0.224 V = 0.224 \angle 90^\circ V \end{cases}$$

$$i(t) = 56.6 \cos(2t)$$

$$\begin{aligned} v(t) &= 0.224 \cos(2t + 90^\circ) \\ &= -0.224 \sin(2t) \end{aligned}$$


SUPERPOSITION

- If all sources have the same frequency, superposition is an alternative to other analysis methods
- If a circuit contains sources with different frequencies, superposition is the only applicable method



Method:

- ① Write the response in terms of circuit response to sources of the same frequency (kill other sources)
- ② Solve each circuit in the frequency domain
- ③ transfer the solution to time domain.
- ④ Sum over all sources.

Example: Find v

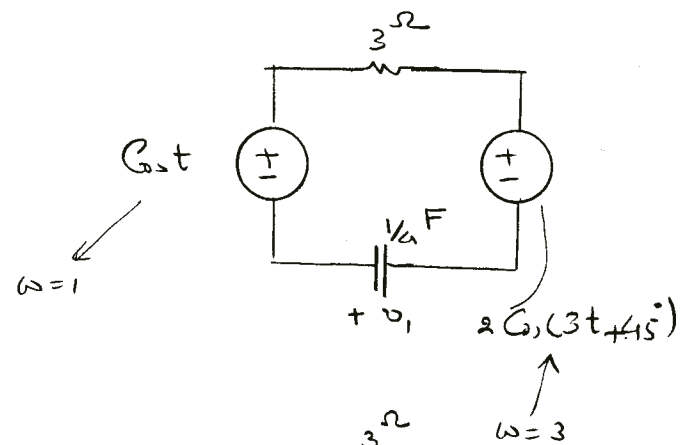


① Superposition in time domain

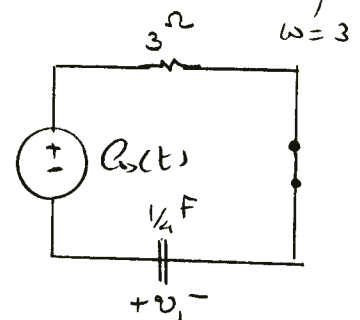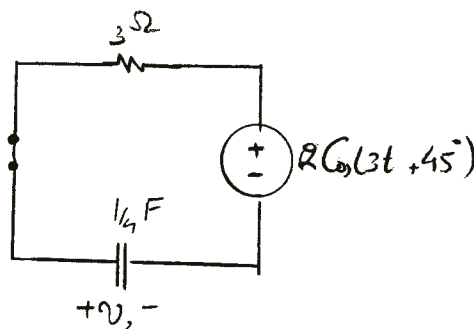

② Solve circuits 1 & 2 in frequency domain

$$\omega=1, \quad \frac{1}{4}F \rightarrow -\frac{j}{\omega C} = -\frac{j}{1/4} = -j4$$
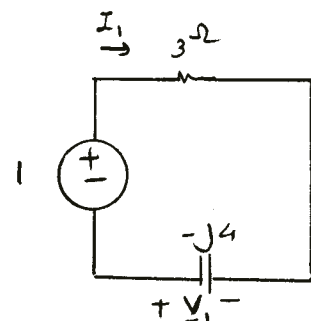
$$\underline{V}_1 = -\underline{I}_1 (j4) = -j4 \frac{1}{3-j4} = \frac{4}{25} (4-j3)$$



$$\underline{V}_1 = \frac{4}{25}(4-j3) = 0.8 \angle -37^\circ$$

$$v_1(t) = 0.8 \cos(t - 37^\circ)$$

Circuit #2

$$\omega = 3$$

$$2\cos(3t + 45^\circ) \rightarrow 2e^{j45^\circ} = 2\left(\frac{\sqrt{2}}{2} + j\frac{\sqrt{2}}{2}\right)$$

$$\frac{1}{4}F \rightarrow -\frac{j}{\omega C} = -\frac{j}{3 \times \frac{1}{4}} = -j\frac{4}{3}$$

$$\underline{V}_2 = \underline{I}_2 \left(-j\frac{4}{3}\right) = \left(-j\frac{4}{3}\right) \frac{\sqrt{2} + j\sqrt{2}}{3 - j4/3}$$


$$\underline{V}_2 = \frac{-j4(\sqrt{2} + j\sqrt{2})}{9 - j4} = 4\sqrt{2} \frac{1 - j}{9 - j4} = 4\sqrt{2} \frac{\sqrt{2} \angle -45^\circ}{\sqrt{97} \angle -24^\circ} = \frac{8}{9.85} \angle -45^\circ + 24^\circ$$

$$\underline{V}_2 = 0.81 \angle -21^\circ$$

$$v_2 = 0.81 \cos(3t - 21^\circ)$$

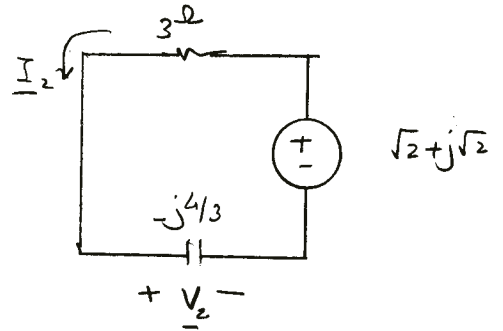(3) Add in time domain.

$$v(t) = v_1(t) + v_2(t) = 0.80 \cos(t - 37^\circ) + 0.81 \cos(3t - 21^\circ)$$




Notes: • You do not need to divide the circuit into sub circuits each containing only one source. Divide the circuit into sub circuits containing sources of same frequency (or DC, i.e. $\omega = 0$). Then solve each circuit with an appropriate analysis method in the frequency domain.

• Always add responses in the time domain & not the frequency domain.

MAXIMUM POWER TRANSFER

AC Circuits
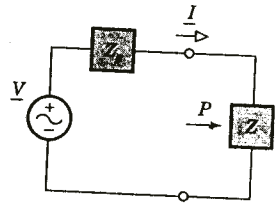
$$\begin{cases} Z_s = R_s + jX_s \\ Z = R + jX \end{cases}$$



$$I = \frac{V}{Z + Z_s}$$

$$P = \frac{1}{2} R I_m^2 = \frac{R}{2} \frac{V_m^2}{|Z + Z_s|^2} = \frac{V_m^2}{2} \cdot \frac{R}{[(R + R_s)^2 + (X + X_s)^2]}$$

To find Z (R & X) values which maximize P , set $\frac{\partial P}{\partial R} = 0$, $\frac{\partial P}{\partial X} = 0$

$$\frac{\partial P}{\partial X} = \frac{V_m^2 R}{2} \cdot \frac{-2(X + X_s)}{[(R + R_s)^2 + (X + X_s)^2]^2} = 0 \Rightarrow X = -X_s$$

$$\frac{\partial P}{\partial R} = \frac{V_m^2}{R} \frac{(R + R_s)^2 + (X + X_s)^2 - 2R(R + R_s)}{[(R + R_s)^2 + (X + X_s)^2]^2} = 0$$

$$\rightarrow (R + R_s)^2 + (X + X_s)^2 - 2R(R + R_s) = 0 \Rightarrow R + R_s - 2R = 0 \Rightarrow R = R_s$$

$$\text{Maximum Power Transfer} \rightarrow \begin{cases} R = R_s \\ X = -X_s \\ Z = Z^* \end{cases}$$

$$\text{Maximum Available Power } P_{max} = \frac{V_m^2}{2} \cdot \frac{R_s}{(2R_s)^2} = \frac{V_m^2}{8R_s} = \frac{V_{rms}^2}{4R_s}$$