


### III. Transistors (Introduction & Large Signal Model)

#### 3.1 III. Bipolar-Junction (BJT) Transistors

A bipolar junction transistor is formed by joining three sections of semiconductors with alternative different dopings. The middle section (base) is narrow and one of the other two regions (emitter) is heavily doped. The other region is called the collector. Two variants of BJT are possible: NPN (base is made of p-type material) and PNP (base is made of n-type material). Let's first consider a NPN transistor.


A BJT has three terminals. Six parameters;  $i_C$ ,  $i_B$ ,  $i_E$ ,  $v_{CE}$ ,  $v_{BE}$ , and  $v_{BC}$ ; define the state of the transistor. However, because BJT has three terminals, KVL and KCL should hold for these terminals:
 
$$i_E = i_C + i_B \qquad v_{BC} = v_{BE} - v_{CE}$$




Thus, only four of these 6 parameters are independent. The relationships among these four parameters ( $i_B$ ,  $v_{BE}$ ,  $i_C$  and  $v_{CE}$ ) represent the “ $i_v$ ” characteristics of the BJT.

At the first glance, a BJT looks like 2 diodes placed back to back. Indeed this is the case if we apply a voltage to only two of the three terminals, letting the third terminal float. This is also the way that we check if a transistor is working: use an am-meter to ensure both diodes are in working conditions. (One should also check the resistance between CE terminals and read a vary high resistance as one may have a burn through the base connecting collector and emitter.)

 

BJT behavior is quite different, however, when voltages are applied to both BE and CE terminals. The BE junction acts like a diode. When this junction is forward biased ( $v_{BE} = V_{D0}$ ), electrons flow from the emitter to the base to combine with holes there. But as the emitter region is heavily doped, there is a large number of electrons crossing into the base compared to available holes. As the base region is narrow, most of these electrons diffuse into the collector region. Then, if a positive voltage is applied between collector and base ( $v_{CB} > 0$  but can be small), these electrons are “collected” by the collector electrode. Note that the BC junction is reverse biased ( $v_{BC} < 0$ ) but a large current flows.

 

Because the BE junction acts as a diode: 1) The number of electrons that cross from the emitter into the base and diffuse into collector region depends exponentially on the voltage applied to the BE junction,  $v_{BE}$  (similar to the diode equation). 2) For a given  $v_{BE}$ , the

number of holes traveling from base to emitter (proportional to  $i_B$ ) is a constant fraction of the number of electrons traveling from emitter to base (proportional to  $i_C$ ). This ratio depends on doping level, temperature, and other manufacturing parameters. In a BJT, because emitter is heavily doped, there are a lot more electrons (from emitter) than holes (from the base), *e.g.*, on the average, out of every 200 electrons traveling from emitter to base only one combines with a hole and the other 199 travel to the collector. As such, the ratio of  $i_C/i_B = \beta$  is a large and a constant (depending on doping, temperature, etc.). Parameter  $\beta$  is called the BJT common-emitter current gain or current gain for short.


The above discussion, identifies two modes of operation for a NPN BJT.

1) BE junction is reverse biased ( $i_B = 0$ ): No electrons would flow from emitter into the base and into the collector, leading to  $i_C = 0$ . This mode is called the cut-off.

 2) BE is forward biased and BC is reverse biased. This is called the active-linear mode (or active mode for short). In this case, a large  $i_C = \beta i_B$  flows. Using diode  $i v$  equation for BE junction:

$$i_B = I_{S,B} \left( e^{v_{BE}/nV_T} - 1 \right) \equiv \frac{I_S}{\beta} \left( e^{v_{BE}/nV_T} - 1 \right) \approx \frac{I_S}{\beta} e^{v_{BE}/nV_T}$$

$$i_C = I_S \left( e^{v_{BE}/nV_T} - 1 \right) \approx I_S e^{v_{BE}/nV_T}$$



We can also construct a circuit model for a BJT which is valid for cut-off and active modes.


In the active mode, BE is forward biased ( $v_{BE} = V_{D0}$ ) while BC is reverse biased ( $v_{BC} < 0$ ). Thus  $v_{CE} = -v_{BC} + v_{BE} \geq V_{D0}$ . Now, let's consider the case when  $v_{CE}$  is reduced below  $V_{D0}$  and BC junction becomes forward biased. In this case, extra holes will be injected into the base region. These extra holes will combine with the electrons traveling from emitter to collector, reducing the collector current. This mode of operation is called the saturation mode and for a given  $v_{BE}$  has a smaller collector current than the active mode, or  $i_C/i_B < \beta$ .

We saw in the diode section that when the junction is forward biased, a negligible current flows until the forward bias voltage is large enough, typically  $\sim 0.3$  V for a Si diode. Thus, as  $v_{CE}$  is decreased below  $V_{D0}$ , for the first  $\sim 0.3$  V ( $v_{CE} \geq 0.4$  V)  $i_C$  changes little as a negligible number of extra holes are injected in the base. This mode is called "soft saturation" and transistor acts nearly as if it is in active mode, *i.e.*,  $i_C \approx \beta i_B$ . For this reason, some text books define the boundary of the active mode to be  $v_{CE} \geq 0.4$  V instead of  $v_{CE} \geq V_{D0} = 0.7$  V for Si BJTs, thereby including the soft saturation operation in the active mode).

When  $v_{BC}$  is increased above  $\sim 0.3$  V, an appreciable number of holes are injected in the base and the collector current drops substantially. For a Si BJT, this part of saturation translates into  $v_{CE} = 0.1 - 0.3$  V and  $i_C$  is substantially smaller than  $\beta i_B$ .

BJT  $i_C$  characteristics are shown as plots of  $i_C$  vs  $v_{CE}$  for different values of  $i_B$  as is shown. The three main modes (or states) of BJT can be clearly seen: cut-off, active-linear, and saturation.

 
Note that a transistor can be damaged if (1) a large positive voltage is applied across the CE junction (breakdown region), or (2) product of  $i_C v_{CE}$  exceed power handling of the transistor, or (3) a large reverse voltage is applied between any two terminals.



Looking at  $i_C v_{CE}$  characteristics above (which is for a real BJT) for the active mode, one notes that for a given  $i_B$ ,  $i_C$  increases slightly as  $v_{CE}$  is increased (as opposed to  $i_C \beta i_B$ ). The reason for this increase in  $i_C$  is that as  $v_{CE}$  is increased, the “effective” width of the base region is reduced and more electrons can reach the collector. This is called the “Early” effect. In fact, we extrapolate all characteristics lines, they would meet at a negative voltage  $v_{CE} = -V_A$  as is shown below. The voltage  $V_A$  is particular to each BJT (depends on its manufacturing) and has a typical value of 50 to 100 V. It is called the “Early” voltage. The Early effect can be accounted for by the following addition to the  $i_C$  equation (Note  $i_B$  equation does NOT change):


$$i_C = I_S e^{v_{BE}/nV_T} \left( 1 + \frac{v_{CE}}{V_A} \right)$$
 
$$i_B = \frac{I_S}{\beta} e^{v_{BE}/nV_T}$$


 
## PNP transistor



A PNP transistor operates in a similar manner to a NPN BJT, expect that the majority carriers are now holes. Emitter region is doped heavily with a p-type material, holes from emitter travel through the base and reach the collector region.



As can be seen, currents and voltages will have to reverse sign compared to a NPN transistor, *e.g.*,  $v_{EB} = V_{D0}$  for EB junction to be forward biased. As holes move slower than electrons in a semiconductor, PNP transistors have a slower response time. They are mainly used in pairs with NPN transistors, *e.g.*, push-pull amplifiers.

### Summary of BJT Large-Signal Models:

	NPN	PNP
<b>Cut-off:</b>		
BE reverse biased	$i_B = 0,$ $i_C = 0$	$i_B = 0$ $i_C = 0$
<b>Active Linear:</b>		
BE forward biased	$i_B = \frac{I_S}{\beta} e^{v_{BE}/nV_T}$	$i_B = \frac{I_S}{\beta} e^{v_{EB}/nV_T}$
CE reverse biased	$i_C = I_S e^{v_{BE}/nV_T} \left(1 + \frac{v_{CE}}{V_A}\right)$	$i_C = I_S e^{v_{EB}/nV_T} \left(1 + \frac{v_{EC}}{V_A}\right)$
<b>Saturation:</b>		
BE forward biased	$i_B = \frac{I_S}{\beta} e^{v_{BE}/nV_T}$	$i_B = \frac{I_S}{\beta} e^{v_{EB}/nV_T}$
CE forward biased	$i_C < \beta i_B, v_{CE} = 0.1 - 0.3 \text{ V}$	$i_C < \beta i_B, v_{EC} = 0.1 - 0.3 \text{ V}$

  

The above model is called a “large signal” model as it applies to any size currents/voltages applied to the BJT (as opposed to a “small-signal” model discussed later). In addition, this is a “low-frequency” model as the junction capacitances are NOT taken into account (you will see high-frequency transistor models in ECE102). PSpice uses the Ebers-Moll model which includes a better treatment of transistor operation in the saturation mode.

Similar to diodes, BJT  $iv$  equations above are non-linear. For analytical calculations, we will develop a simple piecewise linear model for BJT below.

### 3.2 Piecewise Linear, Large Signal Model for BJT

First let's consider a NPN transistor. In the cut-off and active modes, BE junction acts like a diode and  $i_C = \beta i_B(1 + v_{CE}/V_A)$ . As such, we can use our piecewise linear model for the diode to arrive at a piecewise linear model for the BJT.

**Cut-Off:**  $i_B = 0, \quad v_{BE} < V_{D0}$   
 $i_C = i_E = 0$

**Active:**  $v_{BE} = V_{D0}, \quad i_B \geq 0$   
 $i_C = \beta i_B, \quad v_{CE} \geq V_{D0}$


Early Effect is ignored in this simple model as additional accuracy (< 5%) does not justify additional work. Early Effect can be included by setting  $i_C = \beta i_B(1 + v_{CE}/V_A)$ .

Also, in the soft saturation mode, ( $v_{CE} \geq 0.4$  V for Si BJTs),  $i_C \approx \beta i_B$  and thus, we can replace  $v_{CE} \geq V_{D0}$  in the model for the active mode with  $v_{CE} \geq 0.4$  V. However, care should be taken in designing circuit in which a BJT is in soft saturation. As such, in this course, we will use  $v_{CE} \geq V_{D0}$  as the boundary between active and saturation modes.

For a Si BJT in saturation,  $0.1 \leq v_{CE} \leq 0.3$  V. Given that an exact model for saturation mode is complicated, it is sufficient for a piecewise linear model to assume  $v_{CE} = V_{sat}$  (with  $V_{sat} \approx 0.2$  V for Si transistors). Thus:

**Saturation:**  $v_{BE} = V_{D0}, \quad i_B > 0$   
 $v_{CE} \approx V_{sat}, \quad i_C < \beta i_B$


 
The above simple, large-signal model is shown below. A comparison of this simple model with the real BJT characteristics demonstrates the degree of approximation used.



A similar piecewise linear model for PNP transistor can also be constructed:

## Summary of BJT piecewise linear large-signal Model

	NPN	PNP
<b>Cut-off:</b>	$i_B = 0, v_{BE} < V_{D0}$ $i_C = 0$	$i_B = 0, v_{EB} < V_{D0}$ $i_C = 0$
<b>Active Linear:</b>	$v_{BE} = V_{D0}, i_B > 0$ $i_C = \beta i_B > 0, v_{CE} > V_{D0}$	$v_{EB} = V_{D0}, i_B > 0$ $i_C = \beta i_B > 0, v_{EC} > V_{D0}$
<b>Saturation:</b>	$v_{BE} = V_{D0}, i_B > 0$ $v_{CE} = V_{sat}, i_C < \beta i_B$	$v_{EB} = V_{D0}, i_B > 0$ $v_{EC} = V_{sat}, i_C < \beta i_B$

  

### How to solve BJT circuits:

Similar to diode circuits, we need assume that BJT is in a particular state, use BJT model for that state to solve the circuit and check the validity of our assumption.

*Recipe for solving NPN BJT circuits:*

- 1) Write down a KVL including the BE terminals.
- 2) Write down a KVL including CE terminal.
- 3) Assume BJT is in cut-off (this is the simplest). Set  $i_B = 0$ . Calculate  $v_{BE}$  from BE-KVL.
  - 3a) If  $v_{BE} < V_{D0}$ , then BJT is in cut-off,  $i_B = 0$  and  $v_{BE}$  is what you just calculated. Set  $i_C = i_E = 0$ , and calculate  $v_{CE}$  from CE-KVL. You are done.
  - 3b) If  $v_{BE} > V_{D0}$ , then BJT is not in cut-off. Set  $v_{BE} = V_{D0}$ . Solve above KVL to find  $i_B$ . You should get  $i_B > 0$ .
- 4) Assume that BJT is in linear mode. Let  $i_E \approx i_C = \beta i_B$ . Calculate  $v_{CE}$  from CE-KVL.
  - 4a) If  $v_{CE} > V_{D0}$ , then BJT is in active mode. You are done.
  - 4b) If  $v_{CE} < V_{D0}$ , then BJT is not in active mode. It is in saturation. Let  $v_{CE} = V_{sat}$  and compute  $i_C$  from CE-KVL. You should find that  $i_C < \beta i_B$ . You are done.

For PNP transistors, substitute,  $v_{BE}$  with  $v_{EB}$  and  $v_{CE}$  with  $v_{EC}$  in the above recipe.

**Note:** While in BJT circuits, value of  $v_{BC}$  is not calculated (and is not important, value  $i_E$  can appear in our equations. In the active mode,  $i_E = i_C + i_B = (\beta + 1)i_B$  and  $i_E = [(\beta + 1)/\beta]i_C$ . Since  $\beta \gg 1$ , it is convenient to use  $i_E \approx i_C$  for simplicity. Note that for a practical BJT circuit even in saturation mode  $i_C \gg i_B$  and  $i_E \approx i_C$ .

**Example 1:** Compute the parameters of this circuit ( $\beta = 100$ ).

Following the procedure above (for NPN transistor):

$$\text{BE-KVL: } 4 = 40 \times 10^3 i_B + v_{BE}$$

$$\text{CE-KVL: } 12 = 10^3 i_C + v_{CE},$$

Assume BJT is in cut-off. Set  $i_B = 0$  in BE-KVL:

$$\text{BE-KVL: } 4 = 40 \times 10^3 i_B + v_{BE} \rightarrow v_{BE} = 4 > V_{D0} = 0.7 \text{ V}$$

So BJT is not in cut off and BJT is ON. Set  $v_{BE} = 0.7 \text{ V}$  and use BE-KVL to find  $i_B$ .


$$\text{BE-KVL: } 4 = 40 \times 10^3 i_B + v_{BE} \rightarrow i_B = \frac{4 - 0.7}{40,000} = 82.5 \mu\text{A}$$

Assume BJT is in active linear, Find  $i_C = \beta i_B$  and use CE-KVL to find  $v_{CE}$ :

$$i_C = \beta i_B = 100 i_B = 8.25 \text{ mA}$$

$$\text{CE-KVL: } 12 = 1,000 i_C + v_{CE}, \rightarrow v_{CE} = 12 - 8.25 = 3.75 \text{ V}$$

As  $v_{CE} = 3.75 > V_{D0}$ , the BJT is indeed in active-linear and we have:  $v_{BE} = 0.7 \text{ V}$ ,  $i_B = 82.5 \mu\text{A}$ ,  $i_E = (\beta + 1)i_C = 8.33 \text{ mA}$ , and  $v_{CE} = 3.75 \text{ V}$ .

 

**Example 2:** Compute the parameters of this circuit ( $\beta = 100$ ).


Following the procedure above (for PNP transistor):

$$\text{BE-KVL: } -4 = -40 \times 10^3 i_B - v_{EB}$$

$$\text{CE-KVL: } -12 = -10^3 i_C - v_{EC},$$

Assume BJT is in cut-off. Set  $i_B = 0$  in BE-KVL:
 
$$\text{BE-KVL: } -4 = -40 \times 10^3 i_B - v_{EB} \rightarrow v_{EB} = 4 \rightarrow v_{EB} = 4 > V_{D0} = 0.7 \text{ V}$$



So BJT is not in cut off and BJT is ON. Set  $v_{EB} = 0.7 \text{ V}$  and use BE-KVL to find  $i_B$ .

$$\text{BE-KVL: } -4 = -40 \times 10^3 i_B - v_{EB} \quad \rightarrow \quad i_B = \frac{4 - 0.7}{40,000} = 82.5 \mu\text{A}$$

Assume BJT is in active mode. Find  $i_C = \beta i_B$  and use CE-KVL to find  $v_{EC}$ :

$$i_C = \beta i_B = 100 i_B = 8.25 \text{ mA}$$

$$\text{CE-KVL: } -12 = -10^3 i_C - v_{EC}, \quad \rightarrow \quad v_{EC} = 12 - 8.25 = 3.75 \text{ V}$$

As  $v_{EC} = 3.75 > V_{D0}$ , the BJT is indeed in active mode and we have:  $v_{EB} = 0.7 \text{ V}$ ,  $i_B = 82.5 \mu\text{A}$ ,  $i_E = (\beta + 1)i_C = 8.33 \text{ mA}$ , and  $v_{EC} = 3.75 \text{ V}$ .

Note: Comparing Examples 1 and 2, they are identical circuits (expect voltages and currents changed sign) one with a NPN transistor and one with a PNP transistor (similar  $\beta$ s). As can be seen all currents and voltages are the same (expect signs).


**Example 3:** Compute the parameters of this circuit ( $\beta = 100$ ).

$$\text{BE-KVL: } 4 = 40 \times 10^3 i_B + v_{BE} + 10^3 i_E$$

$$\text{CE-KVL: } 12 = 1,000 i_C + v_{CE} + 1,000 i_E$$

Assume BJT is in cut-off. Set  $i_B = 0$  and  $i_E = i_C = 0$  in BE-KVL:
 
$$\text{BE-KVL: } 4 = 40 \times 10^3 i_B + v_{BE} + 10^3 i_E \quad \rightarrow \quad v_{BE} = 4 > 0.7 \text{ V}$$



So BJT is not in cut off and  $v_{BE} = 0.7 \text{ V}$  and  $i_B > 0$ . Here, we cannot find  $i_B$  right away from BE-KVL as it also contains  $i_E$ . Assume BJT is in active linear,  $i_E = (\beta + 1)i_B$ :

$$\text{BE-KVL: } 4 = 40 \times 10^3 i_B + v_{BE} + 10^3 (\beta + 1) i_B = 0.7 + (40 \times 10^3 + 10^3 \times 101) i_B$$

$$i_B = 24 \mu\text{A} \quad \rightarrow \quad i_C = \beta i_B = 2.4 \text{ mA}, \quad i_E = (\beta + 1) i_B = 2.4 \text{ mA}$$

$$\text{CE-KVL: } 12 = 1,000 i_C + v_{CE} + 1,000 i_E, \quad \rightarrow \quad v_{CE} = 12 - 4.8 = 7.2 \text{ V}$$

As  $v_{CE} = 7.2 > V_{D0}$ , the BJT is indeed in active-linear and we have:  $v_{BE} = 0.7 \text{ V}$ ,  $i_B = 24 \mu\text{A}$ ,  $i_E \approx i_C = 2.4 \text{ mA}$ , and  $v_{CE} = 7.2 \text{ V}$ .

**Example 4:** Compute the parameters of the Si transistor ( $\beta = 100$ ) in the circuit below.

Since there is a 10 V supply in the BE-loop, it is a good starting assumption that BJT is ON (PNP:  $v_{EB} = V_{D0} = 0.7$  V and  $i_B > 0$ )

$$\begin{aligned} \text{BE-KVL: } \quad 10 &= 2 \times 10^3 i_E + v_{EB} \\ i_E &= \frac{10 - 0.7}{2 \times 10^3} = 4.65 \text{ mA} \end{aligned}$$


Since  $i_E > 0$ , the assumption of BE ON is justified (since  $i_E > 0$  requires both  $i_B$  and  $i_C > 0$ ). Assuming BJT in active:

$$i_E = i_C + i_B = (\beta + 1)i_B \quad \rightarrow \quad i_B = 4.65/101 \simeq 50 \mu\text{A}$$

$$i_C = i_E - i_B \simeq 4.6 \text{ mA}$$

$$\begin{aligned} \text{CE-KVL: } \quad 10 &= 2 \times 10^3 i_E + v_{EC} + 10^3 i_C - 10 \\ 10 &= 9.3 + v_{EC} + 10^3 \times 4.6 \times 10^{-3} - 10 = v_{EC} + 3.9 \\ v_{EC} &= 6.1 \text{ V} \end{aligned}$$

 
Since  $v_{EC} = 6.1 > 0.7 = V_{D0}$ , the assumption of BJT in active is justified and  $v_{EB} = 0.7$  V,  $i_B = 50 \mu\text{A}$ ,  $v_{EC} = 6.1$  V, and  $i_C = 4.6$  mA,


 
## Load line


The operating point of a BJT can be found graphically using the concept of a load line (similar to diode load line). For BJTs, the load line is the relationship between  $i_C$  and  $v_{CE}$  that is imposed on BJT by the external circuit. For a given value of  $i_B$ , the  $i_C v_{CE}$  characteristics curve of a BJT is the relationship between  $i_C$  and  $v_{CE}$  as is set by BJT internals. The intersection of the load line with the BJT characteristics represent a pair of  $i_C$  and  $v_{CE}$  values which satisfy both conditions and, therefore, is the operating point of the BJT (often called the Q point for Quiescent point).

The equation of a load line for a BJT should include only  $i_C$  and  $v_{CE}$  (no other unknowns). This equation is usually found by writing a KVL around a loop containing  $v_{CE}$ . For the circuit shown, we have:



$$\text{KVL: } 15 = 375i_C + v_{CE}$$

 which is the equation of a line in the  $i_C v_{CE}$  space. This “load line” and the  $i_C v_{CE}$  characteristics lines of the BJT are shown below. The operating point of the BJT (Q-point) is also shown for  $i_B = 150 \mu\text{A}$  (or  $v_i = 6.7 \text{ V}$  in the example above).




Note that if an emitter resistor is present (*e.g.*, Example 3 in page 3-8), the load line can still be constructed noting that  $i_E = [(\beta + 1)/\beta]i_C \approx i_C$ :

$$\text{KVL: } 12 = 1,000i_C + v_{CE} + 1,000i_E \quad \rightarrow \quad 12 \approx 2,000i_C + v_{CE}$$
 
### 3.3 BJT Switches and Logic Gates

The basic element of logic circuits is the transistor switch. A schematic of such a switch is shown. When the switch is open,  $i_C = 0$  and  $v_o = V_{CC}$ . When the switch is closed,  $v_o = 0$  and  $i_C = V_{CC}/R_C$ .

In electronic circuits, mechanical switches are not used. The switching action is performed by a transistor, as is shown. When  $v_i = 0$ , BJT will be in cut-off,  $i_C = 0$ , and  $v_o = V_{CC}$  (open switch). When  $v_i$  is in “high” state, BJT can be in saturation with  $v_o = v_{CE} = V_{sat} \approx 0.2$  V and  $i_C = (V_{CC} - V_{sat})/R_C$  (closed switch). When  $R_c$  is replaced with a load, this circuit can switch a load ON or OFF (see *e.g.*, Problems 12 & 13).




#### 3.3.1 Logic Gates

You have seen binary mathematics and logic gates in ECE25. We will explore some electronic logic gates in this course. Binary mathematics is built upon two states: 0, and 1. We need to relate the binary states to currents or voltages as these are the parameters that we can manipulate in electronic circuits. Similar to our discussion of analog circuits, it is advantageous (from power point of view) to relate these the binary states to voltages. As such, we “choose” two voltages to represent the binary states:  $v_L$  for state 0 or Low state and  $v_H$  for state 1 or High state (for example, 0 V to represent state 0 and 5 V to represent state 1). These voltages are quite arbitrary and can be chosen to have any value.


Similar to analog circuits, we plot the voltage transfer function of a gate. For example, the transfer function of an “ideal” inverter is shown in the figure: when the input is low, the output is high and the when the input is high, the output is low. We can see a difficulty right away. In a practical circuit, there would be an output voltage for any input voltage, so the output voltage makes a “smooth” transition for the high voltage to the low voltage as the input voltage is varied. We have to be also careful as it is extremely difficult, if not impossible, to design an electronic circuit to give exactly a voltage value like 5 V (what if the input voltage was 4.99 V?). So, we need to define a range of voltages (instead of one value) to represent high and low states. We will try very hard to make sure that the output of our gates to be as close as possible to  $V_H$  and  $V_L$ . But, we need to design our gates such that they respond to a range of voltages, *i.e.*, the gate would think that the input is low if the input voltage is smaller than  $v_{IL}$  and would think that the input is high if the input voltage is larger than  $v_{IH}$  (see figure).

With these definitions, the transfer function of a practical inverter (plot of  $v_o$  as a function of  $v_i$ ) is shown. The range of voltages,  $v_L$  to  $v_{IL}$  and  $v_{IH}$  to  $v_H$  are called the noise margins. The range of voltages between  $v_{IL}$  to  $v_{IH}$  is the forbidden region as in this range, the output of the gate does not correspond to any binary state. The maximum speed that a logic gate can operate is set by the time it takes to traverse this region as the input voltage is varied from one state to another state.

 
 
### 3.3.2 Resistor-Transistor Logic (RTL)

The BJT switch circuit discussed above is also an “inverter” or a “NOT” logic gate. This circuit is a member of RTL family of logic gates. Let’s assume that the “low” state is at  $v_L = 0.2$  V ( $V_{sat}$ ) and the “high” state is  $v_H = V_{CC}$ .



To find the transfer function of this gate, we need to find  $v_o$  for a range of  $v_i$  values. This plot will also help identify the values of  $v_{IL}$  and  $v_{IH}$ .

From BE-KVL,  $v_i = R_B i_B + v_{BE}$ , we find that for  $v_i < V_{D0}$ , BJT will be in cut-off,  $i_C = 0$  and  $v_o = V_{CC}$  (high state). Therefore, when  $v_i = v_L = V_{sat}$ ,  $v_o = V_{CC} = v_H$ . Moreover, The output will be high as long as  $v_i < V_{D0}$ , or  $v_{IL} = V_{D0}$ . Note that  $v_{IL}$  corresponds to the case where  $v_{BE} = V_{D0}$  and  $i_B > 0$  but small such that the term  $i_B R_B$  can be ignored compared to  $v_{BE}$ .

When  $v_i$  exceeds  $V_{D0}$ , BE junction will be forward biased and a current  $i_B$  flows into BJT:

$$i_B = \frac{v_i - V_{D0}}{R_B}$$

As BE junction is forward biased, BJT can be either in saturation or active-linear. Let’s assume BJT is in saturation. In that case,  $v_o = v_{CE} = V_{sat}$  and  $i_C/i_B < \beta$ . Then:



$$i_C = \frac{V_{CC} - V_{sat}}{R_C} \rightarrow i_B > \frac{i_C}{\beta} = \frac{V_{CC} - V_{sat}}{\beta R_C}$$

Therefore, BJT will be in saturation only if  $i_B$  exceeds the value given by the formula above. This occurs when  $v_i$  become large enough:

$$v_i = V_{D0} + R_B i_B > V_{D0} + R_B \times \frac{V_{CC} - V_{sat}}{\beta R_C} = v_{IH}$$

If we choose  $R_B$  and  $R_C$  such that  $v_{IH} < V_{CC}$ , then for  $v_i = V_{CC}$ , BJT will be in saturation, and  $v_{CE} = V_{sat}$ . Overall, for  $v_i = v_L = V_{sat}$ ,  $v_o = V_{CC} = v_H$  and for  $v_i = v_H = V_{CC}$ ,  $v_o = V_{sat} = v_L$ . Thus, this is a NOT gate.


For  $v_i$  values between  $v_{IL}$  and  $v_{IH}$ , the BE junction is forward biased but the BJT is NOT in saturation, and thus, it is in active linear. In this case, the output voltage smoothly changes for its high value to its low value as is shown in the plot of transfer function. This range of  $v_i$  is the “forbidden” region and the gate would not work properly in this region. This behavior can also be seen in the plot of the BJT load line. For small values of  $v_i$  ( $i_B = 0$ ) BJT is in cut-off. As  $v_i$  is increased,  $i_B$  is increased and the operating point moves to the left and up on the load line and enters the active-linear region. When  $i_B$  is raised above certain limit, the operating point enters the saturation region.

  

A major drawback of this RTL inverter gate is the limited input range for the “low” signal ( $v_{IL}$ ). For “high” state, the noise margin for “high” state can be controlled by adjusting values of  $R_C$  and  $R_B$ . However, our analysis indicated that  $v_{IL} = V_{D0}$ , that is the gate input is low for voltages between 0.2 V and  $V_{D0} \approx 0.7$  V which is quite a small noise margin. For the above analysis, we have been using a constant-voltage piecewise linear model for the BE junction diode. In reality, the BJT will come out of cut-off (BE junction will conduct) at smaller voltages ( $\sim 0.5$  V), making the noise margin for “low” state even smaller.


In order to build a gate with a larger noise margin for “low” voltage, we examine the BE-KVL:  $v_i = R_B i_B + v_{BE}$ . Note that  $v_i = v_{IL}$  corresponds to  $v_{BE} = V_{D0}$  and  $i_B > 0$  but small. Two approaches are possible: 1) Add an element in series with  $R_B$  which would have a large voltage drop for a small current, *e.g.*, a diode, 2) Allow the current in  $R_B$  to be larger than  $i_B$ . We explore both options below:

For this circuit, BE-KVL gives:  $v_i = v_D + R_B i_B + v_{BE}$ . Then to find  $v_{IL}$ , we substitute for  $v_{BE} = V_{D0}$  and  $i_B > 0$  but small to get:  $v_{IL} \approx v_D + V_{D0}$ . Since  $i_D = i_B > 0$  but small, the diode should also be forward biased and  $v_D = V_{D0}$ . Thus,  $v_{IL} \approx 2V_{D0} = 1.4$  V. Note that  $v_{IL}$  can be increased further in increments of  $V_{D0}$  by adding more diodes in the input.

 

This approach works reasonably well in ICs as the diode and BE junction can be constructed with similar reverse saturation currents. However, for a circuit built with discrete components (*e.g.*, a BJT switch) this approach may not work well as the reverse saturation current for discrete diodes,  $I_{sD}$ , is typically 2 to 3 orders of magnitude larger than reverse saturation current for the BE junction. As such, the small current needed to make  $v_{BE} \simeq V_{D0}$  only leads to  $v_D = 0.2 - 0.3$  V. (see Lab 4 for a solution to this problem).

 The second method to increase the noise margin is to add a resistor between the base and ground as is shown. To see the impact of this resistor, note that  $V_{IL}$  is the input voltage when BJT is just leaving the cut-off region. At this point,  $v_{BE} = V_{D0}$ , and  $i_B$  is positive but very small (effectively zero). Since a voltage  $v_{BE}$  has appeared across  $R_1$ , we have:



$$i_1 = \frac{v_{BE}}{R_1} \quad i_2 = i_B + i_1 \approx i_1 = \frac{v_{BE}}{R_1}$$


$$v_{IL} = v_i = R_B i_2 + v_{BE} = v_{BE} \frac{R_B}{R_1} + v_{BE} = V_{D0} \left( 1 + \frac{R_B}{R_1} \right)$$

This value should be compared with  $v_{IL} = V_{D0}$  in the absence of resistor  $R_1$ . It can be seen that for  $R_B = R_1$ ,  $v_{IL}$  can be raised from 0.7 to 1.4 V. Moreover, arbitrary values of  $v_{IL}$  can be achieved by proper choice of  $R_B$  and  $R_1$ . Typically,  $R_1$  does not affect  $v_{IH}$  as  $i_B$  needed to put the BJT in saturation is typically several times larger than  $i_1$ .
 
## RTL NOR Gate

Logic circuits are typically constructed from “basic” logic gates like NOR or NAND. You have seen in ECE25 that all higher level logic gates, *e.g.*, flip-flops, can be made by a combination of NOR gates or NAND gates. So, for each logic gate that we will work on, we have to remember that the output of the logic gate is attached to the input of another logic gate.


By combining two or more RTL inverters, one obtains the basic logic gate circuit of RTL family, a “NOR” gate, as is shown (see Problem 15). More BJTs can be added for additional input signals.



RTLs were the first digital logic circuits using transistors. They require at least one resistor and one BJT per input. They were replaced with diode-transistor logic, DTL (reduced number of resistors and BJTs) and transistor-transistor logic, TTL (which “packs” all of the didoes in a special transistor). Most popular BJT gates today are TTL or emitter coupled logic, ECL. With the advent of CMOS technology, BJT-based gates are now only used for special purpose circuits (for example, high speed gates utilizing ECL).
 
### 3.3.3 Diode-Transistor Logic (DTL)

The basic gate of DTL logic circuits is a NAND gate which is constructed by a combination of a diode AND gate (analyzed in pages 2-12) and a BJT inverter gate as is shown below (left figure). Because  $R_B$  is large, on ICs, this resistor is usually replaced with two diodes. The combination of the two diodes and the BE junction diode leads to a voltage of 2.1 V for the inverter to switch and a  $v_{IL} = 1.4$  V for the NAND gate (Why?). Resistor  $R_1$  is necessary because without this resistor, current  $i_B$  will be too small and the voltage across  $D_3$  and  $D_4$  will not reach 0.7 V although they are both forward biased.



**Example:** Verify that the DTL circuit above (with  $R_A = 5 \text{ k}\Omega$ ,  $R_C = 1 \text{ k}\Omega$ ,  $R_1 = 5 \text{ k}\Omega$ , and  $V_{CC} = 5 \text{ V}$ ) is a NAND gate. Assume that “low” state is 0.2 V, “high” state is 5 V, and BJT  $\beta_{min} = 40$ .

Case 1:  $v_1 = v_2 = 0.2 \text{ V}$  It appears that the 5-V supply will forward bias  $D_1$  and  $D_2$ . Assume  $D_1$  and  $D_2$  are forward biased:  $v_{D1} = v_{D2} = V_{D0} = 0.7 \text{ V}$  and  $i_1 > 0$ ,  $i_2 > 0$ . In this case:

$$v_3 = v_1 + v_{D1} = v_2 + v_{D2} = 0.2 + 0.7 = 0.9 \text{ V}$$

Voltage  $v_3 = 0.9 \text{ V}$  is not sufficient to forward bias  $D_3$  and  $D_4$  as  $v_3 = v_{D3} + v_{D4} + v_{BE}$  and we need at least 1.4 V to forward bias the two diodes. So both  $D_3$  and  $D_4$  are OFF and  $i_4 = 0$ . (Note that  $D_3$  and  $D_4$  can be forward biased without BE junction being forward biased as long as the current  $i_4$  is small enough such that voltage drop across the 5 k $\Omega$  resistor parallel to BE junction is smaller than 0.7 V. In this case,  $i_5 = i_4$  and  $i_B = 0$ .) Then:

$$i_1 + i_2 = i_A = \frac{5 - v_3}{5,000} = \frac{5 - 0.9}{5,000} = 0.82 \text{ mA}$$

And by symmetry,  $i_1 = i_2 = 0.5i_A = 0.41 \text{ mA}$ . Since both  $i_1$  and  $i_2$  are positive, our assumption of  $D_1$  and  $D_2$  being ON are justified. Since  $i_4 = 0$ ,  $i_B = 0$  and BJT will be in cut-off with  $i_C = 0$  and  $v_o = 5 \text{ V}$ .

So, in this case,  $D_1$  and  $D_2$  are ON,  $D_3$  and  $D_4$  are OFF, BJT is in cut-off, and  $v_o = 5 \text{ V}$ .

Case 2:  $v_1 = 0.2 \text{ V}$ ,  $v_2 = 5 \text{ V}$  Following arguments of case 1, assume  $D_1$  is ON. Again,  $v_3 = 0.7 + 0.2 = 0.9 \text{ V}$ , and  $D_3$  and  $D_4$  will be OFF with  $i_4 = 0$ . We find that voltage across  $D_2$  is  $v_{D2} = v_3 - v_2 = 0.9 - 5 = -4.1 \text{ V}$  and, thus,  $D_2$  will be OFF and  $i_2 = 0$ . Then:

$$i_1 = i_A = \frac{5 - v_3}{5,000} = \frac{5 - 0.9}{5,000} = 0.82 \text{ mA}$$

and since  $i_1 > 0$ , our assumption of  $D_1$  ON is justified. Since  $i_4 = 0$ ,  $i_B = 0$  and BJT will be in cut-off with  $i_C = 0$  and  $v_o = 5 \text{ V}$ .

So, in this case,  $D_1$  is ON,  $D_2$  is OFF,  $D_3$  and  $D_4$  are OFF, BJT is in cut-off, and  $v_o = 5 \text{ V}$ .

Case 3:  $v_1 = 5 \text{ V}$ ,  $v_2 = 0.2 \text{ V}$  Because of the symmetry in the circuit, this is exactly the same as case 2 with roles of  $D_1$  and  $D_2$  reversed.

So, in this case,  $D_1$  is OFF,  $D_2$  is ON,  $D_3$  and  $D_4$  are OFF, BJT is in cut-off, and  $v_o = 5 \text{ V}$ .

Case 4:  $v_1 = v_2 = 5 \text{ V}$  Examining the circuit, it appears that the 5-V supply will NOT be able to forward bias  $D_1$  and  $D_2$ . Assume  $D_1$  and  $D_2$  are OFF:  $i_1 = i_2 = 0$ ,  $v_{D1} < V_{D0}$  and

$v_{D2} < V_{D0}$ . On the other hand, it appears that  $D_3$  and  $D_4$  will be forward biased. Assume  $D_3$  and  $D_4$  are forward biased:  $v_{D3} = v_{D4} = V_{D0} = 0.7$  V and  $i_4 > 0$ . Further, assume the BJT is not in cut-off  $v_{BE} = V_{D0} = 0.7$  V and  $i_B > 0$ . In this case:

$$v_3 = v_{D3} + v_{D4} + v_{BE} = 0.7 + 0.7 + 0.7 = 2.1 \text{ V}$$

$$v_{D1} = v_3 - v_1 = 2.1 - 5 = -2.9 \text{ V} < V_{D0} \quad v_{D2} = v_3 - v_2 = 2.1 - 5 = -2.9 \text{ V} < V_{D0}$$

Thus, our assumption of  $D_1$  and  $D_2$  being OFF are justified. Furthermore:

$$i_4 = i_A = \frac{5 - v_3}{5,000} = \frac{5 - 2.1}{5,000} = 0.58 \text{ mA}$$

$$i_5 = \frac{v_{BE}}{5,000} = \frac{0.7}{5,000} = 0.14 \text{ mA}$$

$$i_B = i_4 - i_5 = 0.58 - 0.14 = 0.44 \text{ mA}$$

and since  $i_4 > 0$  our assumption of  $D_3$  and  $D_4$  being ON are justified and since  $i_B > 0$  our assumption of BJT not in cut-off is justified.

We still do not know if BJT is in active-linear or saturation. Assume BJT is in saturation:  $v_o = v_{CE} = V_{sat} = 0.2$  V and  $i_C/i_B < \beta$ . Then, assuming no gate is attached to the circuit, we have

$$i_C = \frac{5 - V_{sat}}{1,000} = \frac{5 - 0.2}{1,000} = 4.8 \text{ mA}$$

and since  $i_C/i_B = 4.8/0.44 = 11 < \beta = 40$ , our assumption of BJT in saturation is justified.


So, in this case,  $D_1$  and  $D_2$  are OFF,  $D_3$  and  $D_4$  are ON, BJT is in saturation and  $v_o = 0.2$  V.

Overall, the output in “low” only if both inputs are “high”, thus, this is a NAND gate.

**Note:** It is interesting to note that at the input of this gate, the current actually flows out of the gate. In the example above, when both inputs were high  $i_1 = i_2 = 0$ , when both were low  $i_1 = i_2 = 0.4$  mA, and when one input was low, *e.g.*,  $v_1$  was low,  $i_1 = 0.8$  mA. The input current flowing in (or out of the gate in this case) has an important implication as this current should be supplied by the previous logic gate. As such, an important parameter for a logic gate is its “fan-out” (defined as the maximum number of similar gates that can be attached to it).

 
### 3.3.4 Transistor-Transistor Logic (TTL)

A simplified version of an IC-chip NPN transistor is shown. The device is fabricated on a p-type substrate (or body) in a vertical manner by embedding alternating layers of N and P-type semiconductors. By embedding more than one N-type emitter region, one can obtain a multiple-emitter NPN transistor as shown. The multiple-emitter NPN transistors can be used to replace the input diodes of a DTL NAND gate and arrive at a NAND gate entirely made of transistors, hence Transistor-Transistor Logic (TTL) gates.



A simple TTL gate is shown with the multiple-emitter BJT replacing the input diodes. This transistor operates in “reverse-active” mode, *i.e.*, like a NPN transistor in active-linear mode but with collector and emitter switched. Operationally, this BJT acts as two diodes back to back as shown in the circle at the bottom of the figure. As such the operation of this gate is essentially similar to the DTL NAND gate described above (note position of driver transistor and  $D_4$  diode is switched).

Similar to DTL NAND gates, a typical TTL NAND gate has three stages: 1) Input stage (multi-emitter transistor), 2) driver stage, and 3) output stage. Modern TTL gates basically have the same configuration as is shown with the exception that the output stage is replaced with the “Totem-Pole” output stage to increase switching speed and gate fan-out. For a detailed description of TTL gate with “Totem-Pole” output stage, consult Sedra and Smith, 6th Ed (page 1191).

 


### 3.4 Field-Effect (FET) Transistors

In a field-effect transistor (FET), the width of a conducting channel in a semiconductor and, therefore, its current-carrying capability, is varied by the application of an electric field (thus, the name field-effect transistor). The most widely used FETs are Metal-Oxide-Semiconductor FETs (MOSFET or MOS for short). MOSFETs can be manufactured as enhancement-type or depletion-type and each can be fabricated either as a  $n$ -channel device or a  $p$ -channel device. We will focus below on the operation of enhancement MOSFETs that are the most popular (depletion-type) MOS operation is similar to enhancement type. There exists another type of FET, the Junction Field-Effect Transistors (JFET) which is not based on metal-oxide fabrication technique.
 
#### $n$ -Channel Enhancement-Type MOSFET (NMOS)


The physical structure of a  $n$ -Channel Enhancement-Type MOSFET (NMOS) is shown. The device is fabricated on a  $p$ -type substrate (or Body). Two heavily doped  $n$ -type regions (Source and Drain) are created in the substrate. A thin (fraction of micron) layer of  $\text{SiO}_2$ , which is an excellent electrical insulator, is deposited between source and drain region. Metal is deposited on the insulator to form the Gate of the device (thus, metal-oxide semiconductor). Metal contacts are also made to the source, drain, and body region.



To see the operation of a NMOS, let's ground the source and the body and apply a voltage  $v_{GS}$  between the gate and the source, as is shown above. This voltage repels the holes in the  $p$ -type substrate near the gate region, lowering the concentration of the holes. As  $v_{GS}$  increases, hole concentration decreases, and the region near gate behaves progressively more like intrinsic semiconductor material (when excess hole concentration is zero) and then, finally, like a  $n$ -type material as electrons from  $n^+$  electrodes (source and drain) enter this region. As a result, when  $v_{GS}$  become larger than a threshold voltage,  $V_t$ , a narrow layer between source and drain regions is created that is populated with  $n$ -type charges (see figure). The thickness of this channel is controlled by the applied  $v_{GS}$  (it is proportional to  $v_{GS} - V_t$ ).


As can be seen, this device works as a channel is induced in the semiconductor and this channel contains  $n$ -type charges (thus,  $n$ -channel MOSFET). In addition, increasing  $v_{GS}$  increases channel width (enhances it). Therefore, this is an  $n$ -channel Enhancement-type MOSFET or Enhancement-type NMOS.

Now for a given values of  $v_{GS} > V_t$  (so that the channel is formed), let's apply a small and positive voltage  $v_{DS}$  between drain and source. Then, electrons from  $n^+$  source region enter the channel and reach the drain. If  $v_{DS}$  is increased, current  $i_D$  flowing through the channel increases. Effectively, the device acts like a resistor; its resistance is set by the dimension of the channel and its  $n$ -type charge concentration. In this mode, plot of  $i_D$  versus  $v_{DS}$  is a straight line (for a given values of  $v_{GS} > V_t$ ) as is shown.

 


The slope of  $i_D$  versus  $v_{DS}$  line is the conductance of the channel. For  $v_{GS} \leq V_t$  no channel exists (zero conductance). As value of  $v_{GS} - V_t$  increases, channel becomes wider and its conductivity increases (because its  $n$ -type charge concentration increases). Therefore, the channel conductance (slope of  $i_D$  versus  $v_{DS}$  line) increases with any increase in  $v_{GS} - V_t$  as is shown above.


The above description is correct for small values of  $v_{DS}$  as in that case,  $v_{GD} = v_{GS} - v_{DS} \approx v_{GS}$  and the induced channel is fairly uniform (*i.e.*, has the same width near the drain as it has near the source). For a given  $v_{GS} > V_t$ , if we now increase  $v_{DS}$ ,  $v_{GD} = v_{GS} - v_{DS}$  becomes smaller than  $v_{GS}$ . As such the size of channel near drain becomes smaller compared to its size near the source, as is shown. As the size of channel become smaller, its resistance increases and the curve of  $i_D$  versus  $v_{DS}$  starts to roll over, as is shown below.

 

For values of  $v_{GD} = V_t$  (or  $v_{DS} = v_{GS} - V_t$ ), width of the channel approaches zero near the drain (channel is “pinched” off). Increasing  $v_{DS}$  beyond this value has only a small effect on the channel length, and the current through the channel remains “relatively” constant at the value reached when  $v_{DS} = v_{GS} - V_t$ . So when the channel is pinched off.  $i_D$  only depends on  $v_{GS}$  (approximately). In reality,  $i_D$  increases slightly when  $v_{DS}$  is increased. This effect is called “channel-width modulation” and is similar to Early effect in BJTs

 

NMOS Characteristic Curves

 


$i_D$  versus  $v_{GS}$  in the saturation (or active) mode

In sum, a MOSFET can operate in three modes:

 - 1) Cut-off mode in which no channel exists ( $v_{GS} < V_t$  for NMOS) and  $i_D = 0$  for any  $v_{DS}$ .
- 2) Triode or Ohmic mode in which the channel is formed and not pinched off ( $v_{GS} > V_t$  and  $v_{DS} \leq v_{GS} - V_t$  for NMOS).
- 3) Saturation or Active mode in which the channel is pinched off ( $v_{GS} \geq V_t$  and  $v_{DS} > v_{GS} - V_t$  for NMOS) and  $i_D$  changes little with  $v_{DS}$ .


As can be seen from NMOS physical structure, the device is symmetric, that is position of drain and source can be replaced without any change in device properties. The circuit symbol for a NMOS is shown on the right. For most applications, however, the body is connected to the source, leading to a 3-terminal element. In that case, source and drain are not interchangeable. A simplified circuit symbol for this configuration is usually used. By convention, current  $i_D$  flows into the drain for a NMOS (see figure). As  $i_G = 0$ , the same current will flow out of the source.



Direction of “arrows” used to identify semiconductor types in a transistor may appear confusing. The arrows do NOT represent the direction of current flow in the device. Rather, they denote the type of the underlying  $pn$  junction: arrow pointing inward for  $p$ -type, arrow pointing outward for  $n$ -type. For a NMOS, the arrow is placed on the body and pointing inward as the body is made of  $p$ -type material. (Arrow is not on source or drain as they are interchangeable.) In the simplified symbol for the case when body and source is connected, arrow is on the source (device is not symmetric now) and is pointing outward as the source is made of  $n$ -type materials. .
 
### 3.5 NMOS Large Signal Model

Like BJT, a NMOS (with the source connected to the body) has six circuit parameters (three voltages and three currents), two of which ( $i_S$  and  $v_{GD}$ ) can be found in terms of the other four by KVL and KCL. MOS is simpler than BJT because  $i_G = 0$  (and  $i_S = i_D$ ). Therefore, NMOS has one characteristics equation relating  $i_D$  to  $v_{GS}$  and  $v_{DS}$ .



<b>Cut-off:</b>	$v_{GS} < V_{tn},$	$i_D = 0$
<b>Triode:</b>	$v_{GS} > V_{tn}, v_{DS} \leq v_{GS} - V_{tn}$	$i_D = \frac{1}{2} k'_n \frac{W}{L} [2v_{DS}(v_{GS} - V_{tn}) - v_{DS}^2]$
<b>Saturation:</b>	$v_{GS} > V_{tn}, v_{DS} \geq v_{GS} - V_{tn}$	$i_D = \frac{1}{2} k'_n \frac{W}{L} (v_{GS} - V_{tn})^2 (1 + \lambda v_{DS})$

Where  $V_{tn}$  is the threshold voltage (subscript  $n$  is introduced to differentiate this from that of a PMOS).  $k'_n = \mu_n C_{ox}$  where  $\mu_n$  is the mobility of electrons in the n-type material and  $C_{ox}$  is the gate capacitance per unit area (typically in F/m<sup>2</sup>).  $W$  and  $L$  are width and length of the channel, respectively. Parameter  $\lambda$  is the channel-length modulation coefficient. Manufacturers sometime quote the parameter  $V_A = 1/\lambda$  (using  $V_A$  notation, the channel-length modulation correction formula,  $1 + v_{DS}/V_A$ , becomes similar to that of the Early effect in BJTs). Note that  $V_A$  is much larger than the threshold voltage.



As the factor  $(1/2)\mu_n C_{ox}(W/L)$  occurs in both formulas, in some text books this quantity is denoted by  $K_n = (1/2)\mu_n C_{ox}(W/L)$ . Unfortunately, in some text book,  $k_n = \mu_n C_{ox}(W/L)$  is introduced (Note  $K_n = 0.5k_n!$ ). To avoid confusion while minimizing notation, we follow Sedra and Smith notation here and have defined  $k'_n = \mu_n C_{ox}$

As mentioned above, for small values of  $v_{DS}$  ( $v_{DS} \ll v_{GS} - V_{tn}$ ), NMOS behaves as resistor,  $r_{DS}$ , and the value of  $r_{DS}$  is controlled by  $v_{GS} - V_{tn}$ . This can be seen by dropping  $v_{DS}^2$  in  $i_D$  equation of triode mode:

$$r_{DS} = \frac{v_{DS}}{i_D} \approx \frac{1}{k'_n (W/L) (v_{GS} - V_{tn})}$$
  
## $p$ -Channel Enhancement-Type MOSFET (PMOS)

The physical structure of a PMOS is identical to a NMOS except that the semiconductor types are interchanged, *i.e.*, body and gate are made of  $n$ -type material and source and drain are made of  $p$ -type material and a  $p$ -type channel is formed. As the sign of the charge carriers are reversed, all voltages and currents in a PMOS are reversed. By convention, the drain current is flowing out of the drain as is shown. With this, all of the NMOS discussion above applies to PMOS as long as we multiply all voltages by a minus sign:



**Cut-off:**  $v_{SG} < |V_{tp}|, \quad i_D = 0$

**Triode:**  $v_{SG} > |V_{tp}|, v_{SD} \leq v_{SG} - |V_{tp}| \quad i_D = \frac{1}{2} k'_p \frac{W}{L} [2v_{SD}(v_{SG} - |V_{tp}|) - v_{SD}^2]$

**Saturation:**  $v_{SG} > |V_{tp}|, v_{SD} \geq v_{SG} - |V_{tp}| \quad i_D = \frac{1}{2} k'_p \frac{W}{L} (v_{SG} - |V_{tp}|)^2 (1 + \lambda v_{SD})$

Note that  $V_{tp}$  is negative for a PMOS and  $k'_p = \mu_p C_{ox}$  where  $\mu_p$  is the mobility of holes.

Several important point should be noted:

- 1) No current flows into the gate,  $i_G = 0$  (note the insulator between gate and the body).
- 2) When MOSFET is in cut-off,  $i_D = 0$ . However,  $i_D = 0$ , does not mean that MOSFET is in cut-off. MOSFET is in cut-off only when no channel exists ( $v_{GS} < V_t$ ) and  $i_D = 0$  for any applied  $v_{DS}$ . However, MOSFET can be in triode mode, *i.e.*, a channel is formed, but  $i_D = 0$  because  $v_{DS} = 0$ .
- 3) The MOSFET saturation mode is called “saturation” because  $i_D$  is “saturated” (does not change with  $v_{DS}$  if we ignore channel length modulation effect). This mode is equivalent to the BJT active mode and not to the BJT saturation mode. As such, some of the modern books call this mode, active.
- 4) The  $i_D v_{DS}$  characteristic curves of a MOSFET look similar to  $i_C v_{CE}$  curves of a BJT. Both devices are in cut-off when the “input” voltage is below a threshold value:  $v_{BE} < V_{D0}$  for NPN BJT and  $v_{GS} < V_{tn}$  for NMOS. They exhibit an active mode in which the “output” current ( $i_C$  or  $i_D$ ) is proportional to the input voltage. There are, however, major differences. Most importantly, a BJT requires  $i_B$  to operate but in a MOSFET  $i_G = 0$  (actually very small). These differences become clearer as we explore MOSFETs.

### Recipe for solving NMOS & PMOS Circuits:

Solution method is very similar to BJT circuit. For a NMOS circuit :

- 1) Write down a KVL including GS terminals (call it GS-KVL) and a KVL including DS terminals (call it DS-KVL).
- 3) From GS-KVL, compute  $v_{GS}$  (using  $i_G = 0$ )
  - 3a) If  $v_{GS} < V_{tn}$ , NMOS is in cut-off. Let  $i_D = 0$ , solve for  $v_{DS}$  from DS-KVL. We are done.
  - 3b) If  $v_{GS} > V_{tn}$ , NMOS is not in cut-off. Go to step 4.
- 4) Assume NMOS is in saturation mode. Compute  $i_D$  for NMOS equation Then, use DS-KVL to compute  $v_{DS}$ . If  $v_{DS} > v_{GS} - V_{tn}$ , we are done. Otherwise go to step 5.
- 5) NMOS has to be in triode mode. Substitute for  $i_D$  from NMOS equation in DS-KVL to get a quadratic equation in  $v_{DS}$ . Find  $v_{DS}$  (one of the two roots would be unphysical). Check that  $v_{DS} < v_{GS} - V_{tn}$ . Substitute  $v_{DS}$  in DS-KVL to find  $i_D$ .

(For PMOS, replace  $v_{GS}$ ,  $v_{DS}$ , and  $V_{tn}$  with  $v_{SG}$ ,  $v_{SD}$ , and  $|V_{tp}|$  in the NMOS recipe.)

**Example:** Consider NMOS circuit below with  $k'_n(W/L) = 0.5 \text{ mA/V}^2$ ,  $V_{tn} = 2 \text{ V}$ , and  $\lambda = 0$ . Find  $v_o$  when  $v_i = 0, 6$ , and  $12 \text{ V}$  for  $R_D = 1 \text{ K}\Omega$  and  $V_{DD} = 12 \text{ V}$ .

GS-KVL:  $v_{GS} = v_i$

DS-KVL:  $V_{DD} = R_D i_D + v_{DS}$

A)  $v_i = 0 \text{ V}$ . From GS-KVL, we get  $v_{GS} = v_i = 0$ . As  $v_{GS} < V_{tn} = 2 \text{ V}$ , NMOS is in cut-off,  $i_D = 0$ , and  $v_{DS}$  is found from DS-KVL:

DS-KVL:  $v_o = v_{DS} = V_{DD} - R_D i_D = 12 \text{ V}$

B)  $v_i = 6 \text{ V}$ . From GS-KVL, we get  $v_{GS} = v_i = 6 \text{ V}$ . Since  $v_{GS} = 6 > V_{tn} = 2$ , NMOS is not in cut-off. Assume NMOS in saturation mode. Then:

$$i_D = 0.5k'_n(W/L)(v_{GS} - V_{tn})^2 = 0.25 \times 10^{-3}(6 - 2)^2 = 4 \text{ mA}$$

DS-KVL:  $v_{DS} = V_{DD} - R_D i_D = 12 - 4 \times 10^3 \times 10^{-3} = 8 \text{ V}$

Since  $v_{DS} = 8 > v_{GS} - V_{tn} = 4$ , NMOS is indeed in saturation mode and  $i_D = 4 \text{ mA}$  and  $v_o = v_{DS} = 8 \text{ V}$ .

C)  $v_i = 12 \text{ V}$ . From GS-KVL, we get  $v_{GS} = 12 \text{ V}$ . Since  $v_{GS} > V_{tn}$ , NMOS is not in cut-off. Assume NMOS in saturation mode. Then:

$$i_D = 0.5k'_n(W/L)(v_{GS} - V_{tn})^2 = 0.25 \times 10^{-3}(12 - 2)^2 = 25 \text{ mA}$$

DS-KVL:  $v_{DS} = V_{DD} - R_D i_D = 12 - 25 \times 10^3 \times 10^{-3} = -13 \text{ V}$

Since  $v_{DS} = -13 < v_{GS} - V_{tn} = 12 - 2 = 10$ , NMOS is NOT in saturation mode.


Assume NMOS in triode mode. Then:

$$i_D = 0.5k'_n(W/L)[2v_{DS}(v_{GS} - V_{tn}) - v_{DS}^2] = 0.25 \times 10^{-3}[2v_{DS}(12 - 2) - v_{DS}^2]$$

$$i_D = 0.25 \times 10^{-3}[20v_{DS} - v_{DS}^2]$$

Substituting for  $i_D$  in DS-KVL, we get:

 DS-KVL:  $V_{DD} = R_D i_D + v_{DS} \rightarrow 12 = 10^3 \times 0.25 \times 10^{-3}[20v_{DS} - v_{DS}^2] + v_{DS}$   
 $v_{DS}^2 - 24v_{DS} + 48 = 0$




This is a quadratic equation in  $v_{DS}$ . The two roots are:  $v_{DS} = 2.2$  V and  $v_{DS} = 21.8$  V. The second root is not physical as the circuit is powered by a 12 V supply. Therefore,  $v_{DS} = 2.2$  V. As  $v_{DS} = 2.2 < v_{GS} - V_{tn} = 10$ , NMOS is indeed in triode mode with  $v_o = v_{DS} = 2.2$  V and

$$\text{DS-KVL: } v_{DS} = V_{DD} - R_D i_D \quad \rightarrow \quad i_D = \frac{12 - 2.2}{1,000} = 9.8 \text{ mA}$$

**Load Line:** Operation of NMOS circuits can be better understood using the concept of load line. Similar to BJT, load line is basically the line representing DS-KVL in  $i_D$  versus  $v_{DS}$  space. Load line of the example circuit is shown here.

 **Exercise:** Mark the  $Q$ -points of the previous example for  $v_i = 0, 6,$  and  $12$  V on the load line figure below.




## Body Effect

In deriving NMOS (and other MOS)  $i_D$  versus  $v_{DS}$  characteristics, we had assumed that the body and source are connected. This is not possible in an integrated chip which has a common body and a large number of MOS devices (connection of body to source for all devices means that all sources are connected). The common practice is to attach the body of the chip to the smallest voltage available from the power supply (zero or negative). In this case, the  $pn$  junction between the body and source of all devices will be reverse biased. The impact of this is to lower threshold voltage for the MOS devices slightly and it's called the body effect. Body effect can degrade device performance. For analysis here, we will assume that body effect is negligible.


### 3.6 MOSFET Inverters and Switches
 
#### NMOS Inverters and Switches

The basic NMOS inverter circuit is shown; the circuit is very similar to a BJT inverter. This circuit was solved in page 3-24 for  $V_{DD} = 12$  and  $R_D = 1 \text{ k}\Omega$ . We found that if  $v_i = 0$  (in fact  $v_i < V_{tn}$ ), NMOS will be in cut-off with  $i_D = 0$  and  $v_o = V_{DD}$ . When  $v_i = 12 \text{ V}$ , NMOS will be in triode mode with  $i_D = 10 \text{ mA}$  and  $v_{DS} = 2.2 \text{ V}$ . Therefore, the circuit is an inverter gate. It can also be used as switch.



There are some important difference between NMOS and BJT inverter gates. First, BJT needs a resistor  $R_B$ . This resistor “converts” the input voltage into an  $i_B$  and keep  $v_{BE} \approx V_{D0}$ . NMOS does not need a resistor between the source and the input voltage as  $i_G = 0$  and  $v_i = v_{GS}$  can be directly applied to the gate. Second, if the input voltage is “high,” the BJT will go into saturation with  $v_o = v_{CE} = V_{sat} = 0.2 \text{ V}$ . In the NMOS gate, if the input voltage is “high,” NMOS is in the triode mode. In this case,  $v_{DS}$  can


 


have any value between 0 and  $v_{GS} - V_i$ ; the value of  $v_o = v_{DS}$  is set by the value of the resistor  $R_D$ . This effect is shown in the figure.

**Exercise:** Compute  $v_o$  for the above circuit with  $V_{DD} = 12$  and  $R_D = 10 \text{ k}\Omega$  when  $v_i = 12 \text{ V}$ .
  
#### Complementary MOS (CMOS)

Complementary MOS technology employs MOS transistors of both polarities as is shown below. CMOS devices are more difficult to fabricate than NMOS, but many more powerful circuits are possible with CMOS configuration. As such, most of MOS circuits today employ CMOS configuration and CMOS technology is rapidly taking over many applications that were possible only with bipolar devices a few years ago.



## CMOS Inverter

The CMOS inverter, the building block of CMOS logic gates, is shown below. The “low” and “high” states for this circuit correspond to 0 and  $V_{DD}$ , respectively. CMOS gates are built on the same chip such that both NMOS and PMOS have the same threshold voltage  $V_{tn} = \bar{V}_t$ ,  $V_{tp} = -\bar{V}_t$  ( $|V_{tp}| = \bar{V}_t$ ). This circuit works only if  $V_{DD} > 2\bar{V}_t$  by a comfortable margin.

$$1) \text{ by KVL } v_{GS1} = v_i, v_{SG2} = V_{DD} - v_i, v_o = v_{DS1} = V_{DD} - v_{SD2},$$

$$2) \text{ by KCL } i_{D1} = i_{D2}$$

$v_i = 0$  Since  $v_{GS1} = v_i = 0 < \bar{V}_t$ , NMOS will be in cut-off. Therefore,  $i_{D1} = 0$ . Since  $v_{SG2} = V_{DD} - v_i = V_{DD} > \bar{V}_t$ , PMOS will be ON while  $i_{D2} = i_{D1} = 0$ .

$$\begin{aligned} v_{GS1} = v_i = 0 < \bar{V}_t & \rightarrow \text{Q1 is OFF} \rightarrow i_{D1} = 0 \\ v_{GS2} = V_{DD} - v_i = V_{DD} > \bar{V}_t & \rightarrow \text{Q2 is ON} \end{aligned}$$

Since PMOS is ON, a channel is formed between its source and drain. In this case,  $i_{D2} = 0$  only if  $v_{SD2} = 0$  and PMOS is in triode mode and acts as resistor. (Recall  $i_D$  versus  $v_{DS}$  characteristic curves of a MOSFET, each labeled with a values of  $V_{GS} > \bar{V}_t$ . This lines cross  $i_D = 0$ ,  $v_{DS} = 0$  point when MOSFET is in triode region.)

$$\begin{aligned} v_{GS1} = v_i = 0 < \bar{V}_t & \rightarrow \text{Q1 is OFF} \rightarrow i_{D1} = 0 \\ v_{GS2} = V_{DD} - v_i = V_{DD} > \bar{V}_t & \rightarrow \text{Q2 is ON} \quad i_{D2} = 0 \rightarrow v_{SD2} = 0 \end{aligned}$$

Output voltage can now be found by KVL:  $v_o = V_{DD} - v_{SD2} = V_{DD}$ . So, when  $v_i = 0$ ,  $v_o = V_{DD}$ .

$v_i = V_{DD}$  Since  $v_{GS1} = v_i = V_{DD} > \bar{V}_t$ , NMOS will be ON. Since  $v_{SG2} = V_{DD} - v_i = 0 < \bar{V}_t$ , PMOS will be in cut-off and  $i_{D2} = 0$ .

$$\begin{aligned} v_{GS1} = v_i = V_{DD} > \bar{V}_t & \rightarrow \text{Q1 is ON} \\ v_{GS2} = v_i - V_{DD} = 0 < \bar{V}_t & \rightarrow \text{Q2 is ON} \rightarrow i_{D2} = 0 \end{aligned}$$


Since  $i_{D1} = i_{D2} = 0$  and NMOS is ON, NMOS should be in triode mode with  $v_{DS1} = 0$ .

$$\begin{aligned} v_{GS1} = v_i = V_{DD} > \bar{V}_t & \rightarrow \text{Q1 is ON} \quad i_{D1} = 0 \rightarrow v_{SD1} = 0 \\ v_{GS2} = v_i - V_{DD} = 0 < \bar{V}_t & \rightarrow \text{Q2 is ON} \rightarrow i_{D2} = 0 \end{aligned}$$

Then  $v_o = v_{DS1} = 0$ . So, when  $v_i = V_{DD}$ ,  $v_o = 0$

In sum, when  $v_i = 0$ ,  $v_o = V_{DD}$  and when  $v_i = V_{DD}$ ,  $v_o = 0$ . Therefore, this is an inverter (or a NOT gate). The transfer function of the CMOS inverter is shown below.

CMOS inverter has many advantages compared to the NMOS (or BJT) inverter. The “low” and high” states are clearly defined (low state of NMOS depended on the value of  $R_D$ ). It does not include any resistors and thus takes less area on the chip. Lastly,  $i_{D1} = i_{D2} = 0$  for both cases of output being low or high. This means that the gate consumes very little power (theoretically zero) in either state. A non-zero  $i_{D1} = i_{D2}$ , however, flows in the circuit when the gate is transitioning from one state to another as is seen in the figure.

 

If the transistors have the same  $k'_n(W/L)_n = k'_p(W/L)_p$ , the CMOS will have a “symmetric” transfer function, *i.e.*,  $v_o = 0.5V_{DD}$  when  $v_i = 0.5V_{DD}$  as is shown below. For  $v_i = 0.5V_{DD}$ ,  $v_{GS1} = v_i = 0.5V_{DD}$  and  $v_{SG2} = V_{DD} - v_i = 0.5V_{DD}$ . Since,  $v_{GS1} = v_{SG2} > \bar{V}_t$ , both transistors will be ON. Furthermore, as transistors have same threshold voltage, same  $k'(W/L)$ ,  $i_{D1} = i_{D2}$ , and  $v_{GS1} = v_{SG2}$ , both transistor will be in the same state (either triode or saturation) and will have identical  $v_{DS}$ :  $v_{DS1} = v_{SD2}$ . Since  $v_{DS1} - v_{SD2} = V_{DD}$ , then  $v_{DS1} = 0.5V_{DD}$ ,  $v_{SD2} = -0.5V_{DD}$ , and  $v_o = 0.5V_{DD}$ . Note that since  $V_{DD} > 2V_t$ , both transistors are in the saturation mode. In this case, the maximum value of  $i_D$  that flows through the gate occurs when  $v_i = 0.5V_{DD}$  and  $v_o = 0.5V_{DD}$ .

For example, consider the CMOS inverter with  $V_{DD} = 12$  V,  $\bar{V}_t = 2$  V, and  $k'_n(W/L)_n = k'_p(W/L)_p = 0.5$  mA/V<sup>2</sup>. Maximum  $i_D$  flows when  $v_i = v_{GS1} = 0.5V_{DD} = 6$  V. At this point,  $v_{DS1} = v_o = 0.5V_{DD} = 6$  V. As,  $v_{DS1} = 6 > v_{GS1} - V_t = 4$  V, NMOS is in saturation mode. Then:

$$i_{D1} = 0.5k'_n(W/L)_n(v_{GS1} - V_{tn})^2 = 0.25 \times 10^{-3}(6 - 2)^2 = 4 \text{ mA}$$

## CMOS NAND Gate

As mentioned before CMOS logic gates have “low” and “high” states of 0 and  $V_{DD}$ , respectively. We need to consider all possible cases to show that this a NAND gate. To start, we can several general observations:

1) by KVL  $v_{GS1} = v_1$ ,  $v_{GS2} = v_2 - v_{DS1}$ ,  $v_{SG3} = V_{DD} - v_1$ , and  $v_{SG4} = V_{DD} - v_2$ ,

2) by KCL  $i_{D1} = i_{D2} = i_{D3} + i_{D4}$

3) by KVL  $v_o = v_{DS1} + v_{DS2} = V_{DD} - v_{SD3}$  and  $v_{SD3} = v_{SD4}$ .

The procedure to solve/analyze CMOS gates are as follows:

A) For a given set of input voltages, use KVLs (1 above) to find  $v_{GS}$  of all transistors and find which ones are ON or OFF.

B) Set  $i_D = 0$  for all transistors that are OFF. Use KCLs to find  $i_D$  for other transistors.

C) Look for transistors that are ON and have  $i_D = 0$ . These transistors have to be in triode mode with  $v_{DS} = 0$ .

D) Use KVLs (3 above) to find  $v_o$  based on  $v_{DS}$ .

$v_1 = 0, v_2 = 0$  We first find  $v_{GS}$  and state of all transistors by using KVLs in no. 1 above.


$$\begin{aligned} v_{GS1} = v_1 = 0 < \bar{V}_t & \rightarrow \text{Q1 is OFF} \rightarrow i_{D1} = 0 \\ v_{GS2} = v_2 - v_{DS1} = -v_{DS1} & \rightarrow \text{Q2 is ?} \\ v_{SG3} = V_{DD} - v_1 = V_{DD} > \bar{V}_t & \rightarrow \text{Q3 is ON} \\ v_{SG4} = V_{DD} - v_2 = -V_{DD} > \bar{V}_t & \rightarrow \text{Q4 is ON} \end{aligned}$$

Since  $i_{D1} = 0$ , by KCLs in no. 2 above,  $i_{D2} = i_{D1} = 0$  and  $i_{D3} + i_{D4} = i_{D1} = 0$ . Since  $i_D \geq 0$  for both PMOS and NMOS, the last equation can be only satisfied if  $i_{D3} = i_{D4} = 0$ . We add the value of  $i_D$  to the table above and look for transistors that are ON and have  $i_D = 0$ . These transistors (Q3 and Q4) have to be in triode mode with  $v_{SD3} = v_{SD4} = 0$ .

$$\begin{aligned} v_{GS1} = v_1 = 0 < \bar{V}_t & \rightarrow \text{Q1 is OFF} \rightarrow i_{D1} = 0 \\ v_{GS2} = v_2 - v_{DS1} = -v_{DS1} & \rightarrow \text{Q2 is ?} \quad i_{D2} = 0 \\ v_{SG3} = V_{DD} - v_1 = V_{DD} > \bar{V}_t & \rightarrow \text{Q3 is ON} \quad i_{D3} = 0 \rightarrow v_{SD3} = 0 \\ v_{SG4} = V_{DD} - v_2 = -V_{DD} > \bar{V}_t & \rightarrow \text{Q4 is ON} \quad i_{D4} = 0 \rightarrow v_{SD4} = 0 \end{aligned}$$

Finally, from KVLs in no. 3. above, we have  $v_o = V_{DD} - v_{SD3} = V_{DD}$ . So, when both inputs are low, the output is HIGH.

 If needed, we can go back and find the state of Q2. Assume Q2 is ON. This requires  $v_{GS2} > \bar{V}_t$ . Since  $i_{D2} = 0$  and Q2 is ON,  $v_{DS2} = 0$  (Q2 in triode). From KVLs in no. 3.



above, we have  $v_o = v_{DS1} + v_{DS2} = V_{DD}$ . This gives  $v_{DS1} = V_{DD}$  and  $v_{GS2} = v_2 - v_{DS1} = 0 - V_{DD} = -V_{DD} < \bar{V}_t$ , a contradiction of Q2 being ON. Therefore, Q2 should be OFF.

$$\underline{v_1 = 0, v_2 = V_{DD}}$$

$$\begin{aligned} v_{GS1} = v_1 = 0 < \bar{V}_t & \rightarrow \text{Q1 is OFF} \rightarrow i_{D1} = 0 \\ v_{GS2} = v_2 - v_{DS1} = V_{DD} - v_{DS1} & \rightarrow \text{Q2 is ?} \\ v_{SG3} = V_{DD} - v_1 = V_{DD} > \bar{V}_t & \rightarrow \text{Q3 is ON} \\ v_{SG4} = V_{DD} - v_2 = 0 < \bar{V}_t & \rightarrow \text{Q4 is OFF} \rightarrow i_{D4} = 0 \end{aligned}$$

Since  $i_{D1} = 0$ , by KCLs in no. 2 above,  $i_{D2} = i_{D1} = 0$ . Also,  $i_{D3} + i_{D4} = i_{D1} = 0$  leading to  $i_{D3} = 0$ . We add the value of  $i_D$  to the table above and look for transistors that are ON and have  $i_D = 0$ . This transistor (Q3) have to be in triode mode with  $v_{SD3} = 0$ .

$$\begin{aligned} v_{GS1} = v_1 = 0 < \bar{V}_t & \rightarrow \text{Q1 is OFF} \rightarrow i_{D1} = 0 \\ v_{GS2} = v_2 - v_{DS1} = V_{DD} - v_{DS1} & \rightarrow \text{Q2 is ?} \quad i_{D2} = 0 \\ v_{SG3} = V_{DD} - v_1 = V_{DD} > \bar{V}_t & \rightarrow \text{Q3 is ON} \quad i_{D3} = 0 \rightarrow v_{SD3} = 0 \\ v_{SG4} = V_{DD} - v_2 = 0 < \bar{V}_t & \rightarrow \text{Q4 is OFF} \rightarrow i_{D4} = 0 \end{aligned}$$

Finally,  $v_o = V_{DD} - v_{SD3} = V_{DD}$ . So, when  $v_1$  is LOW and  $v_2$  is HIGH, the output is HIGH.

We can go back and find the state of Q2. We will find Q2 to be OFF (left as an exercise).

$$\underline{v_1 = V_{DD}, v_2 = 0}$$

$$\begin{aligned} v_{GS1} = v_1 = V_{DD} > \bar{V}_t & \rightarrow \text{Q1 is ON} \\ v_{GS2} = v_2 - v_{DS1} = -v_{DS1} < \bar{V}_t & \rightarrow \text{Q2 is OFF} \rightarrow i_{D2} = 0 \\ v_{SG3} = V_{DD} - v_1 = 0 < \bar{V}_t & \rightarrow \text{Q3 is OFF} \rightarrow i_{D3} = 0 \\ v_{SG4} = V_{DD} - v_2 = V_{DD} > \bar{V}_t & \rightarrow \text{Q4 is ON} \end{aligned}$$

In the above, we used the fact that  $v_{DS1} \geq 0$ . Since  $i_{D2} = 0$ , by KCLs,  $i_{D1} = i_{D2} = 0$ . Also,  $i_{D3} + i_{D4} = i_{D2} = 0$  leading to  $i_{D4} = 0$ . We add the value of  $i_D$  to the table above and look for transistors that are ON and have  $i_D = 0$ . These transistors (Q1 and Q4) have to be in triode mode with  $v_{DS1} = v_{SD4} = 0$ .

$$\begin{aligned} v_{GS1} = v_1 = V_{DD} > \bar{V}_t & \rightarrow \text{Q1 is ON} \quad i_{D1} = 0 \rightarrow v_{DS1} = 0 \\ v_{GS2} = v_2 - v_{DS1} = -v_{DS1} < \bar{V}_t & \rightarrow \text{Q2 is OFF} \rightarrow i_{D2} = 0 \\ v_{SG3} = V_{DD} - v_1 = 0 < \bar{V}_t & \rightarrow \text{Q3 is OFF} \rightarrow i_{D3} = 0 \\ v_{SG4} = V_{DD} - v_2 = V_{DD} > \bar{V}_t & \rightarrow \text{Q4 is ON} \quad i_{D4} = 0 \rightarrow v_{SD4} = 0 \end{aligned}$$

Finally,  $v_o = V_{DD} - v_{SD4} = V_{DD}$ . So, when  $v_1$  is HIGH and  $v_2$  is LOW, the output is HIGH.

$$\underline{v_1 = V_{DD}, v_2 = V_{DD}}$$

$$\begin{aligned} v_{GS1} = v_1 = V_{DD} > \bar{V}_t &\rightarrow \text{Q1 is ON} \\ v_{GS2} = v_2 - v_{DS1} = V_{DD} - v_{DS1} &\rightarrow \text{Q2 is ?} \\ v_{SG3} = V_{DD} - v_1 = 0 < \bar{V}_t &\rightarrow \text{Q3 is OFF} \rightarrow i_{D3} = 0 \\ v_{SG4} = V_{DD} - v_2 = 0 < \bar{V}_t &\rightarrow \text{Q4 is OFF} \rightarrow i_{D4} = 0 \end{aligned}$$

From KCLs in no. 2 above,  $i_{D2} = i_{D1} = i_{D3} + i_{D4} = 0$ . We add the value of  $i_D$  to the table above and look for transistors that are ON and have  $i_D = 0$ . These transistors (Q1 and Q2) have to be in triode mode with  $v_{DS1} = v_{DS2} = 0$ .

$$\begin{aligned} v_{GS1} = v_1 = V_{DD} > \bar{V}_t &\rightarrow \text{Q1 is ON} & i_{D1} = 0 &\rightarrow v_{DS1} = 0 \\ v_{GS2} = v_2 - v_{DS1} = V_{DD} - v_{DS1} = V_{DD} > \bar{V}_t &\rightarrow \text{Q2 is ON} & i_{D2} = 0 &\rightarrow v_{DS2} = 0 \\ v_{SG3} = V_{DD} - v_1 = 0 < \bar{V}_t &\rightarrow \text{Q3 is OFF} & i_{D3} = 0 & \\ v_{SG4} = V_{DD} - v_2 = 0 < \bar{V}_t &\rightarrow \text{Q4 is OFF} & i_{D4} = 0 & \end{aligned}$$


In the above, we used  $v_{DS1} = 0$  to find the state of Q2 leading to  $v_{DS2} = 0$ .

Finally,  $v_o = v_{DS1} + v_{DS2} = 0$ . So, when  $v_1$  is HIGH and  $v_2$  is HIGH, the output is LOW.

From the “truth table,” the output of this gate is LOW only if both input states are HIGH. Therefore, this is a NAND gate.

## CMOS NOR Gate

 
**Exercise:** Show that this is a NOR gate.




### 3.7 Exercise Problems

**Problems 1 to 6.** In circuits below find  $v_{BE}$ ,  $i_C$ ,  $v_{CE}$ , and state of the transistor (Si BJTs with  $\beta = 100$ ).


**Problem 7.** Find  $I$  (Si BJTs with  $\beta = 100$ ).

 


Problem 1

 


Problem 2

 


Problem 3

 


Problem 4

 

Problem 5

 


Problem 6

 


Problem 7

**Problem 8.** This configuration is called a Darlington Pair. Show that A) If Q1 is OFF, Q2 will be OFF, if Q1 is ON Q2 will ON, B) Show that if both BJTs are in active mode, the transistor pair act like one BJT in saturation with  $\beta = i_{C2}/i_{B1} = \beta_1\beta_2$ .


**Problems 9 and 10.** Find  $i_B$ ,  $v_{BE}$ ,  $i_C$ ,  $v_{CE}$ , and state of both transistors (Si BJTs with  $\beta = 100$ ).

 

Problem 8

 

Problem 9

 

Problem 10


**Problem 11.** Find  $i_B$ ,  $v_{BE}$ ,  $i_C$ ,  $v_{CE}$ , and state of both transistors for A)  $v_i = 1$  V, B)  $v_i = 3$  V, C)  $v_i = 5$  V. Si BJTs with  $\beta_1 = 100$  and  $\beta_2 = 50$ .

**Problem 12.** The diode in the circuit is a light-emitting diode (LED). It is made of GaAs and has a  $V_{D0} = 1.7$  V. This is a switching circuit.  $v_i$  is the output of a logic gate which turns the diode on or off depending on the state of the logic gate. A) Show that for  $v_i = 0$ , LED will be OFF, B) Show that for  $v_i = 5$  V, LED will be ON, and C) Starting from  $v_i = 0$ , we slowly increase  $v_i$ . At what voltage LED starts to light up? (Si BJTs with  $\beta = 100$ .)

**Problem 13.** Design a switch circuit similar to problem 12 which turns an LED OFF and ON such that the LED is OFF for  $v_i < 2.5$  V and is ON for  $v_i > 2.5$  V. (Hint: See page 3-14 of lecture notes).

**Problem 14.** The circuit shown is a Resistor-Transistor Logic (RTL) NOR gate configured with two identical BJTs. Show that this is NOR gate with the LOW state of 0.2 V and the HIGH state of 5 V.

 
**Problem 15.** Prove that the circuit below is a NAND Gate. Assume that low state is 0.4 V and high state is 1.2 V. Use  $\beta = 200$ .




**Problems 16 to 22.** In circuits below find  $v_{GS}$ ,  $i_D$ ,  $v_{DS}$ , and state of the transistor (Use  $k'_n(W/L)_n = k'_p(W/L)_p = 0.4$  mA/V<sup>2</sup>,  $\lambda = 0$ ,  $V_{tn} = 3$  V and  $V_{tp} = -3$  V).




**Problem 23.** Find  $v_o$  when  $v_i = 0$  and  $12\text{ V}$  (Use  $k'_n(W/L)_n = 0.5\text{ mA/V}^2, \lambda = 0, V_{tn} = 2\text{ V}$ ).

 


Problem 20

 

Problem 21

 

Problem 22

 


Problem 23


**Problem 24.** Show that this circuit is a NOR gate with a LOW state of  $0.2\text{ V}$  and a HIGH state of  $12\text{ V}$  (Use  $k'_n(W/L)_n = 0.5\text{ mA/V}^2, V_{tn} = 1\text{ V}$ ).

**Problem 25.** Show that this is a three-input NOR gate.


**Problem 26.** Show that this is a three-input NAND gate.

 

Problem 24

 

Problem 25

 

Problem 26


### 3.8 Solution to Selected Exercise Problems

**Problem 1.** In circuit below find  $v_{BE}$ ,  $i_C$ ,  $v_{CE}$ , and state of the transistor (Si BJTs with  $\beta = 100$ ).

This is a NPN transistor with  $i_C = 2 \text{ mA}$  and  $i_E = 2.5 \text{ mA}$ .

$$i_B = i_E - i_C = 0.5 \text{ mA} > 0 \rightarrow \text{BJT is ON} \rightarrow v_{BE} = 0.7 \text{ V}$$

$$\frac{i_C}{i_B} = \frac{2}{0.5} = 4 < 100 = \beta \rightarrow \text{BJT is in saturation} \rightarrow v_{CE} = 0.2 \text{ V}$$

 

**Problem 2.** In circuit below find  $v_{EB}$ ,  $i_C$ ,  $v_{EC}$ , and state of the transistor (Si BJTs with  $\beta = 100$ ).


This is a PNP transistor with  $i_B = 20 \mu\text{A}$  and  $v_{CB} = -4 \text{ V}$ .

Since  $i_B > 0$ , EB is ON and  $v_{EB} = 0.7 \text{ V}$ .

Since  $v_{CB} = -4 < V_{D0} = 0.7 \text{ V}$ , CB is reverse biased and this transistor is in active mode:

$$v_{EC} = v_{EB} + v_{BC} = 0.7 + 4 = 4.7 \text{ V}$$

$$i_C = \beta i_B = 2 \text{ mA}$$

 


**Problem 3.** In circuit below find  $v_{BE}$ ,  $i_C$ ,  $v_{CE}$ , and state of the transistor (Si BJTs with  $\beta = 100$ ).

This is a NPN transistor with  $i_B = 100 \mu\text{A}$  and  $v_{CE} = 5 \text{ V}$ .

$$i_B = 100 \mu\text{A} > 0 \rightarrow \text{BJT is ON} \rightarrow v_{BE} = 0.7 \text{ V}$$

$$v_{CE} = 5 \text{ V} > V_{D0} = 0.7 \text{ V} \rightarrow \text{BJT is in active} \rightarrow i_C = \beta i_B = 10 \text{ mA}$$

 


**Problem 4.** In circuit below find  $v_{EB}$ ,  $i_C$ ,  $v_{EC}$ , and state of the transistor (Si BJTs with  $\beta = 100$ ).

This is a PNP transistor with  $v_{EB} = -1 \text{ V}$  and  $v_{CB} = -4 \text{ V}$ .

$$v_{EB} = -1 \text{ V} < 0.7 = V_{D0} \rightarrow \text{BJT is in cut-off} \rightarrow i_B = 0 \quad \& \quad i_C = 0$$

$$v_{EC} = v_{EB} + v_{BC} = -1 + 4 = 3 \text{ V}$$

 

**Problem 5.** In circuit below find  $v_{BE}$ ,  $i_C$ ,  $v_{CE}$ , and state of the transistor (Si BJTs with  $\beta = 100$ ).

$$\text{BE-KVL: } 15 = 10^6 i_B + v_{BE}$$

$$\text{CE-KVL: } 15 = 4.7 \times 10^3 i_C + v_{CE}$$

Assume BJT is ON,  $v_{BE} = 0.7 \text{ V}$ ,  $i_B > 0$ . BE-KVL gives:


$$\text{BE-KVL: } 15 = 10^6 i_B + 0.7 \rightarrow i_B = 14.3 \mu\text{A}$$

Since  $i_B > 0$ , our assumption of BJT is ON is justified.

Assume BJT is in active:  $i_C = \beta i_B = 100 i_B = 1.43 \text{ mA}$  and  $v_{CE} > 0.7 \text{ V}$ . CE-KVL gives:

$$\text{CE-KVL: } 15 = 4.7 \times 10^3 \times 1.43 \times 10^{-3} + v_{CE} \rightarrow v_{CE} = 8.28 \text{ V}$$

Since  $v_{CE} = 8.28 > 0.7 \text{ V}$  our assumption of BJT in active is justified with  $i_B = 14.3 \mu\text{A}$ ,  $i_C = 1.43 \text{ mA}$ , and  $v_{CE} = 8.28 \text{ V}$ .

 

**Problem 6.** In circuit below find  $v_{EB}$ ,  $i_C$ ,  $v_{EC}$ , and state of the transistor (Si BJTs with  $\beta = 100$ ).

$$\text{BE-KVL: } 15 = v_{EB} + 220 \times 10^3 i_B$$

$$\text{CE-KVL: } 15 = v_{EC} + 3.9 \times 10^3 i_C$$

Assume BJT (PNP) is ON,  $v_{EB} = 0.7 \text{ V}$ ,  $i_B > 0$ . BE-KVL gives:

$$\text{BE-KVL: } 15 = 0.7 + 220 \times 10^3 i_B \rightarrow i_B = 65 \mu\text{A}$$

Since  $i_B > 0$ , our assumption of BJT ON is justified.

Assume BJT is in active:  $i_C = \beta i_B = 100 i_B = 6.5 \text{ mA}$  and  $v_{EC} > 0.7 \text{ V}$ . CE-KVL gives:


$$\text{CE-KVL: } 15 = v_{EC} + 3.9 \times 10^3 \times 6.5 \times 10^{-3} \rightarrow v_{EC} = -10.4 \text{ V}$$

Since  $v_{EC} = -10.4 < 0.7 \text{ V}$  our assumption of BJT in active is NOT justified.

Assume BJT in saturation,  $v_{EC} = 0.2 \text{ V}$ , and  $i_C < \beta i_B$ . CE-KVL gives:

$$15 = 0.2 + 3.9 \times 10^3 i_C \rightarrow i_C = 3.79 \text{ mA}$$


Since  $i_C/i_B = 3.79/0.065 = 58 < 100 = \beta$ , our assumption of BJT in saturation is justified with  $i_B = 65 \mu\text{A}$ ,  $i_C = 3.79 \text{ mA}$ , and  $v_{EC} = 0.2 \text{ V}$ .

 

 **Problem 7.** Find  $I$  (Si BJTs with  $\beta = 100$ ).

$$\text{BE-KVL: } 15 = 10^3 i_E - v_{BE}$$

$$\text{CE-KVL: } 15 = 10^3 i_E - v_{CE} + 10^3 i_C - 15$$



Assume BJT (NPN) is OFF,  $i_B = i_C = i_E = 0$  and  $-v_{BE} < 0.7$  V. BE-KVL gives:

$$\text{BE-KVL: } 15 = -v_{BE}$$

Since  $-v_{BE} = 15 > 0.7$  V, BJT is NOT in cut-off.

Assume BJT is ON,  $v_{BE} = -0.7$  V,  $i_B > 0$ . BE-KVL gives:

$$\text{BE-KVL: } 15 = 10^3 i_E - (-0.7) \rightarrow i_E = 14.3 \text{ mA}$$

Assume BJT is in active:  $i_E \approx i_C = \beta i_B$  and  $-v_{CE} > 0.7$  V. Therefore  $i_C \approx i_E = 14.3$  mA and  $i_B = i_C/100 = 143 \mu\text{A}$ . CE-KVL gives

$$\text{CE-KVL: } 15 = 10^3 \times 14.3 \times 10^{-3} - v_{CE} + 10^3 \times 14.3 \times 10^{-3} - 15 \rightarrow v_{CE} = -1.4 \text{ V}$$

Since  $-v_{CE} = 1.4 > 0.7$  V, BJT is in active with  $i_B = 143 \mu\text{A}$ ,  $i_C = 14.3$  mA, and  $v_{CE} = -1.4\text{V}$ .


**Problem 8.** This configuration is called a Darlington Pair. Show that A) If Q1 is OFF, Q2 will be OFF, if Q1 is ON Q2 will ON, B) Show that if both BJTs are in active, the transistor pair act like one BJT in active with  $\beta = i_{C2}/i_{B1} = \beta_1\beta_2$ .

Darlington pair are arranged such that  $i_{E1} = i_{B2}$ .

 Part A:

If Q1 is OFF,  $i_{B1} = i_{C1} = i_{E1} = 0$ . Because of Darlington pair arrangement,  $i_{B2} = i_{E1} = 0$  and Q2 would also be OFF.

If Q1 is ON,  $i_{E1} > 0$ . Because of Darlington pair arrangement,  $i_{B2} = i_{E1} > 0$  and Q2 would also be ON.



Part B:

If Q1 & Q2 are both in active:

$$i_{C2} = \beta_2 i_{B2} = \beta_2 i_{E1} \approx \beta_2 i_{C1} = \beta_1 \beta_2 i_{B1} \rightarrow \frac{i_{C2}}{i_{B1}} = \beta_1 \beta_2$$

So, the Darlington pair act as a super high  $\beta$  BJT.

**Problem 9.** Find  $i_B, v_{BE}, i_C, v_{CE}$ , and state of both transistors (Si BJTs with  $\beta = 100$ ).


$$\text{BE1-KVL: } 15 = 1.3 \times 10^6 i_{B1} + v_{BE1}$$

$$\text{CE1-KVL: } 15 = 10 \times 10^3 i_1 + v_{CE1}$$

$$\text{BE2-KVL: } v_{CE1} = v_{BE2} + 10^3 i_{E2}$$

$$\text{CE2-KVL: } 15 = v_{CE2} + 10^3 i_{E2}$$

$$\text{KCL: } i_1 = i_{C1} + i_{B2}$$

 

Assume Q1 is ON,  $V_{BE1} = 0.7$  V and  $i_{B1} > 0$ . BE1-KVL gives:

$$\text{BE1-KVL: } 15 = 1.3 \times 10^6 i_{B1} + 0.7 \rightarrow i_{B1} = 11 \mu\text{A}$$

Since  $i_{B1} > 0$ , our assumption of Q1 ON is justified.

Assume Q1 is active,  $i_{C1} = 100i_{B1} = 1.1$  mA and  $v_{CE1} > 0.7$  V. In principle, we should move forward and assume state of Q2 and solve the remaining three equations together. However, solution can be simplified if we assume  $i_{B2} \ll i_{C1}$  and check this assumption after solution.

If  $i_{B2} \ll i_{C1}$ , then  $i_1 \approx i_{C1}$ . CE1-KVL gives:

$$\text{CE1-KVL: } 15 = 10 \times 10^3 i_{C1} + v_{CE1} = 10 \times 10^3 \times 1.1 \times 10^{-3} + v_{CE1} \rightarrow v_{CE1} = 3.9 \text{ V}$$

Since  $v_{CE1} > 0.7$  V, our assumption of Q1 in active is correct. State of Q2 can be found from BE2-KVL and CE2-KVL. Assume Q2 active:  $V_{BE2} = 0.7$  V,  $i_{B2} > 0$ ,  $i_{C2} = 100i_{B2}$ , and  $v_{CE2} > 0.7$  V. Then  $i_{E2} \approx i_{C2}$  and:

$$\text{BE2-KVL: } v_{CE1} = v_{BE2} + 10^3 i_{E2}$$

$$3.9 = 0.7 + 10^3 i_{C2} \rightarrow i_{C2} = 3.2 \text{ mA}$$

$$\text{CE2-KVL: } 15 \approx v_{CE2} + 10^3 i_{C2} = v_{CE2} + 10^3 \times 3.2 \times 10^{-3} \rightarrow v_{CE2} = 11.8 \text{ V}$$

Since  $v_{CE2} > 0.7$  V, our assumption of Q2 in active is correct. Then  $i_{B2} = i_{C2}/100 = 32 \mu\text{A}$ . We note that  $i_{B2} = 32 \mu\text{A} \ll i_{C1} = 1.1$  mA. Therefore that assumption was also correct.

In sum, both BJTs are in active and  $v_{BE1} = 0.7$  V,  $i_{B1} = 11 \mu\text{A}$ ,  $i_{C1} = 1.1$  mA,  $v_{CE1} = 3.9$  V,  $v_{BE2} = 0.7$  V,  $i_{B2} = 32 \mu\text{A}$ ,  $i_{C2} = 3.2$  mA,  $v_{CE2} = 11.8$  V.

**Problem 10.** Find  $i_B, v_{BE}, i_C, v_{CE}$ , and state of both transistors (Si BJTs with  $\beta = 100$ ).


Note that Q2 is a PNP transistor

$$\text{BE1-KVL: } 15 = 1.5 \times 10^6 i_{B1} + v_{BE1}$$

$$\text{CE1-KVL \& BE2-KVL: } 15 = v_{EB2} + v_{CE1}$$

$$\text{CE2-KVL: } 15 = v_{EC2} + 10^3 i_{C2}$$

$$\text{KCL: } i_{C1} = i_{B2}$$

 

Assume Q1 is ON,  $v_{BE1} = 0.7$  V and  $i_{B1} > 0$ . BE1-KVL gives:

$$\text{BE1-KVL: } 15 = 1.5 \times 10^6 i_{B1} + 0.7 \quad \rightarrow \quad i_{B1} = 9.5 \mu\text{A}$$

Since  $i_{B1} > 0$ , our assumption of Q1 ON is correct. Also, since  $i_{B2} = i_{C1} > 0$ , Q2 is ON and  $v_{EB2} = 0.7$  V. Then CE1-KVL gives  $v_{CE1} = 14.3$  V. Since  $v_{CE1} > 0.7$  V, Q1 is in active and  $i_{C1} = 100i_{B1} = 0.95$  mA.

KCL gives  $i_{B2} = i_{C1} = 0.95$  mA. Assume Q2 is in active:  $i_{C2} = 100i_{B2} = 95$  mA and  $v_{EC2} > 0.7$  V. CE2-KVL gives

$$\text{CE2-KVL: } 15 = v_{EC2} + 10^3 i_{C2} = v_{EC2} + 10^3 \times 95 \times 10^{-3} \quad \rightarrow \quad v_{EC2} = -80 \text{ V}$$

Since  $v_{EC2} = -80 < 0.7$  V, our assumption of Q2 in active is incorrect. Assume Q2 is in saturation:  $v_{EC2} = 0.2$  V and  $i_{C2}/i_{B2} < 100$ . CE2-KVL gives:

$$\text{CE2-KVL: } 15 = v_{EC2} + 10^3 i_{C2} = 0.2 + 10^3 i_{C2} \quad \rightarrow \quad i_{C2} = 14.8 \text{ mA}$$


Since  $i_{C2}/i_{B2} = 14.8/0.95 = 15.6 < 100$ , our assumption of Q2 in saturation is correct.

In sum, Q1 is in active, Q2 is in saturation, and  $v_{BE1} = 0.7$  V,  $i_{B1} = 9.5 \mu\text{A}$ ,  $i_{C1} = 0.95$  mA,  $v_{CE1} = 14.3$  V,  $v_{EB2} = 0.7$  V,  $i_{B2} = 0.95$  mA,  $i_{C2} = 14.82$  mA,  $v_{EC2} = 0.2$  V.

 **Problem 11.** Find  $i_B, v_{BE}, i_C, v_{CE}$ , and state of both transistors for A)  $v_i = 1$  V, B)  $v_i = 3$  V, C)  $v_i = 5$  V. Si BJTs with  $\beta_1 = 100$  and  $\beta_2 = 50$ .

Note that BJTs are arranged as a Darlington pair with  $i_{E1} = i_{B2}$ . So they will be either both ON or both OFF.

$$\begin{aligned} \text{BE1-KVL:} \quad & V_i = 470 \times 10^3 i_{B1} + v_{BE1} + v_{BE2} \\ \text{CE1-KVL \& BE2-KVL:} \quad & 10 = 4.7 \times 10^3 i_{C1} + v_{CE1} + v_{BE2} \\ \text{CE2-KVL:} \quad & 10 = 470 i_{C2} + v_{CE2} \\ \text{KCL:} \quad & i_{C1} = i_{B2} \end{aligned}$$



Part A:  $v_i = 1$  V.

Assume both BJTs are ON:  $v_{BE1} = v_{BE2} = 0.7$  V,  $i_{B1} > 0$ , and  $i_{B2} > 0$ . BE1-KVL gives:

$$\text{BE1-KVL:} \quad 1 = 470 \times 10^3 i_{B1} + 0.7 + 0.7 \quad \rightarrow \quad i_{B1} = -0.8 \mu\text{A}$$

Since  $i_{B1} < 0$ , our assumption is incorrect and both BJTs are in cut-off with  $i_{B1} = i_{C1} = i_{B2} = i_{C2} = 0$ . CE2-KVL gives  $v_{CE2} = 10$  V. CE1-KVL gives  $v_{CE1} + v_{BE2} = 10$  V. Our simple large-signal model for the BJT cannot resolve the values of  $v_{CE1}$  and  $v_{BE2}$  because any values of  $v_{BE2} < 0.7$  V and the corresponding value of  $v_{CE1} = 10 - v_{BE2}$  will be acceptable.

The problem of not finding unique values for  $v_{CE1}$  and  $v_{BE2}$  is due to our simple diode model of the BE junction. In reality both BE junctions will be forward biased with voltages smaller than 0.7 V (so both  $i_B$ 's will be very small) and BJTs will have small values of  $i_C$ 's.

Part B:  $v_i = 3$  V.

Assume both BJTs are ON:  $v_{BE1} = v_{BE2} = 0.7$  V,  $i_{B1} > 0$ , and  $i_{B2} > 0$ . BE1-KVL gives:

$$\text{BE1-KVL:} \quad 3 = 470 \times 10^3 i_{B1} + 0.7 + 0.7 \quad \rightarrow \quad i_{B1} = 3.4 \mu\text{A}$$

Since  $i_{B1} > 0$ , our assumption is correct and both BJTs are ON.

Assume Q1 in active:  $i_{C1} = 100i_{B1} = 0.34$  mA and  $v_{CE1} > 0.7$  V. Then CE1-KVL gives:

$$\begin{aligned} \text{CE1-KVL \& BE2-KVL:} \quad & 10 = 4.7 \times 10^3 i_{C1} + v_{CE1} + v_{BE2} \\ & 10 = 4.7 \times 10^3 \times 0.34 \times 10^{-3} + v_{CE1} + 0.7 \quad \rightarrow \quad v_{CE1} = 7.7 \text{ V} \end{aligned}$$

Since  $v_{CE1} = 7.7 > 0.7$  V, our assumption of Q1 in active is correct. Then,  $i_{B2} = i_{E1} \approx i_{C1} = 0.34$  mA.

Assume Q2 is in active:  $i_{C2} = 50i_{B2} = 17$  mA and  $v_{CE2} > 0.7$  V. Then CE2-KVL gives:

$$\text{CE2-KVL: } 10 = 470i_{C2} + v_{CE2} = 470 \times 17 \times 10^{-3} + v_{CE2} \rightarrow v_{CE2} = 2.01 \text{ V}$$

Since  $v_{CE2} = 2.01 > 0.7$  V, our assumption of Q2 in active is correct.

Therefore, Q1 & Q2 are in active, and  $v_{BE1} = v_{BE2} = 0.7$  V,  $i_{B1} = 3.4$   $\mu$ A,  $i_{C1} = 0.34$  mA,  $v_{CE1} = 7.7$  V,  $i_{B2} = 0.34$  mA,  $i_{C2} = 17$  mA, and  $v_{CE2} = 2.01$  V.

Part C:  $v_i = 5$  V.

Assume both BJTs are ON:  $v_{BE1} = v_{BE2} = 0.7$  V,  $i_{B1} > 0$ , and  $i_{B2} > 0$ . BE1-KVL gives:

$$\text{BE1-KVL: } 5 = 470 \times 10^3 i_{B1} + 0.7 + 0.7 \rightarrow i_{B1} = 7.66 \mu\text{A}$$

Since  $i_{B1} > 0$ , our assumption is correct and both BJTs are ON.

Assume Q1 is in active:  $i_{C1} = 100i_{B1} = 0.77$  mA and  $v_{CE1} > 0.7$  V. Then CE1-KVL gives:

$$\begin{aligned} \text{CE1-KVL \& BE2-KVL: } 10 &= 4.7 \times 10^3 i_{C1} + v_{CE1} + v_{BE2} \\ 10 &= 4.7 \times 10^3 \times 0.77 \times 10^{-3} + v_{CE1} + 0.7 \rightarrow v_{CE1} = 5.70 \text{ V} \end{aligned}$$

Since  $v_{CE1} = 5.70 > 0.7$  V, our assumption of Q1 in active is correct. Then,  $i_{B2} = i_{E1} \approx i_{C1} = 0.77$  mA.

Assume Q2 is in active:  $i_{C2} = 50i_{B2} = 38.3$  mA and  $v_{CE2} > 0.7$  V. Then CE2-KVL gives:

$$\text{CE2-KVL: } 10 = 470i_{C2} + v_{CE2} = 470 \times 38.3 \times 10^{-3} + v_{CE2} \rightarrow v_{CE2} = -8.0 \text{ V}$$

Since  $v_{CE2} = -8.0 < 0.7$  V, our assumption is incorrect and Q2 is in saturation:  $v_{CE2} = 0.2$  V and  $i_{C2}/i_{B2} < 50$ . Then CE2-KVL gives:

$$\text{CE2-KVL: } 10 = 470i_{C2} + v_{CE2} = 470i_{C2} + 0.2 \rightarrow i_{C2} = 20.9 \text{ mA}$$

Since  $i_{C2}/i_{B2} = 20.9/0.77 = 27 < 50$ , our assumption is correct.


Therefore, Q1 is in active, Q2 is in saturation, and  $v_{BE1} = v_{BE2} = 0.7$  V,  $i_{B1} = 7.66$   $\mu$ A,  $i_{C1} = 0.77$  mA,  $v_{CE1} = 5.7$  V,  $i_{B2} = 0.77$  mA,  $i_{C1} = 20.9$  mA, and  $v_{CE2} = 0.2$  V.

**Problem 12.** The diode in the circuit is a light-emitting diode (LED). It is made of GaAs and has a  $V_{D0} = 1.7$  V. This is a switching circuit.  $v_i$  is the output of a logic gate which turns the diode on or off depending on the state of the logic gate. A) Show that for  $v_i = 0$ , LED will be OFF, B) Show that for  $v_i = 5$  V, LED will be ON, and C) Starting from  $v_i = 0$ , we slowly increase  $v_i$ . At what voltage LED starts to light up? (Si BJTs with  $\beta = 100$ .)

$$\text{BE-KVL: } v_i = 47 \times 10^3 i_B + v_{BE}$$

$$\text{CE-KVL: } 5 = 10^3 i_C + v_D + v_{CE}$$

$$i_C = i_D$$

 

Part A:  $v_i = 0$ :

Assume BJT is OFF,  $i_B = 0$  and  $v_{BE} < 0.7$  V. BE-KVL gives:

$$\text{BE-KVL: } 0 = 47 \times 10^3 i_B + v_{BE} = 0 + v_{BE} \rightarrow v_{BE} = 0$$

Since  $v_{BE} = 0 < 0.7$  V, our assumption of BJT in cut-off is correct and  $i_C = 0$ . Since  $i_D = i_C = 0$ , the diode will be OFF.

Part B:  $v_i = 5$  V:

Assume BJT is ON,  $v_{BE} = 0.7$  V,  $i_B > 0$ . BE-KVL gives:

$$\text{BE-KVL: } 5 = 47 \times 10^3 i_B + 0.7 \rightarrow i_B = 91.5 \mu\text{A}$$

Since  $i_B > 0$  our assumption of BJT is ON is justified. When BJT is ON,  $i_C > 0$  and since  $i_D = i_C > 0$ , the LED will be on with  $v_D = 1.7$  V.

Assume BJT is in active:  $i_C = \beta i_B = 100 i_B = 9.15$  mA and  $v_{CE} > 0.7$  V. CE-KVL gives:

$$\text{CE-KVL: } 5 = 10^3 i_C + v_D + v_{CE}$$

$$5 = 10^3 \times 9.15 \times 10^{-3} + 1.7 + v_{CE} \rightarrow v_{CE} = -5.85 \text{ V}$$

Since  $v_{CE} = -5.85 < 0.7$  V our assumption of BJT in active is NOT justified.

Assume BJT in saturation,  $v_{CE} = 0.2$  V, and  $i_C < \beta i_B$ . CE-KVL gives:

$$\text{CE-KVL: } 5 = 10^3 i_C + v_D + v_{CE} = 10^3 i_C + 1.7 + 0.2 \rightarrow i_C = 3.1 \text{ mA}$$

Since  $i_C/i_B = 3.1/0.0915 = 34 < 100 = \beta$ , our assumption of BJT in saturation is justified.

Therefore, for  $v_i = 5$  V, LED is ON, BJT is in saturation, and  $v_{BE} = 0.7$  V,  $v_D = 1.7$  V,  $i_B = 91.5$   $\mu$ A,  $i_C = 3.1$  mA, and  $v_{CE} = 0.2$  V.

Part C:

LED is ON when  $i_D > 0$ . Since  $i_C = i_D > 0$ , the BJT should be ON.

We found that for  $v_i = 0$ , BJT is in cut-off and LED is OFF. As we increase  $v_i$  and while BJT is still in cut-off, BE-KVL gives  $v_{BE} = v_i$  since  $i_B = 0$ . So as we increase  $v_i$ ,  $v_{BE}$  increases while  $i_B$  remains zero.

When  $v_i$  reaches 0.7 V,  $v_{BE}$  also reaches 0.7 V while  $i_B$  is still zero.

If we increase  $v_i$  beyond this point,  $v_{BE}$  cannot increase, rather  $i_B$  becomes positive and BJT will be turned ON leading to  $i_C > 0$  and LED turning ON.

So, LED will light up when  $v_i \geq 0.7$  V.

**Problem 13.** Design a switch circuit similar to problem 12 which turns an LED OFF and ON such that the LED is OFF for  $v_i < 2.5$  V and is ON for  $v_i > 2.5$  V. (Hint: See page 3-14 of lecture notes).


Addition of a resistor  $R$  (see circuit) will raise  $v_i$  that turns the LED ON.

In problem 12, we saw that LED will just turn ON when  $v_{BE} = 0.7$  V and  $i_B \approx 0$ . BE-KVL gives:

$$\begin{aligned} \text{BE-KVL: } \quad v_i &= 47 \times 10^3 i + v_{BE} \\ 2.5 &= 47 \times 10^3 i + 0.7 \quad \rightarrow \quad i = 38.3 \mu\text{A} \end{aligned}$$

Since  $i_B = 0$ ,  $i_R = i = 38.3$   $\mu$ A. Ohm's law for the resistor  $R$  gives:
 
$$v_{BE} = Ri_R \quad \rightarrow \quad 0.7 = 38.3 \times 10^{-6} R \quad \rightarrow \quad R = 18.3 \text{ k}\Omega$$




**Problem 14.** The circuit shown is a Resistor-Transistor Logic (RTL) NOR gate configured with two identical BJTs. Show that this is NOR gate with a LOW state of 0.2 V and a HIGH state of 5 V (Si BJTs with  $\beta = 100$ ).

We first find the state of Q1 for the two cases of  $V_1 = 0.2$  and 5 V.

$$\text{BE1-KVL: } v_1 = 500i_{B1} + v_{BE1}$$

For  $v_1 = 0.2$  V, assume that Q1 is in cut-off ( $i_{B1} = 0$  and  $v_{BE1} < V_{D0} = 0.7$  V). Then, BE1-KVL gives  $V_{BE1} = 0.2 < 0.7$  V and, thus, Q1 is indeed in cut-off. So:
 
$$v_1 = 0.2 \text{ V} \rightarrow i_{B1} = i_{C1} = 0, \quad v_{BE1} = 0.2 \text{ V}, \quad v_{CE1} \text{ can be anything}$$



For  $v_1 = 5$  V, assume that Q1 is NOT in cut-off ( $i_{B1} > 0$  and  $v_{BE1} = V_{D0} = 0.7$  V). Substituting for  $v_{BE1} = 0.7$  in BE1-KVL, we get  $I_{B1} = 4.3/5,000 = 0.86$  mA. Since  $i_{B1} > 0$ , Q1 is indeed NOT in cut-off. Therefore,

$$v_1 = 5 \text{ V} \rightarrow \text{BJT is ON (not in cut-off)} \quad i_{B1} = 0.86 \text{ mA} \quad v_{BE1} = 0.7 \text{ V} \quad i_{C1} > 0$$

Note that because the circuit is symmetric (*i.e.*, there is no difference between Q1 circuit and Q2 circuit), the above results also applies to Q2.

Case a:  $v_1 = v_2 = 0.2$  V From above, both BJTs will be in cut-off and  $i_{C1} = i_{C2} = 0$ . By KCL,  $I = i_{C1} + i_{C2} = 0$ , and  $v_o$  can be found from Ohm's Law:

$$5 - v_o = 500I = 0 \rightarrow v_o = 5 \text{ V}$$

Case b:  $v_1 = 0.2$  V,  $v_2 = 5$  V Since  $v_1 = 0.2$  V, Q1 will be in cut-off with  $i_{C1} = 0$ . Since  $v_2 = 5$  V, Q2 will not be in cut-off with  $i_{B2} = 0.86$  mA. Assume Q2 is in saturation ( $v_{CE2} = 0.2$  V and  $i_{C2}/i_{B2} < \beta$ ). In this case,  $v_o = v_{CE2} = 0.2$  V and  $I = i_{C1} + i_{C2} = i_{C2}$ . By Ohm's Law:

$$500I = 500i_{C2} = 5 - V_o = 5 - v_{CE2} = 4.8 \rightarrow i_{C2} = 4.8/500 = 9.6 \text{ mA}$$

Since  $i_{C2}/i_{B2} = 11 < \beta = 100$ , Q2 is indeed in saturation. So, in this case,  $v_o = 0.2$  V.

Case c:  $v_1 = 5$ ,  $v_2 = 0.2$  V Because the circuit is symmetric (*i.e.*, there is no difference between Q1 circuit and Q2 circuit), results from Case b can be applied here. Thus, Q2 will be in cut-off with  $i_{C2} = 0$  and Q1 will be in saturation with  $i_{C1} = 9.6$  mA and  $v_o = v_{CE2} = 0.2$  V.

Case d:  $v_1 = v_2 = 5 \text{ V}$  Both BJTs will be ON with  $i_{B1} = i_{B2} = 0.86 \text{ mA}$  and  $v_{BE1} = v_{BE2} = 0.7 \text{ V}$ . Since from the circuit,  $v_{CE1} = v_{CE2}$ , both BJTs will be in saturation or both in active-linear. Assume that both are in saturation. Then,  $v_o = v_{CE1} = v_{CE2} = 0.2 \text{ V}$  and we should have  $i_{C1}/i_{B1} < \beta$  and  $i_{C2}/i_{B2} < \beta$ . By Ohm's Law:

$$500I = 5 - v_o = 5 - 0.2 = 4.8 \quad \rightarrow \quad I = 4.8/500 = 9.6 \text{ mA}$$

Since BJTs are identical and have same  $i_B$ , we should have  $i_{C1} = i_{C2}$  and current  $I$  should be equally divided between two BJTs. Thus,  $i_{C1} = i_{C2} = 0.5I = 4.8 \text{ mA}$ . To check if BJTs are in saturation:  $i_{C1}/i_{B1} = 4.8/0.86 = 5 < \beta = 100$  and  $i_{C2}/i_{B2} = 4.8/0.86 = 5 < \beta = 100$  so both BJTs are indeed in saturation and  $v_o = 0.2 \text{ V}$ .

In summary, the output is high when both inputs are low and the output is low otherwise. Therefore, this is a NOR gate.

**Problem 15.** Show that this is NAND gate with a LOW state of 0.4 V and a HIGH state of 1.2 V (Si BJTs with  $\beta = 200$ ).


$$i_{E1} = i_{C2}$$

$$\text{CE-KVL:} \quad 1.2 = 10^3 i_{C1} + v_{CE1} + v_{CE2}$$

$$v_o = v_{CE1} + v_{CE2} = 1.2 - 10^3 i_{C1}$$

$$\text{BE1-KVL:} \quad v_1 = 2 \times 10^3 i_{B1} + v_{BE1} + v_{CE2}$$
 
$$\text{BE2-KVL:} \quad v_2 = 2 \times 10^3 i_{B2} + v_{BE2}$$



Case 1:  $v_1 = 0.4, v_2 = 0.4$ : Assume Q2 is off ( $i_{B2} = 0, v_{BE2} < V_{D0}$ ). Substituting for  $i_{B2} = 0$  in the BE2-KVL above, we get:  $v_{BE2} = v_2 = 0.4 < 0.7 = V_{D0}$ . Thus, Q2 is off and  $i_{C2} = 0$ . Since  $i_{E1} = i_{C2} = 0$  and  $i_{E1} = i_{C1} + i_{B1} = 0$ , we should have  $i_{C1} = 0$  (because  $i_{C1} \geq 0$  and  $i_{B1} \geq 0$ ). Then, from CE-KVL above:

$$v_o = 1.2 - 10^3 i_{C1} = 1.2 \text{ V}$$

Case 2:  $v_1 = 1.2, v_2 = 0.4$ : Similar to Case 1, assume Q2 is off to find  $i_{C1} = 0$  and  $v_o = 1.2 \text{ V}$ .

Case 3:  $v_1 = 0.4, v_2 = 1.2$ : Assume Q1 is off ( $i_{B1} = 0, v_{BE1} < V_{D0}$ ). Substituting for  $i_{B1} = 0$  in the BE1-KVL above, we get:  $v_{BE1} = 0.4 - v_{CE2}$ . Since  $v_{CE2}$  cannot be negative (powered by 1.2 V),  $v_{BE1} = 0.4 - v_{CE2} < 0.7 = V_{D0}$  and Q1 is off ( $i_{C1} = 0$ ). Then:

$$v_o = 1.2 - 10^3 i_{C1} = 1.2 \text{ V}$$

*Case 4:*  $v_1 = 1.2$ ,  $v_2 = 1.2$ : Since both inputs are high, we start by assuming that both BJTs are ON (we still need to prove it):  $i_{B2} > 0$ ,  $v_{BE2} = V_{D0} = 0.7$  V and  $i_{B1} > 0$ ,  $v_{BE1} = V_{D0} = 0.7$  V. Four possible combinations exist with Q1 and Q2 being respectively in active & active, active & saturation, saturation & active, and saturation & active. Since problem states that this is NAND gate and the low voltage is 0.4 V, a good guess is that both BJTs are in saturation  $v_{CE1} = V_{sat} = 0.2$  V,  $i_{C1}/i_{B1} < \beta$  and  $v_{CE2} = V_{sat} = 0.2$  V,  $i_{C2}/i_{B2} < \beta$ .

Starting with BE1-KVL and BE2-KVL above, we get:

$$\begin{aligned} 1.2 &= 2 \times 10^3 i_{B2} + 0.7 && \rightarrow && i_{B2} = 0.25 \text{ mA} \\ 1.2 &= 2 \times 10^3 i_{B1} + 0.7 + 0.2 && \rightarrow && i_{B1} = 0.15 \text{ mA} \end{aligned}$$

Since  $i_{B2} > 0$ , and  $i_{B1} > 0$ , assumption of both BJTs ON is correct. Then, CE-KVL gives:

$$1.2 = 10^3 i_{C1} + 0.2 + 0.2 \quad \rightarrow \quad i_{C1} = 0.8 \text{ mA}$$

Since  $i_{C1}/i_{B1} = 0.8/0.15 = 5.3 < \beta = 200$ , our assumption of Q1 being in saturation is justified. To find  $i_{C2}$ , we note  $i_{C2} = i_{E1} = i_{C1} + i_{B1} = 0.8 + 0.15 = 0.95$  mA. Then  $i_{C2}/i_{B2} = 0.95/0.25 = 3.8 < \beta = 200$ , so our assumption of Tr2 being in saturation is also justified. Lastly,

$$v_o = v_{CE1} + v_{CE2} = 0.2 + 0.2 = 0.4 \text{ V}$$

Overall,  $v_o = 1.2$  V or HIGH State (cases 1, 2, and 3) unless both inputs are HIGH (case 4). Therefore, this is a NAND gate.


**Problem 16.** In circuit below find  $v_{GS}$ ,  $i_D$ ,  $v_{DS}$ , and state of the transistor (Use  $k'_n(W/L)_n = k'_p(W/L)_p = 0.4 \text{ mA/V}^2$ ,  $\lambda = 0$ ,  $V_{tn} = 3 \text{ V}$  and  $V_{tp} = -3 \text{ V}$ ).

This is a NMOS transistor with  $v_{GS} = 4 \text{ V}$  and  $v_{DS} = 10 \text{ V}$ .

Since  $V_{GS} = 4 > 3 = V_{tn}$ , NMOS is ON

Since  $v_{DS} = 10 > v_{GS} - V_{tn} = 1 \text{ V}$ , NMOS is in Saturation:
 
$$i_D = 0.5k'_n(W/L)_n(v_{GS} - V_{tn})^2 = 0.2 \times 10^{-3}(1)^2 = 0.2 \text{ mA}$$




**Problem 17.** In circuit below find  $v_{SG}$ ,  $i_D$ ,  $v_{SD}$ , and state of the transistor (Use  $k'_n(W/L)_n = k'_p(W/L)_p = 0.4 \text{ mA/V}^2$ ,  $\lambda = 0$ ,  $V_{tn} = 3 \text{ V}$  and  $V_{tp} = -3 \text{ V}$ ).

This is a PMOS transistor with  $v_{SG} = -1 \text{ V}$  and  $v_{DG} = 5 \text{ V}$ .

Since  $v_{SG} = -1 < 3 = |V_{tp}|$ , PMOS is OFF and  $i_D = 0$ .

 Also,  $v_{SD} = v_{SG} + v_{GD} = -1 - 5 = -6 \text{ V}$ .



**Problem 18.** In circuit below find  $v_{SG}$ ,  $i_D$ ,  $v_{SD}$ , and state of the transistor (Use  $k'_n(W/L)_n = k'_p(W/L)_p = 0.4 \text{ mA/V}^2$ ,  $\lambda = 0$ ,  $V_{tn} = 3 \text{ V}$  and  $V_{tp} = -3 \text{ V}$ ).


This is a PMOS transistor with  $v_{SG} = 5 \text{ V}$  and  $v_{DG} = -6 \text{ V}$ .

Since  $v_{SG} = 5 > 3 = |V_{tp}|$ , PMOS is ON.

$v_{SD} = v_{SG} + v_{GD} = 5 + 6 = 11 \text{ V}$ .

Since  $v_{SD} = 11 > v_{SG} - |V_{tp}| = 5 - 3 = 2 \text{ V}$ , PMOS is in saturation:

$$i_D = 0.5k'_p(W/L)_p(v_{GS} - |V_{tp}|)^2 = 0.2 \times 10^{-3}(-5 + 3)^2 = 0.8 \times 10^{-3} = 0.8 \text{ mA}$$

 


**Problem 19.** In circuit below find  $v_{GS}$ ,  $i_D$ ,  $v_{DS}$ , and state of the transistor (Use  $k'_n(W/L)_n = k'_p(W/L)_p = 0.4 \text{ mA/V}^2$ ,  $\lambda = 0$ ,  $V_{tn} = 3 \text{ V}$  and  $V_{tp} = -3 \text{ V}$ ).

This is a NMOS transistor with  $v_{GS} = 4 \text{ V}$  and  $v_{DS} = 1 \text{ V}$ .

Since  $V_{GS} = 4 > 3 = V_{tn}$ , NMOS is ON

Since  $v_{DS} = 1 = v_{GS} - V_{tn} = 1 \text{ V}$ , NMOS is at the boundary of saturation and triode modes. We can use either formulas for  $i_D$ .
 
$$i_D = 0.5k'_n(W/L)_n(v_{GS} - V_{tn})^2 = 0.2 \times 10^{-3}(1)^2 = 0.2 \text{ mA}$$



**Problem 20.** In circuit below find  $v_{GS}$ ,  $i_D$ ,  $v_{DS}$ , and state of the transistor (Use  $k'_n(W/L)_n = k'_p(W/L)_p = 0.4 \text{ mA/V}^2$ ,  $\lambda = 0$ ,  $V_{tn} = 3 \text{ V}$  and  $V_{tp} = -3 \text{ V}$ ).

$$\text{GS-KVL: } 7 = v_{GS} + 10^3 i_D$$

$$\text{DS-KVL: } 10 = v_{DS} + 10^3 i_D$$

Assume NMOS is in cut-off:  $i_D = 0$ ,  $v_{GS} < V_{tn} = 3 \text{ V}$ .


GS-KVL gives  $v_{GS} = 7 > V_{tn} = 3 \text{ V}$ . Therefore, NMOS is NOT in cut-off.

Assume NMOS in saturation:  $i_D = 0.5k'_n(W/L)_n(v_{GS} - V_{tn})^2$  and  $v_{DS} > v_{GS} - V_{tn}$ . Substituting for  $i_D$  in GS-KVL, we get:

$$\begin{aligned} \text{GS-KVL: } 7 &= v_{GS} + 10^3 \times 0.2 \times 10^{-3} (v_{GS} - 3)^2 = v_{GS} + 0.2v_{GS}^2 - 1.2v_{GS} + 1.8 \\ v_{GS}^2 - v_{GS} - 26 &= 0 \quad \rightarrow \quad v_{GS} = -4.62 \text{ V} \quad \text{and} \quad v_{GS} = 5.62 \text{ V} \end{aligned}$$

Negative root is unphysical so  $v_{GS} = 5.62 \text{ V}$ . GS-KVL give  $i_D = 1.35 \text{ mA}$ . DS-KVL gives  $v_{DS} = 10 - 1.35 = 8.65 \text{ V}$  Since  $v_{DS} = 8.65 > v_{GS} - V_{tn} = 5.62 - 3 = 2.62 \text{ V}$ , our assumption of NMOS in saturation is justified.

 In sum, NMOS is in saturation with  $v_{GS} = 5.62 \text{ V}$ ,  $v_{DS} = 8.65 \text{ V}$ , and  $i_D = 1.35 \text{ mA}$



**Problem 21.** In circuit below find  $v_{GS}$ ,  $i_D$ ,  $v_{DS}$ , and state of the transistor (Use  $k'_n(W/L)_n = k'_p(W/L)_p = 0.4 \text{ mA/V}^2$ ,  $\lambda = 0$ ,  $V_{tn} = 3 \text{ V}$  and  $V_{tp} = -3 \text{ V}$ ).

Since  $i_G = 0$ , the two  $1 \text{ M}\Omega$  resistors form a voltage divider and  $v_G = 20 \times (10^6)/(10^6 + 10^6) = 10 \text{ V}$ .

$$\text{GS-KVL: } v_G = v_{GS} + 10^3 i_D$$


$$\text{DS-KVL: } 20 = v_{DS} + 2 \times 10^3 i_D$$

Assume NMOS is in cut-off:  $i_D = 0$ ,  $v_{GS} < V_{tn} = 3 \text{ V}$ .

GS-KVL gives  $v_{GS} = 10 > V_{tn} = 3 \text{ V}$ . Therefore, NMOS is NOT in cut-off.

Assume NMOS in saturation:  $i_D = 0.5k'_n(W/L)_n(v_{GS} - V_{tn})^2$  and  $v_{DS} > v_{GS} - V_{tn}$ . Substituting for  $i_D$  in GS-KVL, we get:
 
$$\begin{aligned} \text{GS-KVL: } 10 &= v_{GS} + 10^3 \times 0.2 \times 10^{-3} (v_{GS} - 3)^2 = v_{GS} + 0.2v_{GS}^2 - 1.2v_{GS} + 1.8 \\ v_{GS}^2 - v_{GS} - 41 &= 0 \quad \rightarrow \quad v_{GS} = -5.92 \text{ V} \quad \text{and} \quad v_{GS} = 6.92 \text{ V} \end{aligned}$$



Negative root is unphysical so  $v_{GS} = 6.92$  V. GS-KVL give  $i_D = 3.08$  mA. DS-KVL gives  $v_{DS} = 20 - 6.16 = 13.8$  V Since  $v_{DS} = 13.8 > v_{GS} - V_{tn} = 6.92 - 3 = 3.92$  V, our assumption of NMOS in saturation is justified.


In sum, NMOS is in saturation with  $v_{GS} = 6.92$  V,  $v_{DS} = 13.8$  V, and  $i_D = 3.08$  mA

**Problem 22.** In circuit below find  $v_{GS}$ ,  $i_D$ ,  $v_{DS}$ , and state of the transistor (Use  $k'_n(W/L)_n = k'_p(W/L)_p = 0.4$  mA/V<sup>2</sup>,  $\lambda = 0$ ,  $V_{tn} = 3$  V and  $V_{tp} = -3$  V).

$$\text{GS-KVL: } 0 = v_{GS} + 10^3 i_D - 15$$

$$\text{DS-KVL: } 15 = 10^3 i_D + v_{DS} + 10^3 i_D - 15$$

$$30 = 2 \times 10^3 i_D + v_{DS}$$

 

Assume NMOS is in cut-off:  $i_D = 0$ ,  $v_{GS} < V_{tn} = 3$  V.

GS-KVL gives  $v_{GS} = 15 > V_{tn} = 3$  V. Therefore, NMOS is NOT in cut-off.

Assume NMOS in saturation:  $i_D = 0.5k'_n(W/L)_n(v_{GS} - V_{tn})^2$  and  $v_{DS} > v_{GS} - V_{tn}$ . Substituting for  $i_D$  in GS-KVL, we get:

$$\begin{aligned} \text{GS-KVL: } 0 &= v_{GS} + 10^3 \times 0.2 \times 10^{-3} (v_{GS} - 3)^2 - 15 \quad \rightarrow \quad 0 = 5v_{GS} + (v_{GS} - 3)^2 - 75 \\ v_{GS}^2 - v_{GS} - 66 &= 0 \quad \rightarrow \quad v_{GS} = -7.64 \text{ V} \quad \text{and} \quad v_{GS} = 8.64 \text{ V} \end{aligned}$$

Negative root is unphysical so  $v_{GS} = 8.64$  V.  $i_D$  relationship gives  $i_D = 6.3$  mA. DS-KVL gives  $v_{DS} = 17.5$  V. Since  $v_{DS} = 17.5 > v_{GS} - V_{tn} = 8.64 - 3 = 5.64$  V, our assumption of NMOS in saturation is justified.

In sum, NMOS is in saturation with  $v_{GS} = 8.64$  V,  $v_{DS} = 17.5$  V, and  $i_D = 6.3$  mA


**Problem 23.** Find  $v_o$  when  $v_i = 0$  and  $12$  V (Use  $k'_n(W/L)_n = 0.5$  mA/V<sup>2</sup>,  $\lambda = 0$ ,  $V_{tn} = 2$  V).

$$\text{GS-KVL: } v_{GS} = v_i$$

$$\text{DS-KVL: } 12 = 2 \times 10^3 i_D + v_{DS}$$

 A)  $v_i = 0$  V. From GS-KVL, we get  $v_{GS} = v_i = 0$ . As  $v_{GS} < V_{tn} = 2$  V, NMOS is in cut-off,  $i_D = 0$ , and  $v_{DS}$  is found from DS-KVL:

$$\text{DS-KVL: } v_o = v_{DS} = 12 - 2 \times 10^3 i_D = 12 \text{ V}$$



B)  $v_i = 12$  V. From GS-KVL, we get  $v_{GS} = 12$  V. Since  $v_{GS} > V_{tn}$ , NMOS is not in cut-off. Assume NMOS in saturation mode. Then:

$$i_D = 0.5k'_n(W/L)_n(v_{GS} - V_{tn})^2 = 0.25 \times 10^{-3}(12 - 2)^2 = 25 \text{ mA}$$

$$\text{DS-KVL: } v_{DS} = 12 - 2 \times 10^3 i_D = 12 - 25 \times 2 \times 10^3 \times 10^{-3} = -38 \text{ V}$$

Since  $v_{DS} = -38 < v_{GS} - V_{tn} = 12 - 2 = 10$ , NMOS is NOT in saturation mode.

Assume NMOS in triode mode. Then:

$$i_D = 0.5k'_n(W/L)_n[2v_{DS}(v_{GS} - V_{tn}) - v_{DS}^2] = 0.25 \times 10^{-3}[2v_{DS}(12 - 2) - v_{DS}^2]$$

$$i_D = 0.25 \times 10^{-3}[20v_{DS} - v_{DS}^2]$$

Substituting for  $i_D$  in DS-KVL, we get:

$$\begin{aligned} \text{DS-KVL: } 12 &= 2 \times 10^3 i_D + v_{DS} \quad \rightarrow \quad 12 = 2 \times 10^3 \times 0.25 \times 10^{-3}[20v_{DS} - v_{DS}^2] + v_{DS} \\ v_{DS}^2 - 22v_{DS} + 24 &= 0 \end{aligned}$$

This is a quadratic equation in  $v_{DS}$ . The two roots are:  $v_{DS} = 1.15$  V and  $v_{DS} = 20.8$  V. The second root is not physical as the circuit is powered by a 12 V supply. Therefore,  $v_{DS} = 1.15$  V. As  $v_{DS} = 1.15 < v_{GS} - V_{tn} = 10$ , NMOS is indeed in triode mode with  $v_o = v_{DS} = 1.15$  V and


**Problem 24.** Show that this circuit is a NOR gate with a LOW state of 0.2 V and a HIGH state of 12 V (Use  $k'_n(W/L)_n = 0.5 \text{ mA/V}^2$ ,  $V_{tn} = 1$  V).

By KVL and KCL:

$$v_{GS1} = v_1, \quad v_{GS2} = v_2, \quad v_o = v_{DS1} = v_{DS2}$$

$$i_1 = i_{D1} + i_{D2}$$

$$12 = 10,000i_1 + v_o$$

 

Case 1:  $v_1 = v_2 = 0.2$ . Since  $v_{GS1} = 0.2 < V_{tn} = 1$  and  $v_{GS2} = 0.2 < V_{tn} = 1$ , both transistors will be in cut-off:  $i_{D1} = i_{D2} = 0$ . Then,  $i_1 = i_{D1} + i_{D2} = 0$  and from KVL,

$v_o = 12$  V.

So, When  $v_1 = 0.2$  (LOW) and  $v_2 = 0.2$  (LOW),  $v_o = 12$  V (HIGH).

Case 2:  $v_1 = 0.2, v_2 = 12$  V. Since  $v_{GS1} = 0.2 < V_{tn} = 1$ ,  $Q_1$  will be in cut-off and  $i_{D1} = 0$ . Since  $V_{GS2} = 12 > V_{tn} = 1$ ,  $M_2$  will not be in cut-off. Assume  $M_2$  is in saturation mode. Then:

$$i_{D2} = 0.5k'_n(W/L)_n(v_{GS2} - V_{tn})^2 = 0.25 \times 10^{-3}(12 - 1)^2 = 30 \text{ mA}$$
$$v_{DS2} = v_o = 12 - 10,000(i_{D2} + i_{D1}) = -288 \text{ V}$$

Since  $V_{DS2} < v_{GS2} - V_{tn} = 12 - 1 = 11$  V,  $M_2$  is not in saturation mode. Assume  $M_2$  is in triode:

$$i_{D2} = K[2v_{DS2}(v_{GS2} - V_{tn}) - v_{DS2}^2] = 0.25 \times 10^{-3}[22v_{DS2} - v_{DS2}^2]$$
$$12 = 10,000i_{D2} + v_{DS2} \quad \rightarrow \quad 12 = 2.5[22v_{DS2} - v_{DS2}^2] + v_{DS2}$$
$$v_{DS2}^2 - 22.4v_{DS2} + 4.8 = 0$$

The two roots are:  $v_{DS2} = 22.2$  V and  $v_{DS2} = 0.22$  V. First root is not physical as the circuit is powered by a 12 V supply. So,  $v_{DS2} = 0.2$  V. Since  $v_{DS2} = 0.2 < v_{GS2} - V_{tn} = 12 - 1 = 11$ , our assumption of  $M_2$  in triode mode is justified.

So, When  $v_1 = 0.2$  (LOW) and  $v_2 = 12$  V (HIGH),  $v_o = 0.2$  V (LOW).

Case 3:  $v_1 = 12, v_2 = 0.2$  V. This is similar to case 2. By symmetry:  
When  $v_1 = 12$  V (HIGH) and  $v_2 = 0.2$  (LOW),  $v_o = 0.2$  V (LOW).

Case 4:  $v_1 = 12, v_2 = 12$  V. Since  $v_{GS1} = 12 > V_{tn} = 1$ , and  $v_{GS2} = 12 > V_{tn} = 1$ , both transistors will be ON. Since the two transistors are identical,  $i_{D1} = i_{D2} = 0.5i_1$  and  $v_{DS1} = v_{DS2}$  and both transistors will be in the same state (we only need to analyze one of them). Assume both transistors are in triode mode:

$$i_{D2} = K[2v_{DS2}(v_{GS2} - V_{tn}) - v_{DS2}^2] = 0.25 \times 10^{-3}[22v_{DS2} - v_{DS2}^2]$$
$$12 = 2 \times 10,000i_{D2} + v_{DS2} \quad \rightarrow \quad 12 = 5[22v_{DS2} - v_{DS2}^2] + v_{DS2}$$
$$v_{DS2}^2 - 22.2v_{DS2} + 2.4 = 0$$

The two roots are:  $v_{DS2} = 22.1$  V and  $v_{DS2} = 0.11$  V. First root is not physical as the circuit is powered by a 12 V supply. So,  $v_{DS2} = 0.11$  V. Since  $v_{DS2} = 0.11 < v_{GS2} - V_{tn} = 12 - 1 = 11$ , our assumption of  $M_2$  in triode mode is justified. Similarly, we find  $v_{DS1} = 0.11$  V.

So, When  $v_1 = 12$  V (HIGH) and  $v_2 = 12$  V (HIGH),  $v_o = 0.1$  V (LOW).

Since the output is HIGH only when both inputs are LOW, this is NOR gate.