


University of California, San Diego
Department of Electrical and Computer Engineering

ECE65, Fall 2010

Lab 2: Diode i_v Characteristics, Zener Diode

Experiment 1: General Purpose diode i_v Characteristics

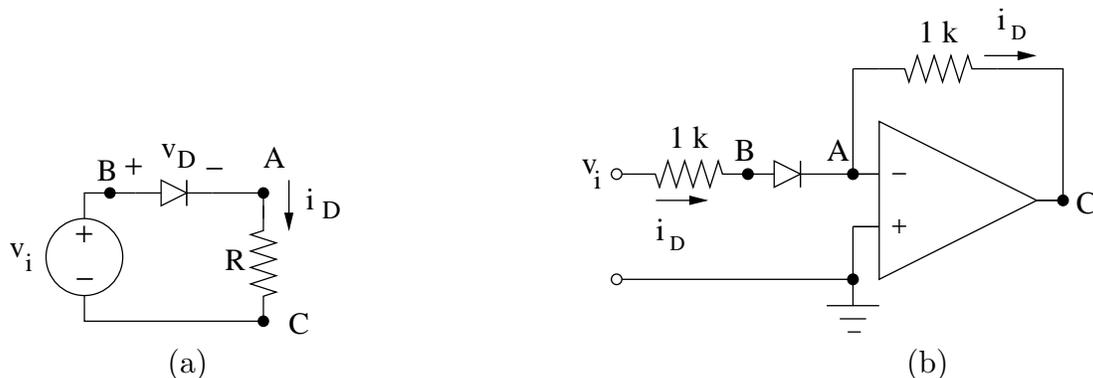This simulation shows how to measure i_v characteristics of a diode. The circuit is made of an 1N4148 diode and $R = 1\text{ k}\Omega$.



Pspice Simulation: Simulate circuit (a) above with v_i being a 1-kHz triangular wave with a peak to peak value of 15 V and a DC offset of -5 V (*i.e.*, input signal ranges from -10 to $+5\text{ V}$). Run the simulation for a few periods.


Plot i_D vs v_D . On your plot, identify forward-bias and reverse-bias regions.

Lab Exercise: It turns out that we cannot use the simple circuit above to measure the i_v characteristics of the diode in the lab and we need a more complicated circuit: Build the circuit (b) above with a 741 OpAmp chip. The chip should be powered with $\pm 15\text{ V}$ supplies. Set the function generator to produce a triangular wave with a frequency of 1 kHz and DC off set of zero. Set the amplitude to be zero. Attach the function generator to the circuit (v_i). Attach the scope ground to the non-inverting terminal of the OpAmp which is grounded (because of the “virtual short” principle of OpAmps, inverting and non-inverting terminals have the same voltage and, thus, point A is effectively grounded). Attach Channel 1 probe to point B (so Channel 1 reads v_D) and channel 2 probe to point C (which will read $10^3 i_D$). Set the scope of show (x vs y). Set both channels to 1 V/division. Scope should show one point. Move the point such that it is at the lowest, right-most voltage division marks on the scope. Slowly increase the amplitude of the input. The scope shows the $i - v$ characteristics of the diode. Increase the amplitude of input wave until the the diode i_v curves “fills” the scope display. Print out the scope output and mark and label the axis.

Explain why we could not use circuit (a) to the show the i_v characteristics of the diode on the scope (corresponding points A,B, and C are shown).

Experiment 2: Zener Diode Power Supply

Set up the circuit below with a 1N5232B Zener diode ($V_Z = 5.6\text{ V}$). In this circuit, the 9-V supply represents the “unregulated voltage.” The elements in the box (1 k Ω resistor and the Zener diode) form the regulator circuit. The combination of the variable resistor (potentiometer) and 100 Ω resistor, represents the “load” in this circuit (call their combination R_L). With varying the resistance of the potentiometer, we can draw different amount of current from the regulator circuit. What is the purpose of the 100 Ω resistor?

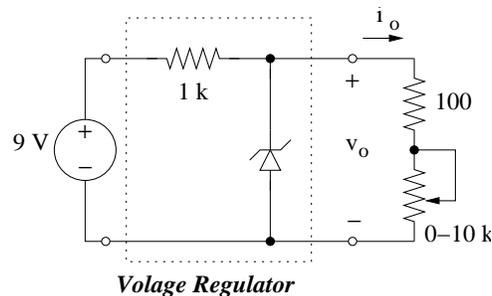

Circuit Analysis: Using a “Constant voltage” model for the Zener region, calculate the output voltage of the regulator (v_o) as a function of its output current (i_o). Estimate the maximum load current for the circuit to act as a voltage regulator.

PSpice Simulation: Simulate the circuit with PSpice with R_L (combination of the potentiometer and 100 Ω resistor) as a parameter with a range of 100 Ω to 10 k Ω (do NOT include the 100 Ω resistor in your simulation!). Plot v_o versus i_o and compare with your analytical results.

Lab Exercise: Assemble the circuit. Start with the potentiometer set at maximum resistance (*i.e.*, about 10 k Ω). Measure the load current and the load voltage. Then, vary the potentiometer resistance and measure the load voltage for a range of load currents. Plot v_o , versus i_o . Compare with your circuit analysis and PSpice simulation and explain the results (specially the observed slight drop in v_o when i_o is increased).