

**University of California, San Diego**  
**Department of Electrical and Computer Engineering**

**ECE65, Fall 2010**


**Lab 3, Diode wave-form shaping circuits**

In these experiments we examine diode circuits that modify the input wave-form. In these cases (and in many future experiments) you are asked to print out scope traces of input and output voltages of the circuit. You should follow this procedure:

- 1) Attach Scope channel 1 to  $v_i$ , Scope Channel 2 to  $v_o$ , and have both traces be “triggered” by channel 1.
- 2) Move the two traces such that the zero voltage value for both channels are in the middle of the display.
- 3) Expand the time selection so that only 2 to 4 periods of the wave-form are shown.
- 4) Adjust the volt per division knob such that the signal is as large as possible (*i.e.*, fills the display). Ensure that both channels have the same volt per division setting.
- 5) Printout the trace. In this manner  $v_o$  and  $v_i$  can be directly compared.

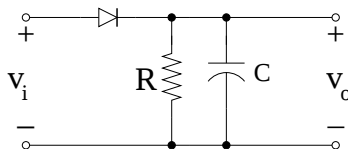**Experiment 1: Rectifier & Peak Detector Circuit**

Consider the circuit below with a 1N4148 general purpose diode and  $R = 100\text{ k}\Omega$ .



*Lab Exercise:*

- 1) Assemble the circuit without the capacitor. Set the function generator to produce a sinusoidal wave with an amplitude of 5 V, zero DC offset, and frequency of 2 kHz. Attach the function generator to  $v_i$ . Attach Scope channel 1 to  $v_i$  and Scope Channel 2 to  $v_o$ . Adjust scope according to the instruction above. Print out  $v_o$  and  $v_i$ .
- 2) Disconnect the function generator without changing the function generator and scope settings. Attach a 10 nF capacitor (see circuit diagram above). Attach the function generator to the circuit and print out  $v_o$  and  $v_i$ .
- 3) Repeat part 2 for  $C = 1\text{ nF}$  and 100 nF.
- 4) Compare the four printout. What are your conclusions?

## Experiment 2: Clipper Circuit

*Design Problem:* Design a clipper circuit using 1N4148 general purpose diodes and a  $R = 1\text{ k}\Omega$  to clip the input signal voltages that are above 5.7 V or less than  $-0.7\text{ V}$ .


*Simulation:* Simulate the circuit you have designed with PSpice with two input voltages:  
 1) A sinusoidal wave with an amplitude of 8 V and a DC offset of zero and 1) A sinusoidal wave with an amplitude of 8 V and a DC offset of 4 V. In each case, plot  $v_o$  and  $v_i$  for two period (both traces on the same graph).

*Lab Exercise:*

- 1) Assemble the circuit that you have designed. Apply a sinusoidal wave with amplitude of 8 V and DC offset of zero to the circuit. Adjust the scope and print out  $v_i$  and  $v_o$ .
- 2) Increase the DC offset of the input. What do you see? Does it follow your simulation. Explain?
- 3) Set the DC offset to +4V. Adjust scope similar to Experiment 1 and print out  $v_i$  and  $v_o$ . Explain the results.
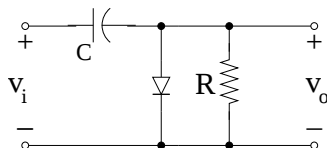
## Experiment 3: Clamp Circuit

Consider the circuit below with a 1N4148 general purpose diode,  $R = 100\text{ k}\Omega$ , and  $C = 100\text{ nF}$ .



*Lab Exercise:*

- 1) Assemble the circuit. Set the function generator to produce a sinusoidal wave with an amplitude of 5 V, zero DC offset, and frequency of 2 kHz. Attach the function generator to  $v_i$ . Attach Scope channel 1 to  $v_i$  and Scope Channel 2 to  $v_o$ . Print out  $v_o$  and  $v_i$  trace.
- 2) Disconnect the function generator without changing the function generator and scope settings. Replace the 100 nF capacitor with a 1 nF one. Print out  $v_o$  and  $v_i$ .
- 3) Compare the two cases. What are your conclusions?