
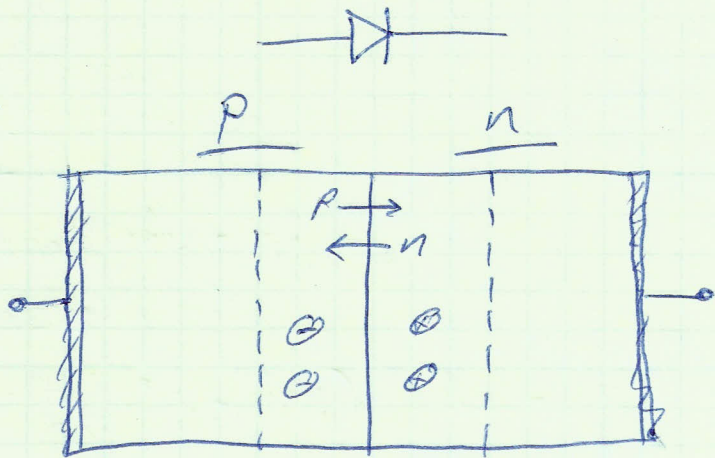

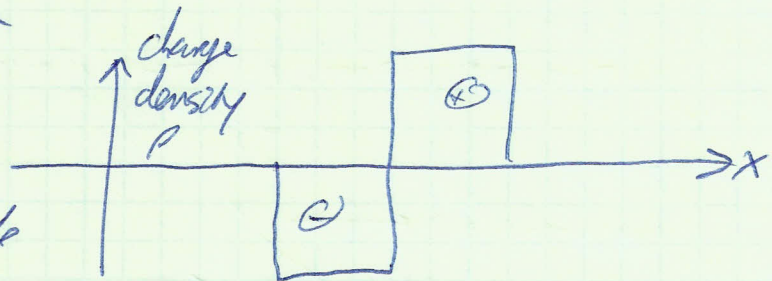
## The Junction Diode

- holes diffuse to n-side
- electrons diffuse to p-side
- these minority carriers recombine, and deplete the majority carriers in a narrow ( $\sim 0.5 \mu\text{m}$ ) region called "depletion region"




- Width is related to dopant density in each side



- Charge density creates electric field in depletion region, and built-in voltage



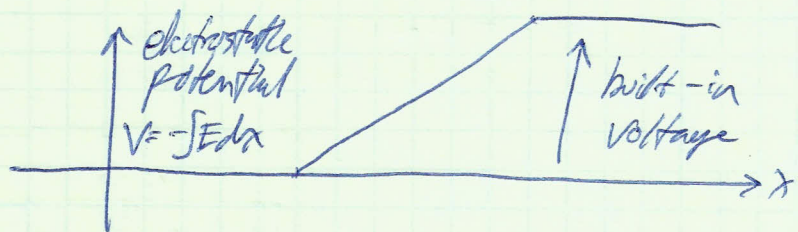- Charge is not due to presence of diffused minority carriers (which have recombined) but due to "unpaired" ions that are exposed





- This cannot be used as a battery or voltage source.

— if attached to a load with no other sources, there will be other voltage drops such as across the contacts, so no current will flow


## I-V characteristics of Diodes

### • Reverse Bias

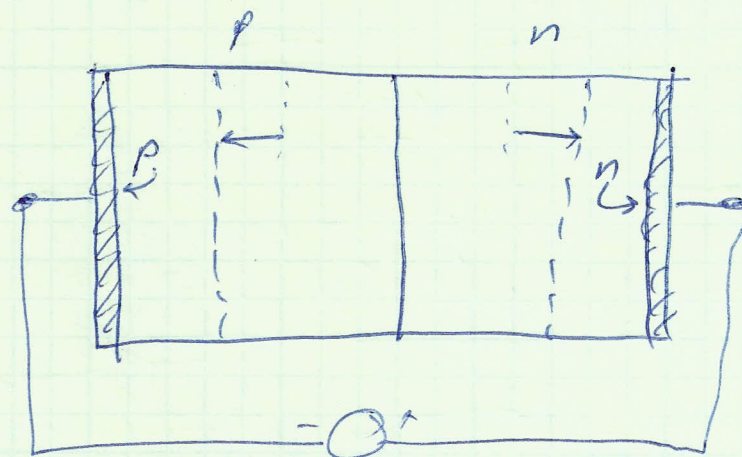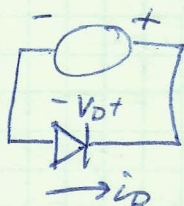

- Some majority carriers flow to the terminals
- p-side becomes more negatively charged, n-side becomes more positively charged
- width of depletion region becomes wider
- potential barrier becomes higher
- no majority carriers can cross the depletion region
- a small current will flow due to minority carriers
  - called "saturation current", typically  $\sim 10^{-9} \text{ A}$  (nA)
  - $i_D = -I_S$
  - $I_S$  is temperature dependent - related to thermal electron-hole pair production
  - $I_S$  doubles every  $\sim 7^\circ \text{C}$  in temperature

### • Forward Bias

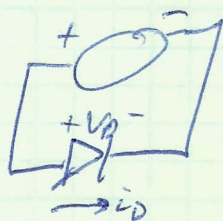

- majority carriers move toward depletion region
- depletion region gets narrower
- potential barrier is reduced
- at high enough voltage, carriers can flow through the depletion region



$$i_D = I_S (e^{V_D/nV_T} - 1)$$

reverse current due to minority carriers  
 $V_T = kT/q \approx 26 \text{ mV at } T = 300 \text{ K}$

• note at  $V_D = 0$ ,  
 $i_D = I_S (1 - 1) = 0$

$$q = 1.6 \times 10^{-19} \text{ C}$$


$$k = 1.38 \times 10^{-23} \text{ J/K}$$

$n$  = emission coefficient

( $n = 2$  for Si diodes,  $1 \leq n \leq 2$  in ICs)

$I_S$  is  $\sim \text{nA}$  range

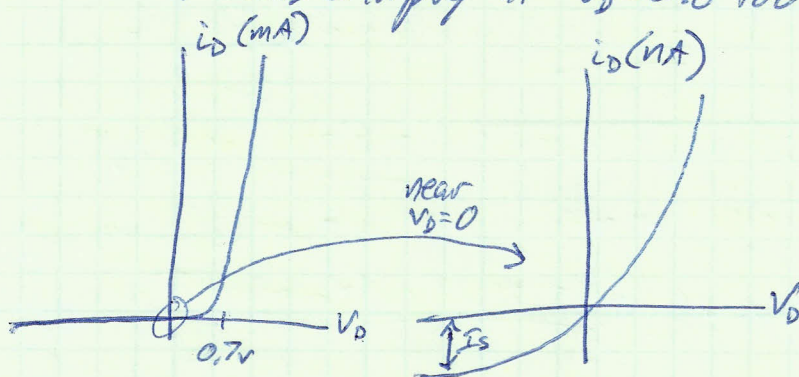Although  $I_S$  is very small,  $e^{V_D/0.05}$  compensates,  
 current rises sharply at  $V_D = 0.6$  to  $0.7 \text{ V}$



Power  $P = i_D V_D$  is dissipated as heat

if high enough currents this can damage the diode


### Reverse Breakdown

- At high enough bias voltage, minority carriers are accelerated through the depletion region
- Impact ionization can create new electron-hole pairs
- Avalanche process leads to sharp increase in current
- Can destroy the diode (except Zener diodes)
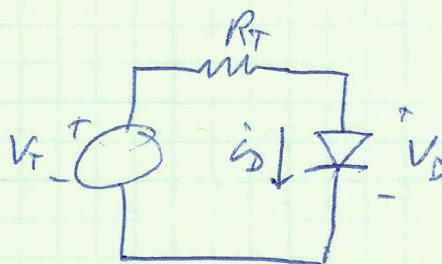
## Solving Diode Circuits

$$① \quad V_T = i_D R_T + V_D$$


$$② \quad i_D = I_S (e^{\frac{V_D}{V_T}} - 1)$$



2 equations and 2 unknowns, but difficult to solve because nonlinear
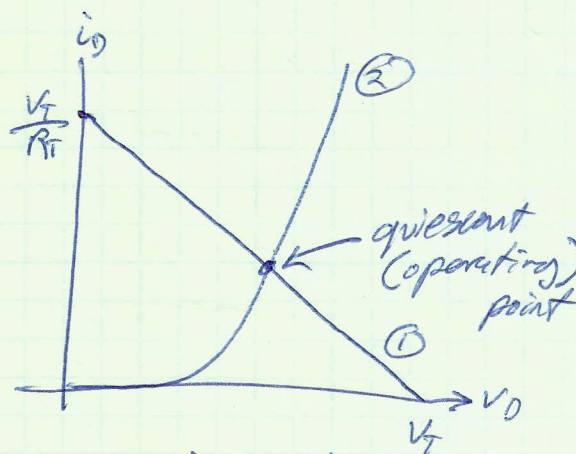
## Load Line


• Useful graphical solution,  
but does not easily give  
numerical result



## Piecewise Linear Model

Diode ON:  $V_D = V_{D0}$ ,  $i_D \geq 0$

Diode OFF:  $i_D = 0$ ,  $V_D < V_{D0}$

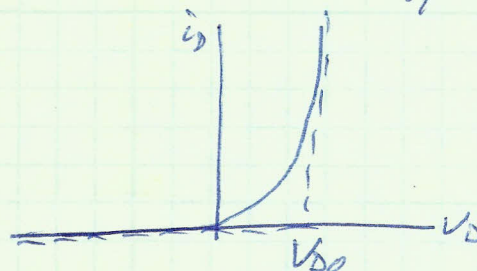


$V_{D0}$  is "cut-in" voltage, for Si:  $V_{D0} \approx 0.6-0.7V$   
for Ge:  $V_{D0} \approx 1.7-1.9V$
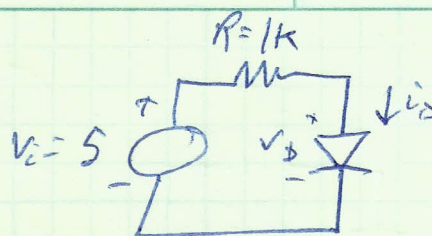
## Recipe for solving:

- ① Write down circuit equations, with  $i_D, V_D$  as parameters
- ② assume either ON or OFF and solve circuit
- ③ check for self-consistency with values of  $i_D, V_D$  that you found



Example

$$V_i = i_D R + V_D$$

$$5 = 10^3 i_D + V_D$$

assume diode is OFF  $\rightarrow i_D = 0$

$$5 = 10^3 \times 0 + V_D \rightarrow V_D = 5V$$

is  $V_D < V_{D0}$  ( $V_{D0} = 0.7V$ )? NO.

assume diode is ON


$$5 = 10^3 i_D + 0.7 \rightarrow i_D = 4.3mA$$

is  $i_D \geq 0$ ? Yes

Diode Circuit Model

Diode ON  $i_D \geq 0$

Diode OFF  $V_D < V_{D0}$

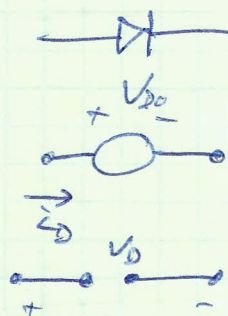

- Can use the same procedure, but check for self-consistency