
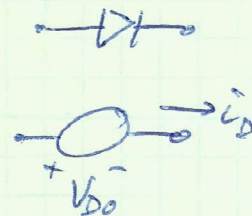


Model for Zener Diodes

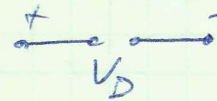
$$\text{ON} : V_D = V_{D0}, \quad i_D \geq 0$$





$$\text{OFF} : -V_Z < V_D < V_{D0}, \quad i_D = 0$$



$$\text{Zener Region} : V_D = -V_Z, \quad i_D \leq 0$$

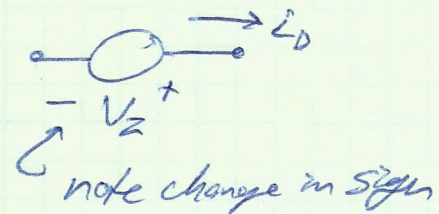A Simple Power Supply

- Assume that a power supply has some variation or ripple
- Zener diodes can be used to take out the ripple

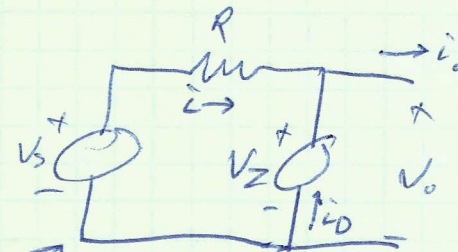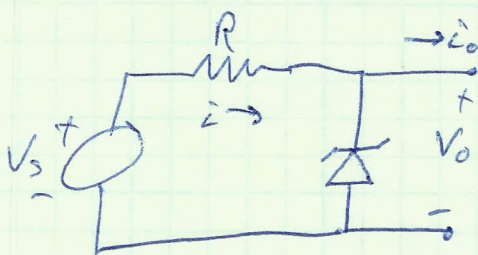

Case 1: Zener region

$$V_O = V_Z = \text{constant}$$

output voltage is independent of i_O - ideal voltage source

$$\text{KCL} : i_D = i - i_O$$

$$\text{KVL} : V_S = R i + V_Z \rightarrow i_D = i - \frac{V_S - V_Z}{R} \leq 0$$

- As long as this condition is satisfied, diode will be in Zener region


$$\rightarrow i_O \leq \frac{V_S - V_Z}{R}$$

Case 2: Reverse bias region

$$i_D = 0$$

$$i = i_0$$


$$V_S - Ri_0 = V_0$$

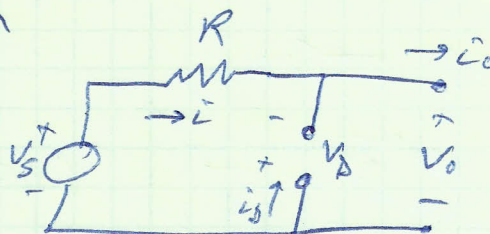

- Output voltage drops as more current is drawn from circuit


Case 3: forward bias region

not possible - V_S is positive.

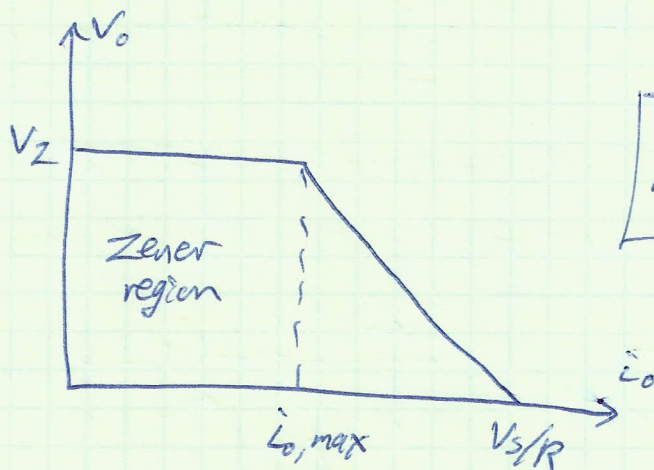


$$i_{0,max} = \frac{V_S - V_Z}{R}$$

- In reality, there is a slight slope to the Zener region of the curve
~ real voltage sources are made with transistors and opamps, etc.

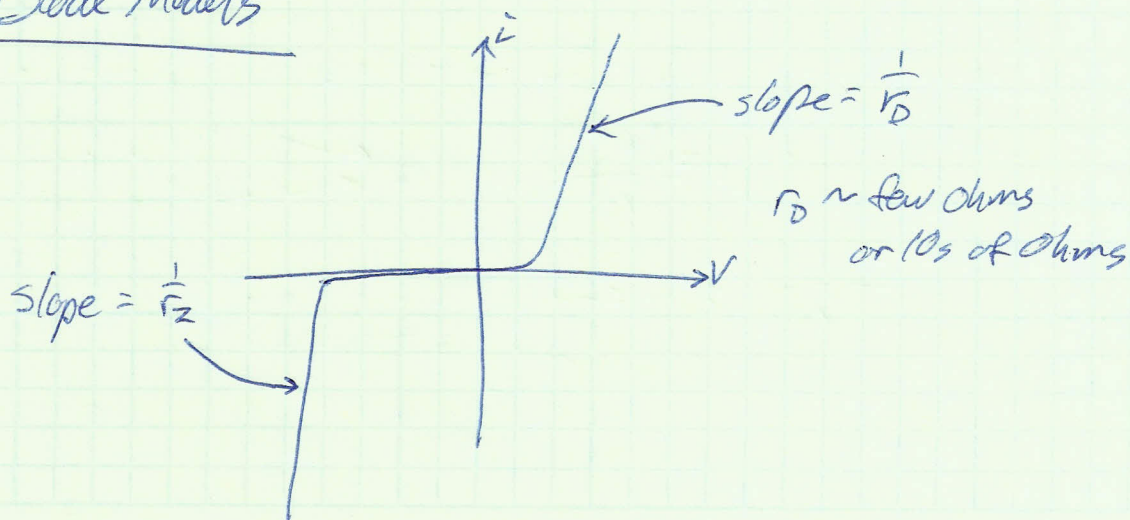Other Diode Models

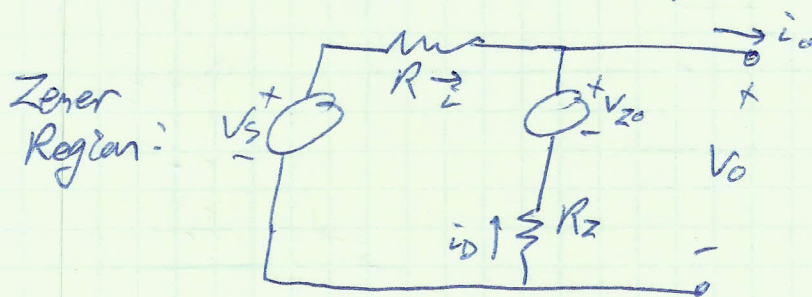For Zener Diode, model as voltage source with resistor



$$i_D + i = i_o$$

$$V_s = R \cdot i + V_{Z0} - R_z i_D$$

Solve for i_D to see if in Zener region ($i_D < 0$)

$$V_s = R(i_o - i_D) + V_{Z0} - R_z i_D$$

$$i_D = - \frac{V_s - V_{Z0} - R i_o}{R + R_z}$$

$$i_D < 0 \text{ when } i_o < \frac{V_s - V_{Z0}}{R} \quad (\text{same as before})$$

$$V_o = V_{Z0} + R_z i_D$$

$$V_o = V_{Z0} + R_z \frac{V_s - V_{Z0} - R i_o}{R + R_z}$$

$$V_o = \frac{R V_{Z0} + R_z V_s}{R + R_z} - \frac{R R_z}{R + R_z} i_o$$



$\hat{V}_{Z0}$ modified V_{Z0} , slightly higher than V_{Z0}

$$\text{assume } R_z \ll R \rightarrow R_z \parallel R \approx R_z$$

$$V_o = \hat{V}_{Z0} - R_z i_o$$

- circuit looks like voltage source $\hat{V}_z$ with output resistance R_z


More additional diode types

We have already covered:

- Zener diodes
- Schottky diodes
- light emitting diodes


There are also:

- Varactor Diodes

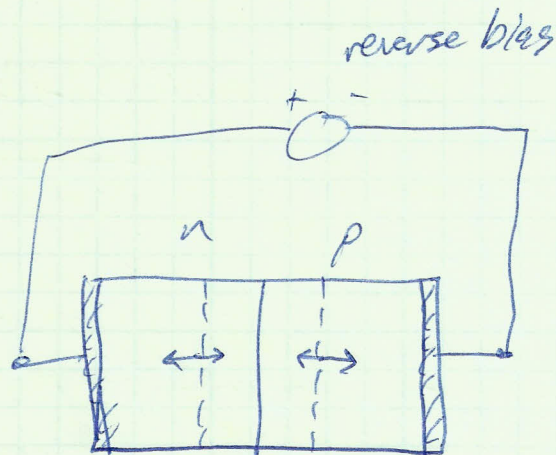

- depletion region moves in response to applied voltage
- appears as capacitor whose width depends on voltage

- Photodiodes

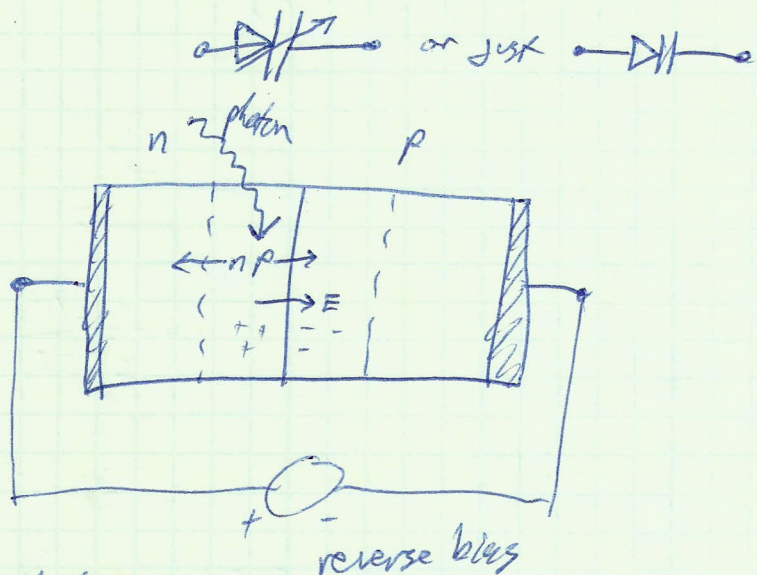

- photon generates electron-hole pair
- current is proportional to light hitting the detector
- these are often PIN diodes

enlarged
depletion
region

