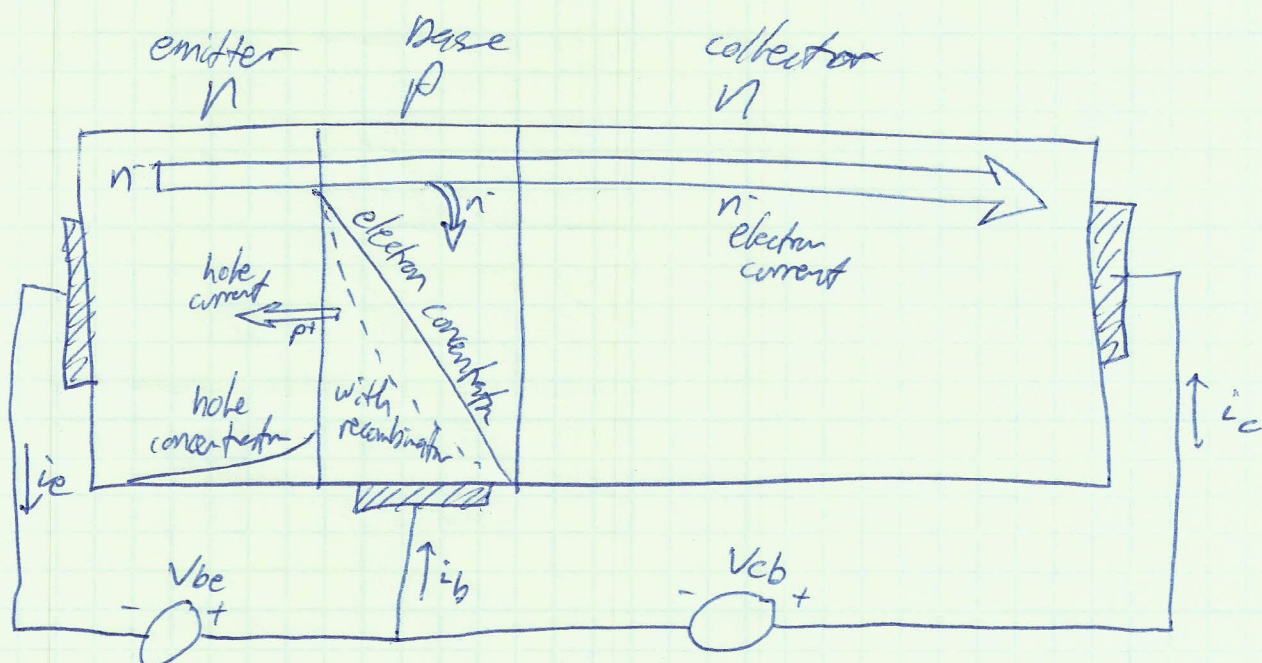


Bipolar Junction Transistors (BJTs)



Six parameters = $i_b, i_e, i_c, V_{be}, V_{ce}, V_{bc}$

using KVL, KCL: $i_e = i_c + i_b$, $V_{bc} = V_{be} - V_{ce}$

only four independent parameters: i_b, i_c, V_{be}, V_{ce}


→ these specify IV characteristics of transistor

Principle of operation:

- In active mode: emitter base junction is forward-biased
collector base junction is reverse-biased
- Level of doping in emitter is much higher than in the base
→ electron current is much greater than hole current into emitter
- Bias conditions set up a concentration gradient across base
→ very high near emitter, very low near collector
→ causes diffusion current across base
→ electrons that reach collector are swept over to collector contact

- Emitter current is primarily electrons, and a small hole current into base
- Base current is small hole current and small electron recombination current
- Collector current is most of the electrons from the emitter

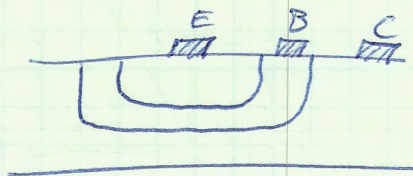Typical design: Base is thin, and lightly doped
Emitter is heavily doped



- Note that current flows across base-collector junction even though it is reverse-biased. It is caused by concentration gradient in base, set up by base-emitter junction
- Number of holes going into emitter (proportional to i_B) is a constant fraction of number of electrons going into base (proportional to i_C)
This ratio depends on doping and design

$$\frac{i_C}{i_B} = \beta \quad \text{— defined as common emitter current gain}$$

typical value is ~ 200

(about 200 electrons travel for each hole)

Mode	E-B Junction	C-B Junction
cutoff	reverse	reverse
active	forward	reverse
saturation	forward	forward

cutoff mode

B-E junction reverse biased, $i_B = 0 \rightarrow i_C = 0$



active mode

most of the current flows to the collector

$$i_C = I_S (e^{V_{BE}/V_T} - 1) \approx I_S e^{V_{BE}/V_T}$$

$$i_B = \frac{I_S}{\beta} (e^{V_{BE}/V_T} - 1) \approx \frac{I_S}{\beta} e^{V_{BE}/V_T}$$

model for cutoff and active circuits:

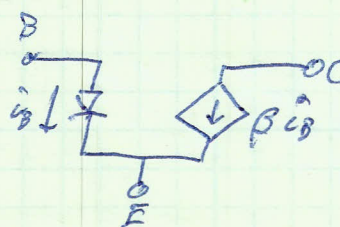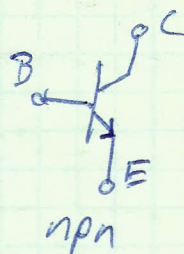saturation mode

when $V_{CE} \leq V_{DO}$, B-C junction becomes forward biased

extra holes injected into base from collector recombine with electrons



$\rightarrow$ reduce collector current

$$i_C/i_B < \beta$$

"soft saturation" may be considered as around $V_{CE} = 0.4V$ ($V_{CE} = 0.3V$)

as transistor behaves similarly to active mode, i_C/i_B not yet reduced significantly

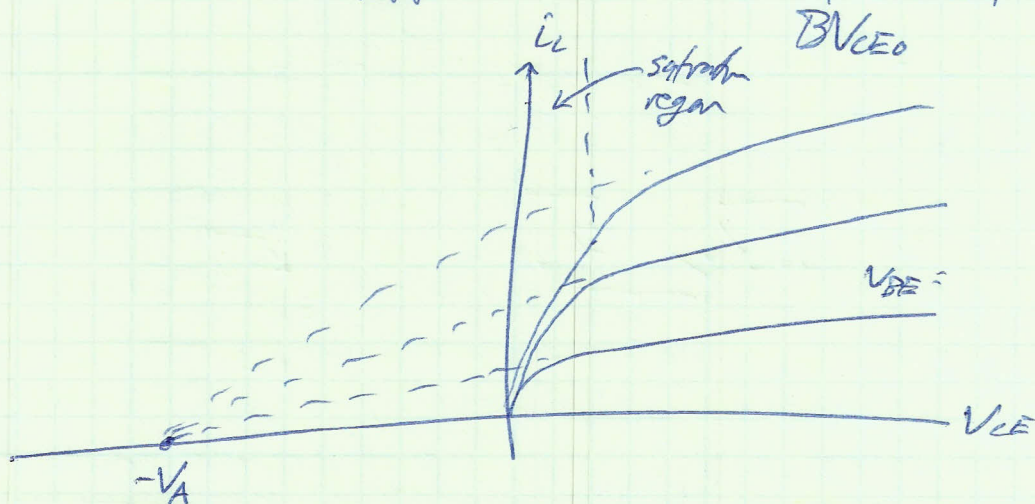
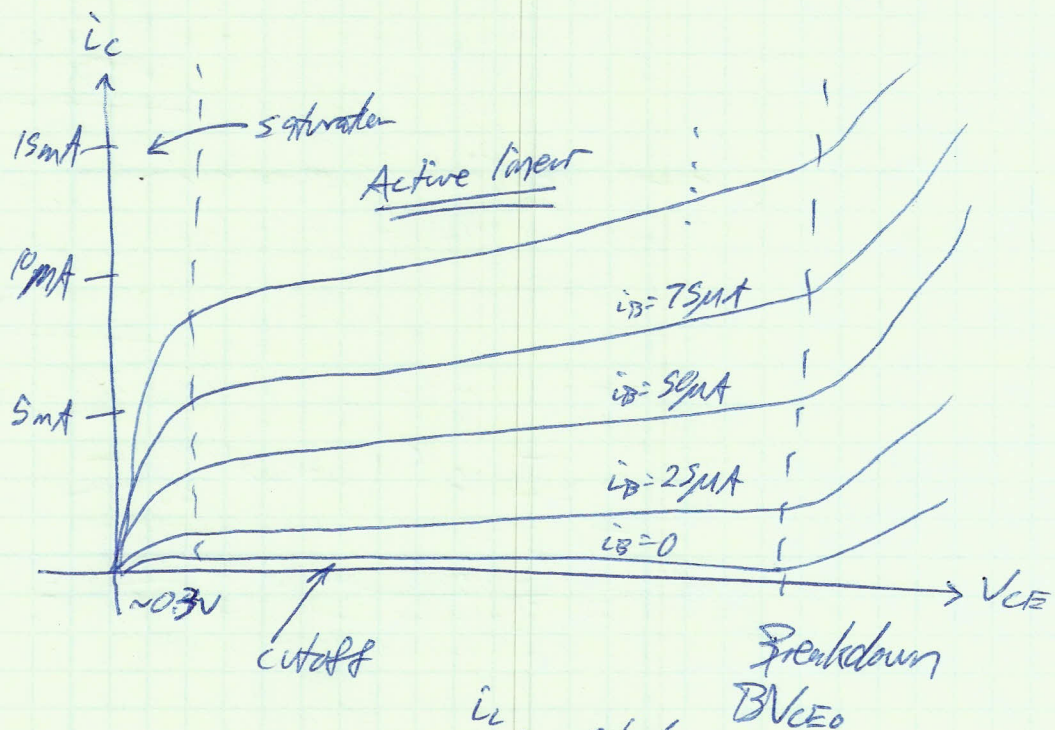
$\rightarrow$ slightly forward biased, but not yet to turn-on



- The slope of the i_C curves in the active region is due to the dependence of the depletion region width on V_{CE}
- Wider depletion region $\rightarrow$ narrower effective base width
- V_A known as "Early voltage"
 - typically $50-100V$

$$i_C = I_S e^{V_{BE}/V_T} \left(1 + \frac{V_{CE}}{V_A} \right)$$

$$i_B = \frac{I_S}{\beta} e^{V_{BE}/V_T} \quad \text{note } i_B \text{ equation doesn't change}$$

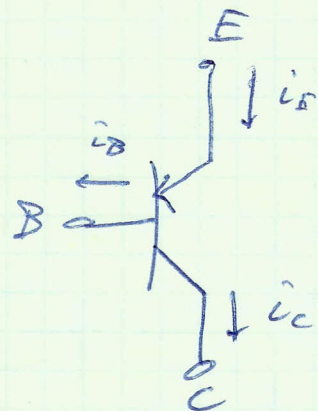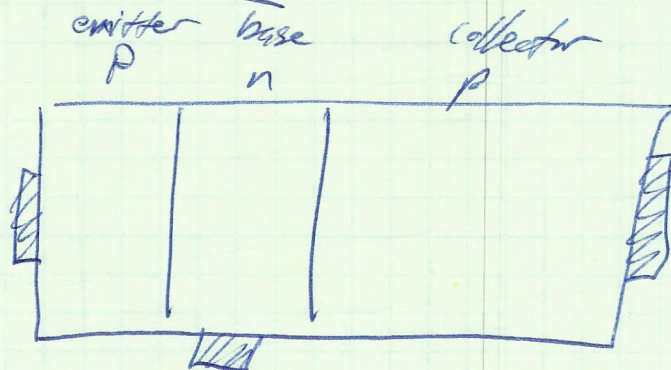PNP transistor

- holes move slower than electrons (lower mobility)
so pnp transistors are typically slower
- usually used in pairs with npn transistors

Summary

cutoff: $i_B = 0, i_C = 0$

active: $i_B = \frac{I_S}{\beta} e^{\frac{V_{BE}}{nV_T}}, i_C = I_S e^{\frac{V_{BE}}{nV_T}} \left(1 + \frac{V_{CE}}{V_A}\right)$

saturation: $i_B = \frac{I_S}{\beta} e^{\frac{V_{BE}}{nV_T}}, i_C < \beta i_B, V_{CE} = 0.1 - 0.3V$

- known as "large signal model"
- low frequency model - does not include capacitance