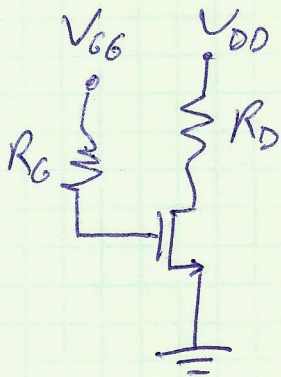


MOSFET fixed bias

- Similar to BJT fixed bias
- Not stable



- No current through R_G
- not necessary, but needed if coupling capacitors are used



$$V_{GS} = V_{GG}$$

$$I_D = \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_T)^2 = \frac{1}{2} k_n' \frac{W}{L} (V_{GG} - V_T)^2$$

$$DS-KVL: I_D R_D + V_{DS} = V_{DD}$$

$$\rightarrow V_{DS} = V_{DD} - \frac{1}{2} k_n' \frac{W}{L} R_D (V_{GG} - V_T)^2$$

- Subject to variations in k_n' and V_T which vary with temperature

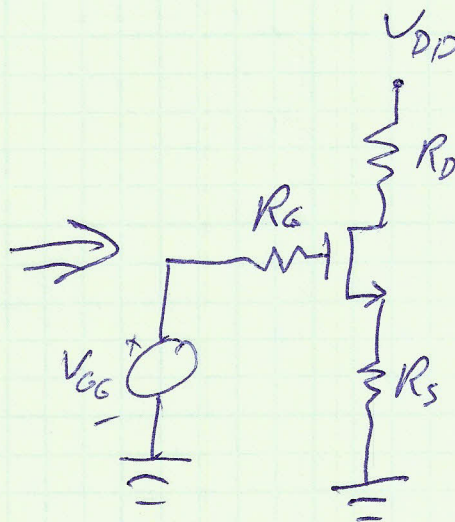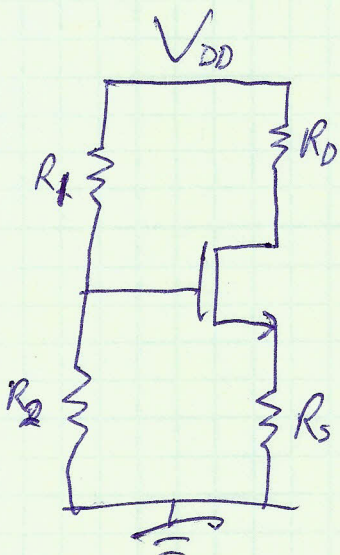MOSFET bias with source degeneration

Thevenin
equivalent
 R_G, V_{GG}

$$V_{G6} = \frac{R_2}{R_1 + R_2} V_{DD}, \quad R_G = R_1 \parallel R_2$$

GS-KVL:

$$V_{G6} = V_{GS} + I_D R_S$$

$$I_D = \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_T)^2$$

} can solve for V_{GS} and I_D

DS-KVL:

$$V_{DD} = I_D R_D + V_{DS} + I_D R_S \quad \leftarrow \text{can solve for } V_{DS}$$

Negative feedback: $V_{GS} = V_{G6} - R_S I_D$

- increase in I_D causes decrease in V_{GS} which causes decrease in I_D .
- not constant because of quadratic relationship but variations are much smaller with feedback
- Don't need to worry about $R_B \ll (1+\beta)R_E$ as in BJT because $I_G = 0$, so R_1 and R_2 can be large (MΩ)

Self Bias - uses R_C as feedback resistor



note $V_{CE} = R_C I_C + V_{BE}$

$$= R_C I_C + V_{DO} > V_{DO}$$

Transistor is always in active mode

$$V_{CC} = R_C I_1 + R_B I_B + V_{BE}, \text{ and } I_1 = I_C + I_B$$

$$= R_C (I_C + I_B) + R_B I_B + V_{BE}$$

$$= R_C I_C + (R_B + R_C) \frac{I_C}{\beta} + V_{BE}$$

$$I_C = \frac{V_{CC} - V_{BE}}{R_C + (R_B + R_C) \frac{1}{\beta}} \approx \frac{V_{CC} - V_{BE}}{R_C} \quad \text{If } R_B \ll (\beta - 1) R_C$$

$$\hookrightarrow \text{note } \frac{R_C + R_B}{\beta} \ll R_C \rightarrow R_C R_B \ll \beta R_C \rightarrow R_B \ll R_C (\beta - 1)$$


Bias point is stable and independent of β

• Negative feedback illustrated here:

$$\text{BE-KVL: } I_B = \frac{V_{CC} - V_{BE} - I_C R_C}{R_B}$$

Increase in I_C will decrease I_B , which decreases I_C

MOSFET self bias

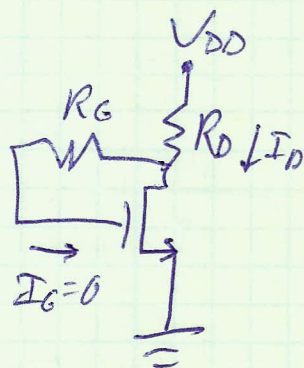

• Transistor always in Saturation $V_{DS} = V_{GS} > V_{GS} - V_T$

$$V_{DD} = I_D R_D + V_{GS}$$

$$I_D = \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_T)^2$$


} can find I_D and V_{GS}

Note: R_D does not affect bias, but cannot be removed

- Removing R_D would mean direct connection from input to output of amp.


Current Mirrors

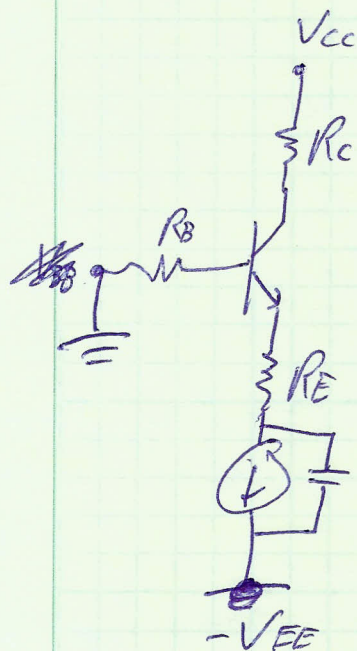- Purpose of stable bias circuit is I_C or I_D independent of transistor parameters and temperature variation
- Can also use current bias



Note that capacitor is needed for signal to pass
 Otherwise current would be constant, including AC part
 Only necessary for ideal current sources
 Not needed with the designs we will use

Identified Transistors

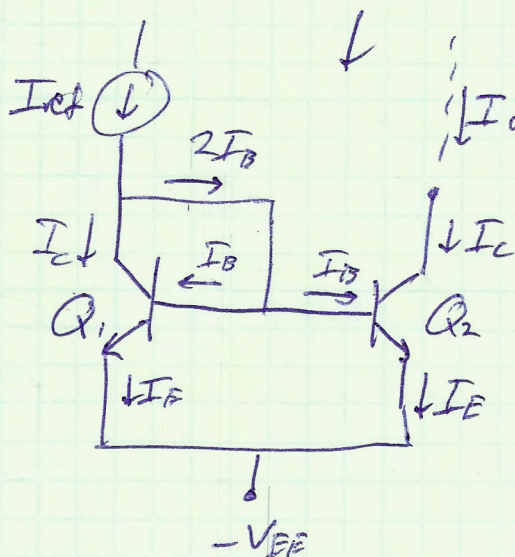

- Q_1 is ON because of I_{ref}
- $V_{CE1} = V_{BE1} = V_{D0} \rightarrow$ active
- $V_{BE2} = V_{BE1} \rightarrow I_{C2} = I_{C1}$
- If Q_2 also in active state:


$$I_B = \frac{I_C}{\beta}, \quad I_0 = I_C = \beta I_B$$

$$I_{ref} = I_C + 2I_B = (\beta + 2)I_B$$

$$\frac{I_0}{I_{ref}} = \frac{\beta}{\beta + 2} = \frac{1}{1 + 2/\beta} \approx 1$$

- $I_0 = I_{ref}$, no matter what is attached to Q_2
- For Q_2 in active state, V_{CE2} must be $\geq V_{D0}$


Current can be set with simple resistor

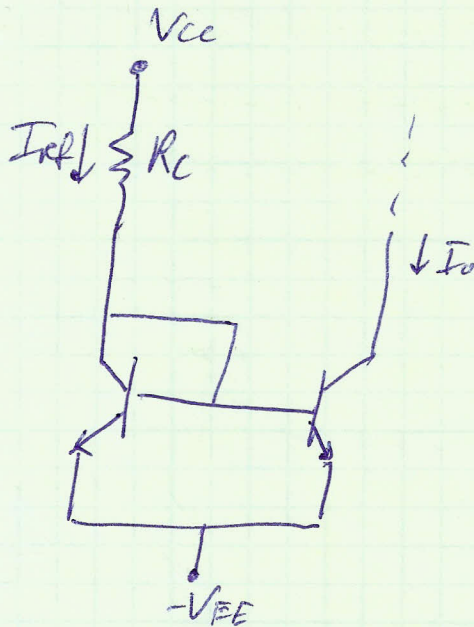

$$V_{CC} = I_{ref} R_C + V_{BE1} - V_{EE}$$

$$I_{ref} = \frac{V_{CC} + V_{EE} - V_{DO}}{R_C} = \underline{\text{constant}}$$

Example

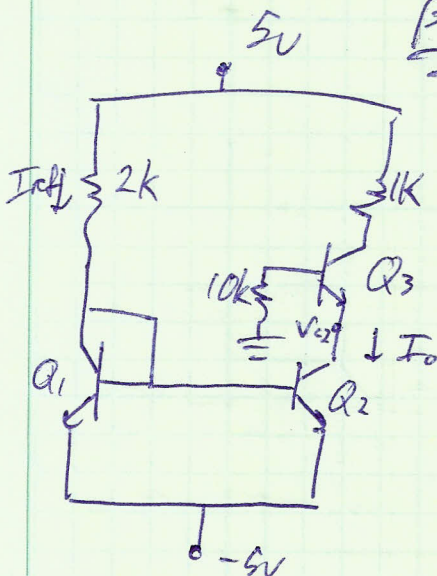

$$BE1-KVL: 5 = 2k I_{ref} + V_{BE1} - 5$$

$$I_{ref} = 4.65 \text{ mA}$$

$$I_{E3} \approx I_O \approx 4.65 \text{ mA}$$

$$I_{B3} = \frac{I_{E3}}{1+\beta} = 46 \mu\text{A}$$

$$I_{C3} = I_{E3} - I_{B3} = 4.6 \text{ mA}$$

$$BE3-KVL: 0 = 10k \cdot I_{B3} + V_{BE3} + V_{C2}$$


$$\rightarrow V_{C2} = -1.16 \text{ V}$$

$$Q_2 \text{ is active: } V_{CE2} = V_{C2} - (-5) = 3.84 \text{ V} > V_{DO}$$



$$CE3-KVL: 5 = 1k \cdot I_{C3} + V_{CE3} + V_{C2}$$

$$\rightarrow V_{CE3} = 1.56 \text{ V} > V_{DO}$$

Q3 is active

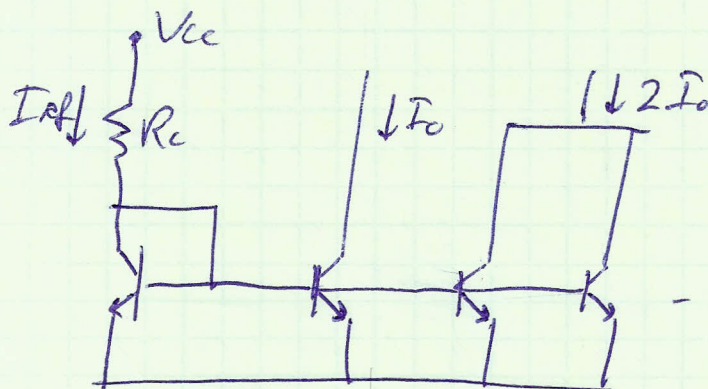Other current mirrorsmultiple outputs

can also sum currents

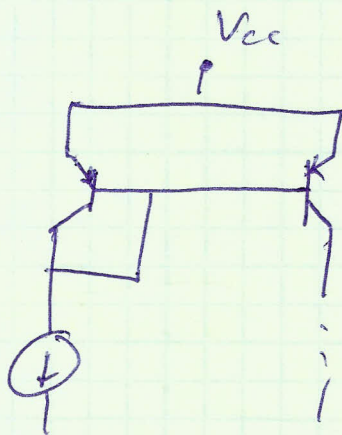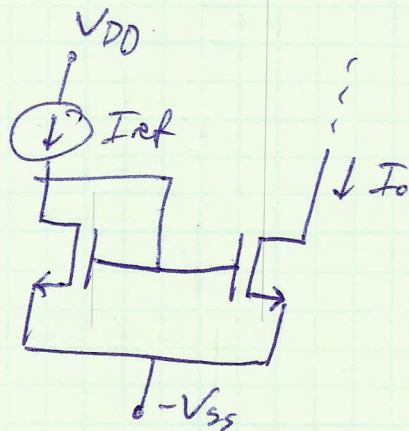PNP versionFET version