
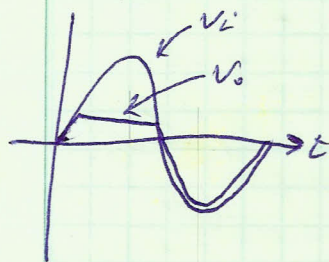


Small Signal Model

- Nonlinear devices behave as linear in small signal limit

Consider clipper circuit:

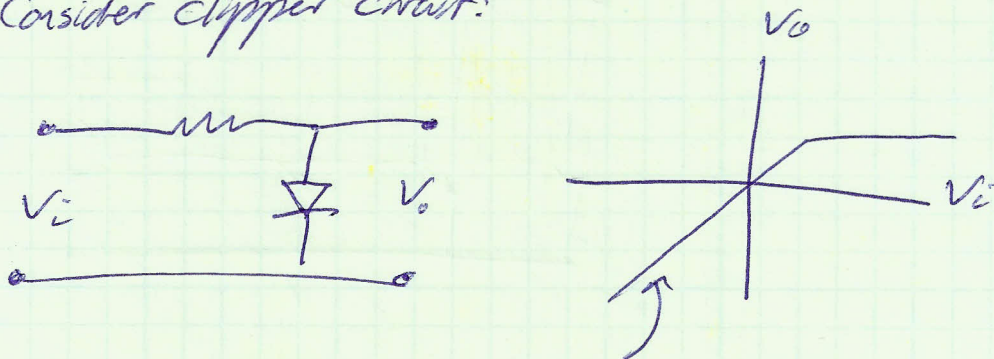

- circuit obviously behaves linearly here
- If we add 2 input voltages, we get sum at output
- Even in the clipped region if we add 2 input voltages, we will see something at the output

Example: $V_i = 5 + 0.05 \cos \omega t$

$\uparrow$ $\uparrow$ signal
 bias

- With our piecewise linear model, $V_o = 0.7V$ always
- In reality, $V_o = 0.6921 + 0.0008 \cos \omega t$ (simulate it!)
- If we double the input signal, $V_i = 5 + 0.1 \cos \omega t$
 we get double the output signal: $V_o = 0.6921 + 0.0012 \cos \omega t$



The clipper circuit behaves linearly for small signals

- Sine wave in $\rightarrow$ Sine wave out
- proportional to input (double input $\rightarrow$ double output)
- we could also add other frequency components
- this is why we can build linear amplifiers with nonlinear devices
- devices must always be in one state, e.g. ON, active, etc.
- note that any nonlinear function can be approximated by its tangent line for values close to a given point

We can see this from the Taylor series expansion:

$$f(x_0 + \Delta x) = f(x_0) + \Delta x \left. \frac{df}{dx} \right|_{x=x_0} + \frac{(\Delta x)^2}{2!} \left. \frac{d^2f}{dx^2} \right|_{x=x_0} + \dots$$

If Δx is small, $(\Delta x)^n$ is small for $n=2, 3, \dots$


Diode small signal model

$$i_D(V_D + v_d) \approx i_D(V_D) + v_d \left. \frac{di_D}{dV_D} \right|_{V_D=V_D}$$

$$= I_D + v_d \left. \frac{di_D}{dV_D} \right|_{V_D=V_D}$$

$\uparrow$
bias current

$\nwarrow$ response to signal

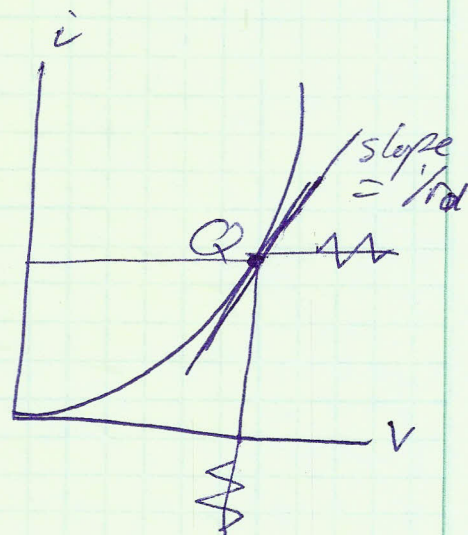

Diode response to small signal is like a resistor

$$i_d = v_d / r_d$$

$$r_d \equiv \left(di_d / dv_d |_{v_d = v_D} \right)^{-1}$$

r_d is inverse of slope of tangent line at bias point

find r_d from full expression for diode current:

$$i_D = I_S e^{v_D / nV_T}$$

$$\frac{di_D}{dv_D} = \frac{1}{nV_T} \times I_S e^{v_D / nV_T}$$



$$\left. \frac{di_D}{dv_D} \right|_{v_D = v_D} = \frac{1}{nV_T} I_S e^{v_D / nV_T} = \frac{I_D}{nV_T}$$

$$r_d = \frac{nV_T}{I_D}$$


I_D is the bias current

r_d changes with temperature through V_T

bias analysis (large sig.)

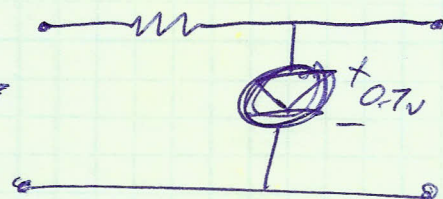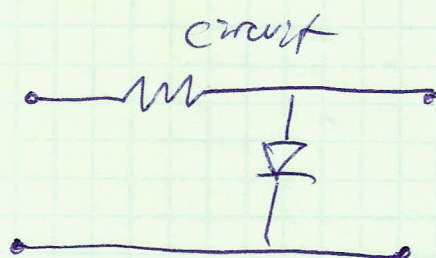

small signal analysis

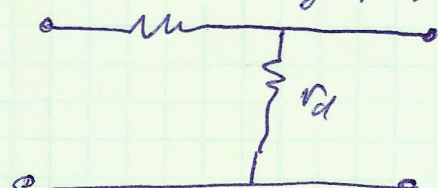


Bias analysis $\rightarrow$ set signal to zero

$$R = 750 \Omega, \quad V_i = 5 + 0.05 \cos \omega t \rightarrow V_i = 5$$

$$V_i = I_D R + V_D$$

$$5 = 750 I_D + 0.7$$

$$I_D = 5.73 \text{ mA}$$

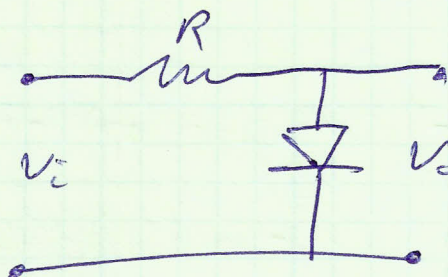

Small signal analysis

$$r_d = \frac{n V_T}{I_D}$$


$n = 2$ for discrete Si diodes
 $V_T = 25 \text{ mV}$ at 300 K

$$r_d = \frac{2 \times 25 \times 10^{-3}}{5.73 \times 10^{-3}} = 8.73 \Omega$$

$$V_{i1} = \frac{r_d}{r_d + R} \times 0.05 \cos \omega t = 0.00058 \cos \omega t$$

$$V_o = 700 + 0.58 \cos \omega t \quad (\text{mV})$$

Voltage-controlled attenuator

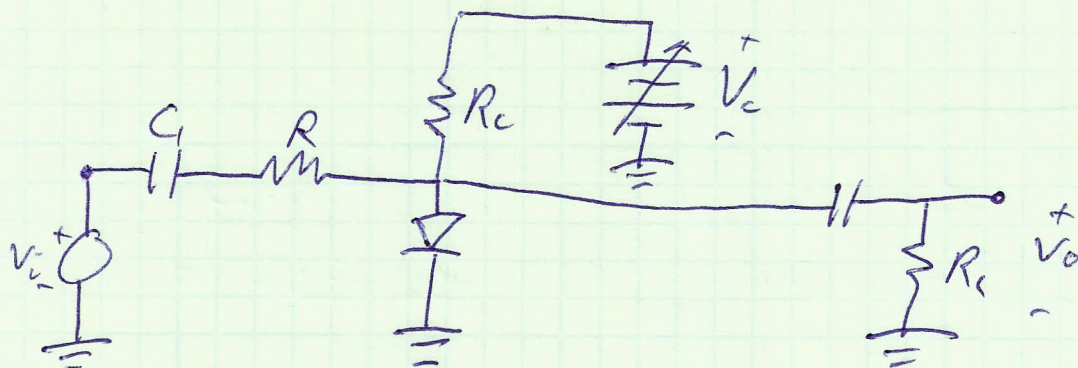

Bias: $I_D = \frac{V_c - V_{D0}}{R_c}$

(note: capacitors are open circuits at DC)

Small signal: define $R_p \equiv R_c \parallel r_D \parallel R_L$

These all appear in parallel when $V_c = 0$

(note: capacitors are short circuits for the signal)

$$\frac{V_o}{V_i} = \frac{R_p}{R_p + R}$$

for $r_D \ll R_c$ and $r_D \ll R_L$, $R_p \approx r_D$

$$\boxed{\begin{aligned} \frac{V_o}{V_i} &= \frac{r_D}{r_D + R} \\ r_D &= \frac{nV_T}{I_D} = \frac{nV_T R_c}{V_c - V_{D0}} \end{aligned}}$$

$$V_c \uparrow \dots \frac{V_o}{V_i} \downarrow$$