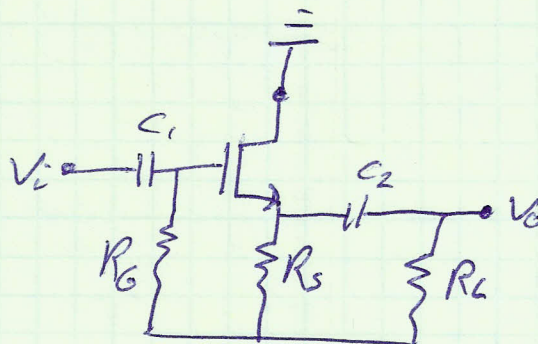



# Common Drain and Common Collector Amplifiers

## • Common Drain (Source follower)


- Note: Drain is grounded for small signals, so it is the "common" terminal of input and output




- Several circuits reduce to this form:

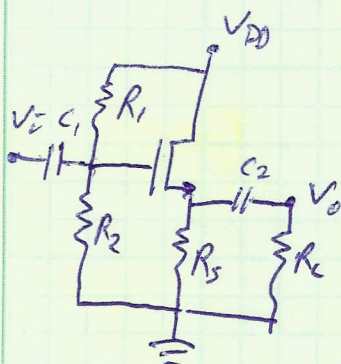

$$R_G = R_1 \parallel R_2$$


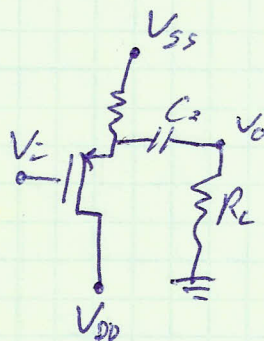


$$R_G \rightarrow \infty$$

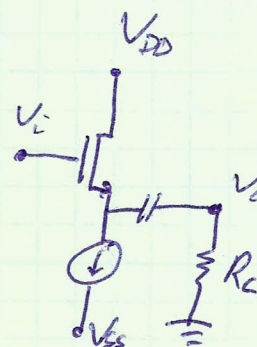

$$R_G \rightarrow \infty, R_S \rightarrow \infty$$

Replace MOSFET with small signal model

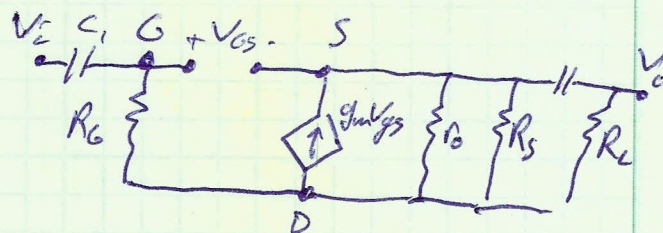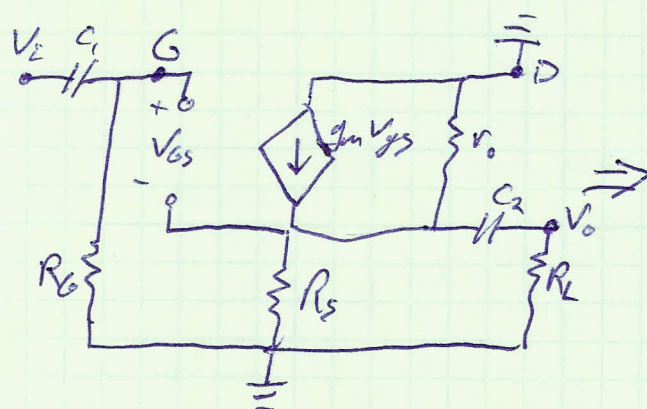

- Note that  $R_S$  parallel to  $R_L$ . In practice,  $R_S$  often replaced by the load
- define  $R_L' = R_S \parallel R_L$
- open-loop gain found by setting  $R_L' \rightarrow \infty$

$$V_{gs} = V_i - V_o$$

$$V_o = g_m V_{gs} (r_o \parallel R_L') = g_m (r_o \parallel R_L') (V_i - V_o)$$

$$A_v = \frac{V_o}{V_i} = \frac{g_m (r_o \parallel R_L')}{1 + g_m (r_o \parallel R_L')} = \frac{g_m r_o R_L'}{r_o + R_L' + g_m r_o R_L'} \approx \frac{g_m R_L'}{1 + g_m R_L'}$$

↑ use  $g_m r_o \gg 1$  to drop this term  
then divide top + bottom by  $r_o$

to find open-loop gain, set  $R_L' \rightarrow \infty$ ,  $r_o \parallel R_L' = r_o$

$$A_{v_o} = \frac{g_m r_o}{1 + g_m r_o} \approx 1$$


Because  $A_{v_o} \approx 1$ ,  $V_o = V_s \approx V_g = V_i \rightarrow$  output "follows" input voltage  
 $\rightarrow$  called source follower

Input resistance:

$$R_i = R_G \text{ — no analysis needed}$$

Output resistance:

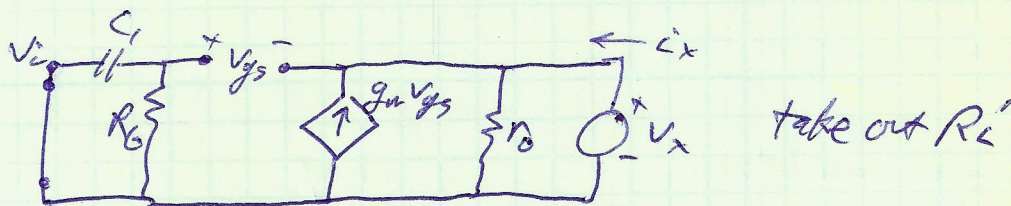Zero out  $V_i$ , then find Thevenin resistance seen at output



$$V_{gs} = V_i - V_x = -V_x$$


$$i_x = -g_m V_{gs} + \frac{V_x}{r_o} = V_x \frac{g_m r_o + 1}{r_o}$$

$$R_o = \frac{r_o}{1 + g_m r_o} \approx \frac{1}{g_m} \rightarrow \text{typically small — a few hundred } \Omega$$


- Source follower has unity gain, but transforms high impedance to low impedance  
— often used as a buffer or for the final stage in power amplifiers
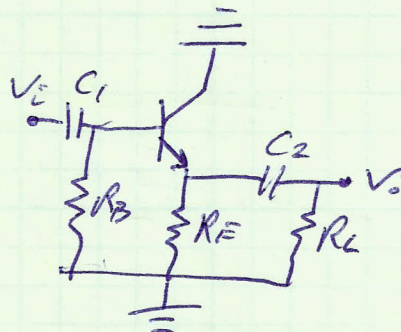
## Common Collector or Emitter Follower


- Same basic idea as source follower
- Note we have zeroed out the bias sources
- Many circuits can be reduced to this form
- Define  $R_L' = R_E \parallel R_L$



Small signal model:

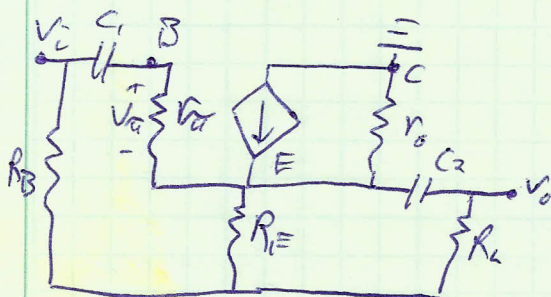

$\Rightarrow$

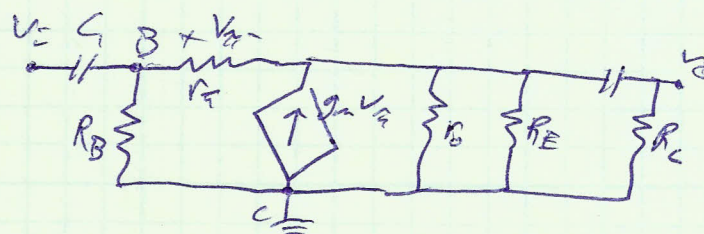

note  $V_{be} = V_i - V_o$

$i_b = V_{be} / r_{be}$

$g_m r_o = \beta \gg 1$

total current flowing through  $r_o$  and  $R_L'$  is  $i_b$  and  $g_m V_{be}$

$$V_o = (g_m V_{be} + \frac{V_{be}}{r_o}) (r_o \parallel R_L') \approx g_m V_{be} (r_o \parallel R_L') = g_m (r_o \parallel R_L') (V_i - V_o)$$

$$A_v = \frac{V_o}{V_i} \approx \frac{g_m (r_o \parallel R_L')}{g_m (r_o \parallel R_L') + 1} = \frac{g_m r_o R_L'}{r_o + R_L' + g_m r_o R_L'} \approx \frac{g_m R_L'}{1 + g_m R_L'}$$

$$A_v = \frac{R_L'}{R_L' + r_e} \quad \text{where } r_e \equiv \frac{1}{g_m}, \text{ typically a few tens of ohms}$$

$$A_{vo} = \frac{g_m r_o}{1 + g_m r_o} \approx 1$$

known as Emitter Follower

To find  $R_i$ :

$$i_i = \frac{v_i}{R_B} + i_b \quad (\text{KCL}) \quad (\text{KVL})$$

$$v_i = i_b r_\pi + (i_b + g_m v_\pi)(r_o \parallel R_i) = i_b [r_\pi + (1 + g_m r_\pi)(r_o \parallel R_i)]$$

$$i_i = \frac{v_i}{R_B} + i_b = \frac{v_i}{R_B} + \frac{v_i}{r_\pi + (1 + \beta)(r_o \parallel R_i)}$$


$$\frac{1}{R_i} = \frac{i_i}{v_i} = \frac{1}{R_B} + \frac{1}{r_\pi + (1 + \beta)(r_o \parallel R_i)}$$

$$R_i = R_B \parallel [r_\pi + (1 + \beta)(r_o \parallel R_i)]$$

- note  $R_i$  depends on  $R_L \rightarrow$  this amplifier is not unilateral

To find  $R_o$ :

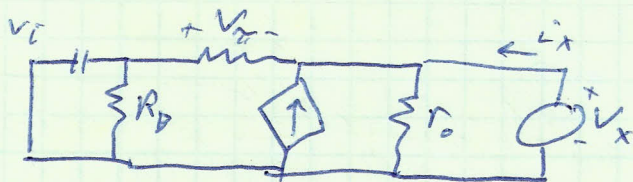Zero out  $v_i$ , Remove  $R_i$ , attach  $V_x$



$$i_x = g_m v_\pi + \frac{V_x}{r_o} + \frac{V_x}{r_\pi}$$

note  $v_\pi = -V_x$

$$\frac{1}{R_o} = \frac{1}{g_m} + \frac{1}{r_o} + \frac{1}{r_\pi} \rightarrow R_o = (1/g_m) \parallel r_o \parallel r_\pi \approx 1/g_m = r_e$$

Since  $g_m r_\pi \gg 1$ ,  $g_m r_o \gg 1$

- Unit gain, large input resistance, small output resistance