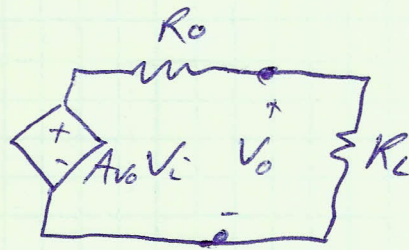


Low-Frequency Response

$$A_v = \frac{V_o}{V_i} = \frac{R_L}{R_o + R_L} A_{v_0}$$

capital V s are phasors

$$\frac{V_i}{V_{sig}} = \frac{R_i}{R_i + R_{sig} + \frac{1}{sC_i}} \quad \underline{s = j\omega}$$

• This will have the form of constant-frequency voltage divider $\times$ frequency response

$$\frac{V_i}{V_{sig}} = \underbrace{\frac{R_i}{R_i + R_{sig}}}_{\text{constant}} \times \frac{s}{s + \omega_{p1}}$$

↪ could set $C \rightarrow \infty$ to find this part, then use that to find ω_{p1}

$$\frac{V_i}{V_{sig}} = \underbrace{\frac{R_i}{R_i + R_{sig} + \frac{1}{sC_i}} \cdot \frac{R_i + R_{sig}}{R_i}}_{\text{constant}} \cdot \frac{R_i}{R_i + R_{sig}}$$

$$\hookrightarrow = \frac{R_i + R_{sig}}{R_i + R_{sig} + \frac{1}{sC_i}} = \frac{s}{s + \frac{1}{C_i(R_i + R_{sig})}} = \frac{s}{s + \omega_{p1}}$$

$$\omega_{p1} = 2\pi f_{p1} = \frac{1}{C_i(R_i + R_{sig})}$$

$$\frac{V_o}{V_{sig}} = \frac{R_i}{R_i + R_{sig}} \times A_v \times \frac{s}{s + \omega_{p1}}$$

More general approach for finding poles:

(have the students taken a linear systems or control class yet?)

• For transfer function $\frac{V_o}{V_i} = \frac{\text{polynomial in } s}{\text{other polynomial in } s}$

• we can find poles and zeros


zeros: let numerator = 0, solve for s

poles: let denominator = 0, solve for s

• Our circuits will not have any zeros, but have one pole for each capacitor

Pole from capacitor at output

example: common drain amplifier

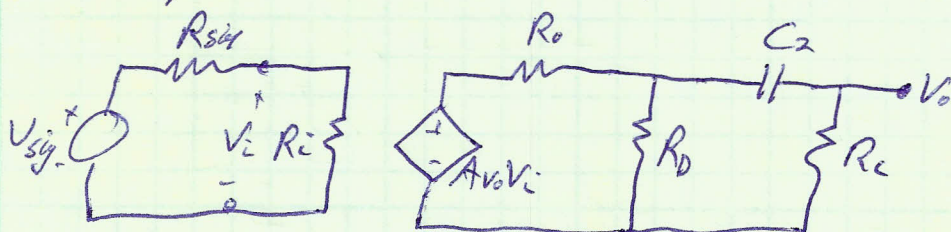

$$\frac{V_o}{V_{sig}} = \frac{R_L}{R_L + R_{sig}} \times A_v \times \frac{s}{s + \omega_{p2}}$$

$$\omega_{p2} = 2\pi f_{p2} = \frac{1}{C_2 (R_L + R_O \parallel R_O)}$$

for unilateral amplifiers, this is the correct value of f_{p2} from C_2

However if not unilateral (R_i depends on R_L) then R_i will include C_2


- note $R_L' = R_O \parallel (R_L + \frac{1}{sC_2})$

How to find poles by inspection:

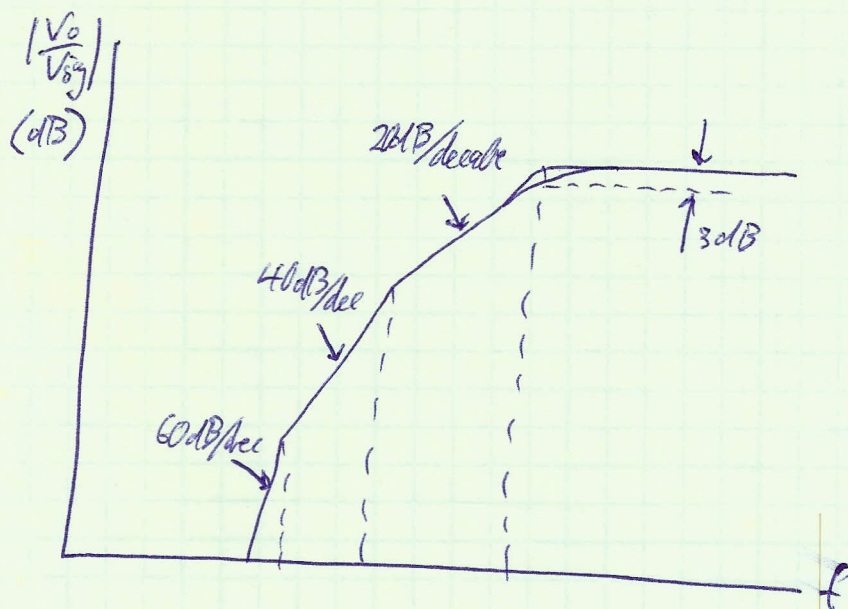1. Zero out V_{sig}
2. Consider each capacitor separately (others are shorts)
3. Compute the total effective resistance between capacitor terminals
the pole is given by $f_p = \frac{1}{2\pi RC}$

• the total response is:

$$\frac{V_o}{V_{sig}} = A_v \times \frac{s}{s + \omega_{p1}} \times \frac{s}{s + \omega_{p2}} \times \frac{s}{s + \omega_{p3}} \times \dots$$



- If the poles are very far apart, then low frequency cutoff is highest pole
- If they are nearby, $f_c \approx f_{p1} + f_{p2} + f_{p3} + \dots$


Note: Output resistance is R_o (output resistance with $V_i = 0$)

R_{out} is output resistance with $V_{sig} = 0$

pole for C_2 includes $\frac{R_i}{R_i + R_{sig}}$ term when not unilateral

same formulas can be used, but replace R_o with R_{out}

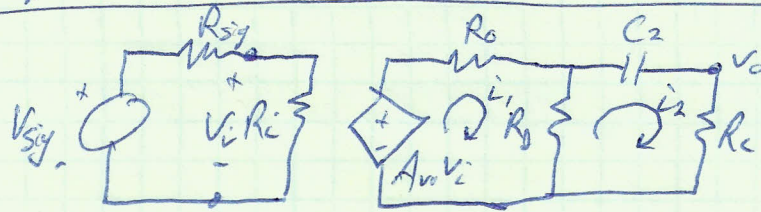compare hard way and easy way to find f_p



$$A_v V_i - R_0 i_1 - R_0 (i_1 - i_2) = 0$$

$$+ R_0 (i_2 - i_1) + \frac{1}{sC_2} i_2 + R_L i_2 = 0$$

$$A_v V_i - i_1 (R_0 + R_0) + i_2 R_0 = 0$$

$$i_2 (R_0 + \frac{1}{sC_2} + R_L) = i_1 R_0$$

$$A_v V_i - i_2 \frac{(R_0 + R_0)(R_0 + \frac{1}{sC_2} + R_L)}{R_0} + i_2 R_0 = 0$$

$$i_1 = i_2 \frac{R_0 + \frac{1}{sC_2} + R_L}{R_0}$$

$$A_v V_i = i_2 \left[\frac{(R_0 + R_0)(R_0 + \frac{1}{sC_2} + R_L)}{R_0} - R_0 \right]$$

$$\text{note } V_o = i_2 R_L \\ \rightarrow i_2 = \frac{V_o}{R_L}$$

$$A_v V_i = \frac{V_o}{R_L} []$$

$$A_v \frac{V_i}{V_o} = \frac{1}{R_L} [] \rightarrow 0 \text{ to find pole. Solve for } s$$

$$(R_0 + R_0)(R_0 + \frac{1}{sC_2} + R_L) = R_0^2$$

$$R_0 R_0 + R_0^2 + (R_0 + R_0)(\frac{1}{sC_2} + R_L) = R_0^2$$

$$(R_0 + R_0)(\frac{1}{sC_2} + R_L) = -R_0 R_0$$

$$\frac{1}{sC_2} + R_L = \frac{-R_0 R_0}{R_0 + R_0}$$

$$\frac{1}{sC_2} = \frac{-R_0 R_0}{R_0 + R_0} - R_L$$


$$s = \frac{-1}{C_2 (R_L + R_0 || R_0)}$$

$$f_{p2} = \frac{1}{2\pi C_2 (R_L + R_0 || R_0)}$$

Now, by inspection =

Zero at $V_{sig} \rightarrow V_i = 0$ too

then $A_v V_i = 0$

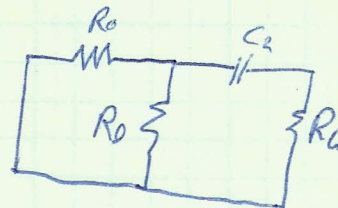

$$f_{p2} = \frac{1}{2\pi C_2 (R_L + R_0 || R_0)}$$