
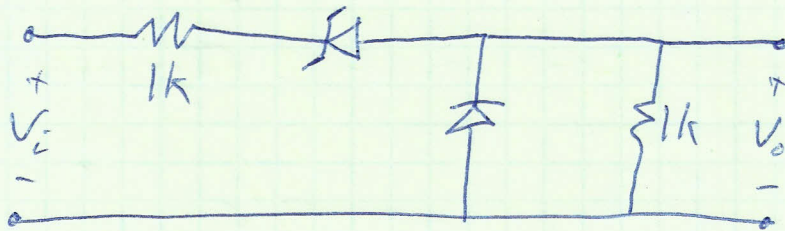

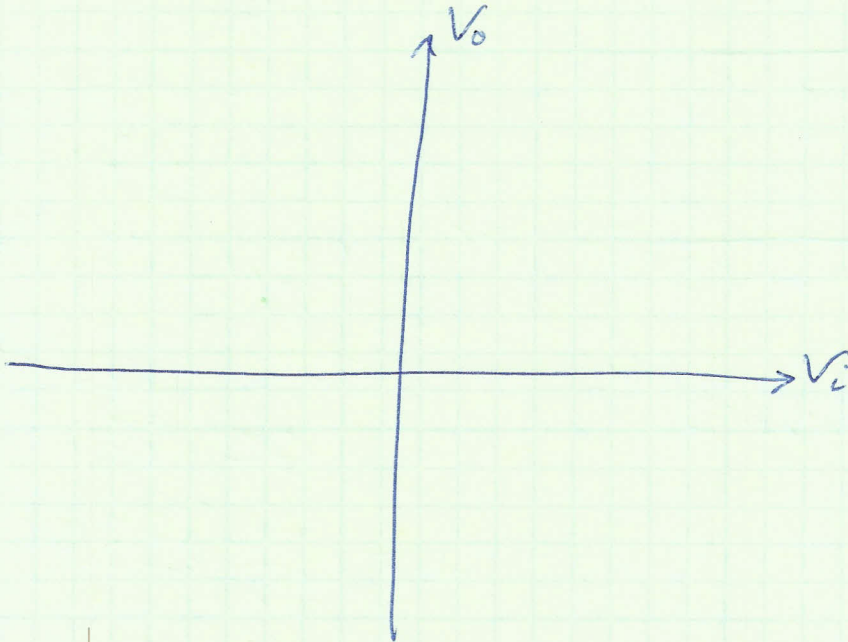
### Problem 1:

Find the transfer function,  $V_o$  for all possible  $V_i$ , and plot it.




$$V_{D0} = 0.7V$$
$$V_Z = 4V$$



Can you solve other similar networks of diodes, zener diodes, and resistors?
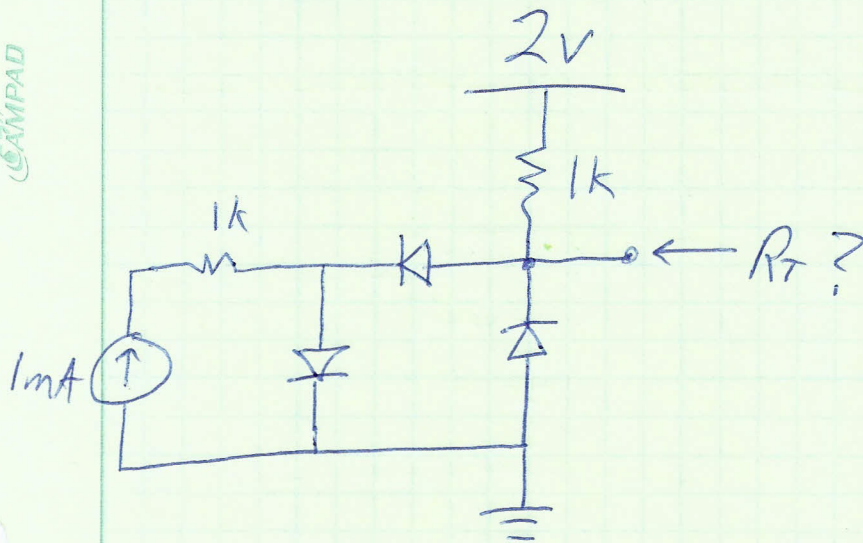
## Problem 2:

Find the small signal Thevenin resistance at the node shown  
Assume discrete silicon diodes at  $300^\circ\text{K}$




Can you find the small signal model for other networks of diodes, resistors, and current/voltage sources?
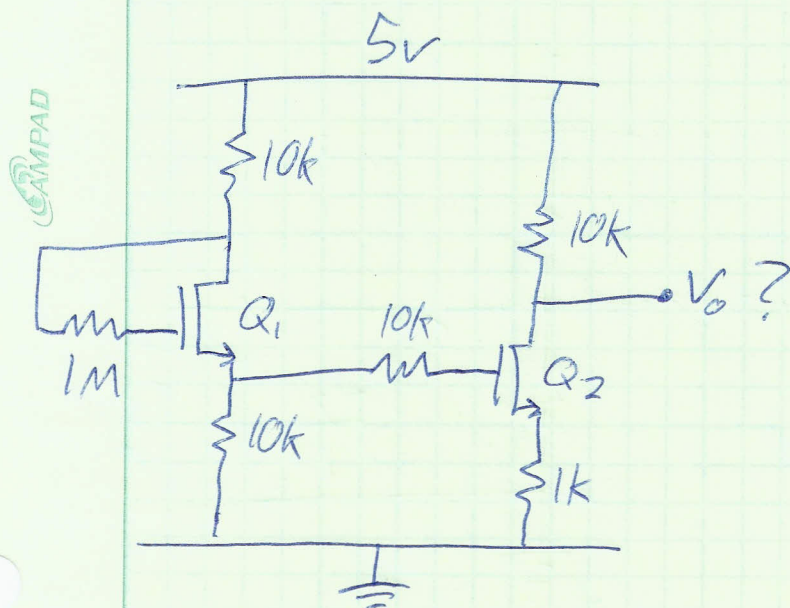
### Problem 3:

Determine the state of both transistors, and  $V_o$

Assume  $k_n' \frac{W}{L} = 1 \text{ mA/V}^2$  and  $V_t = 1 \text{ V}$ .




What conditions would put the transistors in different states?

Can you solve similar problems with other bias states and connections? What about BJTs?
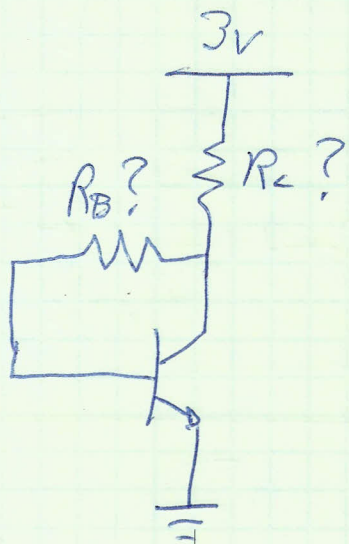
### Problem 4:

Design the following bias circuit so that it is stable with respect to variations in  $\beta$  from 100 to 200. Also design the circuit so that  $I_C = 1\text{mA}$ .




Can you design stable bias circuits for other transistor parameters and bias conditions? Can you design other stable bias circuits?
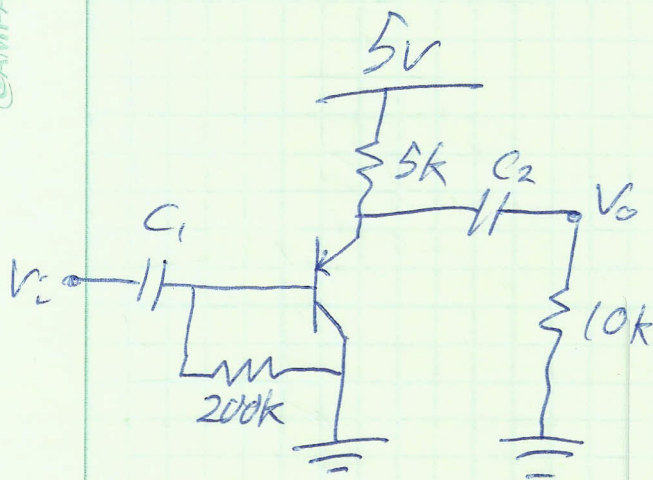
### Problem 5:

Find  $A_v$ ,  $R_i$ , and  $R_o$  for the amplifier below.

Assume  $\beta = 200$ ,  $V_A = 50\text{V}$ , and a discrete Silicon BJT at  $300\text{K}$ .  
Ignore the Early effect for determining bias conditions.



Can you find the amplifier parameters for other types of amplifier circuits? What about with FETs?


### Problem 6:

Determine the low frequency cutoff for this amplifier.

Assume  $k_n' \frac{W}{L} = 1 \text{ mA/V}^2$ ,  $\lambda = 0.02 \text{ V}^{-1}$ , and  $V_T = 1 \text{ V}$

Ignore channel width modulation for determining bias conditions.

Assume  $R_{sig} = 0$ .

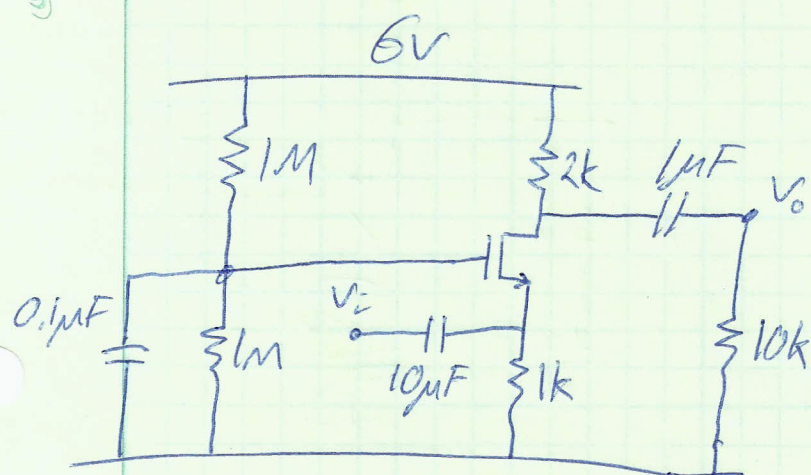

Can you find the low frequency cutoff for other types of amplifier circuits? What about BJTs?