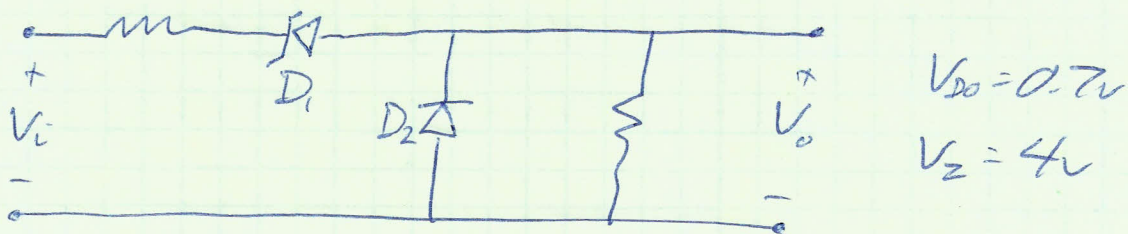


Problem 1:

Find the transfer function, V_o for all V_i , and plot it



As V_i is decreased from 0V, V_o will remain 0 until D_1 turns ON at $-0.7V$

for $V_i < -0.7V$, $V_o = \frac{V_i + 0.7}{2}$, D_1 is ON and D_2 is OFF

as V_i is decreased from $-0.7V$, D_2 will remain OFF until $V_o = -0.7V$


$$\frac{V_i + 0.7}{2} = -0.7$$

$$V_i = -2.1V$$

for $V_i < -2.1V$, $V_o = -0.7V$

As V_i is increased from 0V, V_o will remain 0 until $V_i > V_Z$

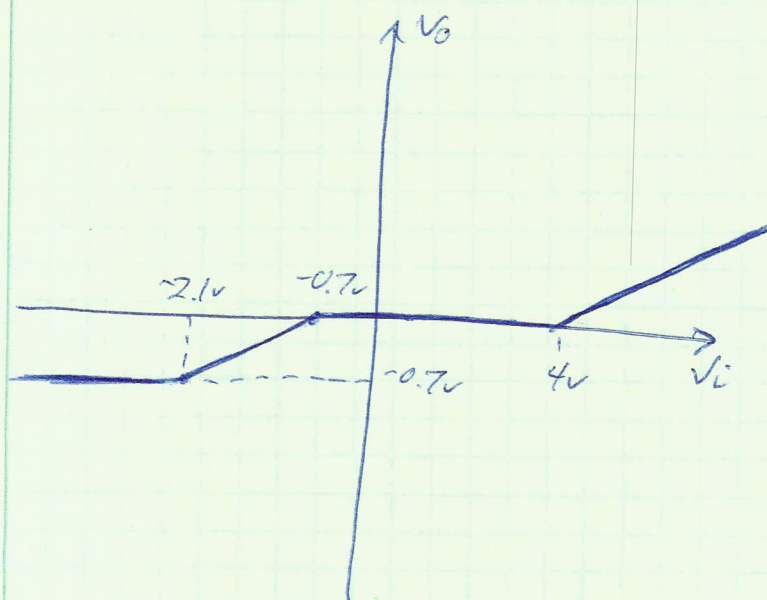for $V_i > 4V$, $V_o = \frac{V_i - 4}{2}$



for $V_i < -2.1V \rightarrow V_o = -0.7V$


for $-2.1V < V_i < -0.7V \rightarrow V_o = \frac{V_i + 0.7}{2}$

for $-0.7V < V_i < 4V \rightarrow V_o = 0$

for $V_i > 4V \rightarrow V_o = \frac{V_i - 4}{2}$

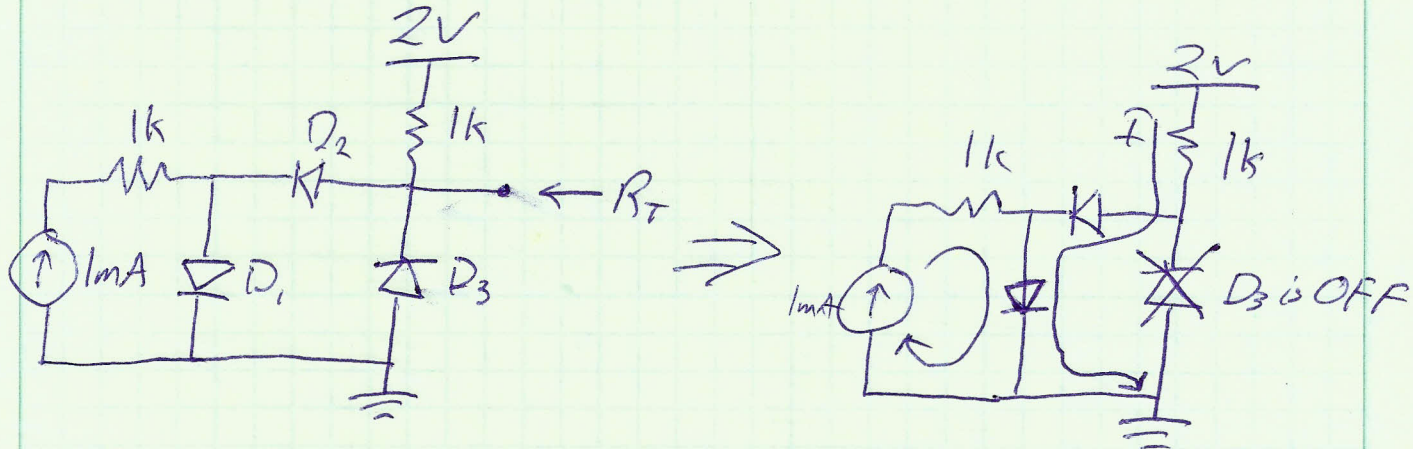Problem 2:

Find the small signal Thevenin resistance at the node shown.
Assume discrete silicon diodes at 300°K .



$$2\text{V} - I \cdot 1\text{k} - V_{D2} - V_{D3} = 0$$


$$2 - 1.4 = I \cdot 1\text{k}$$

$$I = \frac{0.6}{1\text{k}} = 0.6\text{mA}$$

$$I_{D2} = 0.6\text{mA} \rightarrow r_{D2} = \frac{nV_T}{I_{D2}} = \frac{2 \times 25\text{mV}}{0.6\text{mA}} = \frac{0.05}{0.6\text{mA}} = 83\Omega$$

$$I_{D1} = 1.6\text{mA} \rightarrow r_{D1} = \frac{0.05\text{V}}{1.6\text{mA}} = 31\Omega$$

Small signal model:

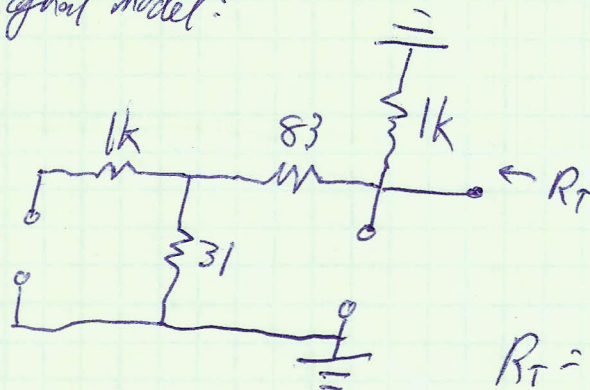


$$R_T = 1\text{k} \parallel (83 + 31)$$

$$\underline{\underline{R_T = 102\Omega}}$$

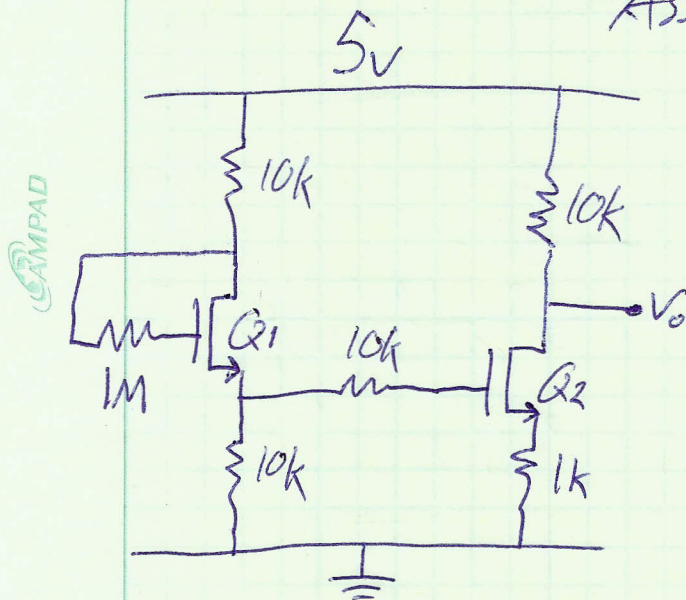Problem 3:

Determine the state of both transistors, and V_o

Assume $k_n' \frac{W}{L} = 1 \text{ mA/V}^2$ and $V_T = 1 \text{ V}$



Self-bias ensures that Q_1 is in saturation

$$5\text{V} - 10\text{k} \cdot I_{D1} - V_{GS1} - 10\text{k} \cdot I_{D1} = 0$$

$$I_D = \frac{5\text{V} - V_{GS1}}{20\text{k}} = \frac{1}{2} k_n' \frac{W}{L} (V_{GS1} - V_T)^2$$

$$5 - V_{GS1} = 10 (V_{GS1}^2 - 2V_{GS1} + 1)$$

$$5 - V_{GS1} = 10V_{GS1}^2 - 20V_{GS1} + 10$$

$$10V_{GS1}^2 - 19V_{GS1} + 5 = 0$$

$$V_{GS1} = \frac{19 \pm \sqrt{361 - 4 \times 10 \times 5}}{20}$$

$$V_{GS1} = \frac{19 \pm 13}{20} = 1.6\text{V} \text{ or } 0.3\text{V}$$

0.3V would be in cutoff, not consistent

$$V_{GS1} = 1.6\text{V}$$

$$I_{D1} = \frac{5\text{V} - 1.6\text{V}}{20\text{k}} = 0.17\text{mA}$$

$$V_{S1} = 1.7\text{V} = V_{G2}$$

$$V_{GS2} = 1.7\text{V} - 1\text{k} \cdot I_{D2}$$

$$I_{D2} = \frac{1.7\text{V} - V_{GS2}}{1\text{k}} = \frac{1}{2} k_n' \frac{W}{L} (V_{GS2} - V_T)^2$$

$$1.7\text{V} - V_{GS2} = 0.5 (V_{GS2}^2 - 2V_{GS2} + 1)$$

$$3.4 - 2V_{GS2} = V_{GS2}^2 - 2V_{GS2} + 1$$

$$V_{GS2}^2 = 2.4$$

$$V_{GS2} = 1.5\text{V} \text{ or } -1.5\text{V}$$

-1.5V is not physical

$$V_{GS2} = 1.5\text{V}$$

$$I_{D2} = \frac{1.7\text{V} - 1.5\text{V}}{1\text{k}} = 0.2\text{mA}$$

$$V_o = 5\text{V} - 10\text{k} \cdot 0.2\text{mA}$$

$$\underline{V_o = 3\text{V}}$$


$$V_{DS2} = 3\text{V} - 1\text{k} \cdot 0.2\text{mA} = 2.8\text{V}$$

$$V_{DS2} > V_T \rightarrow \underline{\text{saturation}} \checkmark$$

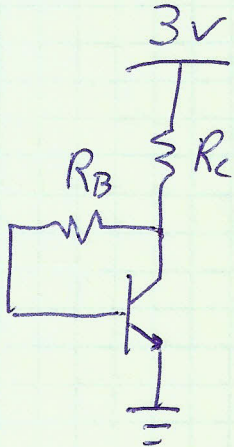Problem 4:

Design the following bias circuit so that it is stable with respect to variations in β from 100 to 200.

Also design the circuit so that $I_C = 1\text{mA}$.



$$V_{CC} - (I_B + I_C)R_C - I_B R_B - V_{BE} = 0$$

$$V_{CC} - R_C I_C - (R_C + R_B) \frac{I_C}{\beta} - V_{BE} = 0$$

$$I_C = \frac{V_{CC} - V_{BE}}{R_C + (R_C + R_B)/\beta}$$

$$\text{Stable with respect to } \beta \text{ if } \frac{R_C + R_B}{\beta} \ll R_C$$

$$R_C + R_B \ll \beta R_C$$

$$R_B \ll (\beta - 1) R_C$$

$$\text{Then } I_C \approx \frac{V_{CC} - V_{BE}}{R_C}$$

$$1\text{mA} = \frac{3 - 0.7}{R_C}$$

$$R_C = \frac{3 - 0.7}{1\text{mA}} = \underline{2.3\text{k}\Omega}$$

$$R_B = 0.1 \times (\beta - 1) R_C = 0.1 \times 99 \times 2.3\text{k}\Omega$$


$$\underline{R_B = 2.2\text{k}\Omega}$$

Problem 5:

Find A_v , R_i , and R_o for the amplifier below.

Assume $\beta = 200$, $V_A = 50V$, for Silicon discrete BJT at $300^\circ K$.

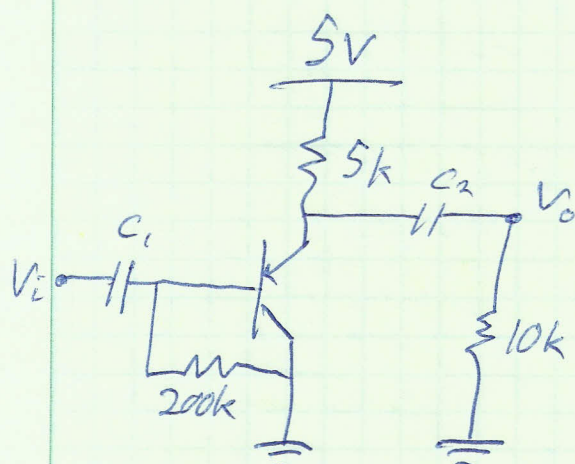Ignore the Early effect for determining bias conditions.



$$5V - 5k(\beta + 1)I_B - 0.7V - 200kI_B = 0$$

$$4.3V = 1.2M \cdot I_B$$

$$I_B = 3.6\mu A$$

$$I_C = \beta I_B = 0.72mA$$

$$V_{EC} = 5 - 5k \cdot 0.72$$

$$V_{EC} = 1.4V$$

$$g_m = \frac{I_C}{nV_T} = \frac{0.72mA}{0.05V} = 14mA/V$$

$$r_\pi = \frac{nV_T}{I_B} = \frac{0.05V}{3.6\mu A} = 14k\Omega$$

$$r_o = \frac{V_A + V_{EC}}{I_C} = \frac{51.4V}{0.72mA} = 72k\Omega$$

$$r_e = \frac{1}{g_m} = 71\Omega$$

Identify as Emitter Follower

$$A_v = \frac{R_E \parallel R_L}{R_E \parallel R_L + r_e} = \frac{3.3k}{3.3k + 71}$$

$$A_v = 0.98$$

$$R_i = R_B \parallel [r_\pi + (1 + \beta)(r_o \parallel R_E \parallel R_L)]$$

$$R_i = 153k\Omega$$

$$R_o = r_e \parallel R_E$$

$$R_o = 71\Omega$$


Problem 6:

Determine the low frequency cutoff for this amplifier.

Assume $k_n' \frac{W}{L} = 1 \text{ mA/V}^2$, $\lambda = 0.02 \text{ V}^{-1}$, and $V_T = 1 \text{ V}$

Ignore channel width modulation for determining bias conditions.

Assume $R_{sig} = 0$.

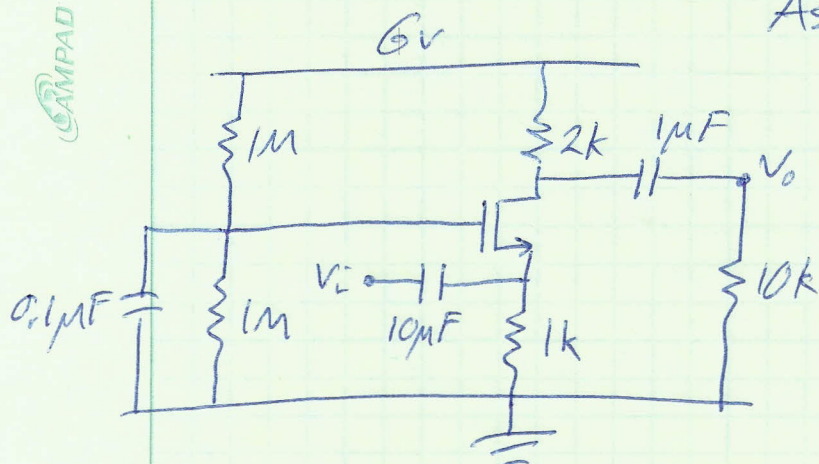

Identify as common gate.

$$R_L = R_S \parallel \left[\frac{1}{g_m} + (R_D \parallel R_L) / g_m r_o \right]$$

$$R_L = 1 \text{ k} \parallel [770 + (2 \text{ k} \parallel 10 \text{ k}) / 82]$$

$$R_L = 440 \Omega$$

$$f_1 = \frac{1}{2\pi C_1 R_L} = 36 \text{ Hz}$$

$$f_2 = \frac{1}{2\pi C_2 (R_L + R_D \parallel R_{out})} = 13 \text{ Hz}$$

$$R_{out} = r_o (1 + g_m R_S) = 145 \text{ k}$$

$$f_b = \frac{1}{2\pi C_b R_G} = 3.2 \text{ Hz}$$

$R_G = 500 \text{ k}$

$$f = f_1 + f_2 + f_b = 36 + 13 + 3.2$$

$$f = \underline{52 \text{ Hz}}$$

$$V_G = 3 \text{ V}$$

$$V_{GS} = 3 \text{ V} - 1 \text{ k} \cdot I_D$$

$$\frac{3 \text{ V} - V_{GS}}{1 \text{ k}} = I_D = \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_T)^2$$

$$6 - 2V_{GS} = V_{GS}^2 - 2V_{GS} + 1$$

$$V_{GS} = \sqrt{5} = 2.2 \text{ V}$$

$$I_D = \frac{3 - 2.2}{1 \text{ k}} = 0.80 \text{ mA}$$

$$g_m = \frac{2I_D}{V_{GS} - V_T} = \frac{2 \times 0.80 \text{ mA}}{2.2 - 1} = 1.3 \text{ mA/V}$$

$$r_o = \frac{V_A}{I_D} = \frac{50 \text{ V}}{0.8 \text{ mA}} = 63 \text{ k}\Omega$$

$$\frac{1}{g_m} = 770 \Omega$$