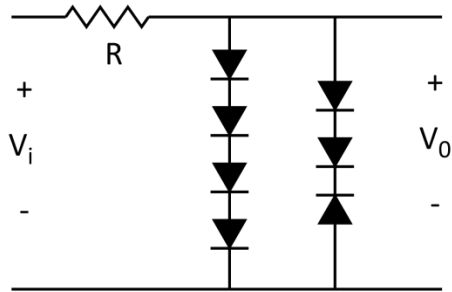


For all questions, assume the piecewise linear model for diodes.

Question 1 (10 points)


$R=1\text{ k}\Omega$, and $V_{D0}=0.7\text{ V}$

(a) Find the transfer function (V_o for all possible V_i) for the following circuit:



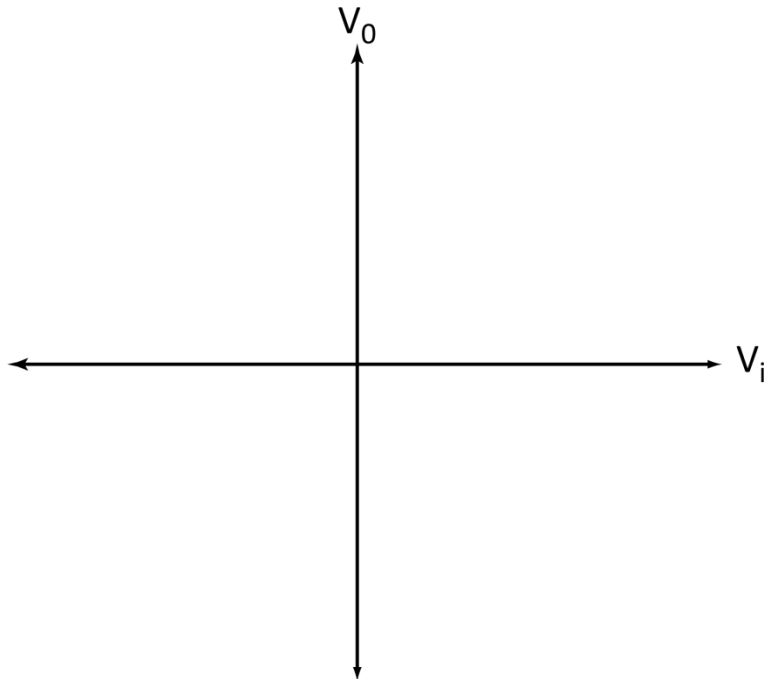(b) Sketch the transfer function.


Indicate the values of V_i or V_o at any points where the slope is discontinuous.



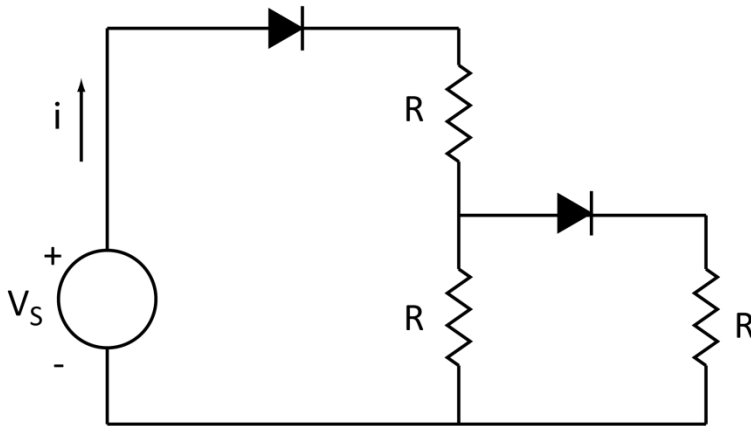Question 2 (10 points)

$R=1\text{k}\Omega$, $V_S=9\text{ V}$, and $V_{D0}=0.7\text{ V}$


Find the current, i , labeled in the circuit below:



Question 3 (10 points)


$R_1=2\text{k}\Omega$, $R_2=2\text{k}\Omega$, $V_{D0}=0.7\text{ V}$, and $V_Z=5\text{ V}$

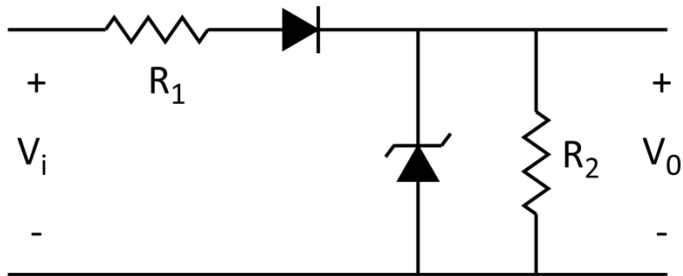(a) Find the transfer function for the circuit below:



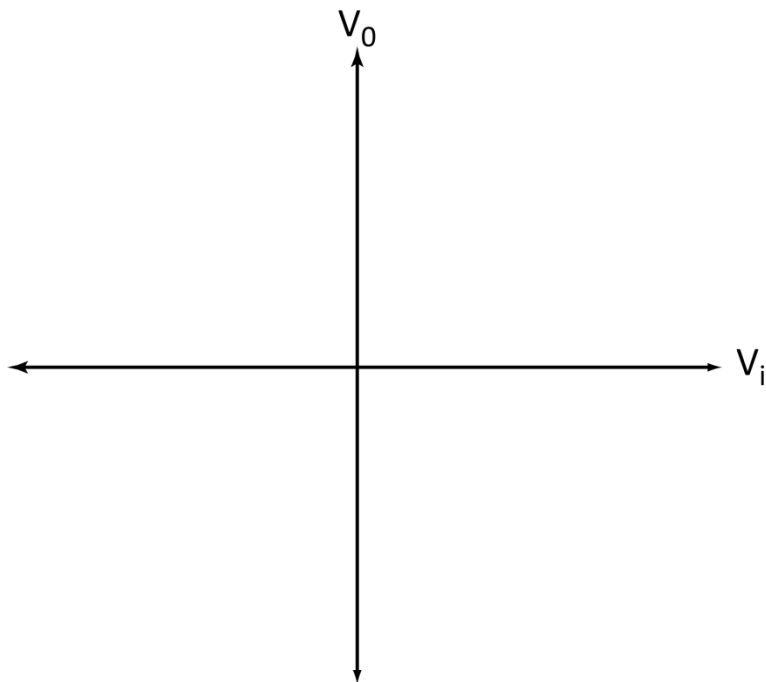(b) Sketch the transfer function.

Indicate the values of V_i or V_o at any points where the slope is discontinuous.



ECE 65 Quiz 1


Name _____ PID _____

For all questions, assume the piecewise linear model for diodes.

Question 1 (10 points)


$R=1\text{ k}\Omega$, and $V_{D0}=0.7\text{ V}$

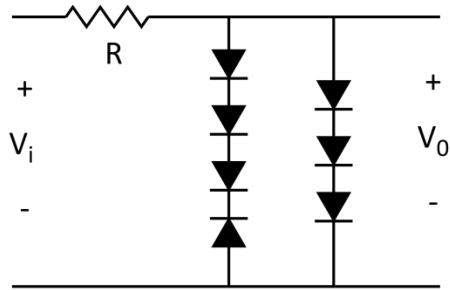(a) Find the transfer function (v_o for all possible v_i) for the following circuit:



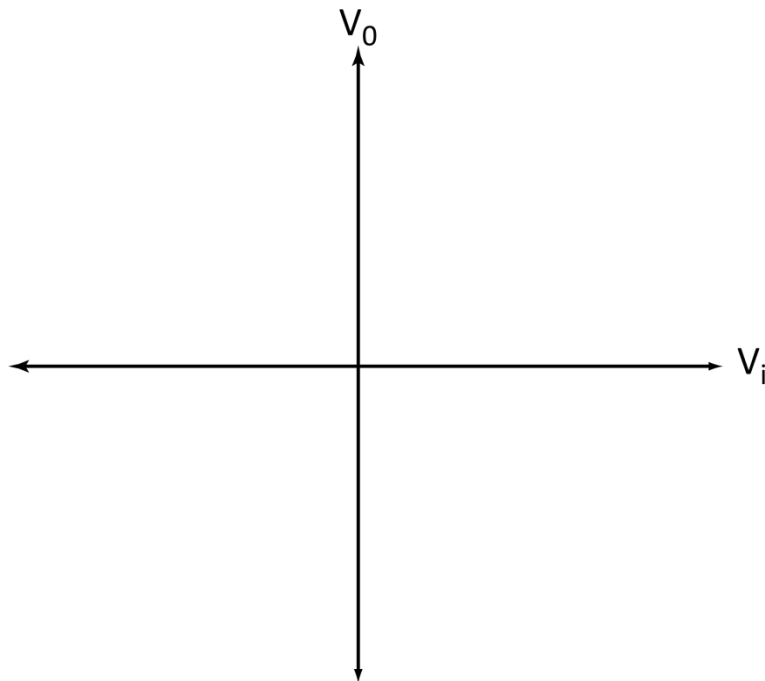(b) Sketch the transfer function.


Indicate the values of V_i or V_o at any points where the slope is discontinuous.



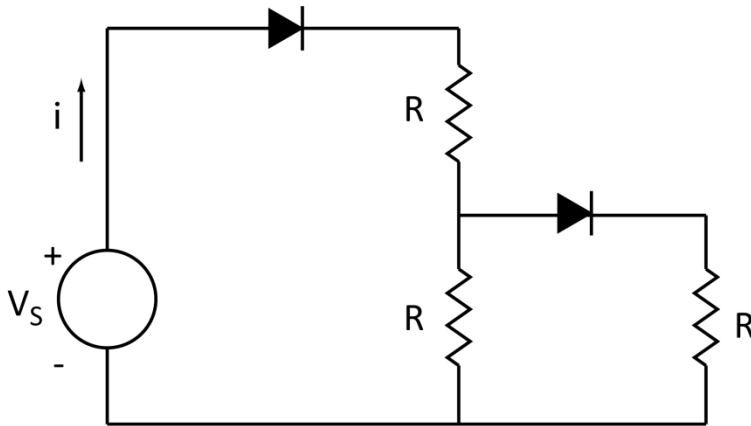Question 2 (10 points)

$R=1\text{k}\Omega$, $V_S=6\text{ V}$, and $V_{D0}=0.7\text{ V}$


Find the current, i , labeled in the circuit below:



Question 3 (10 points)

$R_1=3\text{k}\Omega$, $R_2=1\text{k}\Omega$, $V_{D0}=0.7\text{ V}$, and $V_Z=4\text{ V}$

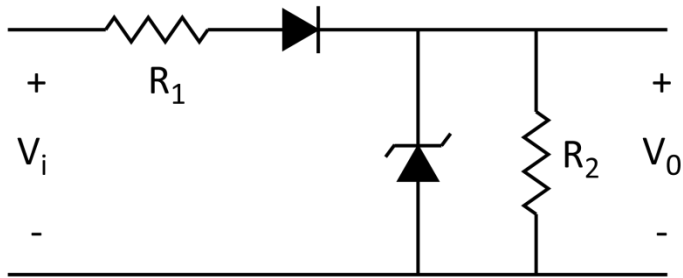(a) Find the transfer function for the circuit below:



(b) Sketch the transfer function.

Indicate the values of V_i or V_o at any points where the slope is discontinuous.

