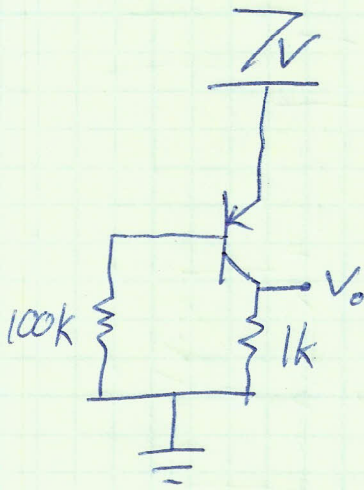


Question 1assume cut-off

$$i_B = 0, i_C = 0$$

$$V_{EB} = 7V > V_{D0}$$

→ not cut-off

assume active linear

$$7V - 0.7V - 100k \cdot i_B = 0$$

$$i_B = \frac{6.3V}{100k} = 63\mu A$$

$$i_C = \beta i_B = 200 \times 63\mu A = 12.6mA$$

$$7V - V_{EC} - 1k \times 12.6mA = 0$$

$$V_{EC} = 7 - 12.6 = -5.6V < V_{D0}$$

→ not active linear

assume saturation


$$V_{EC} = 0.2V$$

$$7V - 0.2V - 1k \cdot i_C = 0$$

$$i_C = \frac{6.8V}{1k} = 6.8mA$$

$$\frac{i_C}{i_B} = \frac{6.8mA}{63\mu A} = 108 < \beta$$

saturation mode with $V_o = 6.8V$

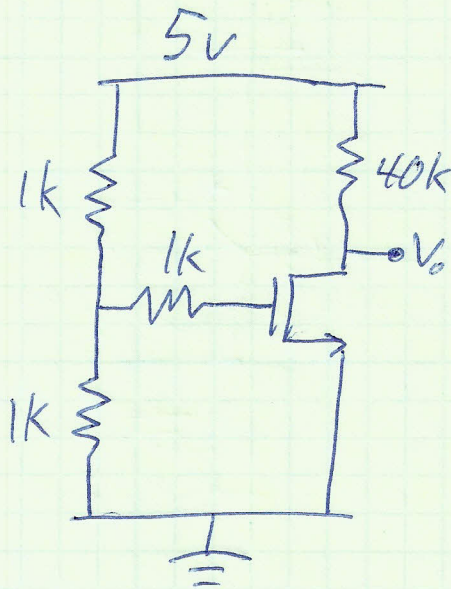Question 2

note: $i_G = 0$ always

- no current through center resistor

$$V_{GS} = 2.5V > V_T$$

→ not in cutoff

assume saturation


$$\begin{aligned} I_D &= \frac{1}{2} k_n \frac{W}{L} (V_{GS} - V_T)^2 \\ &= \frac{1}{2} (0.5 \text{ mA/V}^2) (2.5V - 2V)^2 \\ &= 62.5 \mu\text{A} \end{aligned}$$

$$\begin{aligned} V_{DS} &= 5V - 40k \times 62.5 \mu\text{A} \\ &= 5V - 2.5V \\ &= 2.5V \end{aligned}$$

is $V_{DS} > V_{GS} - V_T$?

$$2.5V > 2.5V - 2V \quad \text{yes}$$

Saturation mode with $V_O = 2.5V$

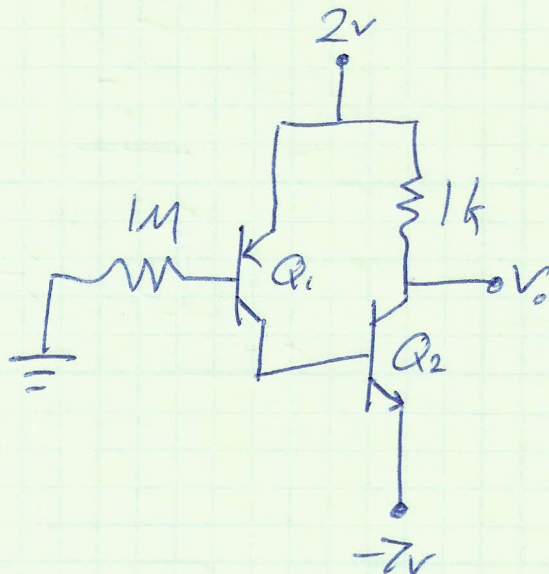Question 3assume Q_1 in cut-off

$$V_{EB} = 2V > V_{D0}$$

 $\rightarrow$ not cut-offassume Q_1 in active linear mode

$$I_{B1} = \frac{2 - 0.7}{1M} = 1.3 \mu A$$

$$I_{C1} = \beta I_{B1} = 65 \mu A$$

assume Q_2 also in active mode

$$I_{B2} = I_{C1} = 65 \mu A$$

$$I_{C2} = \beta I_{B2} = 3.3 mA$$

$$2V - 1k \cdot 3.3mA - V_{CE} + 7V = 0$$

$$V_{CE} = 9V - 3.3V = 5.7V > V_{D0}$$

so Q_2 is in active mode

$$\text{for } Q_1, V_{EB} = 9V - 0.7V = 8.3V > V_{D0}$$

so Q_1 is in active mode

$$V_o = -7V + V_{CE2}$$

$$= -7V + 5.7V$$

$$\underline{V_o = -1.3V}$$