


VI. Transistor Amplifiers

6.1 Introduction

In this section we will use the transistor small-signal model to analyze and design transistor amplifiers. There are two issues that we need to discuss first: 1) What are the important properties of an amplifier? and 2) How can we add a signal to the bias in a real circuit?

 6.1.1 Amplifier Parameters

In Section 1, we showed that the response of a two-port network is completely determined if we solve the simple circuit shown. Three parameters define the properties of a two-port network.




1) The ratio of v_o/v_i is called the voltage transfer function of the circuit. For voltage amplifiers, $v_o/v_i = \text{const}$ and is called the amplifier voltage gain (or gain for short):

$$\text{Voltage Gain: } A_v = \frac{v_o}{v_i}$$

In general A_v depends on the load, R_L . A special case of the gain is of particular interest:

$$\text{Open-loop Gain: } A_{vo} = \frac{v_{oc}}{v_i} = \left. \frac{v_o}{v_i} \right|_{R_L \rightarrow \infty}$$

 
2) As the combination of the two-port network (amplifier) and the load is a two-terminal network, it can be modeled by its Thevenin equivalent. Furthermore, as this combination does not contain an independent source, it reduces to a resistor, called the input resistance:



$$\text{Input Resistance: } R_i = \frac{v_i}{i_i}$$

In general R_i depends on the load, R_L .

 3) The combination of the amplifier and the input (v_{sig} and R_{sig}) is also a two-terminal network and can be modeled by its Thevenin equivalent. We denote the Thevenin resistance of this combination as R_o .



In order to calculate R_o we need to set the independent voltage source $v_{sig} = 0$ and compute the equivalent resistance seen between the output terminals, *i.e.*,

$$\text{Output Resistance: } R_o = - \left. \frac{v_o}{i_o} \right|_{v_{sig}=0} \quad (\text{Thevenin Resistance})$$


In general R_o depends on the load, R_{sig} .

The Thevenin voltage source of the amplifier/input combination, V_T , is the open-circuit voltage, v_{oc} , and is related to the open-loop gain of the amplifier:

$$V_T = v_{oc} = v_o|_{R_L \rightarrow \infty} = A_{vo}v_i$$

Therefore, the load “sees” a Thevenin equivalent circuit with $V_T = A_{vo}v_i$ and $R_T = R_o$.

 Combining models of the input and output ports, we arrive at a model for an amplifier which consists of three circuit elements as is shown below (left).



The amplifier circuit model allows us to solve any amplifier configuration if we know values of A_{vo} , R_i and R_o (similar to using Thevenin Theorem to “label” any two-terminal network with R_T and V_T). For example, we can find the overall voltage gain of the amplifier as:

$$\begin{aligned} \frac{v_o}{v_i} &= \frac{R_L}{R_o + R_L} A_{vo} & \frac{v_i}{v_{sig}} &= \frac{R_i}{R_i + R_{sig}} \\ \frac{v_o}{v_{sig}} &= \frac{v_i}{v_{sig}} \times \frac{v_o}{v_i} = \frac{R_i}{R_i + R_{sig}} \times A_{vo} = \frac{R_i}{R_i + R_{sig}} \times A_{vo} \times \frac{R_L}{R_o + R_L} \end{aligned}$$

We see that the open-loop gain A_{vo} is the maximum value for the amplifier gain A_v . In addition, to maximize v_o/v_{sig} , we need $R_i \rightarrow \infty$ and $R_o \rightarrow 0$. A practical voltage amplifier, thus, is designed to have a “large” R_i and a “small” R_o (*i.e.*, $R_i \gg R_{sig}$ and $R_o \ll R_L$). A voltage-controlled voltage source is an ideal voltage amplifier as $R_i \rightarrow \infty$ and $R_o = 0$.


We will use this amplifier model later to find parameters of multi-stage amplifiers.

6.1.2 Capacitor Coupling

As discussed before, a constant bias voltage should be added to the signal to ensure that MOS is always in saturation (or BJT is active). There are practical ways to accomplish this task.

1) “Direct Coupling:” For a multi-stage amplifier, the biasing scheme can be set up such that the bias voltage of each stage matches the bias voltage of the following stage (see Problem 28, for example). Usually, bias with two voltage supplies is used such that for the first amplifier stage, $V_G = 0$ (or $V_B = 0$ for BJT). Integrated circuit chips use this scheme in order to avoid using capacitors which takes a lot of space on the chip. Because of the direct coupling between stages, biasing becomes a difficult design problem.

 2) Capacitive coupling. Since a capacitor becomes an open circuit for bias, it can be used to couple the signal to the circuit as is shown below for a MOS amplifier.



The first issue with this method is that DC signals cannot be amplified. Secondly, the capacitor impedance, $|Z_C| = 1/(\omega C)$, depends on the frequency. As a result v_o/v_i will also depend on frequency and the amplifier would not behave linearly for an arbitrary signal (which includes many frequencies).

We note, however, that at high enough frequencies, the impedance of a capacitor becomes very small and the capacitor effectively becomes a short circuit. For frequencies higher than this value, v_o/v_i will be independent of frequency and the linear behavior of the amplifier is recovered. The frequency at which we can ignore the impedance of the coupling capacitors is called the lower cut-off frequency of the amplifier. The frequency range above the lower cut-off frequency is called the midband where the amplifier should be operated. (You will see in ECE 102 that the gain of a transistor amplifier drops at high frequencies and there is also an upper cut-off frequency).

As the capacitive coupling scheme confines bias voltages in each stage, biasing is simpler with this scheme.

6.1.3 Analysis of Transistor Amplifier Circuits

Analysis of a transistor amplifier circuit follows three steps as we need to address several issues: bias, linear response (to small signals), and the impact of coupling capacitors.

Bias: Zero out the signal and replace capacitors with open circuits. Compute transistor bias point parameters.

Mid-band Small Signal Response:

- 1) Compute g_m , r_o (and r_π for BJT) from bias point parameters
- 2) Draw the signal circuit (*e.g.*, ground bias voltage sources)
- 3) Assume capacitors are short circuit.
- 4) Inspect the circuit. If you identify the circuit as a prototype circuit, you can directly use the formulas for that circuit. Otherwise, replace the transistor with its small signal model and solve for A_v , A_{vo} , R_i and R_o .

Frequency-response: Coupling and bypass capacitors introduce poles at low frequencies. In Section 6.7, We will introduce a method to compute the low-frequency poles. ECE102 include a more thorough review of the amplifier frequency response.

It turns out that there are four “basic amplifier configurations” (4 for BJT and 4 for MOS). Furthermore, the input and output resistances can be found using “elementary R forms.” These formulas allows one to compute properties of any amplifier readily. These basis form are discussed in the Appendix.

Since we are only focusing on discrete and simple amplifier configurations in this course, amplifier parameters are computed directly from the circuit in the following sections.

Notes:

- 1) Small-signal models of PNP and NPN transistors (or PMOS and NMOS transistors) are similar. Thus, the formulas derived below can be used for either case.
- 2) The small-signal model of a BJT is similar to that of a MOS with the exception of the additional resistor r_π (the input terminals in a MOS is open circuit). As such, we expect that formulas for MOS amplifiers would be the same as those of BJT amplifiers if we set $r_\pi \rightarrow \infty$.
- 3) For MOS circuits, we use the common approximation $g_m r_o \gg 1$ as

$$g_m = \frac{2I_D}{V_{OV}}, \quad r_o \approx \frac{V_A}{I_D} \quad \rightarrow \quad g_m r_o = \frac{2V_A}{V_{OV}} \gg 1$$

typically $g_m r_o$ is 50 or more.

4) For BJT circuits, we also use the common approximation $g_m r_o \gg 1$ as

$$g_m = \frac{I_C}{V_T}, \quad r_o = \frac{V_A + V_{CE}}{I_C} \approx \frac{V_A}{I_C} \rightarrow g_m r_o = \frac{V_A}{V_T} \gg 1$$

typically $g_m r_o$ is several thousands. In addition, $g_m r_\pi = \beta \gg 1$

5) In many text books (*e.g.*, Sedra & Smith), the formulas for BJT amplifiers are given in terms of β & r_e (instead of g_m & r_π) where

$$r_e = \frac{1}{g_m} = \frac{r_\pi}{\beta}$$


with r_e typically in 10s or 100 Ω range. Here we keep the g_m form so we that can see the comparison to MOS amplifiers.

6) Some manufacturer spec sheet for BJTs (*e.g.*, spec sheet for 3N3904) use the older notation (hybrid π model) for BJT which are $h_{fe} \equiv \beta$, $h_{re} \equiv r_\pi$, and $h_{oe} \equiv 1/r_o$

 6.2 Common-Drain and Common-Collector Amplifiers


Common-Drain or Source Follower Configuration

Circuit shown is the generic signal circuit of a common-drain amplifier (*i.e.*, we have “zeroed” out all Bias sources).




Note that the input is applied at the gate and the output is taken at the source. As the drain is grounded (for signal), it is the common terminal of input and output. Thus, this circuit is called the common-drain amplifier.

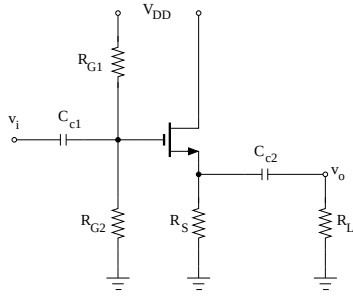
It is important to realize that as a transistor can be biased in many ways, several “complete” circuits (*i.e.*, including bias elements) will reduce to the above “signal” circuit form of a common-drain amplifier. Some examples are given below (v_{sig} and R_{sig} in the input are not shown for simplicity).



$$R_G = R_{G1} \parallel R_{G2}$$

 
 
$$R_G \rightarrow \infty, \\ C_{c1} \rightarrow \infty,$$




$$R_G \rightarrow \infty, R_S \rightarrow \infty, \\ C_{c1} \rightarrow \infty,$$

We now proceed with the signal analysis by replacing the MOS with its small-signal model.

Using node-voltage method (there is one node, v_o):
 
$$\begin{aligned} v_{gs} &= v_i - v_o \\ \text{Node } v_o \quad \frac{v_o}{R_S} + \frac{v_o}{r_o} + \frac{v_o}{R_L} - g_m v_{gs} &= 0 \\ \frac{v_o}{r_o \parallel R_S \parallel R_L} - g_m(v_i - v_o) &= 0 \\ \frac{v_o}{v_i} &= \frac{g_m(r_o \parallel R_S \parallel R_L)}{1 + g_m(r_o \parallel R_S \parallel R_L)} \end{aligned}$$




As can be seen, the gain of this amplifier is less than 1. For large $R_S \parallel R_L$, it achieves a gain of 1 (since $g_m r_o \gg 1$). Thus, this configuration is also called the Source Follower.

Finding R_i is easy as $i_1 = i_i$ and $v_i = R_G i_i$ (see circuit). Therefore, $R_i = R_G$. Note that if R_G were not present (see example complete circuits above). $R_i \rightarrow \infty$.

To find R_o we need to zero out v_{sig} and compute the Thevenin Equivalent resistance seen at the output terminals. Because of the presence of the controlled source, the standard method is to attach a v_x voltage source to the circuit and compute i_x .

 We see from the circuit that $v_g = 0$ and $v_{gs} = -v_x$. Thus:




$$i_x = \frac{v_x}{r_o} + \frac{v_x}{R_S} - g_m v_{gs} = \frac{v_x}{r_o} + \frac{v_x}{R_S} + \frac{v_x}{1/g_m}$$

$$R_o = \frac{v_x}{i_x} = \frac{1}{g_m} \parallel R_S \parallel r_o \approx \frac{1}{g_m} \parallel R_S$$

In summary, the general properties of the common-drain amplifier (source follower) include a voltage gain ≤ 1 , a large input resistance (which can be made infinite in some biasing schemes) and a small output resistance. This type of circuit is called a buffer and often used when there is a mismatch between input resistance of one stage and the output resistance of the previous stage. Additionally, $i_L = i_o \gg i_i$ as $A_v \approx 1$ but $R_i \gg R_o$. As such, this circuit can be used to amplify the signal current (and power) and drive a load (used typically as the last stage of an amplifier circuit).


Common-Collector or Emitter Follower Configuration

 Circuit shown is the generic signal circuit of a common-collector amplifier (*i.e.*, we have “zeroed” out all Bias sources).




Note that the input is applied at the base and the output is taken at the emitter. As the collector is grounded (for signal), it is the common terminal of input and output. Thus, this circuit is called the common-collector amplifier.

 As can be seen this configuration is analogous to MOS common-drain. Similarly to the MOS case, the BJT can be biased many ways. Several “complete” circuits (*i.e.*, including the bias elements) will reduce to the above “signal” form of a common-collector amplifier. Some examples are given below.




$$R_B = R_{B1} \parallel R_{B2}$$

 

$$R_B \rightarrow \infty,$$

$$C_{c1} \rightarrow \infty,$$

 


$$R_B \rightarrow \infty, R_E \rightarrow \infty,$$

$$C_{c1} \rightarrow \infty,$$

We now proceed with the signal analysis by replacing the BJT with its small-signal model.

Using node-voltage method (there is one node, v_o):
 
$$\text{Node } v_o \quad \frac{v_o}{R_E} + \frac{v_o}{r_o} + \frac{v_o}{R_L} + \frac{v_o - v_i}{r_\pi} - g_m v_\pi = 0$$



The last two terms in the above equation can be simplified by noting $1/r_\pi = g_m/\beta$:

$$\frac{v_o - v_i}{r_\pi} - g_m v_\pi = (v_o - v_i) \times \frac{g_m}{\beta} + g_m(v_o - v_i) = g_m(v_o - v_i) \frac{\beta + 1}{\beta} \approx g_m(v_o - v_i)$$

Substituting back in the node equation, we get:

$$\begin{aligned} \frac{v_o}{R_E} + \frac{v_o}{r_o} + \frac{v_o}{R_L} + g_m(v_o - v_i) &= 0 \\ \frac{v_o}{r_o \parallel R_E \parallel R_L} + g_m(v_o - v_i) &= 0 \\ \frac{v_o}{v_i} &= \frac{g_m(r_o \parallel R_E \parallel R_L)}{1 + g_m(r_o \parallel R_E \parallel R_L)} \end{aligned}$$

Similar to the MOS common-drain amplifier, the gain of the common collector amplifier is less than 1, but usually close to 1 because of the large BJT g_m . This configuration is also called the Emitter Follower.

To find $R_i = v_i/i_i$, we note that by KCL $i_i = i_1 + i_\pi$ and

$$\begin{aligned} i_\pi &= \frac{v_i - v_o}{r_\pi} = \frac{v_i}{r_\pi} \times \left(1 - \frac{v_o}{v_i}\right) \\ 1 - \frac{v_o}{v_i} &= 1 - \frac{g_m(r_o \parallel R_E \parallel R_L)}{1 + g_m(r_o \parallel R_E \parallel R_L)} = \frac{1}{1 + g_m(r_o \parallel R_E \parallel R_L)} \\ i_\pi &= \frac{v_i}{r_\pi + g_m r_\pi(r_o \parallel R_E \parallel R_L)} \\ i_i &= i_1 + i_\pi = \frac{v_i}{R_B} + \frac{v_i}{r_\pi + \beta(r_o \parallel R_E \parallel R_L)} = \frac{v_i}{R_B \parallel [r_\pi + \beta(r_o \parallel R_E \parallel R_L)]} \\ R_i &= R_B \parallel [r_\pi + \beta(r_o \parallel R_E \parallel R_L)] \end{aligned}$$

Note that when emitter degeneration biasing is used, we need to have $R_B \ll (1 + \beta)R_E$. In this case, $R_i \approx R_B$ (similar to the common-drain amplifier in which $R_i = R_G$). If R_B is not present, the input resistance would be very large (M Ω level).

To find R_o we need to zero out v_{sig} and compute the Thevenin Equivalent resistance seen at the output terminals. We attach v_x voltage source to the circuit and compute i_x . The calculation is straight forward and is left as an exercise (Hint: $v_\pi = -[r_\pi / (r_\pi + R_B \parallel R_{sig})]$).

$$R_o = R_E \parallel r_o \parallel \frac{r_\pi + R_B \parallel R_{sig}}{1 + \beta}$$

In summary, the general properties of the common-collector amplifier (emitter follower) include a voltage gain close to unity, a large input resistance and a small output resistance (similar to the common-drain amplifier). Thus, emitter follower is also used as a buffer or for amplifying the signal current (and power) and drive a load.


6.3 Common-Source and Common-Emitter Amplifiers


Common-Source Configuration

Circuit shown is the generic signal circuit of a common-source amplifier (*i.e.*, we have “zeroed” out all Bias sources). Note that the input is applied at the gate and the output is taken at the drain. As the source is grounded (for signal), it is the common terminal of input and output. Thus, this circuit is called the common-source amplifier.

If source degeneration biasing is used for the common-source configuration, a resistor R_S should be present. A “by-pass” capacitor is typically used so that the signal by-passes R_S , effectively making the source grounded for the signal as is shown.

 We replace the MOS with its small-signal model.



 

Inspection of the circuit shows that $v_i = v_{gs}$. Furthermore, r_o , R_D , and R_L are in parallel and by KCL a current of $g_m v_{gs}$ flows in $r_o \parallel R_D \parallel R_L$ (from the ground to v_o).

$$\text{Ohm Law: } v_o = -g_m v_{gs} (r_o \parallel R_D \parallel R_L)$$

$$\frac{v_o}{v_i} = -g_m (r_o \parallel R_D \parallel R_L)$$

The negative sign in the gain is indicative of a 180° phase shift in the output signal.

Inspecting the circuit, we find $R_i = v_i / i_i = R_G$.

To find R_o we need to zero out v_{sig} and compute the Thevenin Equivalent resistance seen at the output terminals. Since in this circuit $v_{gs} = 0$ when $v_{sig} = 0$, the controlled source $g_m v_{gs}$ becomes an open circuit and the output resistance can be found by inspection to be $R_o = R_D \parallel r_o$.



In summary, the general properties of the common-source amplifier include a large voltage gain, a large input resistance (and can be made infinite with some biasing schemes) but a medium output resistance.

Common-Emitter Configuration

Circuit shown is the generic signal circuit of a common-emitter amplifier (*i.e.*, we have “zeroed” out all Bias sources). Note that the input is applied at the base and the output is taken at the collector. As the emitter is grounded (for signal), it is the common terminal of input and output. Thus, this circuit is called the common-emitter amplifier.

If emitter degeneration biasing is used for this configuration, a resistor R_E should be present. A “by-pass” capacitor is typically used so that the signal by-passes R_E , effectively making the emitter grounded for the signal as is shown.

 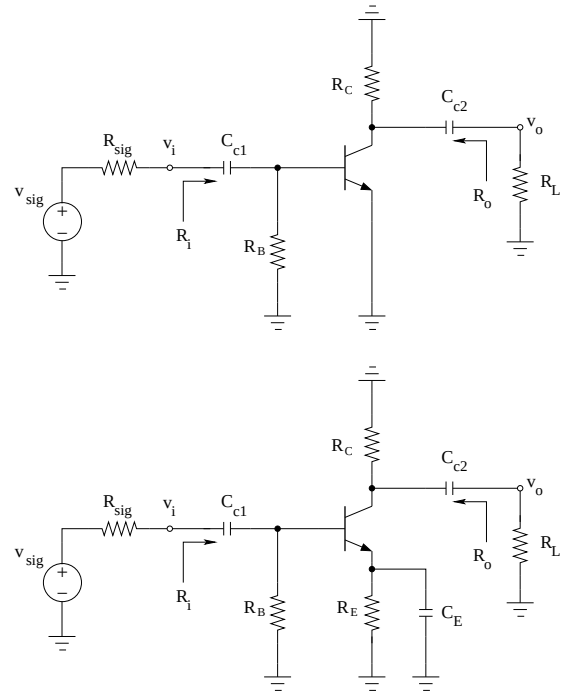We replace the BJT with its small-signal model.



Inspection of the circuit shows that $v_i = v_\pi$. Furthermore, r_o , R_C , and R_L are in parallel and by KCL a current of $g_m v_\pi$ flows in $r_o \parallel R_C \parallel R_L$ (from the ground to v_o).

$$\begin{aligned} \text{Ohm Law: } v_o &= -g_m v_\pi (r_o \parallel R_C \parallel R_L) \\ \frac{v_o}{v_i} &= -g_m (r_o \parallel R_C \parallel R_L) \end{aligned}$$

The negative sign in the gain is indicative of a 180° phase shift in the output signal.

Inspecting the circuit, we find $R_i = v_i/i_i = R_B \parallel r_\pi$.

To find R_o we need to zero out v_{sig} and compute the Thevenin Equivalent resistance seen at the output terminals. Since in this circuit $v_\pi = 0$ when $v_{sig} = 0$, the controlled source $g_m v_\pi$ becomes an open circuit and the output resistance can be found by inspection to be $R_o = R_C \parallel r_o$.

In summary, the general properties of the common-emitter amplifier include a large open-loop voltage, a “medium” input resistance and a “medium” output resistance.

6.4 Common-Source and Common-Emitter Amplifiers with Degeneration

Common-Source Configuration with a Source Resistor

Circuit shown is the generic signal circuit of a common-source amplifier with degeneration (*i.e.*, with a source resistor). Note that the input is applied at the gate and the output is taken at the drain similar to a common-emitter amplifier

We replace the MOS with its small-signal model.

Using node-voltage method (there are two nodes, v_o and v_s):

$$\text{Node } v_s : \quad \frac{v_s}{R_S} + \frac{v_s - v_o}{r_o} - g_m v_{gs} = 0$$

$$\text{Node } v_o : \quad \frac{v_o}{R_D \parallel R_L} + \frac{v_o - v_s}{r_o} + g_m v_{gs} = 0$$

$$\frac{v_s}{R_S} + \frac{v_o}{R_D \parallel R_L} = 0$$

where the last equation is found by summing the first two. Substituting for $v_{gs} = v_i - v_s$ in the first equation, computing v_s , and substituting in the third equation, we get:


$$\frac{v_o}{v_i} = - \frac{g_m r_o (R_D \parallel R_L)}{R_D \parallel R_L + r_o + R_S (1 + r_o g_m)} \approx - \frac{g_m r_o (R_D \parallel R_L)}{R_D \parallel R_L + r_o + g_m r_o R_S}$$

$$\frac{v_o}{v_i} = - \frac{g_m (R_D \parallel R_L)}{1 + g_m R_S + (R_D \parallel R_L)/r_o}$$


Compared to a CS amplifier with no R_S , the amplifier gain is substantially reduced with the presence of R_S . However, the gain has become much less sensitive to changes in g_m .

Inspecting the circuit we find $R_i = v_i/i_i = R_G$, similar to a common-source amplifier.

 To find R_o , we set $v_{sig} = 0$ and compute the Thevenin Equivalent resistance seen at the output terminals. We attach v_x voltage source to the circuit and compute i_x .



 By KCL, a current of $i_1 - g_m v_{gs}$ should flow in r_o and i_1 should flow in R_S . Since $v_{gs} = -R_S i_1$:



$$\text{KVL : } v_x = r_o(i_1 - g_m v_{gs}) + R_S i_1$$

$$v_x = r_o(i_1 + g_m R_S i_1) + R_S i_1 = i_1(r_o + g_m r_o R_S + R_S)$$

$$\frac{v_x}{i_1} = r_o + R_S + g_m r_o R_S \approx r_o(1 + g_m R_S)$$


$$\text{KCL: } i_x = \frac{v_x}{R_D} + \frac{v_x}{i_1} = \frac{v_x}{R_D} + \frac{v_x}{r_o(1 + g_m R_S)}$$

$$R_o = \frac{v_x}{i_x} = R_D \parallel [r_o(1 + g_m R_S)]$$

In summary, source degeneration has led to an amplifier with a lower gain which is less sensitive to transistor parameters.

Common-Emitter Configuration with an Emitter Resistor

 Circuit shown is the generic signal circuit of a common-emitter amplifier with degeneration (*i.e.*, with a emitter resistor). Note that the input is applied at the base and the output is taken at the collector similar to a common-emitter amplifier.




We replace the BJT with its small-signal model.

Using node-voltage method (there are two nodes, v_o and v_e):

$$\text{Node } v_e : 0 = \frac{v_e}{R_E} + \frac{v_e - v_i}{r_\pi} + \frac{v_e - v_o}{r_o} - g_m v_\pi$$

$$\text{Node } v_o : 0 = \frac{v_o}{R_C \parallel R_L} + \frac{v_o - v_e}{r_o} + g_m v_\pi = 0$$
 
$$\frac{v_e}{R_E} + \frac{v_o}{R_C \parallel R_L} + \frac{v_e - v_i}{r_\pi} = 0$$



The third equation is the sum of the first two. Finding v_e from the third equation and substituting in the 2nd equation, we get:

$$\begin{aligned}\frac{v_o}{v_i} &= - \frac{g_m(R_C \parallel R_L)}{g_m R_E + (1 + (R_C \parallel R_L)/r_o)(1 + R_E/r_\pi)} \\ \frac{v_o}{v_i} &= - \frac{g_m(R_C \parallel R_L)}{1 + g_m R_E + R_E/r_\pi + (1 + R_E/r_\pi)(R_C \parallel R_L)/r_o} \\ \frac{v_o}{v_i} &\approx - \frac{g_m(R_C \parallel R_L)}{1 + g_m R_E + (1 + R_E/r_\pi)(R_C \parallel R_L)/r_o}\end{aligned}$$

Where we have used $R_E/r_\pi = g_m R_E/\beta \ll g_m R_E$. If $(R_C \parallel R_L)/r_o \ll \beta$ (a very good approximation), we can drop the last term to find:

$$\frac{v_o}{v_i} \approx - \frac{g_m(R_C \parallel R_L)}{1 + g_m R_E} = - \frac{R_C \parallel R_L}{R_E + 1/g_m}$$

which is the expression often used. Note that the amplifier gain is reduced with the presence of R_E but it has become substantially less sensitive to any change in β (only through $1/g_m$ which is usually $\ll R_E$).

From the circuit we find $R_i = v_i/i_i = R_B \parallel (v_i/i_b)$. The exact formulation for v_i/i_b is cumbersome. A good approximation which leads to a simple expression is $r_o \gg R_E$. In this case, r_o can be removed from the circuit and

$$\begin{aligned}v_i &= i_b r_\pi + (i_b + g_m v_\pi) R_E = i_b r_\pi + (i_b + \beta i_b) R_E = i_b [r_\pi + (1 + \beta) R_E] \\ R_i &= R_B \parallel [r_\pi + (1 + \beta) R_E]\end{aligned}$$

To find R_o , we set $v_{sig} = 0$ and compute the Thevenin Equivalent resistance seen at the output terminals. Because of the presence of the controlled source, we need to attach v_x voltage source to the circuit and compute i_x . Calculations are left as an exercise. The output resistance is given by

$$R_o = R_C \parallel \left[r_o \left(1 + \frac{\beta R_E}{r_\pi + R_E + R_B \parallel R_{sig}} \right) \right] \approx R_C$$

In summary, emitter degeneration has led to an amplifier with a lower gain which is much less sensitive to transistor parameters and a substantially larger input resistance.

6.5 Common-Gate and Common-Base Amplifiers

Common-Gate Configuration

Circuit shown is the generic signal circuit of a common-gate amplifier. Note that the input is applied at the source and the output is taken at the drain. As the gate is grounded (for signal), it is the common terminal of input and output. Thus, this circuit is called the common-gate amplifier.





In some cases, the gate has to be biased to a DC value (for example using voltage divider circuit shown). However, since $i_G = 0$, the gate remains grounded for the signal.

We replace the MOS with its small-signal model. Using node-voltage method (there is one node, v_o):

$$\begin{aligned}
 v_{gs} &= 0 - v_i = -v_i \\
 \frac{v_o}{R_L} + \frac{v_o}{R_D} + \frac{v_o - v_i}{r_o} + g_m(-v_i) &= 0 \\
 \frac{v_o}{r_o \parallel R_D \parallel R_L} &= v_i \times \frac{1 + g_m r_o}{r_o} \\
 \frac{v_o}{r_o \parallel R_D \parallel R_L} &\approx v_i \times \frac{g_m r_o}{r_o} \\
 \frac{v_o}{v_i} &= g_m(r_o \parallel R_D \parallel R_L)
 \end{aligned}$$

To find R_i , it is easier to write $R_i = R_S \parallel \frac{v_i}{i_1}$ (see circuit). By KCL at node S, current $i_1 + g_m v_{gs}$ will flow in r_o and current i_1 will flow in $R_D \parallel R_L$. Thus:
    
$$\begin{aligned}
 v_i &= (i_1 + g_m v_{gs})r_o + i_1(R_D \parallel R_L) \\
 v_i &= i_1 r_o - g_m r_o v_i + i_1(R_D \parallel R_L) \\
 \frac{v_i}{i_1} &= \frac{r_o + (R_D \parallel R_L)}{1 + g_m r_o} \approx \frac{1 + (R_D \parallel R_L)/r_o}{g_m} \\
 R_i &= R_S \parallel \frac{1 + (R_D \parallel R_L)/r_o}{g_m}
 \end{aligned}$$



To find R_o , we set $v_{sig} = 0$ and compute the Thevenin Equivalent resistance seen at the output terminals. Because of the presence of the controlled source, we need to attach v_x voltage source to the circuit and compute i_x .

By KCL, a current of $i_1 - g_m v_{gs}$ should flow in r_o and i_1 should flow in $R_S \parallel R_{sig}$. Then, $v_{gs} = -v_s = -(R_S \parallel R_{sig})i_1$ and


$$\text{KVL : } v_x = r_o(i_1 - g_m v_{gs}) + R_S i_1$$

$$v_x = r_o i_1 + g_m r_o (R_S \parallel R_{sig}) i_1 + (R_S \parallel R_{sig}) i_1$$

$$\frac{v_x}{i_1} \approx r_o (1 + g_m (R_S \parallel R_{sig}))$$

$$\text{KCL: } i_x = \frac{v_x}{R_D} + \frac{v_x}{i_1} = \frac{v_x}{R_D} + \frac{v_x}{r_o (1 + g_m (R_S \parallel R_{sig}))}$$
 
$$R_o = \frac{v_x}{i_x} = R_D \parallel [r_o (1 + g_m (R_S \parallel R_{sig}))]$$



In summary, the general properties of the common-gate amplifier include a large voltage gain, a small input resistance and a medium output resistance (it has the same gain and output resistance values as that of a common-source configuration but has a much lower input resistance).

Common-Base Configuration

Circuit shown is the generic signal circuit of a common-base amplifier. Note that the input is applied at the emitter and the output is taken at the collector. As the base is grounded (for signal), it is the common terminal of input and output. Thus, this circuit is called the common-base amplifier.

In some cases, the base has to be biased to a DC value (for example using voltage divider circuit shown). In this case, a bypass capacitor is needed to keep the base grounded for the signal.




We replace the BJT with its small-signal model. Comparing the small signal circuit of the common base amplifier with that of a common-gate amplifier of the previous page, we see that the two circuits are identical if we replace R_S with $R_E \parallel r_\pi$ (and R_D with R_C). As such we can use the results from the common-gate amplifier analysis to get:

$$\frac{v_o}{v_i} = g_m(r_o \parallel R_C \parallel R_L)$$

$$R_i = R_E \parallel r_\pi \parallel \frac{1 + (R_C \parallel R_L)/r_o}{g_m}$$

$$R_o = R_C \parallel [r_o(1 + g_m(R_E \parallel r_\pi \parallel R_{sig}))]$$

  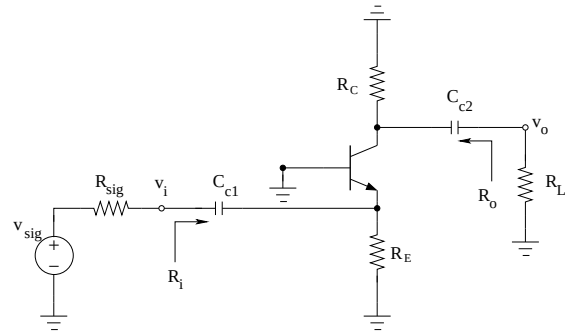In summary, the common-base configuration has a large open-loop voltage, a small input resistance and a medium output resistance (it has the same gain and output resistance values as that of a common-emitter configuration but a much lower input resistance).



6.6 Summary of Amplifier Configurations

- The common-source (CS) and common-emitter (CE) amplifiers have a high gain and are the main configuration in a practical amplifier. Ignoring bias resistors R_G or R_B , the CS configuration has an infinite input resistance while the CE amplifier has a modest input resistance. Both CS and CE amplifier have a rather high output resistance r_o and a limited high-frequency response (you will see this in 102).
- Addition of source or emitter resistor (degenerated CS or CE) leads to several benefits: a gain which is less sensitive to temperature, a much larger input resistance for CE configuration, a better control of amplifier saturation, and a much improved high-frequency response. However, these are realized at the expense of a lower gain.
- The common-gate (CG) and common-base (CB) amplifiers have a high gain (similar to CS and CE) but a low input resistance. As such, they are only used for specialized applications. CG and CB amplifiers have an excellent high-frequency response. They are typically used in combination with a CS or CE stage (such as cascode amplifiers)
- The source-follower and emitter-follower configurations have a high input resistance, a gain close to unity, and a low output resistance. They are employed as a voltage buffer and/or as the output stage to increase the current and power to the load.


6.7 Low Frequency Response of Transistor Amplifiers

Up to now, we have neglected the impact of the coupling and by-pass capacitors (assumed they were short circuit). Each of these capacitors introduce a pole in the response of the circuit. For example, let's consider the coupling capacitor at the input to the amplifier (C_{c1} in amplifier configurations that we examined before). We need to perform the analysis in the frequency domain (voltage are represented by capital letter as they are in “phasor” form):

$$A_v = \frac{V_o}{V_i} = \frac{R_L}{R_o + R_L} A_{vo}$$


$$\frac{V_i}{V_{sig}} = \frac{R_i}{R_i + R_{sig} + 1/(sC_{c1})}$$

$$\frac{V_i}{V_{sig}} = \frac{R_i}{R_i + R_{sig}} \times \frac{s}{s + \omega_{p1}}, \quad 2\pi f_{p1} = \omega_{p1} \equiv \frac{1}{C_{c1}(R_i + R_{sig})}$$
 
$$\frac{V_o}{V_{sig}} = \frac{R_i}{R_i + R_{sig}} \times A_v \times \frac{s}{s + \omega_{p1}}$$


Where A_v is the mid-frequency gain that we have calculated for all transistor configurations (*i.e.*, with capacitors short). As can be seen, the coupling capacitor C_{c1} has introduced a low-frequency pole and the amplifier gain falls at low frequencies.

One can compute the impact of the coupling capacitor at the output in a similar manner. It is straightforward to show (left as an exercise):
 
$$\frac{V_o}{V_{sig}} = \frac{R_i}{R_i + R_{sig}} \times A_v \times \frac{s}{s + \omega_{p2}}, \quad 2\pi f_{p2} = \omega_{p2} \equiv \frac{1}{C_{c2}(R_L + R_o)}$$


Similarly, if a by-pass capacitor is present (see page 5-8), it will introduce yet another pole, f_{p3} .


The following method allows one to compute the poles by “inspection.”

1. Zero out V_{sig} .
2. Consider each capacitor separately (*i.e.*, assume all other capacitors are short)
3. Compute, $\bar{R}$, the “total” resistance between the terminals of the capacitor. The pole introduced by that capacitor is given by

$$f_p \equiv \frac{1}{2\pi C \bar{R}}$$

With all poles associated with by-pass and coupling capacitors in hand, we can find the overall frequency response of the amplifier as
 
$$\frac{V_o}{V_{sig}} = A_v \times \frac{s}{s + \omega_{p1}} \times \frac{s}{s + \omega_{p2}} \times \frac{s}{s + \omega_{p3}} \times \dots$$



and the lower cut-off frequency is located at 3dB below maximum value, A_v (the mid-frequency gain). If poles are sufficiently separated (such as the figure above), the lower cut-off frequency of the amplifier is given by the highest-frequency pole. Otherwise, finding the lower cut-off frequency would be cumbersome.

A simple approximation for hand calculations (which is surprisingly very good) is to set

$$f_l \approx f_{p1} + f_{p2} + f_{p3} + \dots$$

The next two pages include a summary of formulas for discrete transistor amplifiers. These formulas are correct within approximation of $g_m r_o \gg 1$ and $\beta \gg 1$ both of which are always valid. Many of these formulas can be simplified (before plugging in numbers) as they include resistances that are in parallel and “typically” one is much smaller (at least by a factor of ten) than the others. For example, in a common emitter amplifier, we often find that $R_C \ll R_L$ and $R_C \ll r_o$. Then, $r_o \parallel R_C \parallel R_L \approx R_C$ and the gain formula can be simplified to $A_v = -R_C/r_e$.


Summary of Discrete MOS Amplifiers•

Common Drain (Source Follower):

$$A_v = \frac{g_m(r_o \parallel R_S \parallel R_L)}{1 + g_m(r_o \parallel R_S \parallel R_L)}$$

$$R_i = R_G$$

$$R_o = \frac{1}{g_m} \parallel R_S$$

 


Common Source:

$$A_v = -g_m(r_o \parallel R_D \parallel R_L)$$

$$R_i = R_G$$

$$R_o = R_D \parallel r_o$$
 
$$f_{p3} = \frac{1}{2\pi C_s [R_S \parallel (1/g_m)]}$$




Common Source with Source Resistance:

$$A_v = -\frac{g_m(R_D \parallel R_L)}{1 + g_m R_S + (R_D \parallel R_L)/r_o}$$

$$R_i = R_G$$
 
$$R_o = R_D \parallel [r_o(1 + g_m R_S)]$$




Common Gate:

$$A_v = g_m(r_o \parallel R_D \parallel R_L)$$

$$R_i = R_S \parallel \frac{1 + (R_D \parallel R_L)/r_o}{g_m}$$
 
$$R_o = R_D \parallel [r_o(1 + g_m(R_S \parallel R_{sig}))]$$



- $f_l = \Sigma_j f_{pj}$ and $f_{p1} = 1/[2\pi C_{c1}(R_i + R_{sig})]$ and $f_{p2} = 1/[2\pi C_{c2}(R_L + R_o)]$


Summary of Discrete BJT Amplifiers•

Common Collector (Emitter Follower):

$$A_v = \frac{g_m(r_o \parallel R_E \parallel R_L)}{1 + g_m(r_o \parallel R_E \parallel R_L)}$$

$$R_i = R_B \parallel [r_\pi + \beta(r_o \parallel R_E \parallel R_L)]$$
 
$$R_o = R_E \parallel r_o \parallel \frac{r_\pi + R_B \parallel R_{sig}}{1 + \beta}$$




Common Emitter:

$$A_v = -g_m(r_o \parallel R_C \parallel R_L)$$

$$R_i = R_B \parallel r_\pi$$

$$R_o = R_C \parallel r_o$$
 
$$f_{p3} = \frac{1}{2\pi C_e [R_E \parallel (1/g_m + (R_B \parallel R_{sig})/\beta)]}$$




Common Emitter with Emitter Resistor:

$$A_v \approx -\frac{g_m(R_C \parallel R_L)}{1 + g_m R_E}$$

$$R_i = R_B \parallel [r_\pi + (1 + \beta)R_E]$$

$$R_o = R_C \parallel \left[r_o \left(1 + \frac{\beta R_E}{r_\pi + R_E + R_B \parallel R_{sig}} \right) \right]$$

$$R_o \approx R_C$$

 


Common Base:

$$\frac{v_o}{v_i} = g_m(r_o \parallel R_C \parallel R_L)$$

$$R_i = R_E \parallel r_\pi \parallel \frac{1 + (R_C \parallel R_L)/r_o}{g_m}$$

$$R_o = R_C \parallel [r_o(1 + g_m(R_E \parallel r_\pi \parallel R_{sig}))]$$

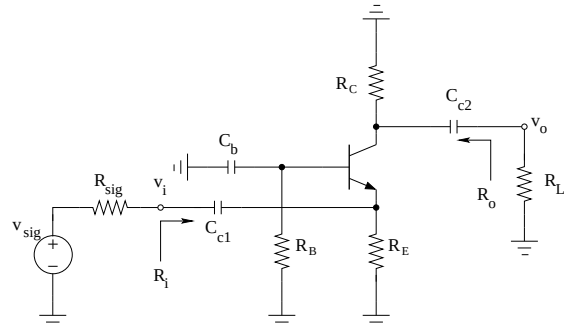
$$f_{p3} = 1/[2\pi C_b R_{CB}] \quad R_{CB} \equiv R_B \parallel [r_\pi + (1 + \beta)(R_{sig} \parallel R_E)]$$




- $f_l = \sum_j f_{pj}$ and $f_{p1} = 1/[2\pi C_{c1}(R_i + R_{sig})]$ and $f_{p2} = 1/[2\pi C_{c2}(R_L + R_o)]$

6.8 Exercise Problems


Problem 1 to 13: Find the bias point and amplifier parameters of this circuit (Si BJT with $\beta = 200$ and $V_A = 150$ V. Ignore the Early effect in biasing calculations).

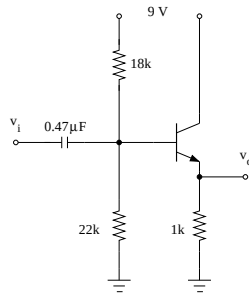


Problem 1

 


Problem 2

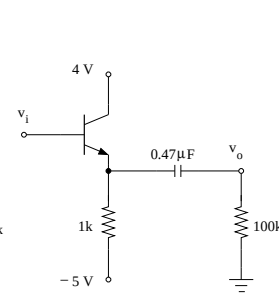


Problem 3

 


Problem 4

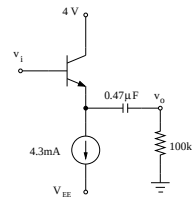


Problem 5

 


Problem 6

 


Problem 7

 


Problem 8

 


Problem 9

 


Problem 8

 


Problem 9

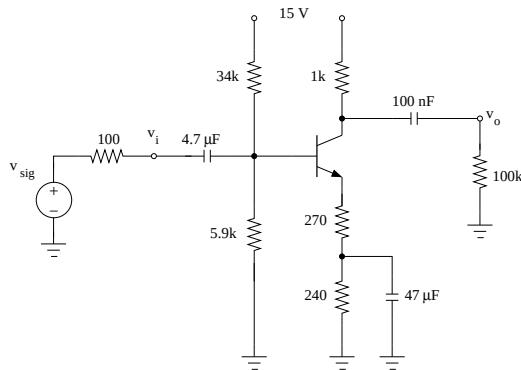

Problem 10

 


Problem 11

 


Problem 12


Problem 14-17. Find the bias point and amplifier parameters of this circuit ($V_{tn} = 4$ V, $V_{tp} = -4$ V, $\mu_p C_{ox}(W/L) = \mu_n C_{ox}(W/L) = 0.4$ mA/V², and $\lambda = 0.01$ V⁻¹. Ignore the channel-width modulation effect in biasing calculations.)

 


Problem 13

 


Problem 14

 

Problem 15

 


Problem 16

 


Problem 17


Problem 18-24. Find the bias point and amplifier parameters of this circuit ($V_{tn} = 1$ V, $V_{tp} = -1$ V, $\mu_p C_{ox}(W/L) = \mu_n C_{ox}(W/L) = 0.8$ mA/V², and $\lambda = 0.01$ V⁻¹. Ignore the channel-width modulation effect in biasing calculations.

 


Problem 18

 


Problem 19

 


Problem 20

 


Problem 21

 

Problem 22

 

Problem 23

 

Problem 24

6.9 Solution to Selected Exercise Problems

Problem 1. Find the bias point and amplifier parameters of this circuit (Si BJT with $\beta = 200$ and $V_A = 150$ V. Ignore the Early effect in biasing calculations).

Bias: Set $v_i = 0$ and capacitors open. Set $v_i = 0$ and capacitors open. Replace R_{B1}/R_{B2} voltage divider with its Thevenin equivalent. Assuming BJT in active,

$$R_B = 18 \text{ k} \parallel 22 \text{ k} = 9.9 \text{ k}\Omega \quad V_{BB} = \frac{22}{18 + 22} \times 9 = 4.95 \text{ V}$$

$$\text{KVL: } V_{BB} = R_B I_B + V_{BE} + 10^3 I_E$$

$$4.95 = 9.9 \times 10^3 I_E / (\beta + 1) + 0.7 + 10^3 I_E$$

$$I_E = 4.05 \text{ mA} \approx I_C, \quad I_B = \frac{I_C}{\beta} = 20.3 \mu\text{A}$$

$$\text{KVL: } 9 = V_{CE} + 10^3 I_E$$

$$V_{CE} = 9 - 10^3 \times 4 \times 10^{-3} = 5 \text{ V}$$

Since $V_{CE} > V_{D0} = 0.7$, assumption of BJT in active is correct.

Bias summary: $I_E \approx I_C = 4.05 \text{ mA}$, $I_B = 20.3 \mu\text{A}$, $V_{CE} = 5 \text{ V}$

Small-Signal: First we calculate the small-signal parameters:

$$g_m = \frac{I_C}{V_T} = \frac{4 \times 10^{-3}}{26 \times 10^{-3}} = 156 \text{ mA/V}$$

$$r_\pi = \frac{\beta}{g_m} = 1.28 \text{ k} \quad r_o \approx \frac{V_A}{I_C} = \frac{150}{4 \times 10^{-3}} = 37.0 \text{ k}$$


Note that we could have ignored V_{CE} compared to V_A in the above expression for r_o . Proceeding with the small signal analysis, we zero bias sources (see circuit). As the input is at the base and output is at the emitter, this is a common-collector amplifier (emitter follower). Using formulas of page 6-21 and noting $R_L \rightarrow \infty$, $R_E \ll r_o$, and $R_E \gg r_e$:

$$A_v = \frac{g_m(r_o \parallel R_E \parallel R_L)}{1 + g_m(r_o \parallel R_E \parallel R_L)} = \frac{152}{153} \approx 1$$

$$R_i \approx R_B \parallel [r_\pi + \beta(r_o \parallel R_E \parallel R_L)] = (9.9 \text{ k}) \parallel (1.28 \text{ k} + 195 \text{ k}) = 9.42 \text{ k} \quad (\approx R_B)$$

$$R_o = R_E \parallel r_o \parallel \frac{r_\pi + R_B \parallel R_{Sig}}{1 + \beta} = 6.4 \Omega \quad (\approx \frac{r_\pi}{\beta} = \frac{1}{g_m})$$

$$f_l = f_{p1} = \frac{1}{2\pi C_{c1}(R_i + R_{sig})} = \frac{1}{2\pi \times 0.47 \times 10^{-6} \times (9.9 \times 10^3 + 0)} = 34.2 \text{ Hz}$$

 

Problem 2. Find the bias point and amplifier parameters of this circuit (Si BJT with $\beta = 200$ and $V_A = 150$ V. Ignore the Early effect in biasing calculations).

This is the same circuit as Problem 1 with exception of C_{c2} and R_L . The bias point is exactly the same. As $R_E \ll R_L$, the amplifier parameters would be the same except $f_l = f_{p1} + f_{p2} = 34.3 + 3.39 = 37.6$ Hz.

Problem 3. Find the bias point and amplifier parameters of this circuit (Si BJT with $n = 2$, $\beta = 200$ and $V_A = 150$ V. Ignore the Early effect in biasing calculations).

This circuit is similar to Problem 1 expect that the transistor is biased with two voltage sources (values are chosen to give approximately the same bias point).

Bias: Set $v_i = 0$ and capacitors open:

$$\text{BE-KVL: } 0 = V_{BE} + 10^3 I_E - 5$$

$$I_E = 4.3 \text{ mA} \approx I_C, \quad I_B = \frac{I_C}{\beta} = 21.5 \text{ } \mu\text{A}$$

$$\text{CE-KVL: } 4 = V_{CE} + 10^3 I_E - 5$$


$$V_{CE} = 9 - 10^3 \times 4.3 \times 10^{-3} = 4.7 \text{ V}$$

Bias summary: $I_E \approx I_C = 4.3 \text{ mA}$, $I_B = 21.5 \text{ } \mu\text{A}$, $V_{CE} = 4.7 \text{ V}$

Small-Signal: First we calculate the small-signal parameters:

$$g_m = \frac{I_C}{V_T} = \frac{4.3 \times 10^{-3}}{26 \times 10^{-3}} = 165.4 \text{ mA/V}$$
 
$$r_\pi = \frac{\beta}{g_m} = 1.21 \text{ k} \quad r_o \approx \frac{V_A}{I_C} = \frac{150}{4.3 \times 10^{-3}} = 34.9 \text{ k}$$



Proceeding with the signal analysis, we zero bias sources (see circuit). As the input is at the base and output is at the emitter, this is a common-collector amplifier (emitter follower). The difference with Problem 1 is that there is no R_B ($R_B = \infty$) which affects R_i only.

$$A_v = \frac{g_m(r_o \parallel R_E \parallel R_L)}{1 + g_m(r_o \parallel R_E \parallel R_L)} = \frac{161}{162} \approx 1$$

$$R_i \approx R_B \parallel [r_\pi + (1 + \beta)(r_o \parallel R_E \parallel R_L)] = \infty \parallel (1.21 \text{ k} + 194 \text{ k}) = 195 \text{ k}$$

$$R_o = R_E \parallel r_o \parallel \frac{r_\pi + R_B \parallel R_{Sig}}{1 + \beta} = 6.0 \text{ } \Omega \quad (\approx \frac{r_\pi}{\beta} = \frac{1}{g_m})$$

$$f_l = f_{p2} = \frac{1}{2\pi C_{c2}(R_L + R_o)} = \frac{1}{2\pi \times 0.47 \times 10^{-6} \times (100 \times 10^3 + 6)} = 3.39 \text{ Hz}$$

Problem 5. Find the bias point and amplifier parameters of this circuit (Si BJT with $\beta = 200$ and $V_A = 150$ V. Ignore the Early effect in biasing calculations).

This circuit is similar to the circuit of Problem 3 except that the transistor is biased with a current source.

Bias: Set $v_i = 0$ and capacitors open.

$$I_E = 4.3 \text{ mA} \approx I_C, \quad I_B = \frac{I_C}{\beta} = 21.5 \text{ } \mu\text{A}$$

$$\text{BE-KVL: } 0 = V_{BE} + V_E \rightarrow V_E = -0.7 \text{ V}$$


$$\text{CE-KVL: } 4 = V_{CE} + V_E \rightarrow V_{CE} = 4.7 \text{ V}$$

Bias summary: $I_E \approx I_C = 4.3 \text{ mA}$, $I_B = 21.5 \text{ } \mu\text{A}$, $V_{CE} = 4.7 \text{ V}$

Small-Signal: First we calculate the small-signal parameters:

$$g_m = \frac{I_C}{V_T} = \frac{4.3 \times 10^{-3}}{26 \times 10^{-3}} = 165.4 \text{ mA/V}$$
 
$$r_\pi = \frac{\beta}{g_m} = 1.21 \text{ k} \quad r_o \approx \frac{V_A}{I_C} = \frac{150}{4.3 \times 10^{-3}} = 34.9 \text{ k}$$



Amplifier Response: we zero bias sources (the current source becomes an open circuit. As the input is at the base and output is at the emitter, this is a common-collector amplifier (emitter follower). The difference with problem 3 is that here $R_E \rightarrow \infty$. Using formulas of page 6-21 and noting $R_E \parallel R_L = R_L \gg r_e$

$$A_v = \frac{g_m(r_o \parallel R_E \parallel R_L)}{1 + g_m(r_o \parallel R_E \parallel R_L)} = \frac{4,279}{4,280} \approx 1$$

$$R_i \approx R_B \parallel [r_\pi + \beta(r_o \parallel R_E \parallel R_L)] = \infty \parallel (1.21 \text{ k} + 5.17 \text{ M}) = 5.17 \text{ M}$$

$$R_o = R_E \parallel r_o \parallel \frac{r_\pi + R_B \parallel R_{Sig}}{1 + \beta} = 6.0 \text{ } \Omega \quad (\approx \frac{r_\pi}{\beta} = \frac{1}{g_m})$$

$$f_l = f_{p2} = \frac{1}{2\pi C_{c2}(R_L + R_o)} = 3.39 \text{ Hz}$$

Comparing results from Problems 1 through 5 highlights the impact of each element on the amplifier performance as in successive problems, R_L and C_{C2} were added, and then R_B , C_{C1} and R_E were eliminated.

Problem 6. Find the bias point and amplifier parameters of this circuit (Si BJT with $\beta = 200$ and $V_A = 150$ V. Ignore the Early effect in biasing calculations).

This circuit is similar to the circuit of Problem 5 except that C_{c2} is removed. The load (100 k resistor) exists in the bias circuit. However, the bias current in the 100 K resistor is small and does not alter the bias. The output voltage, v_o , however, include the DC bias voltage.

Bias: Set $v_i = 0$ and capacitors open.

$$\text{BE-KVL: } 0 = V_{BE} + V_E \rightarrow V_E = -0.7 \text{ V}$$

$$i_1 = \frac{V_E}{100 \times 10^3} = -7 \mu\text{A}$$


$$\text{KCL } I_E = 4.3 \times 10^{-3} + i_1 = 4.3 \text{ mA}$$

$$I_C \approx I_E = 4.3 \text{ mA}, \quad I_B = \frac{I_C}{\beta} = 21.5 \mu\text{A}$$

$$\text{CE-KVL: } 4 = V_{CE} + V_E \rightarrow V_{CE} = 4.7 \text{ V}$$

Bias summary: $I_E \approx I_C = 4.3 \text{ mA}$, $I_B = 21.5 \mu\text{A}$, $V_{CE} = 4.7 \text{ V}$ which are the exactly the same values as of those of Problem 5.

The amplifier parameters are exactly the same as those of Problem 6 expect $f_t = 0$.

 

Problem 7. Find the bias point and amplifier parameters of this circuit (Si BJT with $\beta = 200$ and $V_A = 150$ V. Ignore the Early effect in biasing calculations).

Bias: Set $v_i = 0$ and capacitors open. Replace R_{B1}/R_{B2} voltage divider with its Thevenin equivalent:

$$R_B = 5.9 \text{ k} \parallel 34 \text{ k} = 5.0 \text{ k},$$

$$V_{BB} = \frac{5.9}{5.9 + 34} \times 15 = 2.22 \text{ V}$$



$$\text{BE-KVL: } V_{BB} = R_B I_B + V_{BE} + 510 I_E$$

$$2.22 = 5.0 \times 10^3 I_E / (\beta + 1) + 0.7 + 510 I_E$$

$$I_E = 2.84 \text{ mA} \approx I_C, \quad I_B = \frac{I_C}{\beta} = 14.2 \text{ } \mu\text{A}$$

$$\text{CE-KVL: } 15 = 1000 I_C + V_{CE} + 510 I_E$$

$$V_{CE} = 10.5 \text{ V} > V_{D0}$$

  


Bias summary: $I_C \approx I_E = 2.84 \text{ mA}$, $I_B = 14.2 \text{ } \mu\text{A}$, $V_{CE} = 10.5 \text{ V}$

Small-Signal: First we calculate the small-signal parameters:

$$g_m = \frac{I_C}{V_T} = \frac{2.84 \times 10^{-3}}{26 \times 10^{-3}} = 109 \text{ mA/V}$$
 
$$r_\pi = \frac{\beta}{g_m} = 1.83 \text{ k} \quad r_o \approx \frac{V_A}{I_C} = \frac{150}{2.84 \times 10^{-3}} = 52.8 \text{ k}$$



Proceeding with the small signal analysis, we zero bias sources (see circuit). As the input is at the base and output is at the collector, this is a common-emitter amplifier with NO emitter resistor as there is bypass capacitor.

$$\frac{v_o}{v_i} = -g_m(r_o \parallel R_C \parallel R_L) = -106$$

$$R_i = R_B \parallel r_\pi = 5.0 \parallel 1.83 = 1.34 \text{ k}$$

$$A_v = \frac{v_o}{v_{sig}} = \frac{R_i}{R_i + R_{sig}} \times \frac{v_o}{v_i} = -0.93 \times 106 = -99$$

$$R_o = R_C \parallel r_o = 0.98 \text{ k} \quad (\approx R_C)$$

$$f_{p1} = \frac{1}{2\pi C_{c1}(R_i + R_{sig})} = \frac{1}{2\pi \times 4.7 \times 10^{-6} \times (1,340 + 0)} = 25.3 \text{ Hz}$$

$$f_{p2} = \frac{1}{2\pi C_{c2}(R_L + R_o)} = \frac{1}{2\pi 100 \times 10^{-9}(100 \times 10^3 + 980)} = 15.9 \text{ Hz}$$

$$f_{p3} = \frac{1}{2\pi C_e[R_E \parallel (1/g_m + (R_B \parallel R_{sig})/\beta)]}$$

$$f_{p3} = \frac{1}{2\pi C_e[R_E \parallel 9.67]} = 356 \text{ Hz}$$

$$f_l = f_{p1} + f_{p2} + f_{p3} = 25.3 + 15.9 + 356 = 397 \text{ Hz}$$

Note that although C_b is the largest capacitor in the circuit (*e.g.*, 10 times larger than C_{c1} , f_{p3} is 10 times larger than the other poles.


Problem 9. Find the bias point and amplifier parameters of this circuit (Si BJT with $\beta = 200$ and $V_A = 150 \text{ V}$. Ignore the Early effect in biasing calculations).

Bias: Set $v_i = 0$ and capacitors open. The bias circuit is exactly that of Problem 7 with $R_B = 5.0 \text{ k}$.

Bias summary:

$$I_C \approx I_E = 2.84 \text{ mA}, \quad I_B = 14.2 \mu\text{A}, \quad V_{CE} = 10.5 \text{ V}$$

 Small-Signal: The small-signal parameters are also the same as those of Problem 7: $g_m = 109 \text{ mA/V}$, $r_\pi = 1.83 \text{ k}$, and $r_o = 52.8 \text{ k}$.



Proceeding with the small signal analysis, we zero bias sources (see circuit). As the input is at the base and output is at the collector, this is a degenerated common-emitter amplifier (*i.e.*, with a emitter resistor):

$$\frac{v_o}{v_i} \approx -\frac{g_m(R_C \parallel R_L)}{1 + g_m R_E} = -1.91$$

$$R_i = R_B \parallel [r_\pi + (1 + \beta)R_E] = 4.8 \text{ k} \quad (\approx R_B)$$

$$A_v = \frac{v_o}{v_{sig}} = \frac{R_i}{R_i + R_{sig}} \times \frac{v_o}{v_i} = -0.98 \times 1.91 = -1.87$$


$$R_o = R_C \parallel \left[r_o \left(1 + \frac{\beta R_E}{r_\pi + R_E + R_B \parallel R_{sig}} \right) \right] \approx R_C = 1 \text{ k}$$

$$f_{p1} = \frac{1}{2\pi C_{c1}(R_i + R_{sig})} = \frac{1}{2\pi \times 4.7 \times 10^{-6} \times (4,800 + 100)} = 6.91 \text{ Hz}$$

$$f_{p2} = \frac{1}{2\pi C_{c2}(R_L + R_o)} \approx \frac{1}{2\pi C_{c2}(R_L + R_c)} \approx \frac{1}{2\pi 100 \times 10^{-9}(100 \times 10^3 + 10^3)} = 15.8 \text{ Hz}$$

$$f_l = f_{p1} + f_{p2} = 6.9 + 15.8 = 22.7 \text{ Hz}$$

 Problem 10. Find the bias point and amplifier parameters of this circuit (Si BJT with $\beta = 200$ and $V_A = 150$ V. Ignore the Early effect in biasing calculations).




Bias:

Set $v_i = 0$ and capacitors open. Because the $47 \mu\text{F}$ capacitor across the 240Ω resistor becomes an open circuit, the total R_E for bias is $270 + 240 = 510 \Omega$ and the bias circuit is exactly that of Problem 7 (or Problem 9) with $R_B = 5.0$ k.


Bias summary:

$$I_C \approx I_E = 2.84 \text{ mA}, \quad I_B = 14.2 \mu\text{A}, \quad V_{CE} = 10.5 \text{ V}$$

 Small-Signal: The small-signal parameters are also the same as those of Problem 7: $g_m = 109 \text{ mA/V}$, $r_\pi = 1.83\text{k}$, and $r_o = 52.8 \text{ k}$.



 Proceeding with the small signal analysis, we zero bias sources (see circuit). As the input is at the base and output is at the collector, this is a degenerated common-emitter amplifier (*i.e.*, with a emitter resistor). For midband amplifier parameters calculations, the $47 \mu\text{F}$ capacitor across the 240Ω resistor becomes a short circuit and the total R_E for small-signal is 270Ω .



$$\frac{v_o}{v_i} \approx -\frac{g_m(R_C \parallel R_L)}{1 + g_m R_E} = -3.55$$

$$R_i = R_B \parallel [r_\pi + (1 + \beta)R_E] = 4.6 \text{ k} \quad (\approx R_B)$$

$$A_v = \frac{v_o}{v_{sig}} = \frac{R_i}{R_i + R_{sig}} \times \frac{v_o}{v_i} = -0.98 \times 1.91 = -3.47$$

$$R_o = R_C \parallel \left[r_o \left(1 + \frac{\beta R_E}{r_\pi + R_E + R_B \parallel R_{sig}} \right) \right] \approx R_C = 1 \text{ k}$$



$$f_{p1} = \frac{1}{2\pi C_{c1}(R_i + R_{sig})} = \frac{1}{2\pi \times 4.7 \times 10^{-6} \times (4,600 + 100)} = 7.20 \text{ Hz}$$

$$f_{p2} = \frac{1}{2\pi C_{c2}(R_L + R_o)} \approx \frac{1}{2\pi C_{c2}(R_L + R_c)} \approx \frac{1}{2\pi 100 \times 10^{-9}(100 \times 10^3 + 10^3)} = 15.8 \text{ Hz}$$

We need to find the pole introduced by the $47 \mu\text{F}$ by-pass capacitor, f_{pb} . Although this configuration was not included in the formulas for BJT elementary configuration of page 6-21, we can extend those formulas to cover this case.

The pole introduced by the by-pass capacitor in the common emitter case is (see figure below left)
  
$$f_{p3} = \frac{1}{2\pi C_e [R_E \parallel (1/g_m + (R_B \parallel R_{sig})/\beta)]}$$



Per our discussion of Section 6.7 on how to find poles introduced by each capacitor, $R_E \parallel [1/g_m + (R_B \parallel R_{sig})/\beta]$ is the total resistance seen across the terminal of C_e . As can be seen from the circuit (above right), the resistance across C_e terminals consists of two resistors in parallel, R_E and R_e . R_e is the resistance seen between the emitter of the BJT and the ground and is: $R_e \equiv 1/g_m + (R_B \parallel R_{sig})/\beta$ from the above formula.

For the circuit here (defined $R_{E1} = 240 \Omega$ and $R_{E2} = 270 \Omega$), the resistance across C_e is made of two resistances in parallel: R_{E1} and the combination of R_{E2} and R_e , the resistance seen through the emitter of BJT in series. Thus:

$$f_{p3} = \frac{1}{2\pi C_b [R_{E1} \parallel (R_{E2} + 1/g_m + (R_B \parallel R_{sig})/\beta)]}$$

$$f_{pb} = \frac{1}{2\pi \times C_e [240 \parallel (270 + 9.17 + 0.49)]} = \frac{1}{2\pi \times 47 \times 10^{-6} \times 129} = 26.2 \text{ Hz}$$

$$f_l = f_{p1} + f_{p2} = 7.20 + 15.8 + 26.2 = 49.2 \text{ Hz}$$

Problem 11. Find the bias point and amplifier parameters of this circuit (Si BJT with $\beta = 200$ and $V_A = 150$ V. Ignore the Early effect in biasing calculations).

Bias: Set $v_i = 0$ and capacitors open.

$$\text{BE-KVL: } 3 = 2.3I_E + V_{EB}$$

$$I_E = 1 \text{ mA} \approx I_C, \quad I_B = I_E/(1 + \beta) = 5 \text{ } \mu\text{A}$$

$$\text{CE-KVL: } 3 = 2.3 \times 10^3 I_E + V_{EC} + 2.3 \times 10^3 I_C - 3$$


$$V_{EC} = 6 - 4.6 \times 10^3 \times 1 \times 10^{-3} = 1.4 \text{ V}$$

Bias summary: $I_C \approx I_E = 1 \text{ mA}$, $I_B = 5.0 \text{ } \mu\text{A}$, $V_{CE} = 1.4 \text{ V}$

Small-Signal: First we calculate the small-signal parameters:

$$g_m = \frac{I_C}{V_T} = \frac{1 \times 10^{-3}}{26 \times 10^{-3}} = 38.5 \text{ mA/V}$$
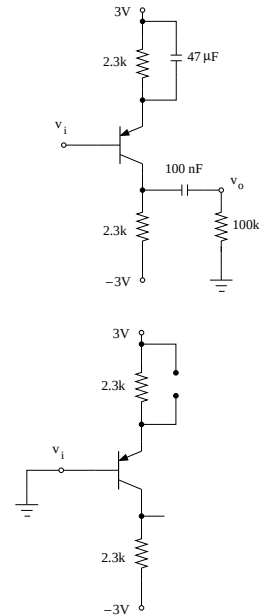
$$r_\pi = \frac{\beta}{g_m} = 5.26 \text{ k} \quad r_o \approx \frac{V_A}{I_C} = \frac{150}{1 \times 10^{-3}} = 150 \text{ k}$$



Proceeding with the small signal analysis, we zero bias sources. As the input is at the base and output is at the collector, this is a common-emitter amplifier. It does not have an emitter resistor as $47 \text{ } \mu\text{F}$ capacitor shorts out R_E for signals.

$$A_v = -g_m(r_o \parallel R_C \parallel R_L) = -38.5 \times 10^{-3}(150 \text{ k} \parallel 1 \text{ k} \parallel 100 \text{ k}) = -37.9$$

$$R_i = R_B \parallel r_\pi = 10.4 \text{ k}$$

$$R_o = R_C \parallel r_o = 0.99 \text{ k}$$

$$f_{p1} = 0$$

$$f_{p2} = \frac{1}{2\pi C_{c2}(R_L + R_o)} = \frac{1}{2\pi 100 \times 10^{-9}(10^5 + 10^3)} = 15.8 \text{ Hz}$$

$$f_{p3} = \frac{1}{2\pi C_e[R_E \parallel (1/g_m + (R_B \parallel R_{sig})/\beta)]} = \frac{1}{2\pi C_e[2, 300 \parallel 26]} = 132 \text{ Hz}$$

$$f_l = f_{p1} + f_{p2} + f_{pb} = 0 + 15.8 + 132 = 148 \text{ Hz}$$

Problem 12. Find the bias point and amplifier parameters of this circuit (Si BJT with $\beta = 200$ and $V_A = 150$ V. Ignore the Early effect in biasing calculations).

This is the same circuit as that of Problem 11 expect that the transistor is biased with a current source

Bias: Set $v_i = 0$ and capacitors open. From the circuit $I_E = 1$ mA

$$I_E = 1 \text{ mA} \approx I_C, \quad I_B = \frac{I_C}{\beta} = 5 \mu\text{A}$$

$$\text{BE-KVL: } V_E = V_{EB} = 0.7 \text{ V}$$

$$\text{CE-KVL: } V_E = V_{CE} + 2.3 \times 10^3 I_C - 3 = V_{CE} - 0.7$$


$$V_{CE} = 1.4 \text{ V}$$

Bias summary: $I_C \approx I_E = 1$ mA, $I_B = 50 \mu\text{A}$, $V_{CE} = 1.4$ V.

Small-Signal: As the bias point is exactly the same as that of problem 11, we have: $g_m = 38.5$ mA/V, $r_\pi = 5.26\text{k}$, and $r_o = 150$ k.

Amplifier response: The only difference with problem 11 is that $R_E \rightarrow \infty$ in this circuit. R_E only appears in f_{p3} but $R_E = \infty$ does not change results:

$A_v = -37.9$, $R_i = 10.4$ k, $R_o = 0.99$ k, and $f_l = 0 + 15.8 + 132 = 148$ Hz.

 

Problem 13. Find the bias point and amplifier parameters of this circuit (Si BJT with $\beta = 200$ and $V_A = 150$ V. Ignore the Early effect in biasing calculations).

Bias: Set $v_i = 0$ and capacitors open.

$$R_B = 12 \text{ k} \parallel 13 \text{ k} = 6.24 \text{ k},$$

$$V_{BB} = \frac{12}{12 + 13} \times 2.5 = 1.2 \text{ V}$$

$$\text{BE-KVL: } V_{BB} = R_B I_B + V_{BE} + 510 I_E$$


$$1.2 = 6.24 \times 10^3 I_E / (1 + \beta) + 0.7 + 400 I_E$$

$$I_E = 1.16 \text{ mA} \approx I_C, \quad I_B = \frac{I_C}{\beta} = 5.8 \mu\text{A}$$

$$\text{CE-KVL: } 2.5 = 1000 I_C + V_{CE} + 400 I_E$$

$$V_{CE} = 2.5 - 1,400 \times 1.16 \times 10^{-3} = 0.88 \text{ V}$$

 Bias summary: $I_C \approx I_E = 1.16$ mA, $I_B = 5.8 \mu\text{A}$, $V_{CE} = 0.88$ V



Small-Signal: First we calculate the small-signal parameters:

$$g_m = \frac{I_C}{V_T} = \frac{1.16 \times 10^{-3}}{26 \times 10^{-3}} = 44.6 \text{ mA/V}$$

$$r_\pi = \frac{\beta}{g_m} = 4.48 \text{ k} \quad r_o \approx \frac{V_A}{I_C} = \frac{150}{1.16 \times 10^{-3}} = 129 \text{ k}$$

Proceeding with the small signal analysis, we zero bias sources. As the input is at the emitter and output is at the collector, this is a common-base amplifier (note $R_L = \infty$).

$$\frac{v_o}{v_i} = g_m(r_o \parallel R_C \parallel R_L) = 44.6 \times 10^{-3}(129 \text{ k} \parallel 1 \text{ k} \parallel \infty) = 44.26$$

$$R_i = R_E \parallel r_\pi \parallel \frac{1 + (R_C \parallel R_L)/r_o}{g_m} = 1 \text{ k} \parallel 4.48 \text{ k} \parallel 22.4 = 21.8 \Omega \quad (\approx 1/g_m)$$

$$R_o = R_C \parallel [r_o(1 + g_m(R_E \parallel r_\pi \parallel R_{sig}))] \approx R_C = 1 \text{ k}$$

$$f_{p1} = \frac{1}{2\pi C_{c1}(R_i + R_{sig})} = \frac{1}{2\pi 1000 \times 10^{-9}(21.8)} = 7.30 \text{ kHz}$$

$$f_{p2} = \frac{1}{2\pi C_{c2}(R_L + R_o)} = 0$$

$$R_{CB} \equiv R_B \parallel [r_\pi + (1 + \beta)(R_{sig} \parallel R_E)] = 6.24 \text{ k} \parallel 84.9 \text{ k} \approx 5.81 \text{ k}$$

$$f_{p3} = \frac{1}{2\pi C_b R_{CB}} = \frac{1}{2\pi \times 100 \times 10^{-9} \times 5.81 \times 10^3} = 274 \text{ Hz}$$

$$f_l = f_{p1} + f_{p2} + f_{p3} = 7,300 + 0 + 274 = 7.57 \text{ kHz}$$


Note the small input resistance of this amplifier and corresponding large f_{p1} .

Problem 14. Find the bias point and amplifier parameters of this circuit ($V_{tn} = 4 \text{ V}$, $V_{tp} = -4 \text{ V}$, $\mu_p C_{ox}(W/L) = \mu_n C_{ox}(W/L) = 0.4 \text{ mA/V}^2$, and $\lambda = 0.01 \text{ V}^{-1}$. Ignore the channel-width modulation effect in biasing calculations.)

Bias: Since $I_G = 0$:

$$V_G = \frac{0.5 \text{ M}}{1.3 \text{ M} + 0.5 \text{ M}} \times 18 = 5 \text{ V}$$
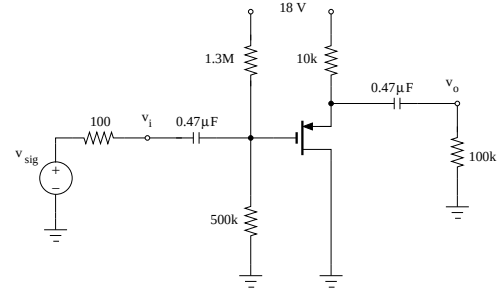
$$R_G = 1.3 \text{ M} \parallel 500 \text{ k} = 361 \text{ k}$$




Assume PMOS is in the active state,

$$I_D = 0.5 \mu_p C_{ox}(W/L) V_{OV}^2$$

$$\text{SG-KVL: } 18 = 10^4 I_D + V_{SG} + V_G = 10^4 I_D + V_{OV} + |V_{tp}| + V_G$$

$$10^4 \times 0.5 \times 0.4 \times 10^{-3} V_{OV}^2 + V_{OV} - 18 + 4 + 5 = 0$$

$$2V_{OV}^2 + V_{OV} - 9 = 0$$

 

Negative root is unphysical, $V_{OV} = 1.89 \text{ V}$ and $V_{SG} = V_{OV} + |V_{tp}| = 5.89 \text{ V}$.

$$I_D = 0.5 \times 0.4 \times 10^{-3} V_{OV}^2 = 0.71 \text{ mA}$$

$$\text{SD-KVL: } 18 = V_{SD} + 10^4 I_D \rightarrow V_{SD} = 18 - 10^4 \times 0.71 \times 10^{-3} = 10.9 \text{ V}$$

Since $V_{SD} = 10.9 \geq V_{OV} = 1.89 \text{ V}$, our assumption of PMOS in active is justified.

Bias summary: $I_D = 0.71 \text{ mA}$, $V_{OV} = 1.89 \text{ V}$, $V_{SG} = 5.89 \text{ V}$, $V_{SD} = 10.9 \text{ V}$.

Small-Signal: First we calculate the small-signal parameters:

$$g_m = \frac{2I_D}{V_{OV}} = \frac{2 \times 0.71 \times 10^{-3}}{1.89} = 0.751 \text{ mA/V}$$

$$r_o = \frac{1}{\lambda I_D} = \frac{1}{0.01 \times 0.71 \times 10^{-3}} = 141 \text{ k}$$

Proceeding with the small signal analysis, we zero bias sources. As the input is at the gate and output is at the source, this is a common-drain amplifier (source follower).

$$\frac{v_o}{v_i} = \frac{g_m(r_o \parallel R_S \parallel R_L)}{1 + g_m(r_o \parallel R_S \parallel R_L)} = \frac{6.41}{7.41} = 0.866$$

$$R_i = R_G = 361 \text{ k}$$

$$A_v = \frac{v_o}{v_{sig}} = \frac{R_i}{R_i + R_{sig}} \times \frac{v_o}{v_i} = 0.866$$

$$R_o = \frac{1}{g_m} \parallel R_S = 1.33 \text{ k} \parallel 10 \text{ k} = 1.17 \text{ k}$$

$$f_{p1} = 1/[2\pi C_{c1}(R_i + R_{sig})] = 0.94 \text{ Hz}$$

$$f_{p2} = 1/[2\pi C_{c2}(R_L + R_o)] = 3.39 \text{ Hz}$$

$$f_l = f_{p1} + f_{p2} = 4.33 \text{ Hz}$$


Problem 15. Find the bias point and amplifier parameters of this circuit ($V_{tn} = 4 \text{ V}$, $V_{tp} = -4 \text{ V}$, $\mu_p C_{ox}(W/L) = \mu_n C_{ox}(W/L) = 0.4 \text{ mA/V}^2$, and $\lambda = 0.01 \text{ V}^{-1}$. Ignore the channel-width modulation effect in biasing calculations.

Answer:

$$I_D = 0.71 \text{ mA}, V_{OV} = 1.89 \text{ V}, V_{SG} = 5.89 \text{ V}, V_{SD} = 10.9 \text{ V}.$$

$$v_o/v_{sig} = 0.866, R_i = \infty, R_o = 1.17 \text{ k},$$
 
$$f_{p1} = 0, f_{p2} = 3.35 \text{ Hz}, f_l = 4.3 \text{ Hz}.$$



Problem 16. Find the bias point and amplifier parameters of this circuit ($V_{tn} = 4 \text{ V}$, $V_{tp} = -4 \text{ V}$, $\mu_p C_{ox}(W/L) = \mu_n C_{ox}(W/L) = 0.4 \text{ mA/V}^2$, and $\lambda = 0.01 \text{ V}^{-1}$. Ignore the channel-width modulation effect in biasing calculations.)

This circuit is also similar to that of problem 14 expect that it is biased with a current source:

$$I_D = 0.71 \text{ mA}$$

$$I_D = 0.5\mu_p C_{ox}(W/L)V_{OV}^2$$

$$0.71 \times 10^{-3} = 0.5 \times 0.4 \times 10^{-3} V_{OV}^2$$

$$V_{OV} = 1.88 \text{ V}$$



$$V_{SG} = V_{OV} + |V_{tp}| = 5.88 \text{ V}$$

$$V_{SG} = V_S - V_G = 5.88 \rightarrow V_S = 5.88 \text{ V}$$

$$V_{SD} = V_S - V_D = 5.88 - (-5) = 10.9 \text{ V} \quad (> V_{OV} = 1.89)$$


Bias summary:
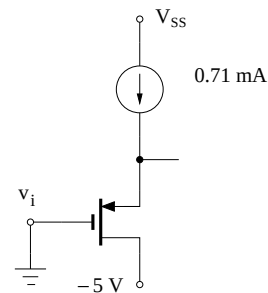 
$$I_D = 0.71 \text{ mA}, V_{OV} = 1.88 \text{ V}, V_{SG} = 5.88 \text{ V}, V_{SD} = 10.9 \text{ V}.$$



$$g_m = \frac{2I_D}{V_{OV}} = \frac{2 \times 0.71 \times 10^{-3}}{1.89} = 0.751 \text{ mA/V}$$
 
$$r_o = \frac{1}{\lambda I_D} = \frac{1}{0.01 \times 0.71 \times 10^{-3}} = 141 \text{ k}$$



This is a common-drain amplifier (source follower). Note $R_G = \infty$, $R_S = \infty$.

$$\frac{v_o}{v_i} = \frac{g_m(r_o \parallel R_S \parallel R_L)}{1 + g_m(r_o \parallel R_S \parallel R_L)} = \frac{43.9}{44.9} = 0.98$$

$$R_i = R_G = \infty$$

$$A_v = \frac{v_o}{v_{sig}} = \frac{R_i}{R_i + R_{sig}} \times \frac{v_o}{v_i} = 0.98$$

$$R_o = \frac{1}{g_m} \parallel R_S = 1.33 \text{ k} \parallel \infty = 1.33 \text{ k}$$

$$f_{p1} = 1/[2\pi C_{c1}(R_i + R_{sig})] = 0$$

$$f_{p2} = 1/[2\pi C_{c2}(R_L + R_o)] = 3.39 \text{ Hz}$$

$$f_l = f_{p1} + f_{p2} = 3.39 \text{ Hz}$$

Problem 17. Find the bias point and amplifier parameters of this circuit ($V_{tn} = 4 \text{ V}$, $V_{tp} = -4 \text{ V}$, $\mu_p C_{ox}(W/L) = \mu_n C_{ox}(W/L) = 0.4 \text{ mA/V}^2$, and $\lambda = 0.01 \text{ V}^{-1}$. Ignore the channel-width modulation effect in biasing calculations.


Answer:

$$I_D = 0.71 \text{ mA}, V_{OV} = 1.88 \text{ V}, V_{SG} = 5.88 \text{ V}, V_{SD} = 10.9 \text{ V}.$$

$$v_o/v_{sig} = 0.866, R_i = \infty, R_o = 1.17 \text{ k},$$

$$f_{p1} = 0, f_{p2} = 3.35 \text{ Hz}, f_l = 4.3 \text{ Hz}.$$

 Amp Response: $A_v = 0.98, R_i = \infty, R_o = 1.33 \text{ k}, \text{ and } f_l = 3.39 \text{ Hz}.$




Problem 18. Find the bias point and amplifier parameters of this circuit ($V_{tn} = 1 \text{ V}$, $V_{tp} = -1 \text{ V}$, $\mu_p C_{ox}(W/L) = \mu_n C_{ox}(W/L) = 0.8 \text{ mA/V}^2$, and $\lambda = 0.01 \text{ V}^{-1}$. Ignore the channel-width modulation effect in biasing calculations.

Bias: Since $I_G = 0$:

$$V_G = \frac{1.2 \text{ M}}{1.2 \text{ M} + 1.8 \text{ M}} \times 15 = 6 \text{ V}$$
 
$$R_G = 1.2 \text{ M} \parallel 1.8 \text{ M} = 720 \text{ k}$$




Assume NMOS is in the active state,

$$I_D = 0.5 \mu_p C_{ox}(W/L) V_{OV}^2$$

$$\text{GS-KVL: } V_G = V_{GS} + 10^4 I_D = V_{OV} + V_t + 10^4 I_D$$

$$10^4 \times 0.5 \times 0.8 \times 10^{-3} V_{OV}^2 + V_{OV} - 6 + 1 = 0$$

$$4V_{OV}^2 + V_{OV} - 5 = 0$$

 

Negative root is unphysical, $V_{OV} = 1.0 \text{ V}$ and $V_{GS} = V_{OV} + V_t = 2.0 \text{ V}$.

$$I_D = 0.5 \times 0.8 \times 10^{-3} V_{OV}^2 = 0.40 \text{ mA}$$

$$\text{DS-KVL: } 15 = 10^4 I_D + V_{DS} + 10^4 I_D \rightarrow V_{DS} = 7 \text{ V} \quad (> V_{OV} = 1.0)$$

Bias summary: $I_D = 0.40 \text{ mA}$, $V_{OV} = 1.0 \text{ V}$, $V_{GS} = 2.0 \text{ V}$, $V_{DS} = 7.0 \text{ V}$.

Small-Signal:

$$g_m = \frac{2I_D}{V_{OV}} = 2 \times 0.4 \times 10^{-3} = 0.8 \text{ mA/V} \quad r_o = \frac{1}{\lambda I_D} = \frac{1}{0.01 \times 0.4 \times 10^{-3}} = 250 \text{ k}$$

As the input is at the gate and output is at the collector, this is a common-source amplifier. There is no R_S because of the by-pass capacitor.

$$\frac{v_o}{v_i} = -g_m(r_o \parallel R_D \parallel R_L) = -0.8 \times 10^{-3}(250 \text{ k} \parallel 10 \text{ k} \parallel 100 \text{ k}) = -7.02$$

$$R_i = R_G = 720 \text{ k}$$

$$A_v = \frac{v_o}{v_{sig}} = \frac{R_i}{R_i + R_{sig}} \times \frac{v_o}{v_i} = -7.02$$

$$R_o = R_D \parallel r_o = 10 \text{ k} \parallel 100 \text{ k} = 9.09 \text{ k}$$

$$f_{p1} = 1/[2\pi C_{c1}(R_i + R_{sig})] = 2.21 \text{ Hz}$$

$$f_{p2} = 1/[2\pi C_{c2}(R_L + R_o)] = 14.6 \text{ Hz}$$

$$f_{p3} = \frac{1}{2\pi C_s[R_S \parallel (1/g_m)]} = \frac{1}{2\pi C_s[10 \text{ k} \parallel 1.25 \text{ k}]} = \frac{1}{2\pi \times 10^{-6} \times 1.11 \times 10^3} = 143 \text{ Hz}$$


$$f_l = f_{p1} + f_{p2} + f_{p3} = 2.21 + 14.6 + 143 = 160 \text{ Hz}$$

Problem 21. Find the bias point and amplifier parameters of this circuit ($V_{tn} = 1 \text{ V}$, $V_{tp} = -1 \text{ V}$, $\mu_p C_{ox}(W/L) = \mu_n C_{ox}(W/L) = 0.8 \text{ mA/V}^2$, and $\lambda = 0.01 \text{ V}^{-1}$. Ignore the channel-width modulation effect in biasing calculations.

Bias: Since $I_G = 0$:

$$V_G = \frac{1.8 \text{ M}}{1.2 \text{ M} + 1.8 \text{ M}} \times 15 = 9 \text{ V}$$
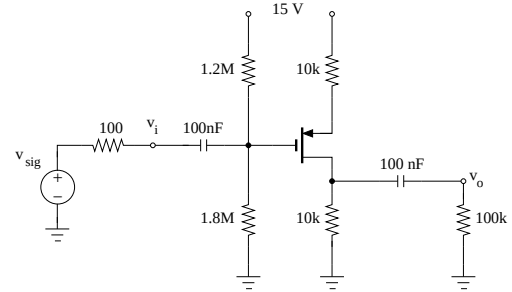
$$R_G = 1.2 \text{ M} \parallel 1.8 \text{ M} = 720 \text{ k}$$




Assume PMOS is in the active state,

$$I_D = 0.5\mu_p C_{ox}(W/L)V_{OV}^2$$

$$\text{SG-KVL: } 15 = 10^4 I_D + V_{SG} + V_G = 10^4 I_D + V_{OV} + |V_{tp}| + V_G$$

$$10^4 \times 0.5 \times 0.8 \times 10^{-3} V_{OV}^2 + V_{OV} - 15 + 9 + 1 = 0$$

$$4V_{OV}^2 + V_{OV} - 5 = 0$$

 

Negative root is unphysical, $V_{OV} = 1.0 \text{ V}$ and $V_{SG} = V_{OV} + |V_{tp}| = 2.0 \text{ V}$.

$$I_D = 0.5 \times 0.8 \times 10^{-3} V_{OV}^2 = 0.40 \text{ mA}$$

$$\text{SD-KVL: } 15 = 10^4 I_D + V_{SD} + 10^4 I_D \rightarrow V_{SD} = 7 \text{ V} \quad (> V_{OV} = 1.0)$$

Bias summary: $I_D = 0.40 \text{ mA}$, $V_{OV} = 1.0 \text{ V}$, $V_{SG} = 2.0 \text{ V}$, $V_{SD} = 7.0 \text{ V}$. Small-Signal:

$$g_m = \frac{2I_D}{V_{OV}} = 2 \times 0.4 \times 10^{-3} = 0.8 \text{ mA/V} \quad r_o = \frac{1}{\lambda I_D} = \frac{1}{0.01 \times 0.4 \times 10^{-3}} = 250 \text{ k}$$

As the input is at the gate and output is at the collector, this is a common-source amplifier with R_S .

$$\frac{v_o}{v_i} = - \frac{g_m(R_D \parallel R_L)}{1 + g_m R_S + (R_D \parallel R_L)/r_o} = - \frac{0.8 \times 10^{-3}(10 \text{ k} \parallel 100 \text{ k})}{1 + 0.8 \times 10^{-3} \times 10^4 + (10 \text{ k} \parallel 100 \text{ k})/(250 \text{ k})}$$

$$\frac{v_o}{v_i} = - \frac{7.27}{9.04} = -0.805$$

$$R_i = R_G = 720 \text{ k}$$

$$A_v = \frac{v_o}{v_{sig}} = \frac{R_i}{R_i + R_{sig}} \times \frac{v_o}{v_i} = -0.805$$

$$R_o = R_D \parallel [r_o(1 + g_m R_S)] = 10 \text{ k} \quad (\approx R_D)$$

$$f_{p1} = 1/[2\pi C_{c1}(R_i + R_{sig})] = 2.21 \text{ Hz}$$

$$f_{p2} = 1/[2\pi C_{c2}(R_L + R_o)] = 14.5 \text{ Hz}$$

$$f_l = f_{p1} + f_{p2} = 16.7 \text{ Hz}$$

Note one needs to choose R_D to be several times R_S for this amplifier to have a gain larger than unity.

Problem 24. Find the bias point and amplifier parameters of this circuit ($V_{tn} = 1 \text{ V}$, $V_{tp} = -1 \text{ V}$, $\mu_p C_{ox}(W/L) = \mu_n C_{ox}(W/L) = 0.8 \text{ mA/V}^2$, and $\lambda = 0.01 \text{ V}^{-1}$. Ignore the channel-width modulation effect in biasing calculations.

Answer:

$$I_D = 0.40 \text{ mA}, V_{OV} = 1.0 \text{ V}, V_{GS} = 2.0 \text{ V}, V_{SD} = 7.0 \text{ V}.$$

$$v_o/v_{sig} = 0.866, R_i = \infty, R_o = 1.17 \text{ k},$$

$$f_{p1} = 0, f_{p2} = 3.35 \text{ Hz}, f_l = 4.3 \text{ Hz}.$$

Amp Response (common-gate amp):

$$A_v = 7.7, R_i = 1.1 \text{ k}, R_o = 10 \text{ k}, \text{ and } f_l = 1.45 \times 10^3 + 22 = 1.47 \text{ kHz},$$

