

University of California, San Diego
Department of Electrical and Computer Engineering

ECE65, Winter 2012


Lab 3, Diode wave-form shaping circuits

In these experiments we examine diode circuits that modify the input wave-form. In these cases (and in many future experiments) you are asked to print out scope traces of input and output voltages of the circuit. You should follow this procedure:

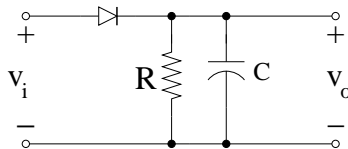- 1) Attach Scope channel 1 to v_i , Scope Channel 2 to v_o , and have both traces be “triggered” by channel 1.
- 2) Move the two traces such that the zero voltage value for both channels are in the middle of the display.
- 3) Expand the time selection so that only 2 to 4 periods of the wave-form are shown.
- 4) Adjust the volt per division knob such that the signal is as large as possible (*i.e.*, fills the display). Ensure that both channels have the same volt per division setting.
- 5) Printout the trace. In this manner v_o and v_i can be directly compared.

Experiment 1: Rectifier & Peak Detector Circuit

Consider the circuit below with a 1N4148 general purpose diode and $R = 100 \text{ k}\Omega$.



Lab Exercise:

- 1) Assemble the circuit without the capacitor. Set the function generator to produce a sinusoidal wave with an amplitude of 5 V, zero DC offset, and frequency of 2 kHz. Attach the function generator to v_i . Attach Scope channel 1 to v_i and Scope Channel 2 to v_o . Adjust scope according to the instruction above. Print out v_o and v_i .
- 2) Disconnect the function generator without changing the function generator and scope settings. Attach a 10 nF capacitor (see circuit diagram above). Attach the function generator to the circuit and print out v_o and v_i .
- 3) Repeat part 2 for $C = 1 \text{ nF}$ and 100 nF.
- 4) Compare the four printout. What are your conclusions?

Experiment 2: Clipper Circuit

Design Problem: Design a clipper circuit using 1N4148 general purpose diodes and a $R = 1 \text{ k}\Omega$ to clip the input signal voltages that are above 5.7 V or less than -0.7 V .


Simulation: Simulate the circuit you have designed with PSpice with two input voltages:
 1) A sinusoidal wave with an amplitude of 8 V and a DC offset of zero and 1) A sinusoidal wave with an amplitude of 8 V and a DC offset of 4 V. In each case, plot v_o and v_i for two period (both traces on the same graph).

Lab Exercise:

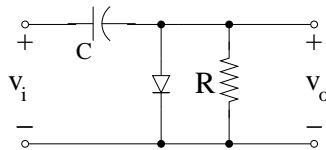- 1) Assemble the circuit that you have designed. Apply a sinusoidal wave with amplitude of 8 V and DC offset of zero to the circuit. Adjust the scope and print out v_i and v_o .
- 2) Increase the DC offset of the input. What do you see? Does it follow your simulation. Explain?
- 3) Set the DC offset to +4V. Adjust scope similar to Experiment 1 and print out v_i and v_o . Explain the results.

Experiment 3: Clamp Circuit

Consider the circuit below with a 1N4148 general purpose diode, $R = 100 \text{ k}\Omega$, and $C = 100 \text{ nF}$.



Lab Exercise:

- 1) Assemble the circuit. Set the function generator to produce a sinusoidal wave with an amplitude of 5 V, zero DC offset, and frequency of 2 kHz. Attach the function generator to v_i . Attach Scope channel 1 to v_i and Scope Channel 2 to v_o . Print out v_o and v_i trace.
- 2) Disconnect the function generator without changing the function generator and scope settings. Replace the 100 nF capacitor with a 1 nF one. Print out v_o and v_i .
- 3) Compare the two cases. What are your conclusions?