

University of California, San Diego
Department of Electrical and Computer Engineering


ECE65, Winter 2012

Lab 6, BJT Biasing and Current Mirror

Note: Manufacturer spec sheet gives $\beta = 100$ for 2N3904 transistor.

Experiment 1: Poor biasing

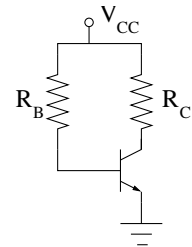Set $R_B = 1.5\text{ M}\Omega$, $R_C = 5\text{ k}\Omega$, $V_{CC} = 15\text{ V}$ and a 2N3904 BJT.



Circuit Analysis:

a) Compute I_C , I_B , and V_{CE} .

PSpice Simulation:

b) Simulate the circuit with PSpice (bias point details only) and compare values of I_C , I_B , V_{CE} , and V_{BE} from PSpice simulations with your circuit analysis.

c) Rerun your PSpice simulations for temperatures of 0 and 60°C. Make a table of I_C , I_B , V_{CE} , and V_{BE} for the above temperatures and that of part b (which is for default temperature). Explain your observations.


Lab Exercise:

d) Set up the circuit and measure I_C , I_B , V_{CE} , and V_{BE} . Note that these measurements are not straightforward. In some cases, you have to measure the quantities “indirectly.” Compare your measurements of I_C , I_B , V_{CE} , and V_{BE} with your PSpice simulations.

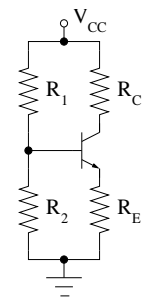e) Set the voltmeter to measure V_{CE} . Hold the transistor between two fingers without touching the rest of the circuit. Transistor will warm up slightly by your body temperature. What happens to V_{CE} as transistor warms up? Explain your observations.

Experiment 2: Good biasing

Set up the circuit with a 2N3904 transistor, $R_2 = 12\text{ k}\Omega$, $R_1 = 39\text{ k}\Omega$, $R_C = 2\text{ k}\Omega$, $R_E = 1\text{ k}\Omega$, and $V_{CC} = 15\text{ V}$.



Circuit Analysis:

a) Compute I_C , I_B , and V_{CE} .

PSpice Simulation:

b) Simulate the circuit with PSpice (bias point details only) and compare values of I_C , I_B , V_{CE} , and V_{BE} from PSpice simulations with your circuit analysis.



c) Rerun your PSpice simulations for temperatures of 0 and 60°C. Make a table of I_C , I_B , V_{CE} , and V_{BE} for the above temperatures and that of part b (which is for default temperature). Explain your observations. Compare your results with Experiment 1.

Lab Exercise:

- d) Set up the circuit and measure I_C , I_B , V_{CE} , and V_{BE} . Compare your measurements with your PSpice simulations. Explain why they may be different.
- e) Set the voltmeter to measure V_{CE} . Hold the transistor between two fingers without touching the rest of the circuit. Transistor will warm up slightly by your body temperature. What happens to V_{CE} as transistor warms up? Explain your observations.
- f) Compare your results from this experiment with those of Experiment 1.

Experiment 3: Current Mirror

Set up the circuit with the matched Si transistors of THAT 300 chip (Note Q1 and Q2 of the chip are matched. So are Q3 and Q4). Set $V_{CC} = 5\text{ V}$, $V_{EE} = -3\text{ V}$, and $R = 1\text{ k}\Omega$. The circuit is powered with two voltage sources. Common of power supply is the ground for this circuit.

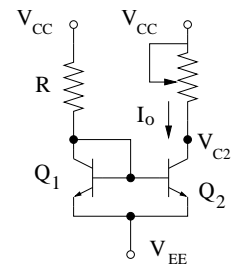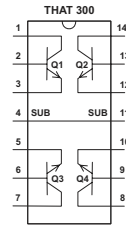*Circuit Analysis:*

- a) For what values of V_{C2} the circuit acts as a current mirror?
 b) Compute I_o for the case that the circuit is a current mirror.

Lab Exercise:

c) With the potentiometer set to a low value, measure current I_o and voltage V_{C2} . Increase the resistance of the potentiometer while monitoring I_o and V_{C2} . Record values of I_o and V_{C2} for $V_{C2} = 5, 4, 3, \dots\text{ V}$. Continue increasing the resistance of potentiometer until the circuit does not behave like a current mirror. Record the corresponding V_{C2} value and compare with part a. Tabulate the data and explain your observations.

Experiment 4: Biasing with a current mirror

We now use the current mirror of experiment 3 to bias a 2N3904 transistor (Q3) with $R_C = 500\ \Omega$.

Circuit Analysis:

- a) Compute I_C , I_B , V_{BE} , and V_{CE} of Q3 (see also part c)

Lab Exercise:

- b) Set up the circuit and measure I_C , V_{CE} , and V_{BE} of Q3. Compare your measurements with circuit analysis of part a.
- c) Remove R_C from the circuit and repeat part a and b.
- d) Summarize your observations of the three biasing schemes of this lab.

