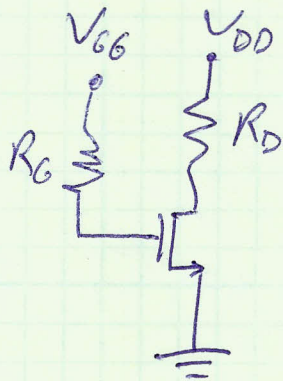


MOSFET fixed bias

- Similar to BJT fixed bias
- Not stable



- No current through R_G
- not necessary, but needed if coupling capacitors are used



$$V_{GS} = V_{GG}$$

$$I_D = \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_T)^2 = \frac{1}{2} k_n' \frac{W}{L} (V_{GG} - V_T)^2$$

$$DS-KVL: I_D R_D + V_{DS} = V_{DD}$$

$$\rightarrow V_{DS} = V_{DD} - \frac{1}{2} k_n' \frac{W}{L} R_D (V_{GG} - V_T)^2$$

- Subject to variations in k_n' and V_T which vary with temperature

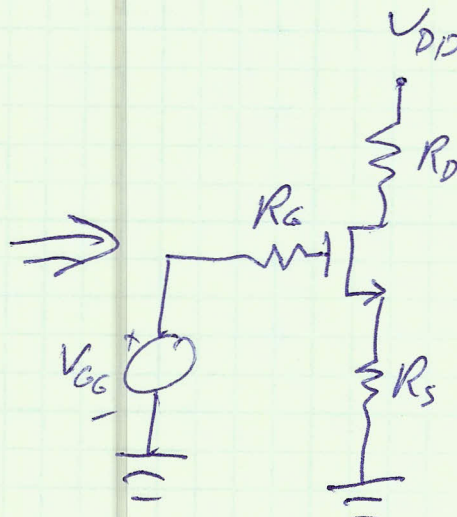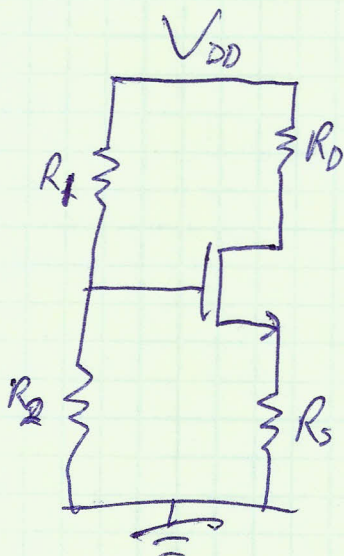MOSFET bias with source degeneration

Theremin
equivalent
 R_G, V_{GG}

$$V_{G6} = \frac{R_2}{R_1 + R_2} V_{DD}, \quad R_G = R_1 \parallel R_2$$

GS-KVL:

$$V_{G6} = V_{GS} + I_D R_S$$

$$I_D = \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_T)^2$$

} can solve for V_{GS} and I_D

DS-KVL:

$$V_{DD} = I_D R_D + V_{DS} + I_D R_S \quad \leftarrow \text{can solve for } V_{DS}$$

Negative feedback: $V_{GS} = V_{G6} - R_S I_D$

- increase in I_D causes decrease in V_{GS} which causes decrease in I_D .
- not constant because of quadratic relationship but variations are much smaller with feedback
- Don't need to worry about $R_B \ll (1+\beta)R_E$ as in BJT because $I_G = 0$, so R_1 and R_2 can be large (MΩ)

Self Bias - uses R_C as feedback resistor



note $V_{CE} = R_D I_D + V_{DE}$
 $= R_D I_D + V_{DD} > V_{DD}$

Transistor is always in active mode

$$V_{CC} = R_C I_C + R_B I_B + V_{BE}, \text{ and } I_i = I_C + I_B$$

$$= R_C (I_C + I_B) + R_B I_B + V_{BE}$$

$$= R_C I_C + (R_B + R_C) \frac{I_C}{\beta} + V_{BE}$$

$$I_C = \frac{V_{CC} - V_{BE}}{R_C + (R_B + R_C) \frac{1}{\beta}} \approx \frac{V_{CC} - V_{BE}}{R_C} \quad \text{if } R_B \ll (\beta - 1) R_C$$

$$\text{note } \frac{R_C + R_B}{\beta} \ll R_C \rightarrow R_C + R_B \ll \beta R_C \rightarrow R_B \ll R_C (\beta - 1)$$


Bias point is stable and independent of β

• Negative feedback illustrated here:

$$\text{BE-KVL: } I_B = \frac{V_{CC} - V_{BE} - I_C R_C}{R_B}$$

Increase in I_C will decrease I_B , which decreases I_C

MOSFET self bias

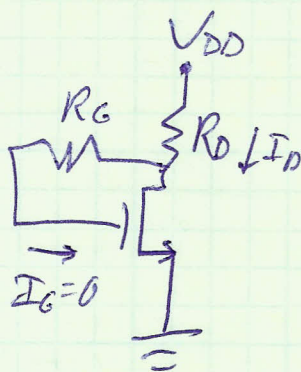

• Transistor always in Saturation $V_{DS} = V_{GS} > V_{GS} - V_T$

$$V_{DD} = I_D R_D + V_{GS}$$



$$I_D = \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_T)^2 \quad \left. \vphantom{I_D} \right\} \text{ can find } I_D \text{ and } V_{GS}$$

Note: R_D does not affect bias, but cannot be removed

- Removing R_D would mean direct connection from input to output of amp.

Fixed biasSummary of Bias Circuits

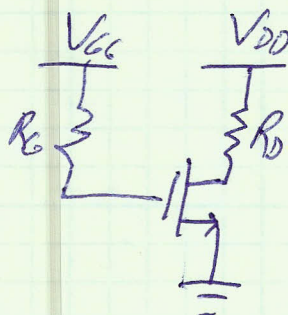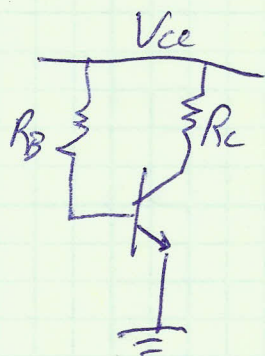
- Simple bias circuit, but not stable
- Q point can vary with β , V_T , and temperature



need 2 voltage sources for MOSFET

Emitter degeneration with voltage divider

- Q point is independent of β and V_{be} variations
thus independent of temperature and device variations

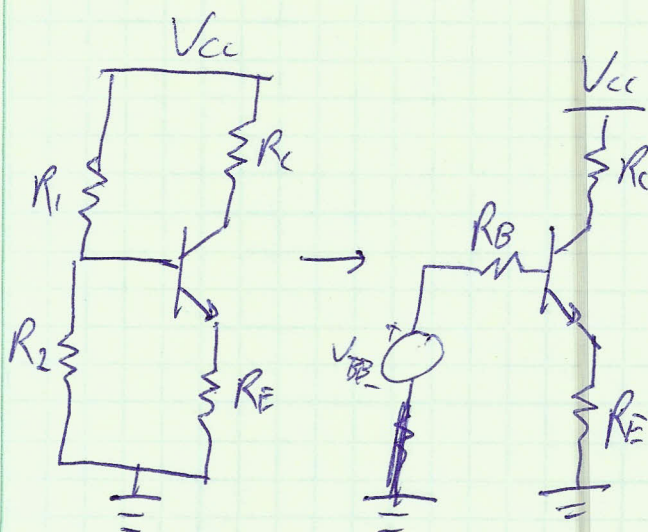Conditions for stability


$$R_B \ll (1 + \beta) R_E$$

$$V_E > 1V$$

$\gg$ means $\sim 10\times$

Self bias

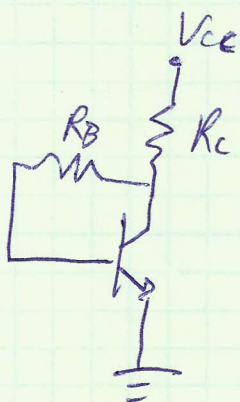- Stable bias circuit, independent of β and V_{be}
- Uses R_c as feedback resistor




Stability condition

$$R_B \ll (\beta - 1) R_c$$


MOSFET bias circuits

Source degeneration:

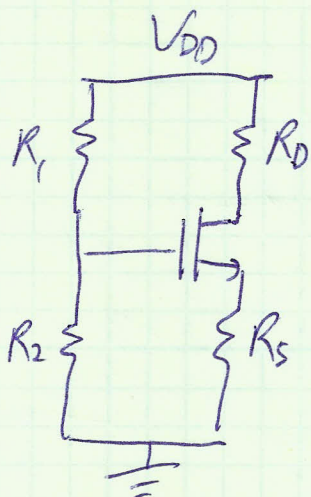

R_1, R_2 can
be large
(M Ω)

Self bias:

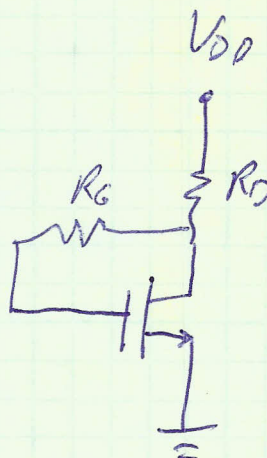

R_G only needed
for amplifier use,
otherwise input
connected to output

These are not as stable as BJT bias circuits because of quadratic I_D - V_{gs} relationship, but relatively stable