


Bias analysis $\rightarrow$ set signal to zero

$$R = 750 \Omega, \quad v_i = 5 + 0.05 \cos \omega t \rightarrow v_i = 5$$

$$v_i = i_D R + V_D$$

$$5 = 750 I_D + 0.7$$

$$I_D = 5.73 \text{ mA}$$

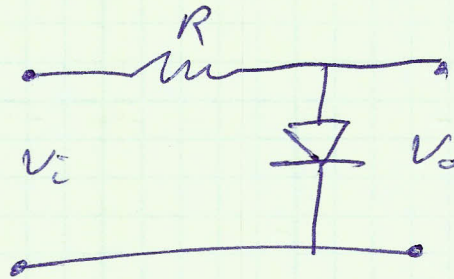

Small signal analysis

$$r_d = \frac{n V_T}{I_D}$$


$n = 2$ for discrete Si diodes
 $V_T = 25 \text{ mV}$ at 300 K

$$r_d = \frac{2 \times 25 \times 10^{-3}}{5.73 \times 10^{-3}} = 8.73 \Omega$$

$$v_i = \frac{r_d}{r_d + R} \times 0.05 \cos \omega t = 0.00058 \cos \omega t$$

$$v_o = 700 + 0.58 \cos \omega t \quad (\text{mV})$$

Voltage-controlled attenuator

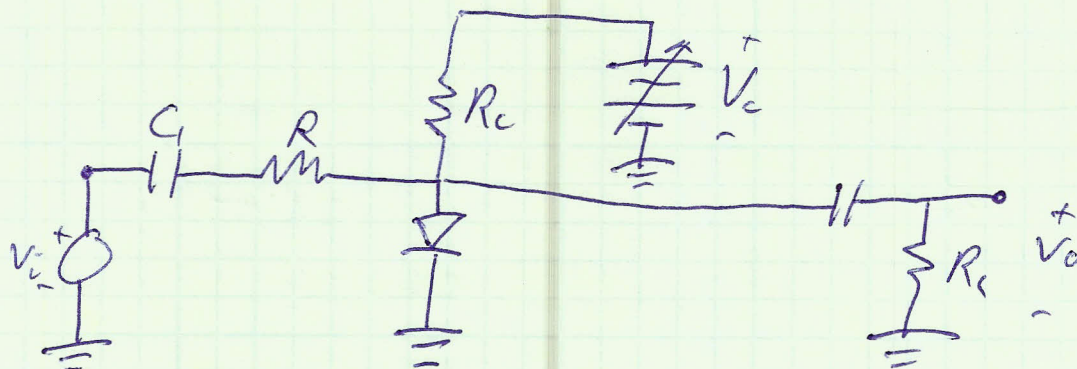

Bias: $I_D = \frac{V_c - V_{D0}}{R_c}$

(note: capacitors are open circuits at DC)

Small signal: define $R_p \equiv R_c \parallel r_d \parallel R_L$

these all appear in parallel when $V_c = 0$

(note: capacitors are short circuits for the signal)

$$\frac{v_o}{v_i} = \frac{R_p}{R_p + R}$$

for $r_d \ll R_c$ and $r_d \ll R_L$, $R_p \approx r_d$

$$\boxed{\begin{aligned} \frac{v_o}{v_i} &= \frac{r_d}{r_d + R} \\ r_d &= \frac{n k T}{I_D} = \frac{n k T R_c}{V_c - V_{D0}} \end{aligned}}$$

$$V_c \uparrow \dots \frac{v_o}{v_i} \downarrow$$

MOSFET small signal model

- assume always in saturation
- 4 independent parameters I_G, I_D, V_{GS}, V_{DS} (NMOS)

$$I_G(V_{GS}, V_{DS}) = 0$$

$$I_D(V_{GS}, V_{DS}) = \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

Bias point parameters are I_D, V_{GS}, V_{DS} ($I_G = 0$)

$$i_D = I_D + \tilde{i}_D, \quad V_{GS} = V_{GS} + v_{gs}, \quad V_{DS} = V_{DS} + v_{ds}$$

Use Taylor series expansion in terms of 2 variables

$$f(x_0 + \Delta x, y_0 + \Delta y) \approx f(x_0, y_0) + \Delta x \left. \frac{df}{dx} \right|_{x_0, y_0} + \Delta y \left. \frac{df}{dy} \right|_{x_0, y_0}$$

$$\tilde{i}_D(V_{GS} + v_{gs}, V_{DS} + v_{ds}) = \tilde{i}_D(V_{GS}, V_{DS}) + \underbrace{v_{gs} \left. \frac{d\tilde{i}_D}{dV_{GS}} \right|_Q + v_{ds} \left. \frac{d\tilde{i}_D}{dV_{DS}} \right|_Q}_{\text{Signal component}}$$

$$\text{Define } g_m \equiv \left. \frac{d\tilde{i}_D}{dV_{GS}} \right|_Q = 2 \times \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_T) (1 + \lambda V_{DS}) \big|_Q$$

$$g_m = \frac{2I_D}{V_{GS} - V_T}$$

$$\text{Define } \frac{1}{r_o} \equiv \left. \frac{d\tilde{i}_D}{dV_{DS}} \right|_Q = \lambda \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_T)^2 \big|_Q$$

$$\frac{1}{r_o} = \frac{\lambda I_D}{1 + \lambda V_{DS}} \longrightarrow r_o = \frac{V_A + V_{DS}}{I_D} \approx \frac{V_A}{I_D} \quad \text{where } V_A = \frac{1}{\lambda}$$

MOSFET small signal equations


$$i_g = 0$$

$$i_d = g_m v_{gs} + \frac{v_{ds}}{r_o}$$

small signal circuit

$$g_m = \frac{2I_D}{V_{GS} - V_T}$$

$$r_o = \frac{V_A + V_{DS}}{I_D} \approx \frac{V_A}{I_D}$$

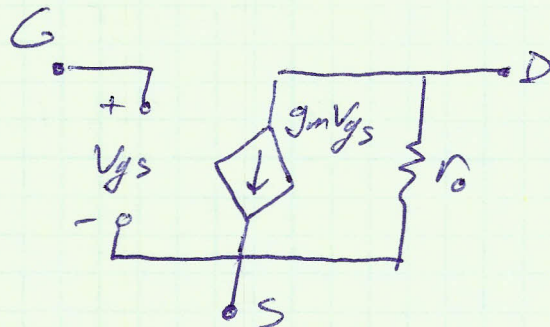for PMOS

$$g_m = \frac{2I_D}{V_{SG} - |V_T|}$$

$$r_o = \frac{V_A + V_{SD}}{I_D} \approx \frac{V_A}{I_D}$$

the circuit looks the same
we do not need to replace v_{gs} with v_{sg}

BJT small signal model

$$I_B = \frac{I_S}{\beta} e^{V_{BE}/nV_T}$$

$$I_C = I_S e^{V_{BE}/nV_T} \left(1 + \frac{V_{CE}}{V_A}\right)$$

- assume active state, bias point parameters I_B, I_C, V_{CE}, V_{BE}

$$I_B = I_B + i_b \quad I_C = I_C + i_c, \quad V_{BE} = V_{BE} + v_{be}, \quad V_{CE} = V_{CE} + v_{ce}$$

Use Taylor series expansion

$$I_B(V_{BE} + v_{be}) = I_B(V_{BE}) + v_{be} \frac{\partial I_B}{\partial V_{BE}} \bigg|_Q$$

$$i_b = \frac{\partial I_B}{\partial V_{BE}} \bigg|_Q v_{be} \equiv \frac{v_{be}}{r_\pi}$$

$$\frac{1}{r_\pi} \equiv \frac{\partial I_B}{\partial V_{BE}} \bigg|_Q = \frac{1}{nV_T} \cdot \frac{I_S}{\beta} e^{V_{BE}/nV_T} = \frac{I_B}{nV_T}$$

$$\rightarrow r_\pi = \frac{nV_T}{I_B}$$

$$I_C(V_{BE} + v_{be}, V_{CE} + v_{ce}) = I_C(V_{BE}, V_{CE}) + v_{be} \frac{\partial I_C}{\partial V_{BE}} \bigg|_Q + v_{ce} \frac{\partial I_C}{\partial V_{CE}} \bigg|_Q$$

$$i_c = v_{be} \frac{\partial I_C}{\partial V_{BE}} \bigg|_Q + v_{ce} \frac{\partial I_C}{\partial V_{CE}} \bigg|_Q \equiv g_m v_{be} + \frac{v_{ce}}{r_o}$$

$$g_m \equiv \frac{\partial I_C}{\partial v_{be}} \bigg|_Q = \frac{1}{nV_T} I_S e^{V_{BE}/nV_T} \left(1 + \frac{V_{CE}}{V_A}\right) = \frac{I_C}{nV_T}$$

$$\frac{1}{r_o} \equiv \frac{\partial I_C}{\partial V_{CE}} \bigg|_Q = \frac{1}{V_A} I_S e^{V_{BE}/nV_T} = \frac{I_C}{V_A(1 + V_{CE}/V_A)} = \frac{I_C}{V_A + V_{CE}}$$

BJT small signal equations

$$i_b = \frac{v_{be}}{r_{\pi}}$$

$$i_c = g_m v_{be} + v_{ce}/r_o$$

small signal circuit

$$r_{\pi} = \frac{n V_T}{I_B}$$

$$g_m = \frac{I_c}{n V_T} = \frac{I_c}{I_B} \cdot \frac{I_B}{n V_T} = \frac{\beta}{r_{\pi}}$$

$$r_o = \frac{V_A + V_{CE}}{I_c} \approx \frac{V_A}{I_c}$$

PNP is the same, but with V_{EC} instead of V_{CE}

