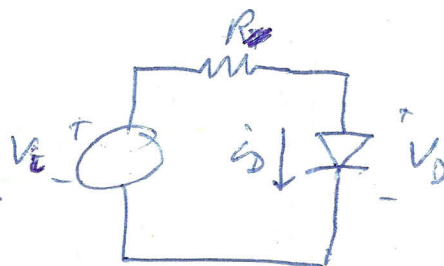


Solving Diode Circuits

$$① \quad V_i = i_D R + V_D \quad \rightarrow \quad V_T = \frac{kT}{q} = 26 \text{ mV}$$


$$② \quad i_D = I_S (e^{V_D/V_T} - 1)$$



2 equations and 2 unknowns, but difficult to solve because nonlinear

Load Line $\rightarrow V_i = i_D R + V_D$

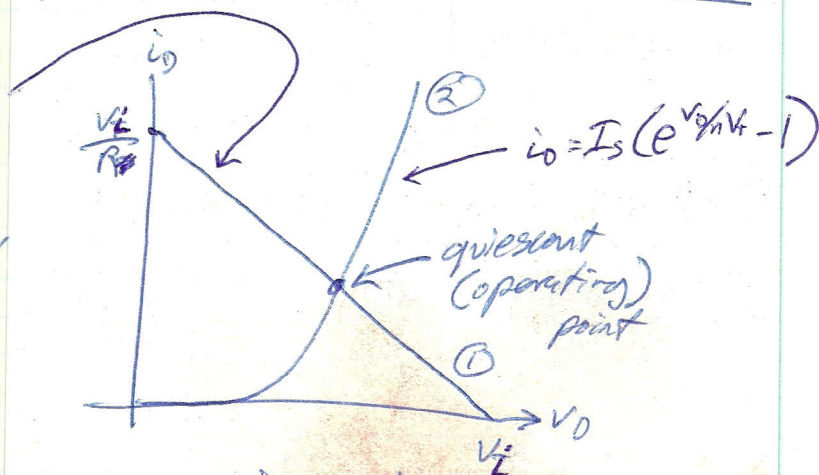
• Useful graphical solution,
but does not easily give
numerical result



Piecewise Linear Model

Diode ON: $V_D = V_{D0}$, $i_D \geq 0$


Diode OFF: $i_D = 0$, $V_D < V_{D0}$

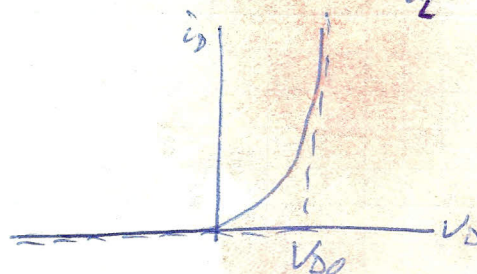

V_{D0} is "cut-in" voltage, for Si $V_{D0} \approx 0.6 - 0.7 \text{ V}$
for Ge, $V_{D0} \approx 1.7 - 1.9 \text{ V}$

Recipe for solving:

- ① Write down circuit equations, with i_D , V_D as parameters
- ② assume either ON or OFF and solve circuit
- ③ check for self-consistency with values of i_D , V_D that you found

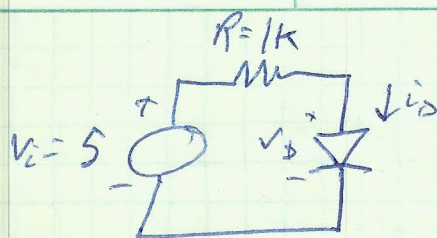Example

$$V_i = i_D R + V_D$$

$$5 = 10^3 i_D + V_D$$

assume diode is OFF $\rightarrow i_D = 0$

$$5 = 10^3 \times 0 + V_D \rightarrow V_D = 5V$$

is $V_D < V_{D0}$ ($V_{D0} = 0.7V$)? NO.

assume diode is ON


$$5 = 10^3 i_D + 0.7 \rightarrow i_D = 4.3mA$$

is $i_D \geq 0$? Yes

Diode Circuit Model

Diode ON $i_D \geq 0$

Diode OFF $V_D < V_{D0}$

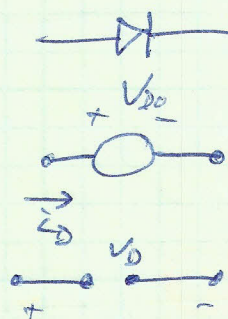

- Can use the same procedure, but check for self-consistency


Recipe for solving with diode circuit model

- Draw circuit for each state of the diode (or all diode combinations)
- solve each circuit, find $i_D + V_D$
- check for self consistency. If not, go on to the next circuit

Diode Logic Gates

- Since diodes are nonlinear devices, they can be used to build simple logic circuits
- Assume a supply of 5V
- Define any voltage $< 1V$ as "0" and $> 1V$ as "1"

Diode AND gate:

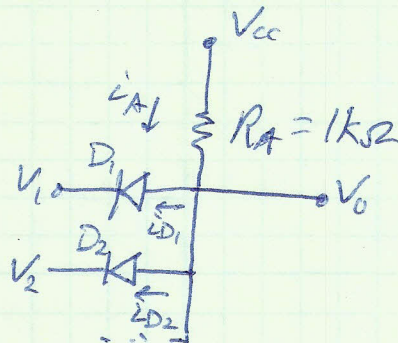

Case 1: $V_1 = V_2 = 0V$

$$V_0 = V_1 + V_{D0} = V_2 + V_{D0} = 0.7V \quad (\text{assume both are ON})$$

$$I_A = \frac{V_{CC} - V_0}{R_A} = \frac{5 - 0.7}{1000} = 4.3mA$$

$$I_{D1} = I_{D2} = \frac{I_A}{2} = 2.1mA \quad (\text{by symmetry})$$

assumption that diodes are ON is correct

$V_0 = 0.7V$, or logical "0"

Case 2: $V_1 = 0, V_2 = 5V$

Assume D_1 is ON

$$I_A = \frac{V_{CC} - V_0}{R_A} = \frac{5 - 0.7}{1000} = 4.3mA$$

$$I_{D1} = 4.3mA \rightarrow \text{yes, } D_1 \text{ is ON}$$

$V_0 = 0.7V$, or logical "0"

note: D_2 must be OFF because it doesn't matter what the current through R_A is, V_0 will always be less than or equal to 5V

Case 3: $V_1 = 5V$, $V_2 = 0V$

Because of symmetry, this is the same as case 2 but with D_1 and D_2 switched

Case 4: $V_1 = V_2 = 5V$

Assume both diodes are off

$$I_A = I_{D1} + I_{D2} = 0$$


$$V_O = V_{CC} - I_A R_A = 5 - 0 = 5V \quad \text{or logical "1"}$$

$$V_{D1} = V_{D2} = 5 - 5 = 0 \rightarrow \text{both are OFF}$$

• Why are simple diode logic gates not used?

- Diodes do not have gain
- signal degrades by 0.7V with each gate.
- only a few gates could be used before signal would fall in "undefined" range

Diode OR Gate

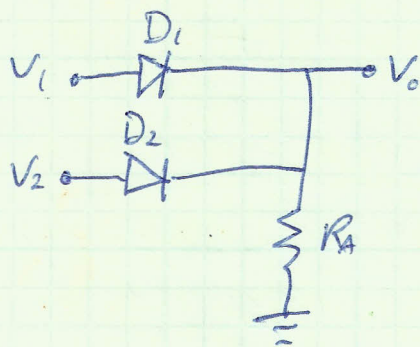


Parametric Solution of Diode Circuits

- Instead of solving for specific values of sources and elements, solve for general transfer function, then apply desired values
- Necessary for dynamic circuits, where values are changing

Recipe:

- 1) Draw all possible circuits for various diode states (2^N , $N = \text{# diodes}$)
- 2) Solve each circuit to find voltages and currents
- 3) Use range of validity of diode states to find range of circuit parameters that lead to that state

Example:

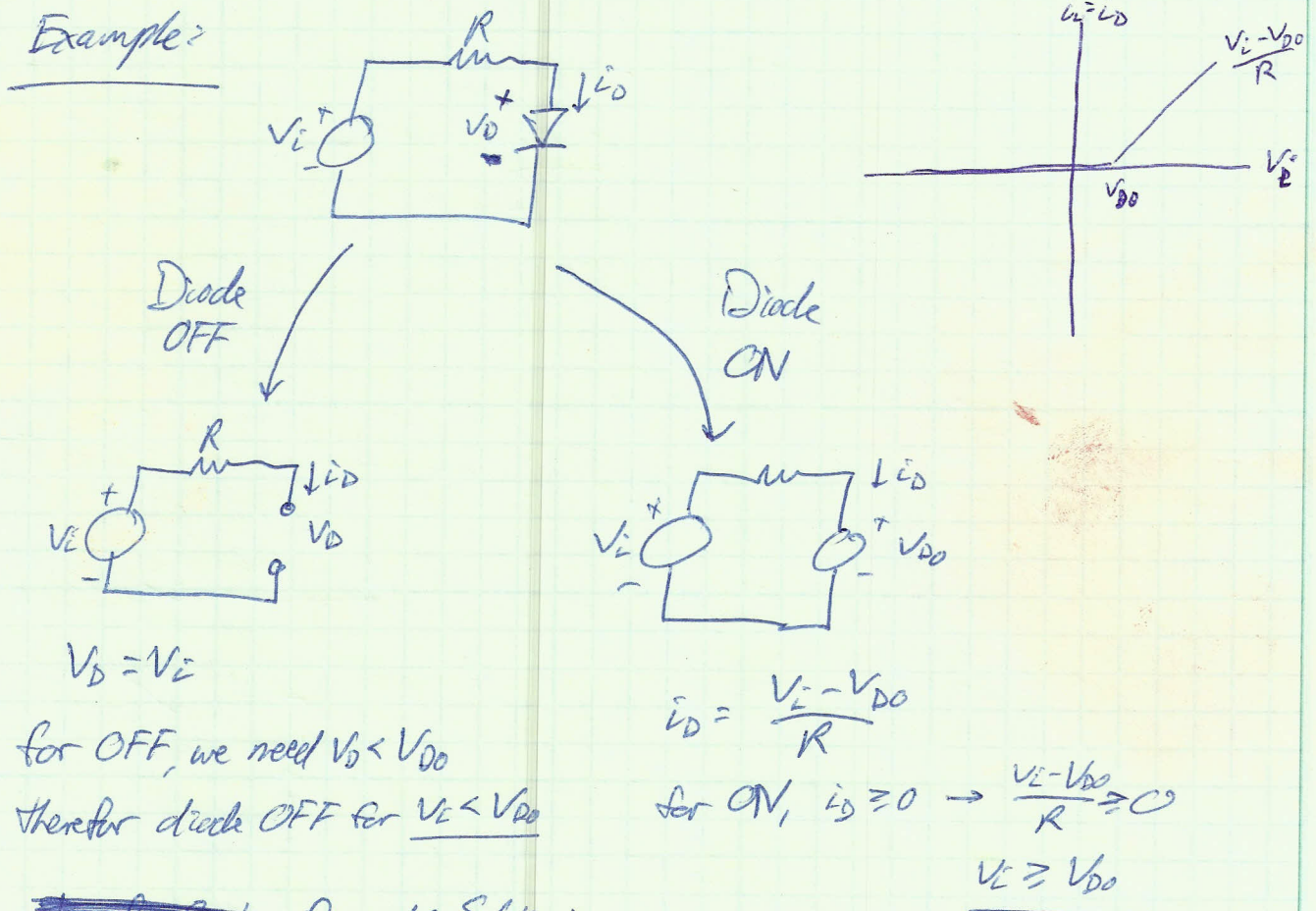

~~Transfer Function~~ Parametric Solution:


$$V_i \geq V_{D0} \rightarrow \text{ON} \rightarrow V_D = V_{D0}, i_D = \frac{V_i - V_{D0}}{R}$$

$$V_i < V_{D0} \rightarrow \text{OFF} \quad V_D = V_i, i_D = 0$$

Other types of Diodes


• Schottky barrier diode

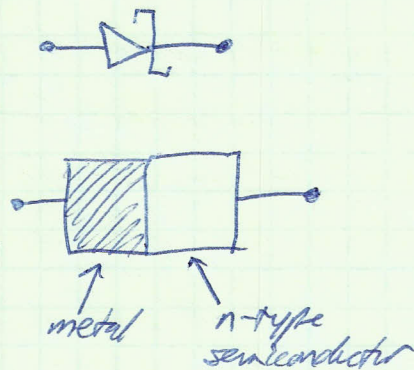- has larger I_s
- $V_{bo} \approx 0.3V$
- faster switching speed
- examples with near-zero turn-on voltage can be made
- early "cat's whisker" detectors are first semiconductor device




• Light-emitting diode (LED)

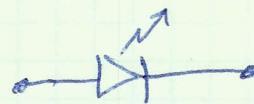- Emits light upon forward biased
- photon energy (frequency) is related to band gap
- IR, Red, Orange, Yellow: usually combination of In, Ga, Al, As, P
- Blue, Violet, UV: usually combination of In, Ga, N
- Green can be various combinations
- However, Green laser pointers are still made by frequency doubling an IR diode
- Must have a direct bandgap to emit light




• Zener diodes

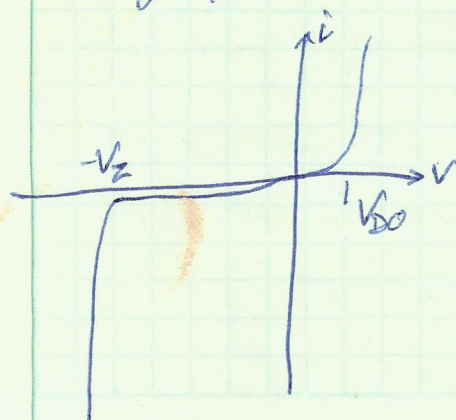- designed to work in the breakdown region




without being destroyed!

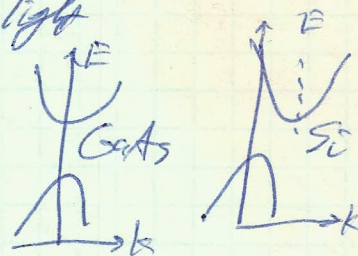


Model for Zener Diodes


$$\text{ON} : V_D = V_{D0}, i_D \geq 0$$

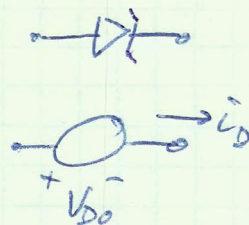


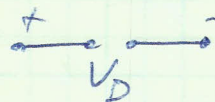
$$\text{OFF} : -V_Z < V_D < V_{D0}, i_D = 0$$



$$\text{Zener Region} : V_D = -V_Z, i_D \leq 0$$

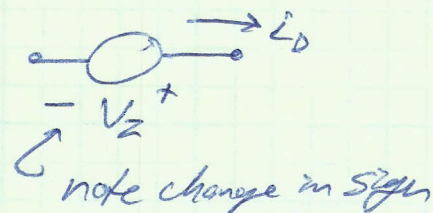A Simple Power Supply

- Assume that a power supply has some variation or ripple
- Zener diodes can be used to take out the ripple

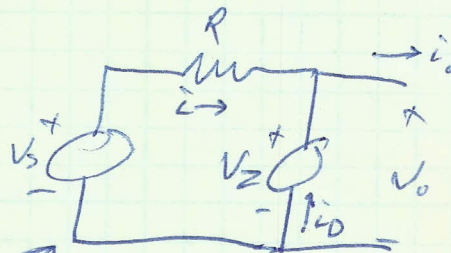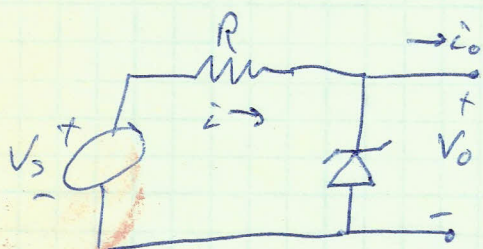

Case 1: Zener region

$$V_D = V_Z = \text{constant}$$

output voltage is independent of i_O - ideal voltage source

$$\text{KCL} : i_D = i - i_O$$

$$\text{KVL} : V_S = Ri + V_Z \rightarrow i_D = i_O - \frac{V_S - V_Z}{R} \leq 0$$

- As long as this condition is satisfied, diode will be in Zener region


$$\rightarrow i_O \leq \frac{V_S - V_Z}{R}$$

Case 2: Reverse bias region

$$\dot{I}_D = 0$$

$$\dot{I} = \dot{I}_0$$


$$V_S - R\dot{I}_0 = V_0$$

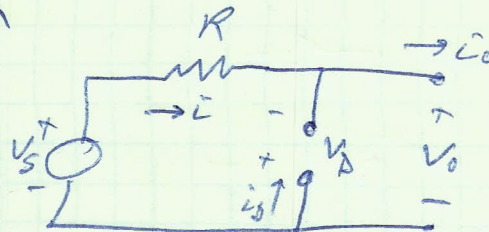

- Output voltage drops as more current is drawn from circuit

Case 3: Forward bias region

not possible - V_S is positive.

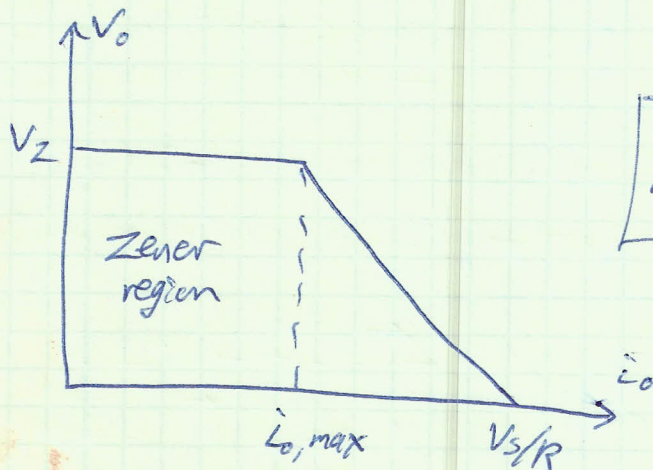

$$\dot{I}_{0,\max} = \frac{V_S - V_Z}{R}$$

- In reality, there is a slight slope to the Zener region of the curve
- real voltage sources are made with transistors and opamps, etc.

Other Diode Models