 


Bipolar Junction Transistors (BJTs)



Six parameters: $i_b, i_e, i_c, V_{be}, V_{ce}, V_{cb}$

using KVL, KCL: $i_e = i_c + i_b$, $V_{cb} = V_{be} - V_{ce}$

only four independent parameters: i_b, i_c, V_{be}, V_{ce}


→ these specify IV characteristics of transistor

Principle of operation:

- In active mode: emitter-base junction is forward-biased
collector-base junction is reverse-biased
- Level of doping in emitter is much higher than in the base
→ electron current is much greater than hole current into emitter
- Bias conditions set up a concentration gradient across base
→ very high near emitter, very low near collector
→ causes diffusion current across base
→ electrons that reach collector are swept over to collector contact

- Emitter current is primarily electrons, and a small hole current into base
- Base current is small hole current and small electron recombination current
- Collector current is most of the electrons from the emitter

 Typical design: Base is thin, and lightly doped
Emitter is heavily doped



- Note that current flows across base-collector junction even though it is reverse-biased. It is caused by concentration gradient in base, set up by base-emitter junction
- Number of holes going into emitter (proportional to I_B) is a constant fraction of number of electrons going into base (proportional to I_C)
This ratio depends on doping and design

$$\frac{I_C}{I_B} = \beta \quad \text{— defined as common emitter current gain}$$

typical value is ~ 200

(about 200 electrons travel for each hole)

Mode	E-B Junction	C-B Junction
cutoff	reverse	reverse
active	forward	reverse
saturation	forward	forward

Cutoff mode

B-E junction reverse biased, $i_B = 0 \rightarrow i_C = 0$



active mode

most of the current flows to the collector

$$i_C = I_S (e^{V_{BE}/V_T} - 1) \approx I_S e^{V_{BE}/V_T}$$

$$i_B \equiv \frac{I_S}{\beta} (e^{V_{BE}/V_T} - 1) \approx \frac{I_S}{\beta} e^{V_{BE}/V_T}$$

model for cutoff and active circuits:

 
 
saturation mode

when $V_{CE} \approx V_{DO}$, B-C junction becomes forward biased

extra holes injected into base from collector recombine with electrons
 $\rightarrow$ reduce collector current

$$i_C/i_B < \beta$$

 
 
"soft saturation" may be considered as around $V_{CE} = 0.4V$ ($V_{BE} = 0.3V$)
 as transistor behaves similarly to active mode, i_C/i_B not yet reduced significantly
 $\rightarrow$ slightly forward biased, but not yet to turn-on



- The slope of the i_C curves in the active region is due to the dependence of the depletion region width on V_{ce}
- Wider depletion region $\rightarrow$ narrower effective base width
- V_A known as "Early voltage"
 - typically 50-100 V

$$i_C = I_S e^{V_{BE}/nV_T} \left(1 + \frac{V_{CE}}{V_A} \right)$$

$$i_B = \frac{I_S}{\beta} e^{V_{BE}/nV_T} \quad \text{note } i_B \text{ equation doesn't change}$$

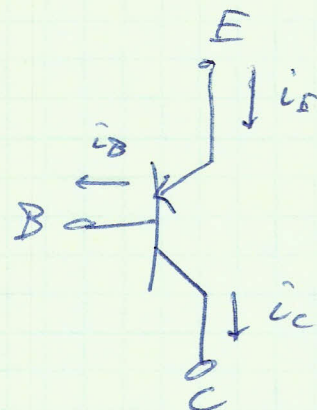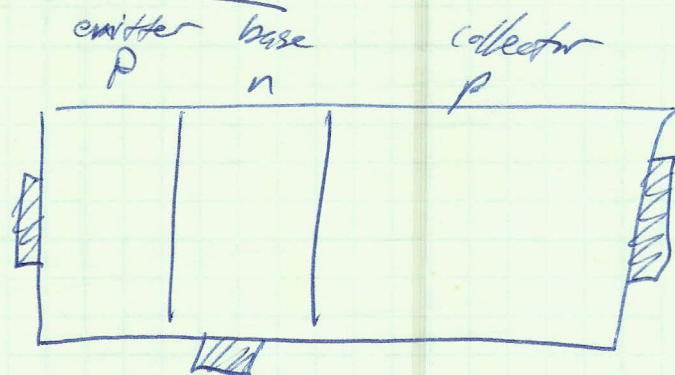PNP transistor

- holes move slower than electrons (lower mobility)
so pnp transistors are typically slower
- usually used in pairs with npn transistors

Summary

cutoff: $i_B = 0, i_C = 0$

active: $i_B = \frac{I_S}{\beta} e^{V_{BE}/V_T}, i_C = I_S e^{V_{BE}/V_T} \left(1 + \frac{V_{CE}}{V_A}\right)$

saturation: $i_B = \frac{I_S}{\beta} e^{V_{BE}/V_T}, i_C < \beta i_B, V_{CE} = 0.1 - 0.3V$

- known as "large signal model"
- low frequency model - does not include capacitance

Piecewise Linear, Large Signal model for BJTCut-off

$$i_B = 0, V_{BE} < V_{D0}$$

$$i_C = i_E = 0$$

for PNP transistors

$$V_{BE} \rightarrow V_{EB}$$

$$V_{CE} \rightarrow V_{EC}$$

Active

$$V_{BE} = V_{D0}, i_B \geq 0$$

$$i_C = \beta i_B, V_{CE} > V_{D0}$$

can ignore Early effect (5% error)

if necessary to include it, use $i_C = \beta i_B (1 + \frac{V_{CE}}{V_A})$ for soft saturation, ($V_{CE} \geq 0.4V$) $i_C \approx \beta i_B$ we can use $V_{CE} \geq 0.4V$ instead of $V_{CE} \geq V_{D0}$

However - difficult to design in this region


- we will still use $V_{CE} \geq V_{D0}$ in this course

Model for saturation mode is complicated - we will use piecewise linear

Saturation mode ($0.1 \leq V_{CE} \leq 0.3V$)

$$V_{BE} = V_{D0}, i_B > 0$$

$$V_{CE} \approx \underline{V_{sat}}, i_C \leq \beta i_B$$

 use 0.2V for V_{sat} 

piecewise linear model



real i-v characteristic

How to solve BJT circuits

Just like diode - assume a state, then check assumptions

- Write KVL for BE terminals
- Write KVL for CE terminals
- assume cut-off (simplest)
 - set $i_B = 0$
 - calculate V_{BE} from BE-KVL
 - * - if $V_{BE} < V_{D0}$, BJT is in cut-off
 - set $i_C = i_E = 0$
 - calculate V_{CE} from CE-KVL $\rightarrow$ you are done
 - * - if $V_{BE} > V_{D0}$, BJT is not in cut-off
- assume linear mode
 - set $i_E \approx i_C = \beta i_B$
 - calculate V_{CE} from CE-KVL
 - * - if $V_{CE} > V_{D0}$, BJT is in active mode $\rightarrow$ you are done
 - * - if $V_{CE} < V_{D0}$, BJT is not in active mode - it is in saturation
 - set $V_{CE} = V_{sat}$
 - calculate i_C from CE-KVL
 - check that $i_C < \beta i_B$

For PNP transistors, substitute V_{BE} with V_{EB}
 V_{CE} with V_{EC}

Note that V_{BC} not used

In active mode $i_E = i_C + i_B = (\beta + 1)i_B$ and $i_E = \frac{\beta + 1}{\beta} i_C$

since $\beta \gg 1$, use $i_E \approx i_C$ for simplicity

Even in saturation mode, $i_C \gg i_B$, $i_E \approx i_C$