 


Question #1:


For the circuit shown, the Zener diode has $V_Z = 5\text{ V}$. All others are standard silicon diodes

- Write the transfer function, V_o for all V_i .
- Plot the transfer function
- For an input sine wave with 10 V amplitude, sketch the output signal.


Question #2:

For the circuit shown, assume $V_{Tp} = -1\text{ V}$ and $\mu_p C_{ox}(W/L) = 1\text{ mA/V}^2$ for the FET, and $\beta = 100$ for the BJT. Neglect the Early effect and the channel length modulation effect.

- Identify the state of the FET
- Find the value of the drain current I_D
- Identify the state of the BJT
- Find the value of the collector current I_C

  Question #3:


Assume you have an NPN BJT with $\beta = 100$, and a voltage source of 20 V. Design a bias circuit to provide $V_{CE} = 10\text{ V}$, and $I_C = 2\text{ mA}$. The bias circuit should be stable with respect to variations in β ranging from 50 to 200, and variations in V_{BE} of 0.1 V. Provide values for all resistors shown.



 Question #4:

For the circuit shown, assume that $\beta=100$, and $V_A=100$ V. Assume ideality factor $n=1$.


- Determine g_m , r_{π} , and r_o for each transistor.
- Draw the small-signal equivalent circuit.
- Determine the Thevenin resistance at the node shown.



 Question #5:

For the amplifier shown,

- Draw the small signal equivalent circuit.
- Find an expression for R_o in terms of the small signal parameters.
- Find an expression for the open loop gain A_{V0} in terms of the small signal parameters.



Question #6:

For the amplifier shown, assume $\beta=100$ and $V_A=100$ V. Assume ideality factor $n=1$.

- Calculate A_{V0} , R_i , and R_o .
- Calculate the low-frequency cut-off.

