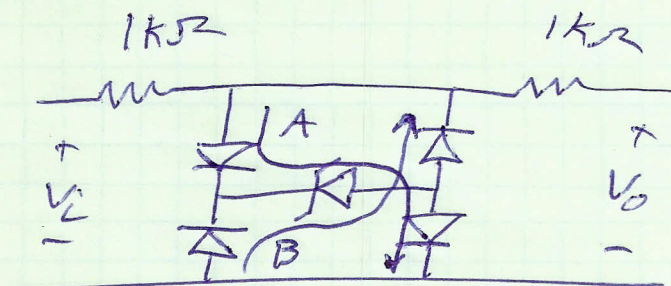


Question 1

Current can flow in either direction (path A or B above)
 With a voltage drop across the diodes of $2V_{D0} + V_Z$


$$2V_{D0} + V_Z = 2(0.7) + 5 = 6.4\text{V}$$

a) For $V_i < -6.4\text{V}$, $V_o = -6.4\text{V}$


For $-6.4\text{V} < V_i < 6.4\text{V}$, $V_o = V_i$

For $V_i > 6.4\text{V}$, $V_o = 6.4\text{V}$

b)

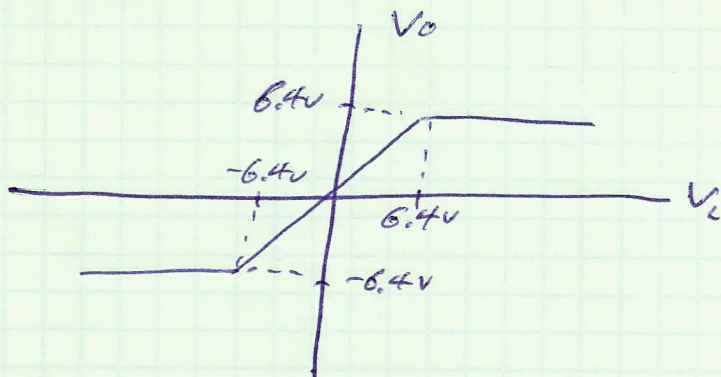

c)

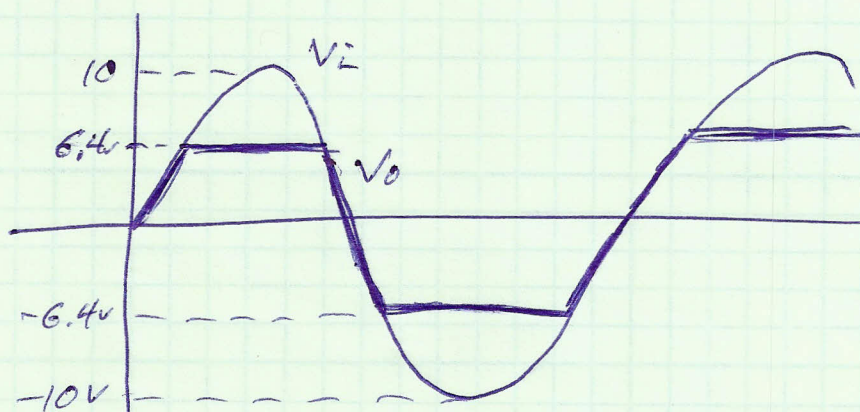

Question 2

$$V_{sg} = 2.5V$$

assume FET is ~~in~~ saturation mode

$$I_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{sg} - |V_{t1}|)^2$$

$$I_D = \frac{1}{2} \cdot 1 (2.5 - 1)^2 = 1.1mA$$

$$V_{SD} = 5 - 1.1 \times 10 = -6V$$

FET is not in saturation mode, assume triode mode

$$I_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} [2(V_{sg} - |V_{t1}|)V_{SD} - V_{SD}^2]$$

$$I_D = \frac{5V - V_{SD}}{10k\Omega}$$

$$5 - V_{SD} = 10 \cdot \frac{1}{2} \cdot 1 [2(1.5)V_{SD} - V_{SD}^2]$$

$$5 - V_{SD} = 15V_{SD} - 5V_{SD}^2$$

$$5V_{SD}^2 - 16V_{SD} + 5 = 0 \rightarrow V_{SD} = \frac{16 \pm \sqrt{16^2 - 4 \cdot 5 \cdot 5}}{10} = 2.8V \text{ or } 0.35V$$


Only 0.35V is consistent with triode mode

a) FET is in triode mode

$$b) I_D = \frac{5 - V_{SD}}{10k} = 0.46mA$$

c) BJT is in cut-off mode because $V_{EB} < V_{D0}$

$$d) I_c = 0$$

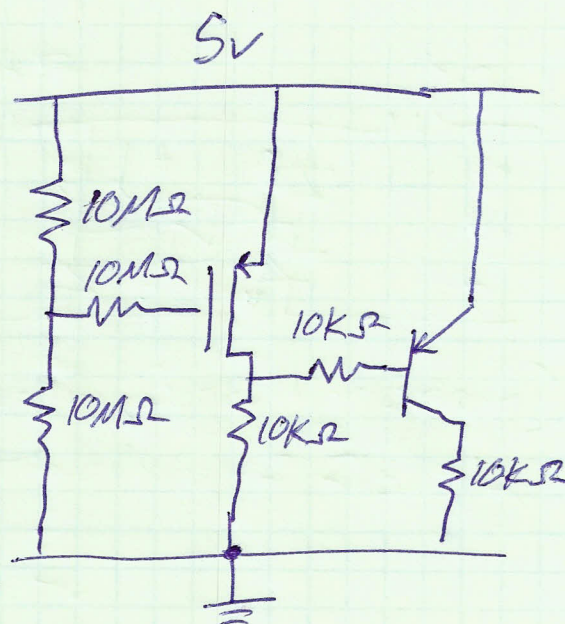

Question 3

$$\text{Set } I_E R_E = 1 \text{ V} \gg 0.1 \text{ V}$$

$$\underline{R_E = 500 \Omega}$$

$$V_{BB} = 20 \frac{R_2}{R_1 + R_2}, \quad R_B = \frac{R_1 R_2}{R_1 + R_2}$$

$$V_{BB} - I_B R_B - 0.7 = V_E = 1 \text{ V}$$

$$\text{choose } R_B \ll (\beta_{\min} + 1) R_E = 51 \times 500$$

$$R_B = 2.5 \text{ k}\Omega$$

$$V_{BB} - 2.5 \text{ k}\Omega \cdot 20 \mu\text{A} - 0.7 = 1$$

$$V_{BB} = 1.75 \text{ V}$$

$$20 \frac{R_2}{R_1 + R_2} = 1.75 \text{ V}$$

$$\frac{R_1 R_2}{R_1 + R_2} = 2.5$$

$$\frac{20}{R_1} = \frac{1.75}{2.5}$$



$$\underline{R_1 = 29 \text{ k}\Omega}$$

$$R_1 R_2 = 2.5 (R_1 + R_2)$$

$$29 R_2 = 72.5 + 2.5 R_2$$

$$26.5 R_2 = 72.5$$
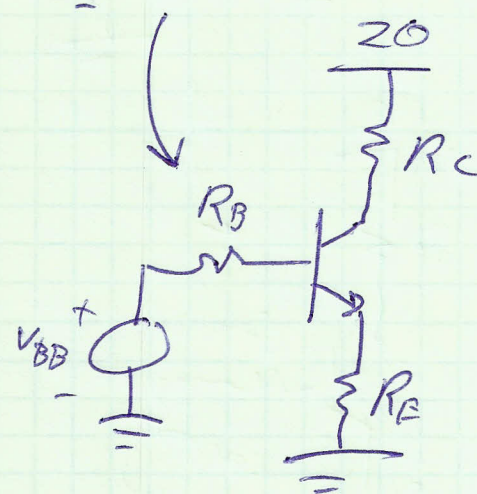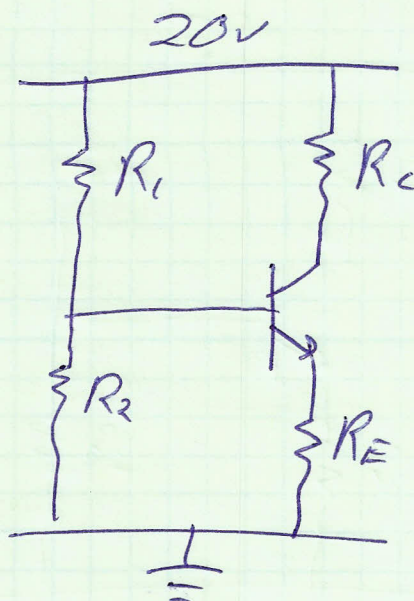
$$\underline{R_2 = 2.7 \text{ k}\Omega}$$



$$20 - I_E R_C - 10 = 1 \text{ V}$$


$$R_C = \frac{9 \text{ V}}{2 \text{ mA}} = 4.5$$

$$\underline{R_C = 4.5 \text{ k}\Omega}$$

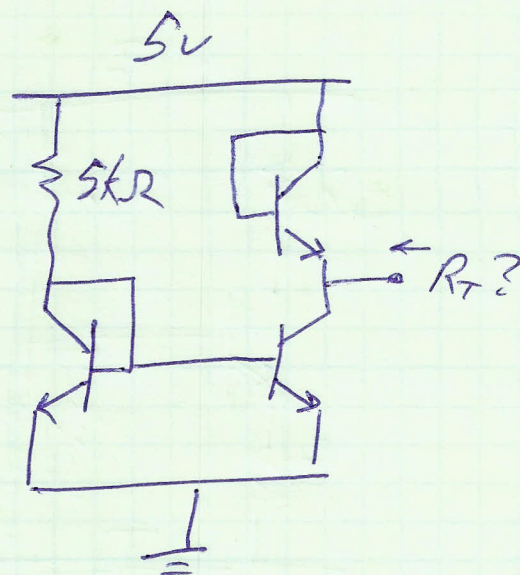Question 4

$$I_{ref} = \frac{5 - 0.7}{5} = 0.86 \text{ mA}$$

All transistors have $I_C = 0.86 \text{ mA}$
and $I_B = 8.6 \mu\text{A}$





a) $r_{\pi} = \frac{V_T}{I_B} = 3 \text{ k}\Omega$

$$r_o = \frac{V_A}{I_C} = 120 \text{ k}\Omega$$

$$g_m = \frac{I_C}{V_T} = 0.033 \text{ A/V}$$

b)

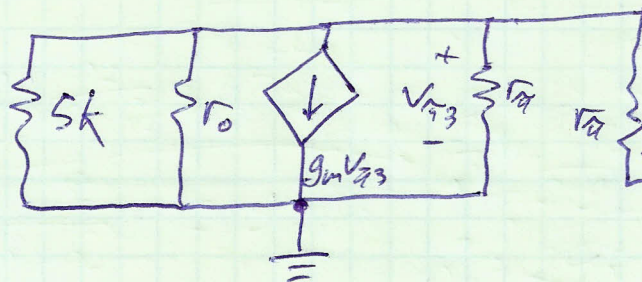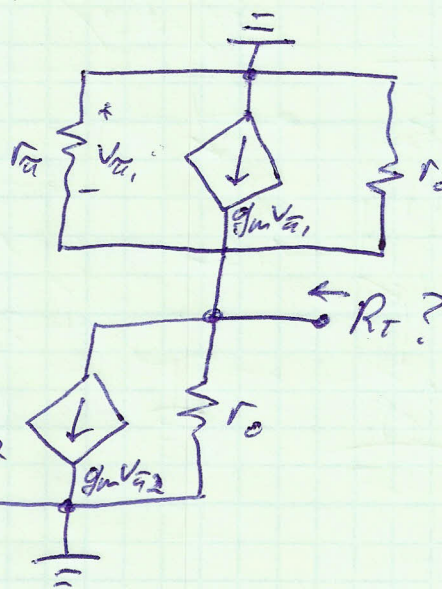


c) $V_{\pi 2} = V_{\pi 3} = 0$ Apply test source V_x , determine I_x
 $V_{\pi 1} = -V_x$


$$I_x = \frac{V_x}{r_{\pi}} + g_m V_x + \frac{V_x}{r_o} + \frac{V_x}{r_o}$$

$$\frac{V_x}{I_x} = r_{\pi} \parallel \frac{1}{g_m} \parallel r_o \parallel r_o \approx \frac{1}{g_m}$$

$$R_T = 30 \Omega$$

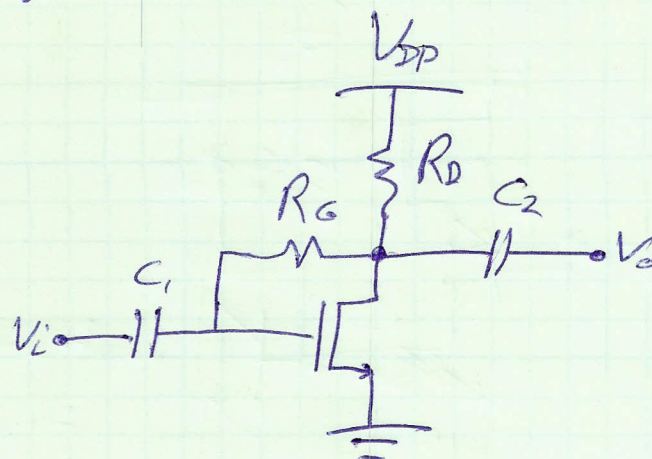Question 5

a)

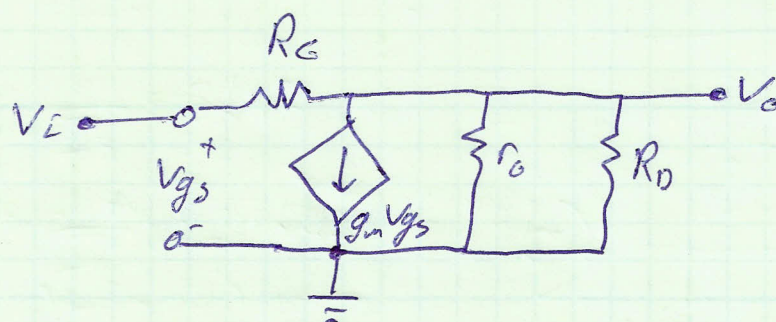

b) Apply test source V_x to output and zero (short) the input $\rightarrow V_{gs} = 0$

$$I_x = \frac{V_x}{R_G} + \frac{V_x}{r_o} + \frac{V_x}{R_D}$$

$$R_o = R_G \parallel r_o \parallel R_D$$


c) $V_i = V_{gs}$

at the output node,

$$\frac{V_o - V_i}{R_G} + V_i g_m + \frac{V_o}{r_o} + \frac{V_o}{R_D} = 0$$

$$V_i \left(\frac{1}{R_G} + g_m \right) = V_o \left(\frac{1}{R_G} + \frac{1}{r_o} + \frac{1}{R_D} \right)$$

$$A_{V_o} = \frac{V_o}{V_i} = \frac{\frac{1}{R_G} + g_m}{\frac{1}{R_G} + \frac{1}{r_o} + \frac{1}{R_D}} = \frac{R_G \parallel r_o \parallel R_D}{R_G \parallel \left(\frac{1}{g_m} \right)}$$

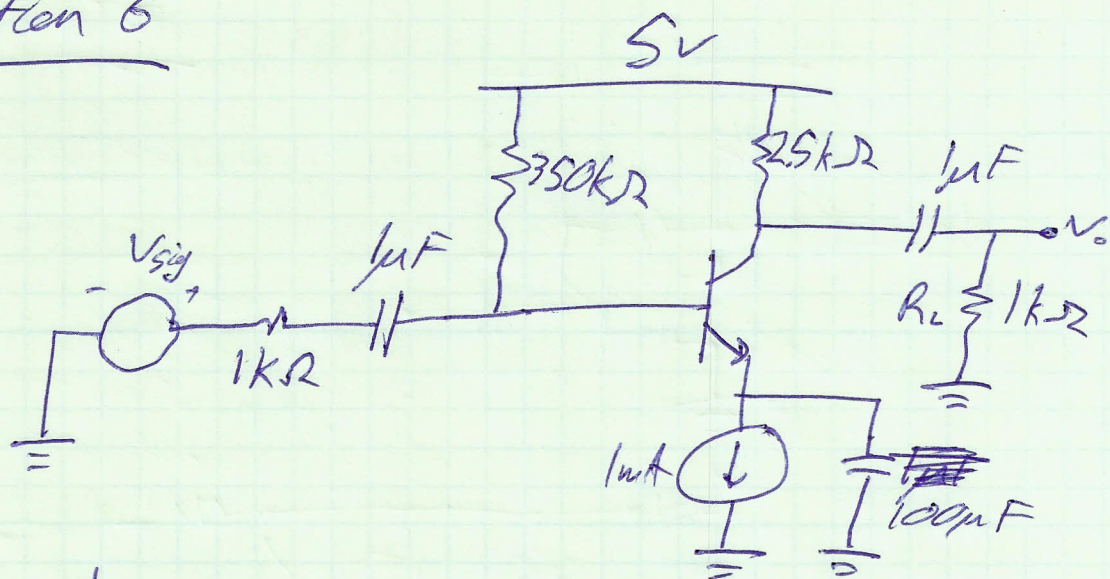Question 6

a) $A_{v0} = A_v |_{R_L \rightarrow \infty}$

$$A_{v0} = -g_m (r_o \parallel R_c)$$

$$g_m = \frac{I_c}{V_T} = \frac{1\text{mA}}{26\text{mV}} = 0.039\text{A/V}$$

$$r_o = \frac{V_A}{I_c} = \frac{100}{1\text{mA}} = 100\text{k}\Omega$$

$$A_{v0} = 95$$

$$r_o = \frac{V_T}{I_B} = \frac{26\text{mV}}{10\mu\text{A}} = 2.6\text{k}\Omega$$

$$R_c = R_B \parallel r_o$$

$$R_c = 350\text{k}\Omega \parallel 2.6\text{k}\Omega$$

$$R_c = 2.6\text{k}\Omega$$

$$R_o = R_c \parallel r_o$$

$$R_o = 2.5\text{k}\Omega \parallel 100\text{k}\Omega$$

$$R_o = 2.4\text{k}\Omega$$

b) $f_{p1} = \frac{1}{2\pi C_1 (R_c + R_{sig})} = 44\text{Hz}$

$$f_{p2} = \frac{1}{2\pi C_2 (R_c + R_o)} = 47\text{Hz}$$

$$f_{p3} = \frac{1}{2\pi C_E [R_E \parallel (\frac{1}{g_m} + (R_B \parallel R_{sig})/\beta)]} = 45\text{Hz}$$

$$f_L = \sum_n f_{pn} = 44 + 47 + 45$$

$$f_L = 136\text{Hz}$$